

RADIO — ELECTRONICS

SEPTEMBER 1956

TELEVISION • SERVICING • HIGH FIDELITY

HUGO GERNSBACH, Editor

Service Check List
for
Transistor Radios

•

Transistorized
Hi-Fi Preamp

•

Speech-Music
Discriminator
for
Music Lovers

•

TV Receivers
with
Remote Controls

•

Set Your Checker
for
New Tube Types

35¢

U. S. and
CANADA


Over-the-Horizon Radio

See

CLIFFORD S. ROYCE 3-57
TOWNSHEND
VERMONT



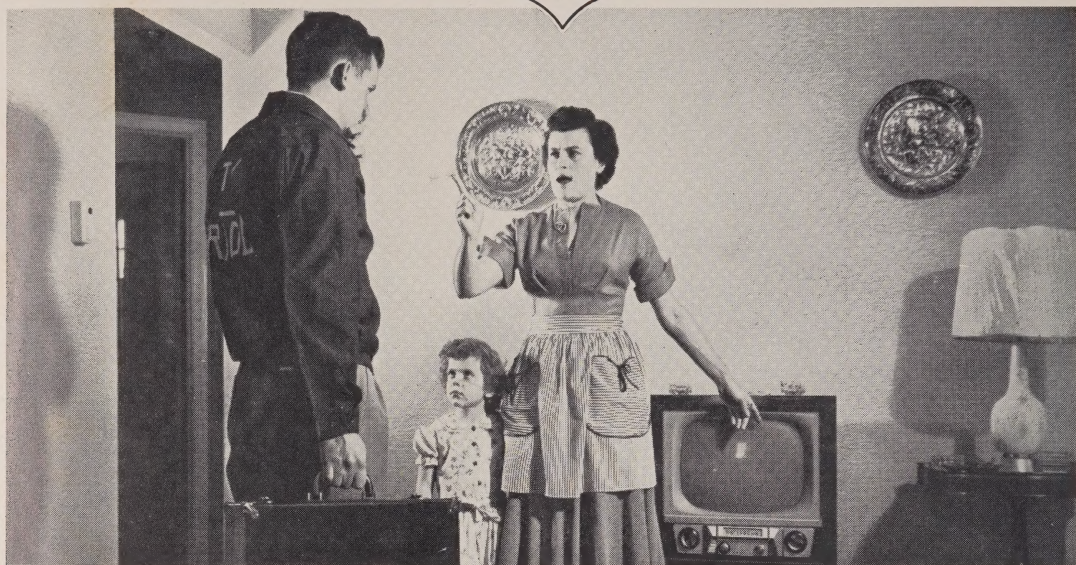YOU PUT THIS TUBE IN AND...
 YAP... YAP... YAP... BLAH... BLAH... BLAH
 ...AND I MISSED MY FAVORITE PROGRAM



...IT'S **YOUR** REPUTATION!

Serviceman, at this point you are on your own! Your customer holds only **you** responsible if the picture tube goes bad because it was **your** selection. If your selection for replacement was a high quality brand, chances are your reputation for quality work wouldn't be under the gun like this.

When you use Du Mont picture tubes your reputation is backed by the pioneer commercial cathode-ray tube manufacturer of the country. The Twin-Screen Hi-Lite* alumi-

nized picture tube is a product of the finest engineering, design, and production features assembled in 25 years of commercial manufacturing. Your confidence is definitely assured because you **know** that the guarantee on Du Mont picture tubes is good—as it has always been.

Your reputation for high quality work is established when you use high quality products. You have a reliable **partner** when you use Du Mont picture tubes.

*The ultimate in aluminized picture tubes

IT'S
 DEALERS
 CHOICE


make it...



Cathode-Ray Tube Division

ALLEN B. DU MONT LABORATORIES, Inc., 750 Bloomfield Avenue, Clifton, N. J.

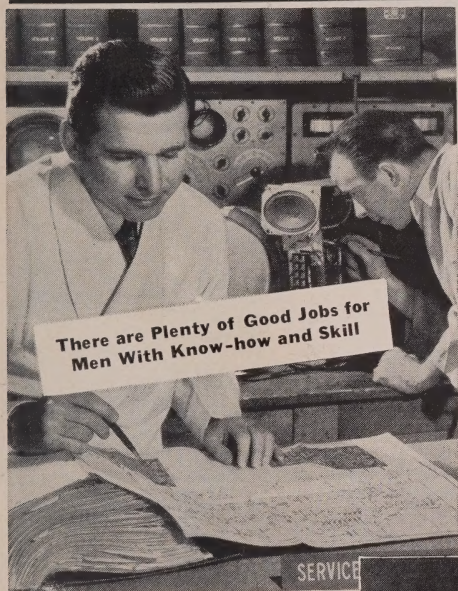Learn to Service TV Sets— any make or model—Quickly



**17" Picture Tube, Components
for a TV Receiver, Scope,
Signal Generator, HF Probe—
all included in introductory
price under \$200—Easy Terms**

If you want to go places in TV servicing, you will act quickly to find out what you get, what you practice, what you learn and how NRI's new course in Professional Television Servicing will help you advance through better technical knowledge and training. See pictures of equipment supplied, read what you practice in book offered FREE to ambitious men with some knowledge of Radio or TV fundamentals. Find out about this ALL PRACTICE Professional TV Servicing Course now.



New ALL PRACTICE Method trains you at home to become a Professional TV Serviceman

*You learn the time saving techniques,
methods used by top TV Servicemen*

This is 100% learn-by-doing, practical training. NRI supplies all necessary equipment, all tubes, including a 17-inch picture tube; and comprehensive manuals covering a thoroughly planned program of practice. You learn how experts diagnose TV receiver defects quickly. You easily learn the causes of defects—audio and video—and how to fix them accurately.

You get actual experience aligning TV receivers, isolating complaints from scope patterns, eliminating interference, using germanium crystals to rectify the TV picture signal, adjusting the ion trap and hundreds of other valuable Professional techniques.

UHF and COLOR Create Growing Opportunities

To cash in on the present UHF and the coming COLOR TV boom you'll need the kind of knowledge and experience NRI's Course gives. You'll get practice installing front-end channel selector strips in modern UHF-VHF receivers. You learn UHF servicing problems and their solution. Mail the coupon now. Discover how NRI's new course in PROFESSIONAL TELEVISION SERVICING meets the needs of the man who wants to get ahead in TV Servicing.

Not for Beginners

If you have some knowledge of Radio-TV fundamentals, or have had some Radio Shop experience or some Radio school training, this course IS FOR YOU. Mail coupon today.

Address National Radio Institute, Dept. 6JFT, 16th and U Sts., N. W., Washington 9, D. C.

**MAIL
NOW**

National Radio Institute, Dept. 6JFT,
16th and U Sts., N.W.
Washington 9, D.C.

Please send my FREE copy of "How to Reach the Top in TV Servicing." I understand no salesman will call.

Name..... Age.....

Address.....

City..... Zone..... State.....

Approved Member National Home Study Council

COUPON BRINGS IMPORTANT BOOK FREE

Get this book and judge for yourself how this course will further your ambition to reach the top in TV Servicing or help to build a more secure business of your own in TV. Many of tomorrow's top TV Servicemen... men who can service any make, any model, UHF, VHF or Color TV... will be graduates of this training. Mail the coupon now. There is no obligation.



RADIO - ELECTRONICS

Formerly RADIO CRAFT • Incorporating SHORT WAVE CRAFT • TELEVISION NEWS • RADIO & TELEVISION*

EDITORIAL

- 33 Airplane Collision Prevention — Hugo Gernsback

TELEVISION

- 34 Remote Controls for TV — Henry O. Maxwell
37 WWTW (World-Wide Television) (Cover Feature) — Fred Shunaman
39 Did You Ever? — H. A. Highstone
40 Heater-Cathode Stress in Full-Wave Doublers
— George C. Chernish
42 TV Service Clinic — Conducted by Jerry Kass
44 ITV Pulse-Generator Techniques, Part II — Edward Noll

TEST INSTRUMENTS

- 46 VTVM Servicing Is Not So Simple! — Robert G. Middleton
47 Daughter of Necessity — Jack Wise
48 Audio Signal Generator — Lyman E. Greenlee
50 Delay and Sweep Generator — Tom Jaski
54 Setting Your Checker for New Type Tubes — Basil C. Barbee

AUDIO—HIGH FIDELITY

- 56 Laboratory Golden Ear, Part II — Joseph Marshall
59 Hi-Fi Preamp for Easy Listening — J. H. Owens
61 For Golden Ears Only: Shure WC10 ceramic cartridge; Elac
Miratwin cartridge — Monitor
62 Speech-Music Discriminator — Edward E. Predmore

RADIO

- 79 Build This Universal Experimental Chassis — Kurt Freund
82 10 Servicing Tips for Transistor Radios — Stan Schenkerman
88 Symmetrical Voltage Doubler — George P. Pearce
91 Transistor Radios, Part IV — I. Queen
100 Phase-Shift Chart — H. P. Manly

ELECTRONICS

- 106 Improved Supply Powers G-M Counter — Thomas G. Knight
108 Photoelectric Light Computer — John R. Satter

- | | |
|----------------------|--------------------------|
| 154 Books | 150 People |
| 147 Business | 127 Question Box |
| 128, 148 Corrections | 6 Radio Month |
| 14 Correspondence | 134 Radio-Electronic |
| 113 New Devices | Circuits |
| 120 New Records | 153 Technical Literature |
| 124 New Tubes and | 110 Technicians' News |
| Transistors | 130 Technotes |
| 138 Patents | 142 Try This One |

Hugo Gernsback
..... Editor and Publisher
M. Harvey Gernsback
..... Editorial Director
Fred Shunamon
..... Managing Editor
Robert F. Scott
..... W2PWG, Technical Editor
Jerome Kass
..... Associate Editor
I. Queen
..... Editorial Associate
Matthew Mandl
..... Television Consultant
Elizabeth Stralcup
..... Production Manager
Angie Pascale
..... Editorial Production
Wm. Lyon McLaughlin
..... Tech. Illustration Director
Sol Ehrlich
..... Art Director
Lee Robinson
..... General Manager
John J. Lamson
..... Sales Manager
G. Aliquo
..... Circulation Manager
Adam J. Smith
..... Director, Newsstand Sales
Robert Faloth
..... Promotion Manager



Average Paid Circulation over 174,000

ON THE COVER

(Story on page 37)

These experimental prototypes of antennas for use in over-the-horizon communications systems are set up at IT&T's Federal Telecommunication Laboratories, Nutley, N. J. Marie Grey, of Federal's drafting department, is studying the construction. Color original by Dean Price, Handy-Boesser Photographs, Newark, N. J.

NEXT MONTH: Underground Antenna • TV Antenna Adjustments for Eliminating Interference • Long-Tailed Cascode Pair Amplifier • Flea-Power Transistor Transmitter

Associate Member of Institute of High Fidelity Mfrs., Inc.

RADIO-ELECTRONICS, September, 1956, Vol. XXVII, No. 9. Published monthly at Mt. Morris, Ill., by Gernsback Publications, Inc. Second-class mail privileges authorized at Mt. Morris, Ill. Copyright 1956 by Gernsback Publications, Inc. All rights reserved under Universal, International and Pan-American Copyright Conventions. GERNSBACK PUBLICATIONS, INC., Executive, Editorial and Advertising Offices, 154 West 14th St., New York 11, N. Y. Telephone ALgonquin 5-7755. Hugo Gernsback, Chairman of the Board; M. Harvey Gernsback, President; G. Aliquo, Secretary. SUBSCRIPTIONS: Address correspondence to Radio-Electronics, Subscription Dept., 404 N. Wesley Ave., Mt. Morris, Ill., or 154 West 14th St., New York 11, N. Y. When ordering a change please furnish an address stencil impression from a recent wrapper. Allow one month for change of address. SUBSCRIPTION RATES: U. S., U. S. possessions and Canada, \$5.50 for one year; \$6.00 for two years; \$8.00 for three years; single copies 35c. Pan-American countries \$4.00 for one year; \$7.00 for two years; \$9.50 for three years. All other countries \$4.50 a year; \$8.00 for two years; \$11.00 for three years. BRANCH ADVERTISING OFFICES and FOREIGN AGENTS listed on page 156. POSTMASTER: If undeliverable, send Form 3578 to: RADIO-ELECTRONICS, 154 West 14th St., New York 11, N. Y.

*Trademark registered U. S. Pat. Office.

RADIO-ELECTRONICS

NATIONAL SCHOOLS

proudly presents

FOR MEN
WHO WANT
TO EARN
MORE MONEY

TELERAMA • ALL 8 BRANCHES OF TELEVISION • ELECTRONICS • RADIO IN ONE DYNAMIC, MODERN SHOP METHOD, HOME TRAINING COURSE

*Registration applied for

Another great advance in **HOME STUDY TRAINING**. Let National Schools, of Los Angeles, a practical Technical Resident Trade School for over 50 years, train you at home by Shop-Method, for today's unlimited opportunities in **ALL 8 BRANCHES** of the Television, Electronics, Radio Industry.

Check all you receive in *One Master Course* at One Low Tuition

1. Television — Including Color TV
2. Radio — FM and AM
3. Industrial Electronics
4. Sound Recording and Hi-Fidelity
5. Preparation for FCC License
6. Automation
7. Radar and Sonar
8. Communications

ALL OF THIS MODERN, NEWEST, PRACTICAL EQUIPMENT IS YOURS TO KEEP!

- Parts to Build a modern TV set, including large screen Picture Tube.
- Parts to build a powerful Superhet Receiver, standard broadcast and short wave.
- Parts to conduct many experiments and build Continuity Checker, RF Oscillator, TV Circuits, Audio Oscillator, TRF Receiver, Signal Generator.
- Professional Multitester
- These are a MUST for all technicians.

YOU DO MANY PRACTICAL JOBS.

You do servicing, circuit analysis and many other down-to-earth experiments. You build a modern TV set from the ground up... with equipment kits we give you, including a new large screen picture tube and professional Multitester, at no additional charge.

EARN AS YOU LEARN! Many of our students earn their entire tuition and more in Spare Time jobs we show them how to do while learning. **YOU GET GRADUATE ADVISORY SERVICE, TOO.**

ALL YOURS
TO KEEP



L. J. ROSENKRANZ
President of NATIONAL SCHOOLS

This Master-Shop-Method course is completely up-to-date. Here in Los Angeles, the TV and Electronics center of the world, we are able to keep in constant touch with the industries' latest developments. As a student, you will quickly master all phases at home... in your spare time. Your earning power will grow with every lesson. Just as thousands of National Schools graduates do every day, you can handle servicing, manufacturing, repairing, hundreds of other jobs, or make good money in your own business. **SECURE YOUR FUTURE—NOW. SEND COUPON BELOW.**



IN THESE MODERN TV STUDIOS, SHOPS AND LABORATORIES, your Shop Method Home Study Course was developed by experienced instructors and engineers. What an advantage that is to you at home — each lesson is tested, proved, easy to understand. You can master the most up-to-date projects, such as color TV set repair, printed circuits — even prepare for F.C.C. License and industrial electronics without taking a special course. **TAKE YOUR FIRST STEP NOW TO A TOP-PAY JOB IN TV, ELECTRONICS, RADIO. SEND COUPON BELOW TODAY.**

APPROVED FOR
VETERANS
AND
NON-VETERANS

NATIONAL SCHOOLS

4000 S. FIGUEROA ST., LOS ANGELES 37, CALIF.
187 N. LA SALLE ST., CHICAGO 1, ILL.

IN CANADA: 811 W. Hastings St., Vancouver, B. C.

NATIONAL SCHOOLS
TECHNICAL TRADE TRAINING SINCE 1905
Los Angeles, California

GET FAST SERVICE—MAIL NOW TO OFFICE NEAREST YOU!

NATIONAL SCHOOLS, DEPT. RG-96

4000 S. FIGUEROA ST. OR 187 N. LA SALLE ST.

LOS ANGELES 37, CALIF. CHICAGO 1, ILL.

Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.

NAME _____ BIRTHDAY _____ 19 _____


ADDRESS _____

CITY _____ ZONE _____ STATE _____

VETERANS: Give Date of Discharge _____

FREE!

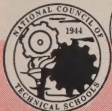Fully illustrated "CAREER" BOOK in TV, Radio, Electronics. AND actual Sample Lesson—yours at no cost, no obligation **SEND COUPON NOW—TODAY!**




TUNG-SOL® TECHNICAL DATA BOOKS FOR 1956



T-58 1250 pages—1000 tube types.



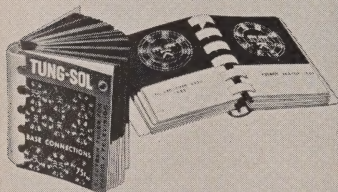T-70 More than 250 pages of data on CR tubes, receiving and special purpose tubes and dial lamps.



T-31 Over 350 blueprint base diagrams for 1400 tube types.

ALL THE INFORMATION AT YOUR FINGER TIPS

The new 1956 Tung-Sol Electron Tube Technical Data books are the most practical set of reference books in the entire industry. They contain all the information you need for everyday use. Clearly indexed and streamlined for fast reading, they open flat for rapid on-the-job reference.

Ask your Tung-Sol supplier how you can get your set.

TUNG-SOL ELECTRIC INC., Newark 4, N. J.
Sales Offices: Atlanta, Columbus, Culver City, Dallas, Denver, Detroit, Melrose Park (Ill.), Newark, Seattle.



Miniature Lamps



Sealed Beam Headlamps



Signal Flashers



Radio and TV Tubes



Aluminized Picture Tubes



Special Purpose Tubes




Semiconductors



Color Picture Tubes

the Radio month

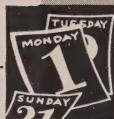

ALL-UHF TV SYSTEM has been proposed by the FCC. Faced with a difficult problem of allocations, the commission has asked for all comments on the proposal by Oct. 1. A major consideration was the usefulness of the lower part of the vhf band to other services.

The FCC report stated, "If suitable means could be found to overcome the difficulties inherent in so major a frequency reallocation as moving television to uhf and if uhf could be sufficiently developed to permit the elimination of vhf channels without loss of service, a number of basic advantages would result. All stations would be able to compete on a much more nearly comparable basis technically . . . competitive opportunities would be considerable enhanced . . ." The FCC is also entertaining the advisability of limiting the shift to uhf to the eastern part of the United States.

AIR-DEFENSE COMPUTER designed for use in the Semiautomatic Ground Environment (SAGE) system is about to be installed at McGuire Air Force Base in New Jersey. SAGE represents a supersensitive continental air-defense system.

It starts with a radar ring—on land, Navy picket ships at sea, offshore Texas towers and airborne early-warning planes ranging far out over the ocean. These radars are linked by telephone lines or uhf radio directly to the high-speed computer (see photo). Information about aircraft anywhere within the radar area is relayed continuously and automatically to the computer. The computer digests all the


information plus ground-observer reports, flight plans of friendly planes and weather information as fast as it is received and translates it into an overall picture of the air situation. Hostile planes can be identified immediately and the most effective defense action taken.

The computer automatically calculates for the operator the most effective application of such defensive weapons as guided missiles, antiaircraft batteries and jet interceptors. In the case of intercepting jets, the aircraft is controlled by directions fed by radio directly from the computer to the automatic pilot in the plane. Missiles are controlled similarly. The computer is designed to operate 24 hours a day, 7 days a week.

The first computer, built at Kingston, N. Y., by International Business Machines for later shipment to the air force base, covers 3 acres of ground and contains 58,000 tubes.

INDUSTRIAL COMMUNICATIONS made a revolutionary advance with the opening of the Sylvania Data Processing Center at Camillus, N. Y., June 26. An 18,000-mile telegraph network leased from Western Union connects 45 factories, 19 laboratories, 10 division headquarters, the company's corporate executive offices, 27 sales offices and 17 warehouses to the data processing center, which will provide complete accounting and statistical services to all 10 Sylvania operating divisions through seventy-one stations in 61 cities and towns.

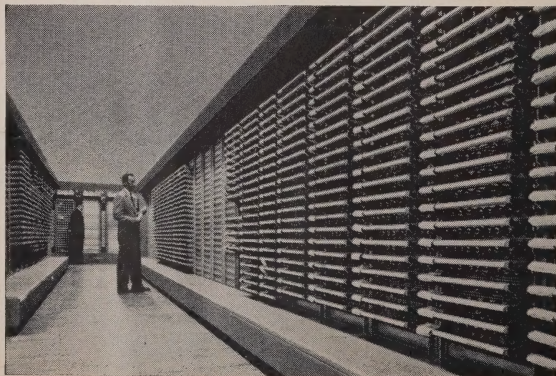Data messages from any one of the outlying points contain three data rout-



A bit of the great computer. White bars are handles of plug-in units holding 6-9 tubes. Panel contains about 2,500 of the instrument's 58,000 tubes.



JACK DEMPSEY
Former World's Heavy-weight Boxing Champion
Long-time friend and supporter of DeVry Tech.

Jack Dempsey says:

**"Find Out TODAY How
YOU MAY TRAIN
AT HOME**

**For Great Opportunities in
TELEVISION
RADIO • ELECTRONICS**



Nick Barton, Illinois,
a DTL grad, now has his own business and tells us he is "literally snowed with work."



George D. Crouch, California,
was a retail store clerk. He took the DeVry Program, and today is in business for himself.

Get the Facts

FREE from

DEVRY TECH

See, too, How DeVry Tech Helps A Man
Get Started in this Field

**Fill Out This Chart and Mail
with Coupon . . .
No Obligation!**



**89 WAYS
TO
EARN MONEY
IN TELEVISION
RADIO
ELECTRONICS**

It costs you nothing to find out, and it may mean the turning point in your life. Let DeVry Tech tell you if you have the basic qualifications. Send in the personal rating chart today. Get the free leaflet, "89 Ways to Earn Money in Television-Radio-Electronics."

Free Sample Lesson



Let us give you without cost a Sample Lesson. See for yourself how easy it is to follow. DeVry Tech's down-to-earth instructions, practical training experiments, the test equipment you build and KEEP, the exclusive home training films . . . make learning simple and fast. Subject matter is broken down small enough and clearly enough for you to absorb it.

Get These Added Benefits

Whether you train at home or in our large, well-equipped, million-dollar Chicago Laboratories, you are not tied to a long-term contract . . . You have the privilege of canceling the program at any time.

ARE YOU DRAFT AGE? Mention it when you mail the coupon. We have valuable information for you.

Member of National Home Study Council



DEVRY TECHNICAL INSTITUTE

CHICAGO 41, ILLINOIS

FORMERLY

DEFOREST'S TRAINING, INC.

"One of America's Foremost Electronics Training Centers"

PERSONAL RATING CHART

1. **AGE**—If you are between the ages of 17 and 55, place the numeral 5 in the square at right. If above or below those ages, mark yourself 3. ☐
2. **EDUCATION**—If you have graduated from high school, mark 5 in the square at right. If you finished 8th grade, mark 3. ☐
3. **DEPENDENTS**—If you are free to come to Chicago, rate yourself 5. If you prefer to study at home and hold your present job, put down the number 3. ☐
4. **ABILITY**—If you've had any experience in handling a soldering iron or doing simple home wiring, rate yourself 5. If you feel you can follow simple "How-to-do-it" instructions, mark down 3. ☐
5. **AMBITION**—Are you interested in training for a real future in a promising field? Mark down 5. Or do you simply want to prepare for a better job with more money? Put down 3. ☐

If you are subject to military service, please mark "X" here. ☐

MAIL CHART AND COUPON NOW!

DEVRY TECHNICAL INSTITUTE
4141 Belmont Ave., Chicago 41, Ill., Dept. RE-9-M

I would like late facts about the many opportunities in Television-Radio-Electronics, including the 3 free publications, and how DeVry Tech may prepare me for my start in this billion-dollar field.



Name _____ Age _____
Please Print

Street _____ Apt. _____

City _____ Zone _____ State _____

DTI's training is also available in Canada
1049

NEW \$70.00

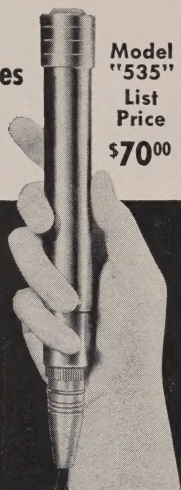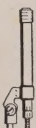SHURE SLENDYNEOMNIDIRECTIONAL
DYNAMIC
PROBE
MICROPHONEIS 5
Microphones
IN 1Model
"535"
List
Price
\$70.00For Public Address
Remote Broadcast
Theater-Stage
Sound Systems

A completely versatile probe microphone of excellent frequency range (60-13,500) that combines ruggedness, beauty and reliability.

Versatility: Can be used (1) on a floor stand; (2) on a desk stand; (3) quickly removed for use as a hand-held microphone; (4) furnished with lavalier cord for wearing around the neck; (5) impedance switch permits use as high or low impedance microphone. Accessory on-off switch requires no wiring.**Ruggedness:** Built to withstand hard usage and extremes of temperature and humidity.**Beauty:** Slender, convenient shape, finished in brushed satin chrome.**Reliability:** High efficiency magnetic materials and circuits assure years of consistent high quality performance. Shure quality control techniques result in an exceptionally high degree of uniformity for microphone interchangeability and multiple use.**SLENDYNE Model "530"**

This deluxe version of the Slendyne has a frequency range of 50-15,000 cps and is furnished with a Cannon XL-3-11 broadcast connector. Strikingly attractive non-reflecting black and gold anodized finish. LIST PRICE \$110.00

*The Mark of Quality***SHURE SHURE BROTHERS, INC.**

222 HARTREY AVENUE • EVANSTON, ILLINOIS



A small part of the equipment in the new data processing center, which in its entirety contains more than 50,000 square feet of floor space.

ing characters. Thus "DPR" would cause the message to be routed to the payroll section of the data center; "DIC" would send it to inventory control. "D" indicates the message is to go to the data center. The network can be used for administrative messages between any two stations.

Messages arriving at the station are received on perforated tape and are "translated" onto magnetic tape for input to the Univac, 10-ton, 5,600-tube electronic brain of the system. Both punched cards and magnetic tape are used.

The combination of instant communication plus almost instant computation produces formerly impossible results. A complete payroll, including preparation and signing of checks, can be processed in a couple of hours from information sent in by the scattered stations. All checks will be mailed in bundles to the various outlying points, rather than prepared at each one, resulting in a tremendous saving. Engineers can calculate complex technical problems—each of the 19 laboratories has easy access to the large and expensive computer. Production can be geared exactly to inventory through instantaneous knowledge of the quantity of any product on hand. The Data Processing System is, the company believes, "the only existing concept of an entire company tied together communications-wise from a data processing viewpoint, and with that function housed in its own facility."


CERAMIC RECEIVING TUBES recently developed by Eitel-McCullough (Eimac) are the forerunners of a complete line which will meet most receiv-

ing requirements with a minimum number of types. The new design permits them to withstand heavy accelerative forces from shock and vibration, and to operate continuously with envelope temperatures of more than 300°C. Tube life is so long that they will be wired directly into electronic equipment, eliminating the need for tube sockets.

The photo shows an exploded view of one of these tubes—an Eimac 33C3A2 dual triode stacked ceramic unit. Its general specifications are: heater voltage, 6.3; amplification factor, 20; transconductance (at 9-ma plate current), 2,600 micromhos. Maximum plate dissipation per section is 2.75 watts; maximum plate current 20 ma. Tube dimensions are 7/8 inch high, 1-1/32 inches in diameter.

Calendar of Events

23d Annual British Radio Show, Aug. 22-Sept. 1, Earls Court, London, England.
 Southern Arizona Hamfest, Sept. 1-3, Fort Huachuca, Ariz.
 RETMA Conference on Reliable Electrical Connections, Sept. 11-12, University of Pennsylvania, Philadelphia, Pa.
 NATESA Convention, Sept. 14-16, Sheraton Hotel, Chicago, Ill.
 11th Annual International Instrument-Automation Conference and Exhibit, Sept. 17-21, New York Coliseum, New York, N. Y.
 National Television Week, Sept. 23-29.
 New York High Fidelity Show, Sept. 26-30 and Audio Engineering Society Convention, Sept. 26-29, New York Trades Show Building, New York, N. Y. (Radio-Electronics will exhibit in Room 523 at the High Fidelity Show.)
 Canadian IRE Show and Convention, Oct. 1-3, Automotive Building, Exhibition Park, Toronto, Canada.
 National Electronics Conference and Exhibition, Oct. 1-3, Chicago, Ill.
 80th Convention of Society of Motion Picture and Television Engineers, Oct. 7-12, Ambassador Hotel, Los Angeles, Calif.
 2d Annual IRE Professional Group, Technical Meeting on Electron Devices, Oct. 25-26, Shoreham Hotel, Washington, D. C.

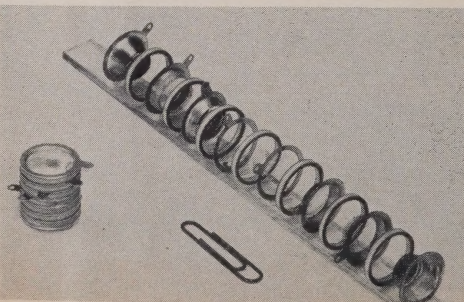

free!

ALLIED'S 1957 value-packed 356-page CATALOG



FEATURING

SUPER-VALUE knight-kits: Finest electronic equipment in money-saving Kit form—Test Instruments, Hi-Fi kits, Hobbyist kits, Ham kits. Easiest to build and you SAVE MORE.

EVERYTHING IN HI-FI: World's largest selection of quality Hi-Fi components and complete music systems—available for immediate shipment from stock. Own the best in Hi-Fi for less!

EASY-PAY TERMS: Only 10% down, up to 18 months to pay. Available on orders over \$45. Fast handling—no red tape.




Our 36th year
ALLIED RADIO
World's Largest Electronic Supply House

SEPTEMBER, 1956

the only **COMPLETE** catalog
for everything in electronics

World's Most Complete Stocks

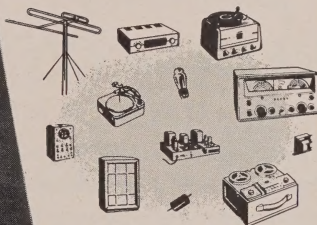- Latest Hi-Fi Systems and Components
- Super-Value KNIGHT-KITS • P. A. Systems and Accessories • Recorders and Supplies • TV Tubes, Antennas, Accessories • Amateur Receivers, Transmitters, Station Gear • Test and Lab Instruments
- Specialized Industrial Electronic Equipment • Huge Listings of Parts, Tubes, Transistors, Tools and Books...



Get ALLIED's 1957 Catalog—it's *complete*, up-to-date—356 pages packed with the world's largest selection of quality electronic equipment at lowest, money-saving prices. Get *every* buying advantage at ALLIED: fastest shipment, expert personal help, lowest prices, guaranteed satisfaction...

send for the leading
electronic supply guide

free

ALLIED RADIO CORP., Dept. 2-J-6
100 N. Western Ave., Chicago 80, Ill.

☐ Send FREE 356-Page 1957 ALLIED Catalog

Name.....

Address.....

City.....Zone....State.....



Zenith Model ZP6G
The Music Maker 4-speed Portable


ZENITH finds that it's
good business to...

RELY on GI PHONOMOTORS

Zenith chooses General Industries phonomotors for its Model ZP6G because GI gives quality, dependability and superb performance. For prompt, dependable deliveries and unsurpassed design and manufacturing excellence, GI phonomotors are the one best choice. When you need phonomotors for original equipment or replacement purposes... RELY on GI!

Other General Industries AC induction type motors for applications ranging from 1/40 HP to 1/1100 HP.

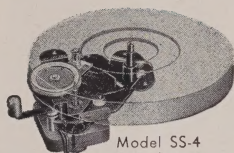Write for specifications and quantity-price quotations.



Model SS-4
Four Speed
Motor



THE GENERAL INDUSTRIES CO.

DEPT GR • ELYRIA, OHIO

SUBSCRIBERS...

If you're moving, please don't forget to send us your old address as it appears on the address label of your current copy of the magazine, including the numbers shown beside your name, as well as your new address. If we receive this information before the 20th of the month, you will continue getting the magazine without interruption. Your co-operation will be most helpful and greatly appreciated.


We, too, have a new address:

Subscription Department
RADIO-ELECTRONICS
154 West 14 St.
New York 11, N.Y.

RADIO MONTH

(Continued)

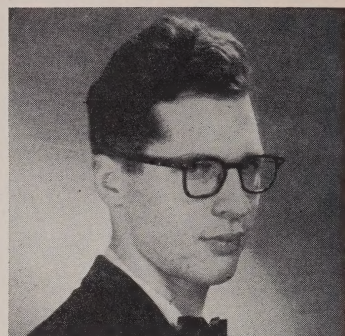GERNSBACK SCHOLARSHIP for the academic year 1956-57 has been awarded to Paul Martin Schnitzler. The scholarship was established by Hugo Gernsback for presentation to an outstanding first-year student, through



the department of electrical engineering of New York University.

Paul Schnitzler was born July 20, 1936. He became interested in matters electronic while a member of the Boy Scouts, building a superregenerative receiver. He entered Brooklyn Technical High School in New York in 1950, majoring in mathematics and sciences. Paul began his college career at NYU in February, 1954. He holds general class license K2KOK with his equipment being strictly home-brew.

TWO NEW TV STATIONS have gone on the air since our last report:

WCKT Miami, Fla.7
WISC-TV Madison, Wis.3

KZTV, Reno, Nev., channel 8, has changed its call letters to KOLO-TV and WBUF-TV, Buffalo, N. Y., channel 17, to WBUF.

Canada now has 35 TV stations. The two latest stations are CFCL-TV, Timmins, Ontario, channel 6, and CFXY-TV, Charlottetown, Prince Edward Island, channel 13.

ARMSTRONG'S MEMORY will be perpetuated in a recently established Armstrong Memorial Research Foundation. Formed by his close friends and associates, the expressed purposes of the foundation include aiding in the continuation of basic research that was carried on by Major Armstrong as professor of electrical engineering at the Marcellus Hartley laboratory at Columbia University and to contribute to the education and training of engineers and scientists capable of doing basic applied research in electronics and related fields of science.

Maj. Edwin Howard Armstrong died in February, 1954, after a life devoted to basic research in electronics. Outstanding among his accomplishments were development of the superheterodyne circuit and frequency modulation. The foundation will perpetuate the name and works of Armstrong through grants of money or property to Columbia University and its affiliates, primarily.

END

**6 months
from today**



**REGRET TO ADVISE
YOU FAILED YOUR
FCC EXAMINATIONS**

OR



**FIRST CLASS
COMMERCIAL
FCC LICENSE**

**Get these valuable
BOOKLETS**

FREE!

**add technical training to your
practical experience. GET YOUR FCC
LICENSE QUICKLY!**



**then use our effective
JOB FINDING SERVICE!**

**WE GUARANTEE
YOUR FCC LICENSE**

If you fail to pass your Commercial License exam after completing our course, we guarantee to continue your training without additional cost of any kind until you successfully obtain your Commercial License.

HERE'S PROOF FCC LICENSES CAN BE SECURED IN A FEW HOURS OF STUDY With Our Training AT HOME In Spare Time.

Name and Address	License	Time
Walter Eggers, Pacific Grove	1st	12 weeks
Paul Reichert, West Salem, Ohio	2nd	10 weeks
Harold Phipps, LaPorte, Indiana	1st	28 weeks
John H. Johnson, Boise City, Okla.	2nd	12 weeks
James Faint, Johnstown, Pa.	1st	26 weeks

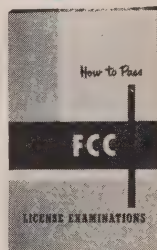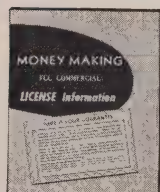

Employers Make OFFERS Like These

to Our Graduates Every Month

Broadcast Station in Illinois: "We are in need of an engineer with a first class phone license, preferably a student of Cleveland Institute of Radio Electronics; 40 hour week plus 8 hours overtime."

West Coast Manufacturer: "We are currently in need of men with electronics training or experience in radar maintenance. We would appreciate your referral of interested persons to us."

Our Trainees Get Jobs Like These Every Month

CHIEF ENGINEER

"Since enrolling with Cleveland Institute I have received my 1st class license, served as a transmitter engineer and am now Chief Engineer of Station WALN. I also have a Motorola 2-Way Service Station. Thanks to the Institute for making this possible."

Lewis M. Owens, Columbia, Ky.

TEST ENGINEER

"I am pleased to inform you that I recently secured a position as Test Engineer with Melpar, Inc. (Subsidiary of Westinghouse). A substantial salary increase was involved. My Cleveland Institute training played a major role in qualifying me for this position."

Boyd Daugherty, Falls Church, Va.



**WE CAN PROVIDE HUNDREDS OF NAMES
IN YOUR AREA ON REQUEST**

Carl E. Smith, E.E., President

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
Desk RE-95, 4900 Euclid Ave., Cleveland 3, Ohio

Member of National Home Study Council

Cleveland Institute of Radio Electronics

Dept. RE-95, 4900 Euclid Ave., Cleveland 3, O.

Please send Free Booklets prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below:

- | | |
|---|---|
| <input type="checkbox"/> Military | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radio-TV Servicing | <input type="checkbox"/> Home Experimenting |
| <input type="checkbox"/> Manufacturing | <input type="checkbox"/> Telephone Company |
| <input type="checkbox"/> Amateur Radio | <input type="checkbox"/> Other _____ |

**In what kind of work are you
now engaged?**

**In what branch of Electronics
are you interested?**

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

Special Tuition Rates to Members of Armed Forces

Rohn

only complete line of

TV and COMMUNICATION TOWERS

proven in Profits and Customer Satisfaction

• • • • HIGHLIGHTS OF THE ROHN LINE • • • •

look at these
ROHN exclusives

• HOT DIPPED GALVANIZED

The finest, most durable finish is available for ROHN Towers and accessories... all done entirely on the ROHN premises under careful ROHN supervision.

• UNEQUALLED DESIGN AND ENGINEERING

ROHN is the only design that has stood up over the years. ROHN has been first and foremost... and always the leader in new products to meet the changing demands.

• MASS PRODUCTION FOR LOW COSTS

ROHN was the first to utilize mass production techniques to build a superior tower at the most competitive prices. This means no sacrifice in quality yet far greater profits for you.

• UNIVERSAL CUSTOMER ACCEPTANCE

Thousands and thousands of installations prove the ROHN line first in customer satisfaction.

• PIONEER MANUFACTURERS

Pioneers in tower manufacturing—and today one of the world's largest manufacturers of this type equipment. The ROHN Company was built on satisfaction on the part of distributor, dealer and customer alike.


• COMPLETE LINE

Only ROHN offers a full line—one dependable one-stop source for all TV installation equipment. Save headaches, save shipping costs, save time... use ROHN unequalled service *exclusively*.

no. 6 tower

"All-Purpose" tower.

Fulfills 75% of your general tower needs—is structurally as sturdy—yet costs less than the well-known Rohn No. 10 Tower. Ideal for home and industrial installations, communication requirements... eliminates stocking many different tower models. Self-supporting to 50 ft. or guyed to 120 ft./ Easy to climb for fast, efficient servicing. Utilizes "Magic Triangle" which insures far greater strength and stability. Permanent hot-dipped galvanized coating. Dependability—a feature customers demand—is assured with the Rohn No. 6 Tower... designed to "stand up" for years to the rigors of weather and climatic conditions.

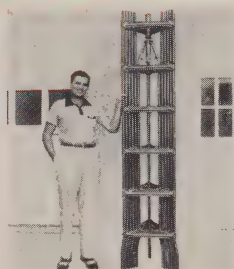


Package Tower

"Space Saver"—cuts storage space 300% or more!

Popular PT-48 has almost 50' of sturdy tower within a compact 8' x 20" package! "Magic Triangle" design is adapted to a pyramid shape using a wide 19" base with progressively decreasing size upward. Decreases your overhead... easy to transport and assemble—cuts shipping costs. Galvanized throughout. Available in heights of 24, 32, 40, 48, 56 and 64 feet!

COMMUNICATIONS TOWER

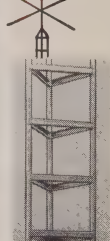

For extreme heights and communication purposes of all kinds, the Rohn No. 40 gives you strength and durability on which you can depend. The time tested and proven

equilateral triangle design using extra heavy duty tubing and corrugated steel cross-bracing is utilized. The No. 40 is structurally sound so you can install it for heights up to 300'; or at lesser heights when considerably greater strength is required because of excessive wind or antenna loading. Use for radio telephone, broadcasting, microwave relay and all other such communication purposes. If a particular job calls for this type tower, save real money by using ROHN towers.

Note: For lesser heights, use the Rohn No. 20 or No. 30 Tower.



Both Towers Feature THE ROHN MAGIC TRIANGLE

For structural superiority, famed wrap-around "magic triangle" design is featured in these all-steel towers. Towers have full 2 1/2" wide corrugated cross-bracing welded to tubular steel legs. The exclusive design assures dependable strength and permanence.



Telescoping Masts

Heavy-duty hot-dipped galvanized steel tubing and rigid joints give extraordinary strength. Quick installation... mast attached to base—antenna fixed, then mast hoisted quickly to desired height. Utilizes special clamp and guy ring arrangement. Flanged interior section; crimped exterior section gives mast stability that can't be beat. Complete with guy rings and necessary erection parts. In 20, 30, 40 and 50 ft. sizes. Bases and ground mounts available.

ROHN FOLD-OVER TOWERS

These unique fold-over towers are perfect for experimentation, TV service departments, amateur use, and special purposes. Uses regular ROHN tower sections with kit. Now available in standard No. 10 tower to 50', and in ROHN No. 30 & No. 40 towers for heavy-duty use.



ALSO a full line of ROHN ACCESSORIES

Rotor posts, house brackets, eave brackets, peak and flat roof mounts, instant drive-in bases, hinged base sections, telescoping mast bases, guying brackets, UHF antenna mounts, erection fixtures, variety of mounts and supports for masts or tubing,

tower installation accessories, TV service tables, mast and TV hot-dipped galvanized tubing, guy rings, "twister-anchors", rubber tower grommets, insulator sections, hinged rotor platform, accessory shelf and platform and dozens of other items. Get the complete catalog TODAY!

ROHN Manufacturing Company

116 LIMESTONE, BELLEVUE
PEORIA, ILLINOIS

MAIL THIS COUPON FOR FREE LITERATURE!

Rohn Manufacturing Company
116 Limestone, Bellevue
Peoria, Illinois

Gentlemen: Please rush me complete details on the full line of Rohn Towers and Accessories.

Firm _____

Name _____ Title _____



Address _____

City _____ State _____

shift into high gear...

with **CLAROSTAT GREENOHM**®

Wire Wound Resistors

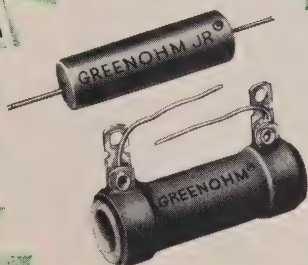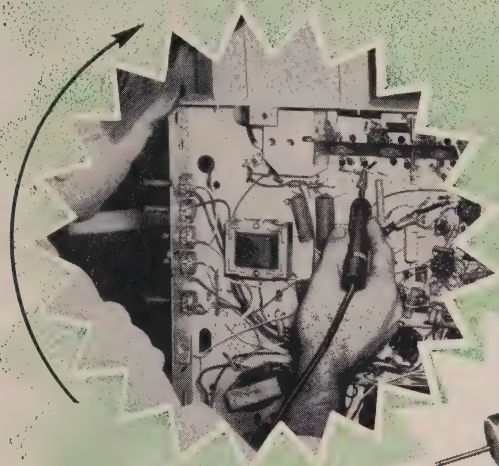

Jobs are done **quicker, better,**
more profitably, with the **right** components.

With **CLAROSTAT GREENOHM** wire-wound resistors you get the complete range of resistances and wattages in both fixed and adjustable. Ideal for radio and television service work when replacing original equipment such as strip-type voltage dividers or regular power resistors.

Best of all, **GREENOHM** resistors won't let you down after the job is completed.

So, **shift into high gear.** Do your servicing quickly and surely with **GREENOHM** resistors. Ask your distributor for complete details on these **GREENOHM** resistors and other service-designed **CLAROSTAT** products.

CLAROSTAT MFG. CO., Inc. • DOVER, NEW HAMPSHIRE
In Canada: Canadian Marconi Co., Ltd., Toronto 4, Ont.


ATTENTION MEN 17 to 55

HERE'S A NEW
OPPORTUNITY
FOR YOU!



PREPARE AT
HOME FOR A
PROFITABLE
CAREER IN

AUTOMATION ELECTRONICS

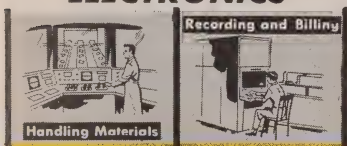

Get in on the Ground Floor of this Fast-Moving Field

Get the right training, and you'll "get places"—with opportunity for money, security and advancement—in Automation Electronics. Automation is already established in many plants. More factories and offices are adding electronic equipment right along. Who's to install, operate and maintain it? You—with the correct training!

HOME MOVIES Praised

"The Congressional Record" records how DTI was praised in Congress for its method of training thousands of men for careers in Television—Radio—Electronics by using movies, experiments, and other valuable aids—a method we've successfully followed for the past 25 years. And now for Automation Electronics, too, you train at home in spare time, or at our big laboratories in Chicago, among America's finest. No previous technical experience or advanced education required.

MILITARY SERVICE—If you are subject to Military Service, we have valuable information for you.

A REAL EMPLOYMENT SERVICE! We help you get started when your training is completed.

GET FREE BOOKLET!

MAIL COUPON TODAY!

DeVry Technical Institute, Dpt. RE-9A-M
4141 Belmont Ave., Chicago 41, Ill.

Please give me information about Automation-Electronics, and how you may help me.

Name _____ Age _____

Street _____ Apt. _____

City _____ Zone _____ State _____

1042A DTI's training is also available in Canada

DeVRY TECHNICAL INSTITUTE

Formerly DeForest's Training, Inc.
Chicago 41, Illinois

(Member National Home Study Council)



Correspondence



MORE ON DO-IT-YOURSELF

Dear Editor:

Mayhaps the fact that I live in the wild West has some influence on my thoughts, although my doubts as to this will be better borne out by any other letters you get in dissent with Mr. Margolis' article, "Dealing With Do-It-Yourself" (April, 1956).

Basically this article points out the selfish and egotistical attitude of many service technicians and one that causes them a considerable loss in volume. I have been bitten by the do-it-yourself bug and I think that it is safe to say that we all tinker a bit with plumbing, wiring, our cars, paint, woodworking, ad infinitum. All these other things could be done by a professional. Yet in our desire to do something by ourselves, and save a buck or two in the process, we all dabble at times.

So let us not climb up on a lofty perch and scream that the soul that tinkers with his TV set is akin to a leper or should be dealt with severely. He is usually a normal guy. Let me warn you! Treated wrongly by you, he will eventually benefit a TV service technician, but it won't be you if you were the only one within 100 miles.

The do-it-yourselfer figures he is not as sharp as the TV man but he has a lot of time he could waste for that \$5 call. And since he has heard how most of his trouble will be a tube, next time maybe he could handle the job, have fun and save the service call.

Here precisely is the point of perhaps no return for some service technician. Bite him, belittle him, cuss him or what, this adolescent period of the TV owner's formative years is very important. He must learn to have, not only confidence in you, but more important: trust. The embryonic set owner has several paths from which to choose at this point and they will mean a difference in money in your till.

Educate him to help with the non-technical problems and he will relieve you of a lot of routine jobs and you will still be in line for that big one coming up. Show him if you can the underside of a set on your bench, show him and demonstrate the easy way he can foul things up so that when in doubt he doesn't experiment. Educate him and win a friend and customer; alienate him and lose all.


ROBERT M. LOHR

Lohr's Lectronic Lab
Bridgeport, Wash.

(Careful consideration of some of
(Continued on page 18)

Merit

FIRST IN EXACT REPLACEMENT.

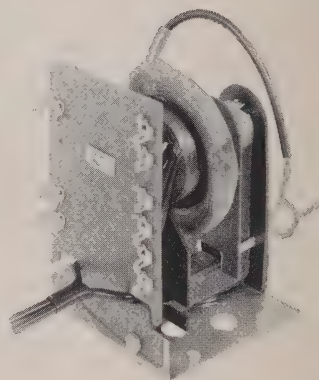


HVO-47 FOR EXACT REPLACEMENT in ANDREA, ARVIN, DUMONT, HOFFMAN, KAYE-HALBERT, PACIFIC MERCURY, PACKARD BELL, SILVERTONE, STROMBERG-CARLSON, TECH-MASTER . . . another in the complete Merit line of exact and universal transformers, yokes and coils. Merit is the only manufacturer of transformers, yokes and coils who has complete production facilities for all parts sold under their brand name.

Merit

MERIT COIL & TRANSFORMER CORP.
4427 N. CLARK ST., CHICAGO 40, ILL.

RADIO-ELECTRONICS

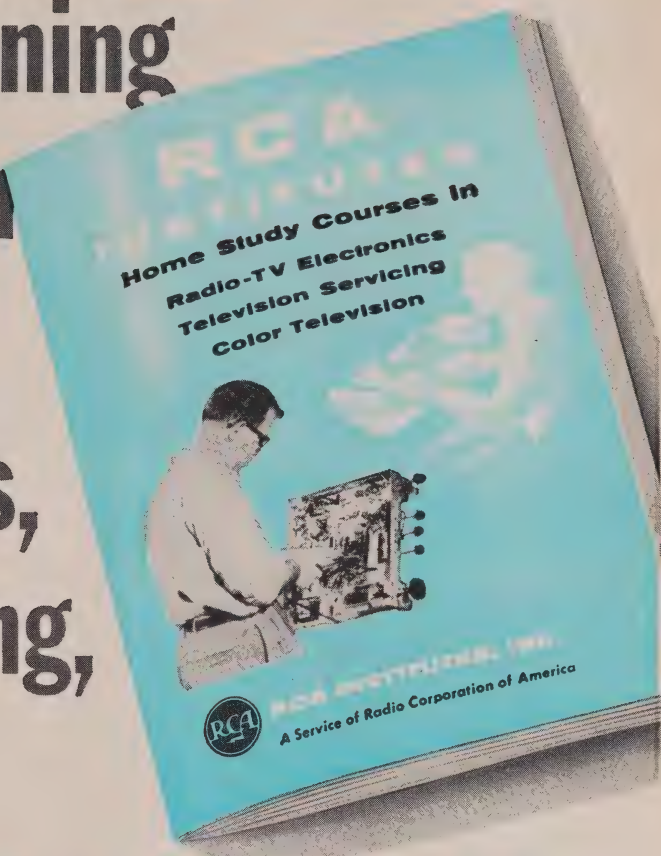RCA offers you the finest training at home in Radio-TV electronics, TV servicing, Color TV



SEND FOR THIS FREE BOOK NOW!



RCA INSTITUTES, INC.
A SERVICE OF RADIO CORPORATION OF AMERICA
350 WEST FOURTH STREET, NEW YORK 14, N.Y.

The instruction you receive and equipment you get (and keep) will start you on your way. Pay-as-you-learn. You pay for only one study group at a time. This 52 page book contains complete information on Home Study Courses for the beginner and the advanced student.

RCA Institutes, Inc., Home Study E-96,
350 West Fourth Street New York 14, N. Y.
Without obligation, send me FREE CATALOG
on Home Study Courses in Radio, Television
and Color TV. No salesman will call.

Name Please Print

Address

City Zone State



FOR THOSE WHO RECOGNIZE QUALITY

TRIO'S 1957

ZEPHYR ANTENNAS

FOR DISTANCE



THE POWER PACKED PAIR

FOR EXTREME DISTANCE



Zephyr

THE POWER PACKED THREESOME

FOR THE MAXIMUM



ZEPHYR
ROYAL

THE POWER PACKED FOURSOME

featuring the

WING
DIPOLE

WING
DIRECTOR

DOUBLE TRANSPOSITION
PHASING

STAGGER TUNING

REJECTOR PHASING



COPYRIGHT 1956 TRIO MFG. CO.

EXPORT SALES DIV. KODAK INTERNATIONAL, INC., 225 N. LaSalle Ave., Chicago, ILL. 6. Phone RA-4400, N.Y. 10007

you
wouldn't
buy




yet that may be all your present system reproduces!

Recent improvements in high-fidelity recording have captured the full tonal color of every instrument in the orchestra... every subtle shading from the brilliance of the violins to the deep roll of the kettle-drums is impressed on discs made with the latest recording techniques. Yet this dazzling other-world of sound may be *beyond the capacity* of your present high-fi equipment... in terms of sound reproduction, *you may be buying only half a record!*

PICKERING professional-quality components—*the best that money can buy*—recreate *all* of the music on fine microgroove recordings—give you the richness of reality that makes listening the extreme pleasure you have dreamed about... but never experienced.

PICKERING components include the world-renowned "FLUXVALVE" magnetic cartridge with one-mil or half-mil diamond styli... the Pickering 410 Audio Input System, combining preamplifier, record compensator, and equalizer network (each of which is available separately)... the famed Pickering Model 190-D distortion-free tone arm... and the revolutionary new PICKERING ISOPHASE electrostatic SPEAKERS, which reproduce music so faithfully *they must be heard to be believed!*

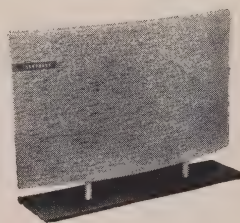

PICKERING & CO., INC. OCEANSIDE, N. Y.

Professional Audio Components

"For those who can hear the difference"

... Demonstrated and sold by Leading Radio Parts Distributors everywhere. For the one nearest you and for detailed literature, write Dept. P-12 EXPORT: AD. AURIEMA, INC., 89 BROAD ST., NEW YORK / CANADA: CHARLES W. POINTON LTD., 6 ALCINA AVE. TORONTO

Chamber Music Society

invites you ... to take any one of these sets of great chamber works



The Pascal String Quartet, one of the world's foremost chamber music ensembles is among the distinguished groups recording for the Society.

FREE

NO STRINGS ATTACHED

Long Playing

SCHUBERT

"TROUT" QUINTET (A MAJOR)
QUARTET IN E MAJOR, Op. 125, No. 2
QUARTET IN C MINOR, "QUARTETTSATZ"

Brilliant readings by the Winterthur String Quartet. Pianist Ping Pong joins them in the "Trout" Quintet.

ITALIAN MASTERS

OF THE XVIII CENTURY


TARTINI: Sonata in G Minor, "The Devil's Trill"
VIVALDI: Sonatas in A Major and F Minor
GEMINIANI: Sonata in B Flat Major
VITALI: Chaconne in G Minor

The celebrated violin virtuoso, Riccardo Odnoposoff, is heard in some of the greatest violin music of the Eighteenth Century.

MOZART

CLARINET QUINTET IN A MAJOR, K. 581
FLUTE QUARTET IN D MAJOR, K. 285
FLUTE QUARTET IN A MAJOR, K. 298

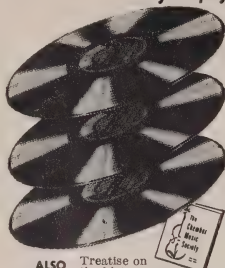Some of the most satisfying music ever written. With Peter Stimenauer, clarinetist, Judith Baker, flutist, and the Pascal String Quartet.



ALSO FREE
Treatise on the history, technique and performance of Chamber Music—from 16th Century origins to today.

Unique Transcription Recordings —

Custom-Pressed of Transparent Ruby-Red Vinyl, in De Luxe Genuine Linen Cases!

HERE is exciting news for every serious music listener! The Chamber Music Society asks you to choose one of these transcribed chamber programs: an all SCHUBERT collection ... or a group of works by four 18th Century ITALIAN MASTERS ... or a MOZART program—as a FREE GIFT. There is no requirement to buy another record from the Society, now or ever!

These are NOT ordinary recordings. Produced by a process hitherto used only for radio transcriptions with tone fidelity from 50 to 15,000 cycles, each Chamber Music Society transcription is pressed on the finest transparent ruby-red vinylite and jacketed in an exquisite linen slip-cover for permanent protection!

Save More than 50% of Usual Retail Cost

When you become a Trial Member of the Society you also have the right to AUDITION—Free of Charge—any or all of the Chamber repertoire listed below ... ranging through three centuries—from Purcell to Hindemith. These superb transcription recordings will be available to members at the rate of about two a month. Only those you decide to keep are billed to you at the Members' low price, which is less than 50% of the cost of similar commercial discs. You may withdraw at any time; in fact, you are not obligated to buy any records at all, unless you wish.

The FREE GIFT you choose is yours to keep in any case! Send the coupon today.

MAIL COUPON—WITHOUT MONEY—TO

The Chamber Music Society, Dept. REL-9, 45 Columbus Ave., N. Y. 23

(Cross out only those you do not want to audition)

Selections are not listed by order of release

Rush me FREE, the long-playing Chamber Program described above. (check one)

- ☐ Italian Masters ☐ Mozart
☐ Schubert

—mine to keep absolutely free, without any obligation.

I have crossed out at the right the Chamber Works I already own. I need do nothing more to enjoy the others in my home for Free Audition, delivered without charge (approximately two 33 1/3 R.P.M. discs a month).

I am not obligated to buy another recording, ever! I may try all Society releases for 5 days, and will be billed only for those I keep at the low membership prices shown below (plus a few cents shipping), a saving of over 50%. I may return any disc and pay nothing. I may cancel my Trial Membership at any time. The FREE GIFT Program is mine to keep in any case.

Name.....

Address.....

City.....Zone.....State.....

© 1956 CHS, INC., N. Y.

1. ITALIAN MASTERS OF THE XVIII CENTURY (see above)
2. MOZART (see above)
3. SCHUBERT (see above)
4. BEETHOVEN: String Quintets Op. 29 and 104
5. SCHUBERT: Duo Concertante in A, Op. 162
6. SONS OF BACH: C.P.E. Bach: Sinfonia in C; J.C. Bach: Sinfonia in B Flat and D; W.F. Bach: Sinfonia in D Minor
7. TCHAIKOVSKY: Quartet No. 3 in E Flat
8. MOZART: The Complete (6) String Quintets (3-12" discs)
9. BRAHMS: Violin Sonata No. 1 in G; Cello Sonata No. 1 in E Minor
10. DEBUSSY: Quartet in G; Duo for Flute, Viola and Harp; Sonata for Violin and Piano
11. HANDEL: Complete Water Music
12. BEETHOVEN: Complete Rasmovsky String Quartets (2-12" discs)
13. A. SCARLATTI: Sinfonias Nos. 4 and 5; Concerti Grossi Nos. 1 and 3
14. MOZART: 3 Salzburg Serenades
15. HINDEMITH: 4 Sonatas for Trumpet and Piano; Viola and Piano; Clarinet and Piano; Bassoon and Piano
16. DVORAK: Piano Quartet in E Flat; Trio in F
17. SCHUBERT: Death and the Maiden Quartet; Variations for Flute and Piano
18. VIVALDI: Il Cimento Dell'Armonia, E Dell'Invenzione (2-12" discs)
19. BRAHMS: Clarinet Quintet in B
20. HAYDN: Seven Last Words of Christ
21. STRAVINSKY: Duo Concertante; Pulcinella Suite
22. PURCELL: Fantasias in 4 Parts
23. MOZART: Complete Piano Trios (2-12" discs)
24. SCHUMANN: Piano Quintet in E Flat; Quartet in A
25. BACH: 4 Sonatas for Violin, Cello and Harpsichord
26. BARTOK: Quartet No. 4; Violin Sonata No. 2
27. CORELLI: Concerti Grossi, Op. 6, Nos. 1, 2, 3 & 4

MEMBERSHIP PRICES

- 1 disc set (appr. 1 hour) \$2.95
2 disc set (appr. 2 hours) \$5.90
3 disc set (appr. 3 hours) \$7.95

(Continued from page 14)

the points brought up by Mr. Lohr may well repay the service technician for the time involved. But a careful re-reading of "Dealing With Do-It-Yourself" indicates that Lohr and Margolis may not be so far apart, after all.—Editor)

CLASSIFYING TRANSISTORS

Dear Editor:

I have been recently spending considerable time studying transistors just to familiarize myself with this important new branch of electronics and to be ready when it attains widespread use. I think I now have a good knowledge of the physics and the electronic applications of transistors.

However, what appears to me to be a serious deficiency in this field is the lack of uniformity in classifying transistors as to types. Most companies appear to have their own designation and I have been unable to find a hint suggesting unification. If we consider that we are just at the beginning, there is good reason for concern as to how messed up things can get.

Why don't manufacturers agree on some uniform classification, as they have with tubes. For example, they could evolve a system in which the first letter of a transistor type will indicate whether it is n-p-n or p-n-p. A second letter or number can indicate the transistor's function (af, rf, power, etc.). Additional numbers or letters can indicate important parameters such as cutoff frequency.

The entire situation can easily become even more confused if future developments produce transistors that vary widely in basic design, such as triodes, tetrodes, pentodes and other types. Thus, now is the time to set up a system of classification.

This is just a suggestion and most likely a more elaborate scheme can be laid out. At any rate some consideration should be given to the technician who will soon be called upon to service transistorized circuits and will not have transistors of every make nor an elaborate cross-indexing systems.

SERGIO CLEMENTI

Caracas, Venezuela

A HOBBYIST'S VIEW

Dear Editor:

I read RADIO-ELECTRONICS because radio and television is my hobby. I do some repair work and have no dissatisfied customers. In connection with this I would like to voice my opinion against licensing.

I couldn't afford to pay a big fee for a license. In the little servicing I do I seek only to break even and maintain my hobby. I am sure there are thousands in a situation similar to mine. Personally, I think that if a service technician is afraid he cannot hold his customers he had better try another occupation.

R. BAILEY


Holt, Mich.

END

You Can Train at Home for Good Pay Jobs in RADIO-TELEVISION

Fast Growing Industry Offers Good Pay, Security, Bright Future

LESSON AND CATALOG FREE MAIL CARD

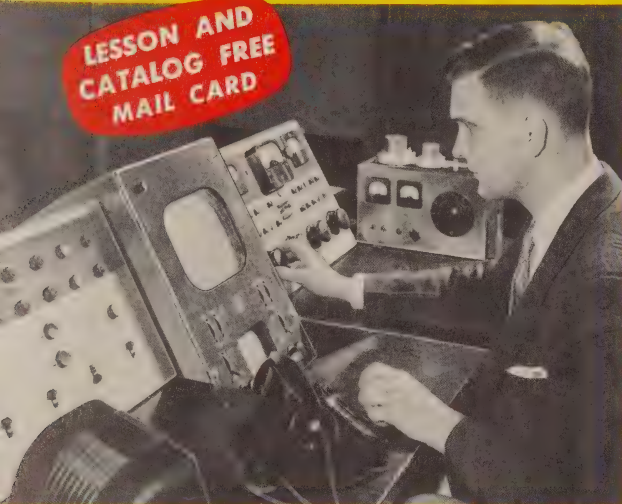

Training PLUS OPPORTUNITY is the ideal combination for success. Today's OPPORTUNITY field is Radio-Television. Over 125 million home Radios plus 30 million sets in cars and 40,000,000 Television sets mean big money, opportunity for trained Radio-Television Technicians. More than 4,000 Radio and TV Broadcasting stations offer interesting and important positions for technicians, operators. Color Television, portable TV sets, Hi-Fi, other developments assure future growth. Radio, Television are both growing. Need for trained technicians is increasing!




**J. E. SMITH
Founder**

Find Out What Oldest and Largest Home Study Radio-Television School Offers You

Since 1914—for more than 40 years—N.R.I. has been training ambitious men at home in spare time for Radio-TV. Thousands of successful graduates say N.R.I.'s 50-50 training method is a fast, easy, effective way to higher earnings, desirable jobs. Carefully planned experiments and practice with equipment supplied free of extra charge, bring basic principles, techniques to life right in your own home. Find out what dependable training can do for you.

You Learn by Doing—Get Practical Experience with Kits N.R.I. Sends

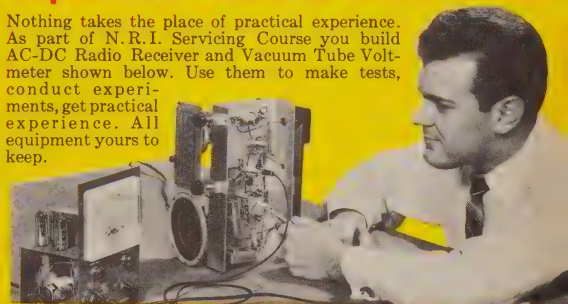
Nothing takes the place of practical experience. As part of N.R.I. Servicing Course you build AC-DC Radio Receiver and Vacuum Tube Voltmeter shown below. Use them to make tests, conduct experiments, get practical experience. All equipment yours to keep.



Add to Your Income Starting Soon

Make \$10-\$15 a Week Extra Fixing Sets in Your Spare Time

Soon after enrolling, many N.R.I. students start earning extra money fixing neighbors' radio sets. Many earn enough extra to pay entire cost of course and provide capital to start their own full time Radio-TV business after getting N.R.I. Diploma. If you want a job with a future, find out how you can train at home for Radio-Television. Mail Postage Free postcard for Sample Lesson. See how practical it is to learn at home. Get 64-Page Catalog, too. See equipment you get, outlines of courses, facts about opportunities in this growing field. Prices of N.R.I. Courses are low, terms easy.

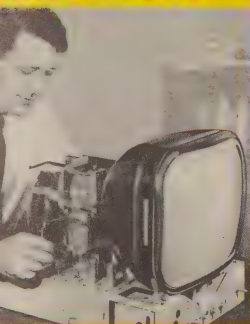

N.R.I. Training leads to good pay jobs like these. BROADCASTING: Chief of Technician, Chief Operator, Remote Control Operator. **SERVICING:** Home and Auto Radios, P. A. Systems, Television Receivers, Electronic Controls, FM Radios, Hi-Fi. **SHIP AND HARBOR RADIO:** Chief Operator, Assistant Operator, Radiotelephone Operator. **POLICE RADIO:** Transmitter Operator, Receiver Serviceman. **GOVERNMENT RADIO:** Operator in Army, Navy, Marine Corps, Coast Guard, Forestry Service, Weather, Airways Radio Operator. **IN RADIO PLANTS:** Design Assistant, Transmitter Design Technician... **AND MANY OTHERS.**

N.R.I. TRAINED THESE MEN

Starts N.R.I. for Good Start

"Right now I am doing spare-time repairs on Radios and Television. Going into full time servicing soon." **C. HIGGINS,** Waltham, Mass.

Engineer with Station WHPE

"I operated a successful Radio repair shop. Then I got a job with WPAQ and now I am an engineer for WHPE." **VAN W. WORKMAN,** High Point, N. C.

Quit Job to Start Business

"I decided to quit my job and do TV work full time. I love my work and am doing all right financially." **W. F. KLINE,** Cincinnati, Ohio

N.R.I. Started His Way up

"I was a cab driver earning \$35 a week. Then I enrolled with N.R.I. Now tester with TV maker." **J. H. SHEPHERD,** Bloomington, Ind.



CUT OUT AND MAIL CARD NOW

SAMPLE LESSON AND CATALOG BOTH FREE

**NO STAMP NEEDED!
WE PAY POSTAGE**

This card entitles you to Actual Lesson on Servicing, shows how you learn Radio-Television at home. You'll also receive 64-Page Catalog.

**NATIONAL RADIO INSTITUTE, Dept. F
Washington 9, D. C.**


Please mail me the FREE sample lesson and 64-Page Catalog. (No Salesman will call.)

Name.....Age.....

Address.....

City.....Zone.....State.....

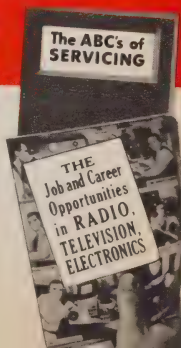Approved Member, National Home Study Council




Practice Servicing-Communications with Kits of Parts N.R.I. Sends




YOU BUILD AC-DC Superhet Receiver

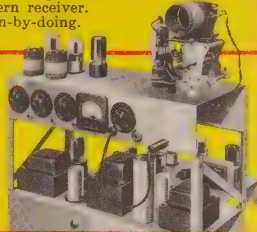N.R.I. Servicing Course includes all needed parts. By introducing defects you get actual servicing experience practicing with this modern receiver. Learn-by-doing.



YOU BUILD Broadcasting Transmitter

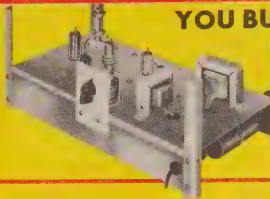As part of N.R.I. Communications Course you build this low power Transmitter, learn commercial broadcasting operators' methods, procedures. Train for your FCC Commercial Operator's License.



YOU BUILD Signal Generator

You build this Signal Generator. Learn how to compensate high frequency amplifiers, practice aligning typical I.F. amplifiers in receiver circuits. Make tests, conduct experiments.


YOU BUILD Vacuum Tube Voltmeter

Use it to earn extra cash fixing neighbors' sets; bring to life theory you learn from N.R.I.'s easy-to-understand texts.




Radio-Television Can Give You a Good Job with a Future

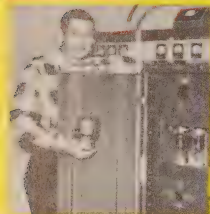N.R.I. Graduates do Important Work — Get Important Pay



Chief Engineer with Station

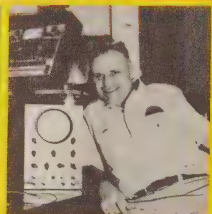"I am Chief Engineer of Station KGCN in Mandan, N. D. I also have my own spare time business servicing high frequency, two-way communications systems." R. BARNETT, Bismarck, N. D.



Paid for Instruments out of Earnings

"I am doing very well in spare time TV and Radio. Sometimes have three TV jobs waiting and also fix car Radios for garages. I paid for instruments out of earnings." G. F. SEAMAN, New York, N. Y.



Has Own Radio-TV Business

"We have an appliance store with our Radio and TV servicing and get TV repairs. During my Army service, N.R.I. training helped get me a top rated job." W. M. WEIDNER, Fairfax, S. D.

Here is a line of work that people respect—a vocation where you can advance, win a place for yourself, earn good pay and gain much personal satisfaction in what you are able to do. And you can learn at home in your spare time. Smart fellows everywhere are using their spare time to develop new knowledge, new skills. They know it is the trained man who gets ahead, gets the better job, drives the better car, is respected for what he knows and can do.

Be a Skilled Technician

The technical man is looked up to. He should be. He does important work, gets good pay for it. Radio-Television offers that kind of work. There are more than 40 million Televisions, 150 million home and auto Radios. Millions more are sold each year. There are splendid opportunities for the man well trained in Radio-Television Servicing or Broadcasting. Micro-Wave Relay, Aviation and Police Radio, Two-Way Communications for buses, taxis, trucks, etc. are expanding—making more jobs, greater opportunity.

You Can Train in Spare Time

Keep your job until you're ready for a better one. Learn at home. N.R.I. Courses are planned for men who can study only during spare time. You get many kits to build equipment, get practical experience. You work on circuits common to both Radio and TV. Equipment you build "brings to life" things you learn in N.R.I.'s easy-to-understand texts. Experienced N.R.I. instructors, technicians, specialists devote full time to making sure you get the best and simplest Radio-TV training. Train as fast or as slow as you like.

Tested Way To Better Pay

N.R.I. Training is practical, thorough. You get the benefit of N.R.I.'s 40 years experience training men for success in Radio-Television. Most successful N.R.I. men start without any knowledge of Radio, many without a high school education. Find out what Radio-Television training can mean to you. Make a decisive move today toward becoming one of that select group—a Radio-TV Technician. Send for Actual Lesson and 64-Page Catalog, both FREE. NATIONAL RADIO INSTITUTE, Dept. F, Washington, D.C.

See Other Side

FIRST CLASS

Permit No. 20-R
(Sec. 34.9, P. L. & R.)
Washington, D. C.

BUSINESS REPLY CARD

No Postage Stamp Necessary If Mailed In The United States

POSTAGE WILL BE PAID BY





NATIONAL RADIO INSTITUTE

16th and U Sts., N. W.

Washington 9, D. C.

SAMPLE LESSON AND CATALOG BOTH FREE

CUT OUT AND MAIL POSTAGE-FREE CARD

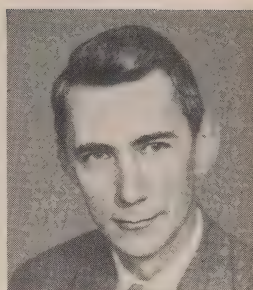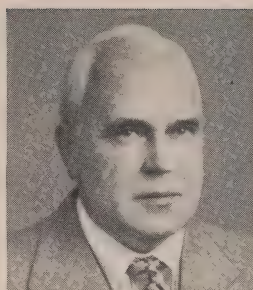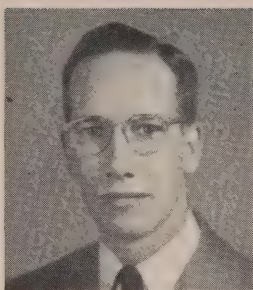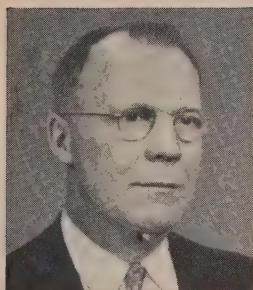

WARREN A. ARISSON. Tompion Gold Medal, Worshipful Company of Clockmakers of the City of London, for pioneer work on development of quartz crystal oscillators as precision standards of time.



W. G. PFANN. Mathewson Gold Medal, American Institute of Mining and Metallurgical Engineers, for discovery of and pioneering research in zone melting.

H. T. FRIIS. Medal of Honor, Institute of Radio Engineers and Valdemar Poulsen Gold Medal, Danish Academy of Technical Sciences; important work in application of short and ultra-short radio waves.

CLAUDE E. SHANNON. Stuart Ballantine Medal, Franklin Institute of the State of Pennsylvania, for contributions to a comprehensive theory of communication.



$$C = W \log_2 (1 + \frac{S}{N})$$

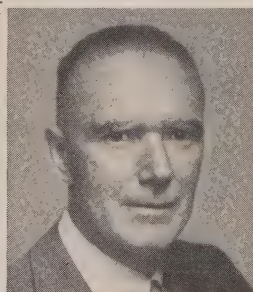
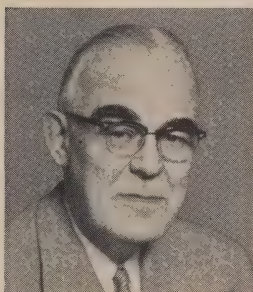


AXEL G. JENSEN. David Sarnoff Gold Medal, Society of Motion Picture and Television Engineers, for technical contributions to television; G.A. Hagemann Gold Medal for Industrial Research, Royal Technical College, Copenhagen.



PIONEERS OF PROGRESS

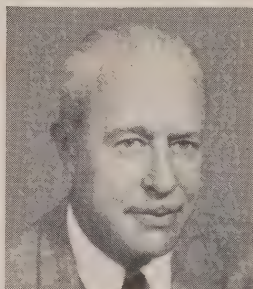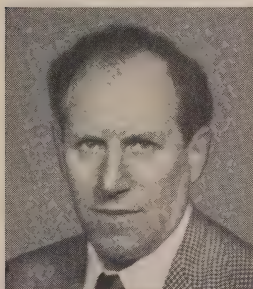H. F. DODGE. Shewhart Medal, American Society for Quality Control, for original contributions to the art of statistical quality control.



R. KOMPNER. Duddell Medal, Physical Society of England, for his original work on the traveling wave tube.

WALTER H. BRATTAIN. Co-winner with Dr. John Bardeen of John Scott Medals, City of Philadelphia, for invention of the transistor.



These are some of our recent medal winners at Bell Laboratories. The awards they have won symbolize recognition for outstanding achievement in the many sciences that bear on telephony. Bell Labs is extremely proud of them—and of the thousands of scientists and engineers who work with them to keep the American telephone system the greatest in the world.



**BELL TELEPHONE
LABORATORIES**

WORLD CENTER OF COMMUNICATIONS RESEARCH AND DEVELOPMENT

RIDER BOOKS HELP YOU LEARN MORE... DO MORE... EARN MORE!

7 NEW Rider Books Published in July and August

ARITHMETIC FOR ENGINEERS (5th Edition, Revised)

by Charles B. Clapham
An outstanding text on practical elementary mathematics for shop machinists, shop mechanic trainees, tool and die maker trainees, mechanical engineering students at the industrial level, mechanical drafting trainees . . . and all others who want to learn the elementary mathematics of Mechanics.
Written for use in schools and for home study. Ideal for industrial upgrading.
More than 390 numerical examples of solutions fully explained. More than 1,950 problem exercises. Answers to problem exercises.
Cloth Bound, 558 pp., 5½ x 8½", illus.
#183 Only \$6.50

TV MFRS' RECEIVER TROUBLE CURES Vol.8

Edited by M. Snitzer
Volume 8 in the series. Devoted to the official design laboratory cures for "bugs" which may be encountered in TV receivers. The cures are positive! The troubles are identified and correlated with specific receiver chassis and models. The most accurate and authentic information on TV receiver trouble cures.
Volume 8 content is NEW. Deals with manufacturers from RCA to Zenith.
Soft Cover, 128 pp., 5½ x 8½", illus.
#143-8 Only \$1.80

RADIO RECEIVER LABORATORY MANUAL by Alex W. Levey, B.A., M.S.

A workbook of experiments designed for students of radio and radio servicing. Covers the construction, analysis, testing, and repair of a radio receiver. Acquaints the student with necessary servicing equipment. There are 33 experiments in all, including 6 demonstration experiments. Soft Cover, 110 pp., 8½" x 11", illus.
#178 Only \$2.00

TV TROUBLESHOOTING & REPAIR GUIDE BOOK

by R. G. Middleton
VOLUME 1: For the serviceman requiring practical, down-to-earth servicing information on TV troubles and their cures. Shows how to spot symptoms through the use of picture tube patterns and scope waveforms. Much valuable data on the use of test equipment, as well as simple techniques for troubleshooting outside the service shop. Soft Cover, 204 pp., 8½ x 11", illus.
#140 Only \$3.90
VOLUME 2: A gold mine of information on troubleshooting front ends, servicing the video I-F strips, faults in video amplifiers, trouble analysis in sound I-F and detector systems, etc. Soft Cover, 160 pp., 8½ x 11", illus.
#140-2 Only \$3.30

TV MFRS' RECEIVER TROUBLE CURES

edited by M. Snitzer
Gives you specific TV receiver troubles, and the cures specified by the set manufacturer. Listings are by manufacturer, model and chassis number. Saves you time, helps you earn more! Soft Cover, 5½ x 8½", illus., each volume over 116 pp.
VOL. 1: Covers complete details on sets produced by mfrs (listed in alphabetical order) from Admiral to Dumont. Only \$1.80
VOL. 2: Covers mfrs from Emerson to Jackson. Only \$1.80
VOL. 3: Covers mfrs from Kaye-Halbert to Philco. Only \$1.80
VOL. 4: Covers mfrs from Philharmonic to Shaw. Only \$1.80
VOL. 5: Covers mfrs from Spartan to Zenith. Only \$1.80
VOL. 6: All new coverage, through 1954, no duplications. Admiral to Firestone. Only \$1.80
VOL. 7: New coverage, from General Electric to Raytheon. Only \$1.80
VOL. 8: Just published. New coverage, from RCA to Zenith. Only \$1.80
#143-8 Only \$1.80

PICTURE BOOK OF TV TROUBLES, Vol. 6 (Horizontal and Vertical Sync Circuits)

by Rider Lab Staff

Volume 6 of an extremely popular practical series. Illustrates the incorrect waveforms and picture tube patterns for defective components in TV receivers. Components are identified. This book teaches the recognition of symptoms of faults in horizontal and vertical sync circuits. Correct waveforms and schematics are also shown.
Does your trouble shooting for you!
Soft Cover, 128 pp., 5½ x 8½", illus.
#168-6 Only \$1.80

BASICS OF PHOTOTUBES AND PHOTOCELLS by David Mark

Phototubes and photocells are prominently used in a great many applications of electronic devices. Science, industry, government agencies, television, and many communication facilities employ them. This book is devoted to the explanation of the principles and practices surrounding phototubes and photocells with the utmost in visual presentation to make the subject most understandable. It is tantamount to a "picture course" . . . yet it is authoritative and modern.
Soft Cover, 136 pp., 5½ x 8½", illus.
#184 Only \$2.90

PICTURE BOOK OF TV TROUBLES by Rider Lab. Staff

A fabulous series of definitive, practical books that teach the recognition of faults in TV receivers. Shows incorrect waveforms and resultant picture tube patterns caused by defective components, which are identified. Correct waveforms and schematics are also shown. Used in many TV schools and by tens of thousands of technicians. Soft Covers, 5½ x 8½", illus.

- VOL. 1: HORIZONTAL AFC-OSCILLATOR CIRCUITS
#168, 80 pp. Only \$1.35
- VOL. 2: VERTICAL SWEEP-DEFLECTION CIRCUITS
#168-2, 96 pp. Only \$1.80
- VOL. 3: VIDEO I-F & VIDEO AMPLIFIER CIRCUITS
#168-3, 96 pp. Only \$1.80
- VOL. 4: AUTOMATIC GAIN CONTROL CIRCUITS
#168-4, 96 pp. Only \$1.80
- VOL. 5: HORIZONTAL OUTPUT & H-V CIRCUITS
#168-5, 108 pp. Only \$1.80
- VOL. 6: HORIZONTAL & VERTICAL SYNC CIRCUITS
#168-6, 120 pp. Only \$1.80



TELEVISION—HOW IT WORKS (2nd Edition)

by J. Richard Johnson

A completely rewritten, up-to-the-minute edition of an authoritative and informative book. It is the newest and most comprehensive text on the subject, and follows the progress of the received signal from the antenna to the picture tube and loudspeaker. Leather Finish MARCO Cover, 352 pp., 5½ x 8½", illus.
#101 Only \$4.50
#101-H, Cloth Bound Only \$5.50

HANDBOOK OF 630-TYPE TV RECEIVERS

by Miller & Bierman
Deals with all versions of the famous 630-type receivers made up to 1955. Explains modifications and circuit improvements made by various manufacturers, and includes 26 pages of troubleshooting charts. A book every technician can use to major advantage! Soft Cover, 200 pp., 5½ x 8½", illus.
#174 Only \$3.50

ELECTRONICS TECHNOLOGY SERIES

edited by A. Schnure, Ph.D., Ed.D.
Written for students, technicians, experimenters, hams, trainees in electronics technology, and all others interested in communication electronics. Soft Covers, 5½ x 8½", illus.

WAVE PROPAGATION

The eleventh book in the series. Devoted to the fundamental theory underlying the propagation of electromagnetic radiations; generation, propagation, sky wave, ground wave, effect of atmosphere, and scatter. Review questions, Index.
#166-11 Only \$9.00

SUPERHETERODYNE CONVERTERS AND I-F AMPLIFIERS

The twelfth book in this series. Deals with the basic principles of superheterodyne operation; the behaviour of converters and mixers; I-F amplifiers and the methods of alignment. Review questions, Index.
#166-12 Only \$9.00

INVERSE FEEDBACK

The fifteenth book in the series. Devoted to this highly important phase of electronics which is finding more and more application every day in all kinds of electronic devices. Review questions, Index.
#166-15 Only \$9.00

INTRODUCTION TO COLOR TV (2nd Edition)

by Kaufman & Thomas
A revised, up-to-date edition of a best seller in books on TV. New edition contains full information on the latest and larger screen picture tubes, simplified receiver circuitry, etc. Most up-to-date introduction to color television available. Soft Cover, 160 pp., 5½ x 8½", illus.
#156 Only \$2.70

COLOR TELEVISION RECEIVER PRACTICES

by Hazeltine Corp. Lab. Staff
Prepared by experts, this book covers every major aspect of color TV receivers, including the latest 21" picture tube and its required circuitry. For anyone who wishes a solid grounding in color television, this volume is ideal. Destined to become a standard reference work on the subject. Soft Cover, 208 pp., 5½ x 8½", illus.
#162 Only \$4.50
#162-H, Cloth Bound Only \$6.00

TV REPAIR QUESTIONS & ANSWERS

by Sidney Platt
A very practical series of questions and answer books on the repair of TV receivers. Each covers a separate section of the receiver, and the series follows the same sequence that the signal itself travels. Soft Covers, 5½ x 8½", illus.

- #173, FRONT ENDS:
128 pp. Only \$2.10
- #173-2, VIDEO CIRCUITS:
128 pp. Only \$2.10
- #173-3, SYNC & SWEEP CIRCUITS:
140 pp. Only \$2.10
- #173-4, DEFLECTION & H-V CIRCUITS:
128 pp. Only \$2.10
- #173-5, SOUND & L-V CIRCUITS:
128 pp. Only \$2.10

ADVANCED TELEVISION SERVICING TECHNIQUES

by RETMA
A complete advanced TV servicing course, developed by the Radio-Electronics-Television Manufacturers Association, and made available to you at the incredibly low price of \$4.55, complete! Shows you how to use every conceivable type of test equipment, how to service every part of a TV receiver. Soft Cover, 8½ x 11".

- MAIN TEXT, 176 pp., illus. Only \$3.60
- #161, LABORATORY WORKBOOK, 32 pp. Only \$.95
- #161-2 Only \$.95

MORE THAN 2,000,000 Rider Published Books Have Taught Electronics Know-How! There Are Rider Books Which Fill YOUR Needs... At Least 3 NEW Titles Appear Each Month!



BASIC ELECTRICITY BASIC ELECTRONICS

BASIC SYNCHROS & SERVOMECHANISMS

by Van Valkenburgh, Nooger & Neville, Inc.
The fabulous picture-text books that teach faster and easier! The theory, principals and practice of electricity, electronics, synchros and servos, are here presented in a manner which permits a rapid grasp of the fundamentals of these vitally important subjects. Over 2,000 specially prepared illustrations present, explain and make every topic discussed picture clear.

BASIC ELECTRICITY

#169 Soft Cover: 5 volumes, 624 pp., 6 x 9"
Only \$9.00 per set

#169-H Cloth Bound: all 5 volumes in a single binding Only \$10.50

BASIC ELECTRONICS

#170 Soft Cover: 5 volumes, 550 pp., 6 x 9"
Only \$9.00 per set

#170-H Cloth Bound: all 5 volumes in a single binding Only \$10.50

BASIC SYNCHROS & SERVOMECHANISMS

#180 Soft Cover: 2 volumes, 270 pp., 6 x 9"
Only \$5.50 per set

#180-H Cloth Bound: both volumes in a single binding Only \$6.95

HOW TO TROUBLESHOOT A TV RECEIVER

by J. Richard Johnson

A book written for the newcomer, to aid in a systematic procedure for troubleshooting. An easily understandable, step-by-step guide. Soft Cover, 128 pp., 6 1/2 x 8 1/2", illus.

#152.....Only \$1.80

FUNDAMENTALS OF TRANSISTORS

by Leonard Krugman

Explains the BIG thing in electronics, today—the transistor! Written by one of the pioneers in transistor development, this book tells you all you need to know about this electronic miracle: basic operation, characteristics, performance, and application. Soft Cover, 144 pp., 5 1/2 x 8 1/2", illus.

#140.....Only \$2.70

HOW TO USE SIGNAL & SWEEP GENERATORS

by J. Richard Johnson

Discusses all types of signal and sweep generators, and their applications in AM, FM radio, and TV. Soft Cover, 144 pp., 5 1/2 x 8 1/2", illus.

#147.....Only \$2.10

UNDERSTANDING VECTORS & PHASE

by Rider & Usan

A book which makes for quick and easy understanding of radio theory, written for anyone in radio and electronics who has not had the advantage of technical training. Soft Cover, 160 pp., 5 1/2 x 7 1/4", illus.

#103.....Only \$.99

HOW TO USE TEST PROBES

by A. Ghirardi & R. Middleton

The only book of its kind, it covers all types of test probes used with VOM's, VTVM's, and scopes. Complete step-by-step explanations, with practical examples of results and effects. Soft Cover, 176 pp., 5 1/2 x 8 1/2", illus.

#165.....Only \$2.90

FM TRANSMISSION & RECEPTION

(2nd Edition)

by Rider & Usan

Covers FM broadcasting of all kinds, and explains the theory, functioning and servicing of various types of FM receivers, including TV receivers. Cloth Bound, 460 pp., 5 1/2 x 8 1/2", illus.

#102.....Only \$4.95

JOHN F. RIDER PUBLISHER, INC.

480 Canal St., New York 13, N.Y.

In Canada: Charles W. Pointon, Ltd.

6 Alcona Ave., Toronto, Ontario

HOW TO USE METERS

by John F. Rider

Explains everything about using meters of all kinds. Tells and shows what to use and what to measure. If you use meters, this is a book you cannot afford to pass by! Soft Cover, 144 pp., 5 1/2 x 8 1/2", illus.

#144.....Only \$2.40

ENCYCLOPEDIA ON CATHODE-RAY OSCILLOSCOPES & THEIR USES

by Rider & Usan

Fully and clearly describes the oscilloscope, its construction and capabilities. Covers a wide variety of scopes, including present day models. Profusely (3,000) illustrated. Cloth Bound, 1008 pp., 8 1/2 x 11".

#133.....Only \$11.50

ELECTRONICS TECHNOLOGY SERIES

edited by A. Schnure, Ph.D., Ed.D.

An economically priced series of books devoted to the explanation of the basic concepts and principles of individual phases of electronics technology. Each book deals with a specialized subject; groups of these books form broad categories in the study of electronics technology. Aimed for use by students in technical institutes, junior colleges, adult education classes, and vocational schools teaching electronics technology. The texts also are intended to serve the operators of communication equipments such as radio amateurs, commercial ship and broadcast station operators, electronics laboratory technicians, and experimenters who desire a more than casual understanding of the subjects covered.

Soft Covers, 5 1/2 x 8 1/2", illus.

RC & RL TIME CONSTANT

#166.....Only \$.90

F-M LIMITERS & DETECTORS

#166-2.....Only \$.90

FREQUENCY MODULATION

#166-3.....Only \$.90

CRYSTAL OSCILLATORS

#166-4.....Only \$1.25

A-M DETECTORS

#166-5.....Only \$1.25

LIMITERS & CLIPPERS

#166-6.....Only \$1.25

MULTIVIBRATOR S

#166-7.....Only \$.90

R-F TRANSMISSION LINES

#166-8.....Only \$1.25

AMPLITUDE MODULATION

#166-9.....Only \$1.25

BLOCKING OSCILLATORS

#166-10.....Only \$1.25

WAVE PROPAGATION

#166-11.....Only \$.90

SUPERHETERODYNE CONVERTERS & I-F AMPLIFIER S

#166-12.....Only \$.90

INVERSE FEEDBACK

#166-15.....Only \$.90

SERVICING TV VERTICAL AND HORIZONTAL OUTPUT SYSTEMS

by Harry Thomas

Technicians and students will here find a complete discussion of vertical and horizontal output systems and their operation. Soft Cover, 176 pp., 5 1/2 x 8 1/2", illus.

#150.....Only \$2.40

OBTAINING & INTERPRETING TEST SCOPE TRACES

by John F. Rider

Explains oscilloscope screen traces in clear, non-mathematical language. Contains over 800 scope traces, and complete instructions on the use of scopes and interpretation of traces. Soft Cover, 190 pp., 5 1/2 x 8 1/2", illus.

#146.....Only \$2.40

HI-FI LOUDSPEAKERS & ENCLOSURES

by Abraham B. Cohen

A long-needed book, destined to become a classic volume in hi-fi literature. Completely covers the subject. Answers all your questions about loudspeakers and enclosures, design, cross-over networks, construction of own networks, etc. Leather Finish MARCO Cover, 5 1/2 x 8 1/2", illus.

#176.....Only \$4.60

#176-H, Cloth Bound.....Only \$5.50

HIGH FIDELITY SIMPLIFIED

by Harold D. Weiler

Gives you the complete hi-fi story, and answers all questions about tuners, changers, amplifiers, tape recorders, speakers, record players, etc. There is no other book like it. Soft Cover, 224 pp., 5 1/2 x 8 1/2", illus.

#142.....Only \$2.50

HOW TO SELECT AND USE YOUR TAPE RECORDER

by David Mark

Written for the USER: music lovers, businessmen, lawyers, engineers, teachers, etc. Step-by-step instructions on set-up and using procedures for all applications in the home, office, and professional activities. Also a buyer's guide in selecting a machine to suit individual requirements. Soft cover, 148 pp., 5 1/2 x 8 1/2", illus.

#179.....Only \$2.95

HOW TO SERVICE TAPE RECORDERS

by C. A. Tuthill

Tells you what you need to know about the tape recorder and its operation. Explains the types of circuits, drive mechanisms, troubleshooting and repair. Soft Cover, 160 pp., 5 1/2 x 8 1/2", illus.

#167.....Only \$2.90

THESE AND MANY
OTHER RIDER BOOKS
ARE AVAILABLE...



Buy these books at your electronics parts jobber or book store.

... Look for this Rider Book Seller. If your jobber or book store does not sell the Rider books you want, mail this coupon for prompt delivery. ORDER TODAY! Add state and city sales tax where applicable. Canadian prices 5% higher.

JOHN F. RIDER PUBLISHER, INC.
480 Canal Street, New York 13, N. Y.

Enclosed is \$..... Please rush the books I have circled.

101	142	143-7	156	166	166-8	167	169	173-4	180
101-H	143	143-8	160	166-2	166-9	168	169-H	173-5	180-H
102	143-2	144	161	166-3	166-10	168-2	170	174	183
103	143-3	146	161-2	166-4	166-11	168-3	170-H	176	184
133	143-4	147	162	166-5	166-12	168-4	173	176-H	
140	143-5	150	162-H	166-6	166-15	168-5	173-2	176	
140-2	143-6	152	165	166-7		168-6	173-3	179	

Name.....

Address.....

City.....


Zone..... State.....

RE-9


This combination of **CDR ROTORS**
and the **Biggest TV Spot Campaign**
in our history

PRE-SELLING your customers

opens the door
for you to

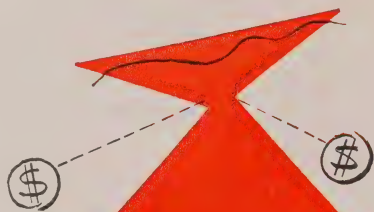

**BIGGER
SALES**

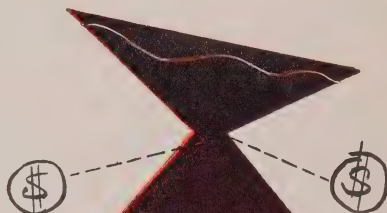

**BIGGER
PROFITS**

CORNELL-DUBILIER
SOUTH PLAINFIELD, N. J.




THE RADIART CORP.
CLEVELAND 18, OHIO




There's more in store
for you...when you feature
CDR ROTORS

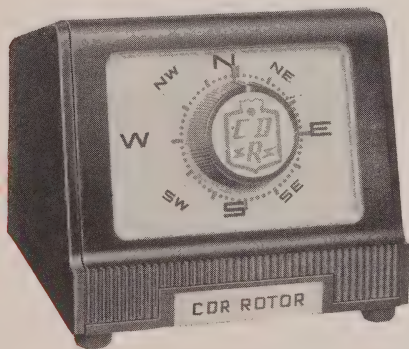
Proven the popular favorite
the complete line...
a model for every need!



AR-1

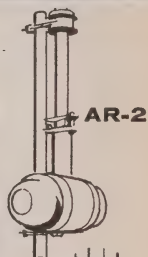

AR-2

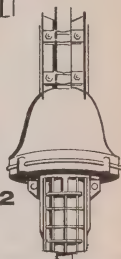

AR-22

featuring
CDR AUTOMATIC Rotors

An outstanding group of rotors... three proven and tested models... ALL 40% SHARPER TUNING than ANY other automatic rotor. Handsome cabinet... dependable performance... proven and tested by thousands and thousands of satisfied users.



- TR-12** a special combination value consisting of complete rotor, including thrust bearing. Handsome new modern cabinet with meter control dial, uses 4 wire cable.
- TR-11** same as TR-12 without thrust bearing.
- TR-4** the heavy duty rotor complete with handsome modern cabinet with METER control dial, uses 4 wire cable.
- TR-2** the heavy duty rotor with plastic cabinet featuring "compass control" illuminated perfect pattern dial, uses 8 wire cable.



CORNELL-DUBILIER South Plainfield, N. J.



The **RADIART** Corporation, Cleveland 13, Ohio



FOR ADVANCED-
ENGINEERED

VR tubes

IT'S



Have you and your customers exacting requirements for stable voltage? Try the reliabilized CBS 6626 and 6627. There are no better VR tubes made. They represent the most advanced engineering concepts in gaseous voltage-regulator tubes. They eliminate sudden discrete voltage shifts in voltage-reference circuits.

It's only natural that CBS VR tubes should be the finest. CBS specializes in VR tubes . . . has made over 20 millions of them. CBS has originated many VR types; for example, the OB2, USN-OA2WA, USN-OB2WA, 6830, 6831 . . . as well as the 6626 and 6627. CBS offers the widest line of 105-volt and 150-volt VR tubes: commercial and military . . . miniature and GT . . . for voltage regulation and voltage reference.

It makes good sense to think of CBS when you think of VR tubes. Be sure of up-to-the-minute design and tightly controlled quality. Follow the leaders, specify the leader. For stable, reliable, advanced-engineered VR tubes . . . always make it CBS.

Seen the new CBS VR Tube Manual? A complete, informative, easy-to-read eight pages. Includes data, theory, and application on voltage regulation and voltage reference. Write for free Bulletin E-267 today.



CBS-HYTRON, Danvers, Massachusetts

A Division of
Columbia Broadcasting System, Inc.

L. C. Lane, B.S., M.A.
President, Radio-Television Training Association. Executive Director, Pierce School of Radio & Television.



VETERANS--NON-VETERANS TRAIN NOW FOR A TOP-PAY JOB IN TELEVISION



No Experience Needed—I train you AT HOME in your SPARE TIME

NOW — while the Television-Radio-Electronics industry is expanding at the fastest rate in history — is the time for you to prepare for a top-pay lifetime job . . . or your own profitable business.


New TV stations are going up constantly . . . sales of TV sets are breaking all past records . . . new products are being announced almost every day . . . new plants are

springing up to meet the heavy demand for these products.


Trained men are needed urgently. The head of CBS-Columbia product service department estimates that the industry will need 200,000 service men by 1959. The best jobs will go to the men who are ready for them. *Right now* is the time for you to prepare yourself. Delay can be costly.

LEARN BY DOING

As part of your training I give you the equipment you need to set up your own home laboratory and prepare for a **BETTER-PAY TV JOB**. You build and keep an Electromagnetic TV RECEIVER designed and engineered to take any size picture tube up to 21-inch, (10-inch tube furnished. Slight extra cost for larger sizes.) . . . also a Super-Het Radio Receiver, AF-RF Signal Generator, Combination Voltmeter-Ammeter-Ohmmeter, C-W Telephone Transmitter, Public Address System, AC-DC Power supply. Everything supplied, including all tubes.

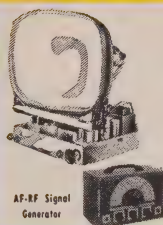

AF-RF Signal Generator

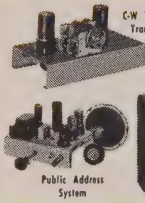

C-W Telephone Transmitter

Public Address System



Super-Het Radio Receiver



Combination Voltmeter-Ammeter-Ohmmeter

STUDY NEWEST DEVELOPMENTS

My training covers all the latest developments in the fast-growing Television-Radio-Electronics industry. You learn about FM — RADAR — COLOR TV — TRANSISTORS — PRINTED CIRCUITS, etc.

EARN WHILE YOU LEARN

Almost from the very start of your course you can earn extra money by repairing sets for friends and neighbors. Many of my students earn up to \$25 a week . . . pay for their entire training with spare time earnings . . . start their own profitable service business.

CHOOSE FROM THREE COMPLETE COURSES covering all phases of Radio, FM and TV

1. Radio, FM and Television Technician Course — no previous experience needed.
2. FM-TV Technician Course — previous training or experience in radio required.
3. TV Cameraman and Studio Technician Course — advanced training for men with Radio or TV training or experience.

EXTRA TRAINING IN N.Y.C. AT NO EXTRA COST!

After you finish your home study training in Course 1 or 2 you can have two weeks, 50 hours, of intensive Lab work on modern electronic equipment at our associate resident school, Pierce School

of Radio & Television. **THIS EXTRA TRAINING IS YOURS AT NO EXTRA COST WHATSOEVER!**

FCC COACHING COURSE

Important for **BETTER-PAY JOBS** requiring FCC License! You get this training **AT NO EXTRA COST!** Top TV jobs go to FCC-licensed technicians.

FREE! I'll send you my new 40-page book, "How to Make Money in Television - Radio - Electronics," a Free sample lesson, and other literature showing how and where you can get a top-pay job in Television.



VETERANS

My School fully approved to train Veterans under new Korean G.I. Bill. Don't lose your school benefits by waiting too long. Write discharge date on coupon.

MAIL THIS COUPON TODAY!

Mr. Leonard C. Lane, President
RADIO-TELEVISION TRAINING ASSOCIATION
Dept. R-9C, 52 East 19th Street, New York 3, N.Y.

Dear Mr. Lane: Send me your **NEW FREE BOOK, FREE SAMPLE LESSON**, and **FREE** aids that will show me how I can make **TOP MONEY** in TELEVISION. I understand I am under no obligation.

(PLEASE PRINT PLAINLY)

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

- I AM INTERESTED IN:
- ☐ Radio-FM-TV Technician Course
 - ☐ FM-TV Technician Course
 - ☐ TV Cameraman & Studio Technician Course

VETERANS!

Write discharge date

Radio-Television Training Association

52 EAST 19th STREET • NEW YORK 3, N. Y.



Licensed by the State of New York • Approved for Veteran Training

RAYTHEON

TUBES


are the best you can buy...

HERE'S WHY

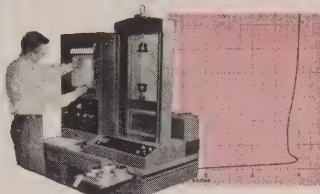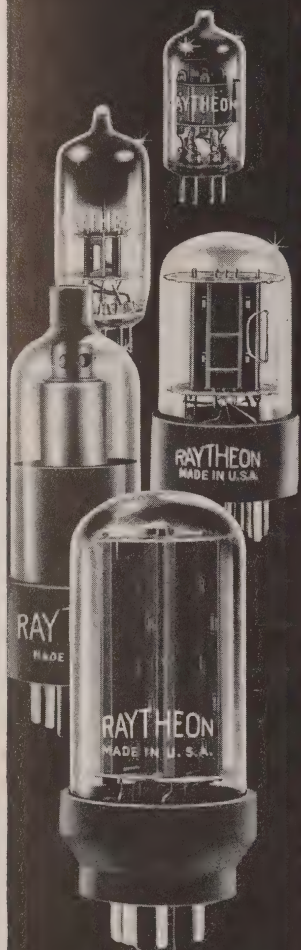

INSTON WIRE TESTING

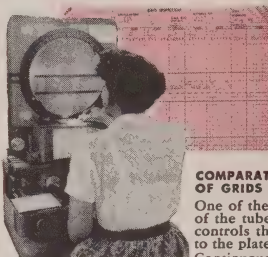
Testing of grid lateral and filament wire on the Instron Tester for specific physical properties as tensile strength, yield point, breaking point and proportional limit insures better tube quality and uniformity for Raytheon tubes.



COMPARATOR INSPECTION OF GRIDS


One of the most critical parts of the tube is the grid which controls the flow of electrons to the plate.

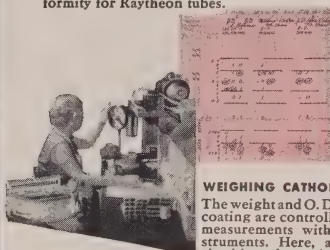Continuous comparator inspection of critical parts such as the above grid (magnified 20x) supplies information for better quality control and guards against deviations from Raytheon's high quality standards.




WEIGHING CATHODE COATING

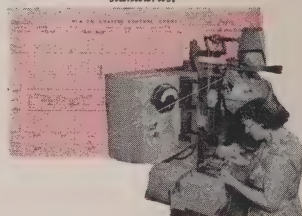The weight and O.D. of the cathode coating are controlled by periodic measurements with precision instruments. Here, an operator is checking the weight of cathode coating at the operation.




HEATER COATING CHECK

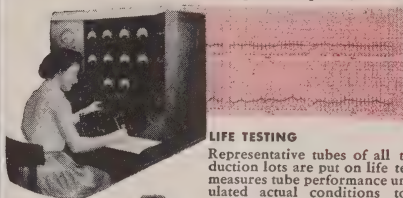Heater wire must have uniform and closely toleranced coating thickness to insure short and uniform warm-up-time and durability. Raytheon makes continuous inspections of the heater wire coating to make certain of uniformity.




LIFE TESTING

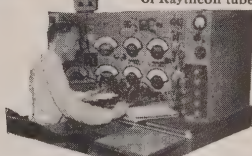Representative tubes of all tube production lots are put on life test which measures tube performance under simulated actual conditions to ensure original and continuing performance of Raytheon tubes.



ENGINEER CHECKS DESIGN CHARACTERISTICS

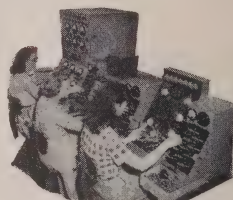Behind all these quality activities stands a large group of experienced, capable engineers whose sole concern is maintaining and developing Raytheon tube quality performance. This engineer is measuring tube design characteristics with the purpose of developing a tube for a customer with special applications.



1ST FINISHED TUBE TEST

All Raytheon tubes undergo a rigid 100% First Test where they must pass strict requirements on both physical and electrical characteristics.

These girls are testing tubes for excessive noise and microphone characteristics and physical appearance.

These and many other vital tests and checks add up to
UNIFORMITY OF CHARACTERISTICS THROUGH RIGID QUALITY CONTROL

RAYTHEON MANUFACTURING COMPANY

Receiving and Cathode Ray Tube Operations

Newton, Mass. • Chicago, Ill. • Atlanta, Ga. • Los Angeles, Calif.

Raytheon makes all these: } Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes,
} Semiconductor Diodes and Transistors, Nucleonic Tubes, Microwave Tubes.




MONEYBACK GUARANTEE ON THE WORLD'S FINEST SERVICE DATA!

Howard W. Sams will prove to you that
PHOTOFACT will help you solve any service problem
FASTER, EASIER, BETTER, MORE PROFITABLY

GET THE PROOF...DO THIS NOW:

1.

Choose a "Tough Nut"

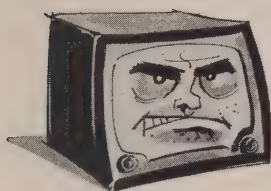

Pick a set that's been giving you plenty of trouble—the tougher the test, the better the proof. Get the make and chassis number of the set...

2.


See Your Parts Distributor



Look up the set in the Sams Index to PHOTOFACT Folders. In just 60 seconds you'll find the applicable Folder Set. Buy it—take it back to your shop...

3.

Give PHOTOFACT the "Acid Test"

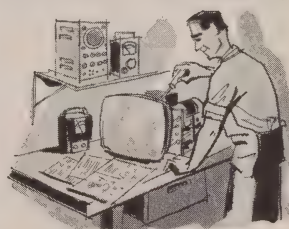

With the proper PHOTOFACT Folder by your side, start solving your service problem...

THEN, YOU BE THE JUDGE:


If PHOTOFACT doesn't save you time, doesn't make the job easier and more profitable for you, Howard W. Sams wants you to return the complete Folder Set direct to him and he'll refund your purchase price promptly.

**TRY THE PHOTOFACT
MONEYBACK OFFER NOW**

**LEARN FOR YOURSELF HOW PHOTOFACT
SAVES YOU TIME ON EVERY SERVICE JOB...
HELPS YOU EARN MORE DAILY**

HOWARD W. SAMs, INC. • 2205 E. 46th ST. • INDIANAPOLIS, IND.

WIDE

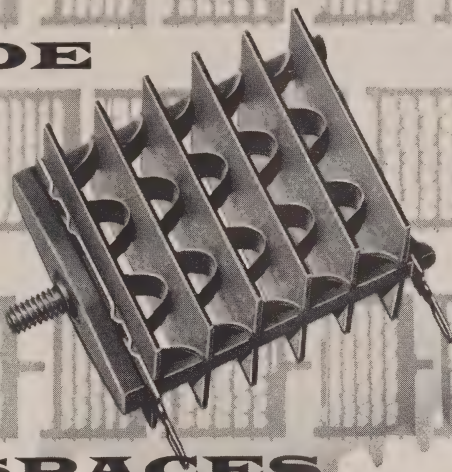

OPEN

SPACES

keep operating temperatures down—dependability up!

RCA SELENIUM RECTIFIERS utilize modern design—*full surface ventilation* with no chance of center-core hot-spots. Note the corrugated spring-steel separators which provide positive multiple-area contacts with each plate. This open construction facilitates free-flow of air and efficient cooling of the plates, and minimizes the possibilities of overheated components in compact TV, radio, and phonograph designs.


The one-piece assembly-yoke with the molded mounting stud prevents *twisting* or *squeezing* the stack during installation. Rigid construction minimizes the possibility of "barrier" breakdowns—*gives greater assurance of dependability in operation.*

So, when you need a replacement selenium rectifier, ask your distributor for a dependable, long life RCA SELENIUM RECTIFIER. Available now in 12 types, ratings from 65 Ma to 500 Ma.



SELENIUM RECTIFIERS

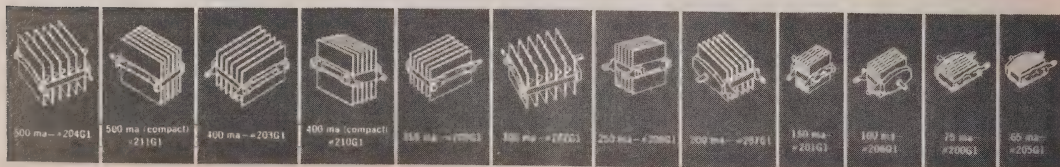Radio Corporation of America • Harrison, N. J.



**NEW! COLOR and Black-&White
LAB & TV 5" OSCILLOSCOPE #460
KIT \$79.95. Wired \$129.50**

The FINEST professional 5 mc wide-band scope value. Ideal for research, h-f & complex waves, plus Color & Monochrome TV servicing. Flat from DC to 3.58 mc ± 1 db (color burst freq.), flat DC to 4.5 mc ± 1 , 3 db. Vert. sens. 25 rms mv/in. Vert. Z 3 megs. Has the following outstanding features not found in scopes up to several times its price, kit or wired:

VERTICAL AMPLIFIER: direct-coupled (DC) thruout to eliminate l-f phase shift; push-pull thruout for negligible distortion; K-follower coupling between push-pull pentode stages for extended h-f resp. (minimizes h-f phase shift, extends useful resp. to 10 mc); full-screen undistorted vert. defl; 4-step freq-compensated decade step attenuator up to 1000:1. **SWEEP CIRCUIT:** perfectly linear sweeps, 10 cps - 100 kc (ext. cap. for down to 1 cps); pre-set TV vert. & hor. positions (30 & 7875 cps); automatic sync. ampl. & limiter eliminates sync amplitude adj. **PLUS:** direct or cap. coupling; bal. or unbal. inputs; edge-lit engraved lucite graph screen; dimmer; anti-glare filter; bezel fits std photo aperture. **OTHER IMPORTANT FEATURES:** High intensity trace CRT. Finest sq. wave resp. (.06 usec rise time). Push-pull hor. ampl., flat to 400 kc, sens. 0.6 rms mv/in. Built-in voltage calibration. Intensity mod. Sawtooth & 60 cps outputs. Astigmatism control. Retrace blanking. Full-screen vert. positioning & 2X full-screen hor. positioning. **EXTERNAL ACCESSORIES:** 5U1 CRT, 2-6AU8, 2-6CB6, 1-12AU7A, 2-6J6, 1-6AX5, 1-1V2. Deep-etched satin aluminum panel, rugged grey wrinkle steel cabinet. Designed for easy building at home with no special equipment. 13" x 8 1/2" x 16". 30 lbs.

ing. Instant, drift-free positioning. Bal. cal., astig. adj. externally accessible. 5U1 CRT, 2-6AU8, 2-6CB6, 1-12AU7A, 2-6J6, 1-6AX5, 1-1V2. Deep-etched satin aluminum panel, rugged grey wrinkle steel cabinet. Designed for easy building at home with no special equipment. 13" x 8 1/2" x 16". 30 lbs.

SCOPE DIRECT PROBE* #PD: KIT \$2.75. Wired \$3.95. Eliminates stray-pick-up & signal re-radiation.

SCOPE DEMODULATOR PROBE* #PSD: KIT \$3.75. Wired \$5.75. Demodulates AM carriers between 150 kc and 250 mc.

SCOPE LOW CAPACITY PROBE* #PLC: KIT \$3.75. Wired \$5.75. For signal tracing in high frequency, high impedance & wide-band circuits (as in TV) without distortion from overloading or frequency discrimination.

for COLOR and Monochrome TV servicing

**New! PEAK-TO-PEAK VTM #232
& UNI-PROBE (pat. pend.)
KIT \$29.95. Wired \$49.95**

UNI-PROBE: exclusive with EICO! Terrific time-saver! Only 1 probe performs all functions—a half-turn of probe-tip selects DC or AC-Ohms.

The new leader in professional peak-to-peak VTM's. Latest circuitry, high sensitivity & precision, wide ranges & versatility. Calibration without removing from cabinet. New balanced bridge circuit. High Z input for negligible loading. 4 1/2" meter, can't-burn-out circuit. 7 non-skip ranges on every function, 4 functions: +DC Volts, -DC Volts, AC Volts, Ohms.

Uniform 3 to 1 scale ratio for extreme wide-range accuracy. Zero center. One zero-adj. for all functions & ranges. 1% precision ceramic multiplier resistors. Measure directly peak-to-peak voltage of complex & sine waves: 0-4, 14, 42, 140, 420, 1400, 4200. DC/RMS sine volts: 0-1.5, 5, 15, 50, 150, 500, 1500 (up to 30,000 v. with HVP probe, & 250 mc with PRF probe). Ohms: 0.2 ohms to 1000 megs. 12AU7, 6AL5, selenium rectifier; xfmr-operated. 8 1/2" x 5" x 5". Deep-etched satin aluminum panel, rugged grey wrinkle steel cabinet. 7 lbs.

**New! DELUXE PEAK-TO-PEAK VTM #249
with 7 1/2" METER & UNI-PROBE (pat. pend.)
KIT \$39.95. Wired \$59.95**

All the advanced & exclusive features of #232—PLUS the extra convenience and readability of its big 7 1/2" meter. Your ideal bench instrument.


VTVM RF PROBES* #PRF-11 or PRF-25: KIT \$3.75. Wired \$4.95. Accuracy $\pm 10\%$. Use with any 11 or 25 megohm VTVM.

VTVM HV PROBE #HVP-2: Wired \$4.95. Complete with multiplier resistor. Measures up to 30 kv with any VTVM or 20,000 ohms/volt VOM.



Calibration without removing from cabinet.

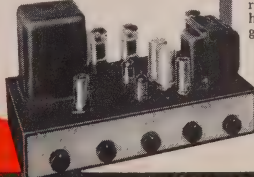*Only EICO Probes have all these features: fully shielded; rugged terminal board parts mounting; shock-mounted floating construction; swivel-action; color-coding; easy parts accessibility.



EICO

84 Withers Street, Brooklyn 11, New York

150 kc to 435 mc
with ONE generator!

**New! RF SIGNAL GENERATOR #324
KIT \$26.95. Wired \$39.95**

for COLOR and Monochrome TV servicing

New wide-range, stable generator—better value than generators selling at 2 or 3 times its cost! Ideal for: IF-RF alignment, signal tracing & trouble-shooting of TV, FM & AM sets; marker gen.; 400 cps audio testing; lab. work. 6 fund. ranges: 150-400 kc, 400-1200 kc, 1.2-3.5 mc, 3.5-11 mc, 11-37 mc, 37-145 mc; 1 harmonic band 111-435 mc. Freq. accurate to $\pm 1.5\%$; 6:1 vernier tuning & excellent spread at most important alignment freqs. Etched tuning dial, plexiglass windows, edge-lit hairlines. Colpitts RF osc., directly plate-modulated by K-follower for improved mod. Variable depth of int. mod. 0-50% by 400 cps Colpitts osc. Variable gain ext. mod. amplifier: only 3.0 volts needed for 30% mod. Turret-mounted coils slug-tuned for max. accuracy. Fine & Coarse (3-step) RF attenuators. RF output 100,000 uv; AF sine wave output to 10 volts. 50-ohm output Z. 5-way jack-top binding posts for AF in/out; coaxial connector & shielded cable for RF out. Tubes: 12AU7, 12AV7, selenium rectifier; xfmr-operated. Deep-etched satin aluminum panel, rugged grey wrinkle steel cabinet. 8" x 10" x 4 3/4". 10 lbs.



The specs are the proof...

**4 NEW BEST BUYS
by EICO**

**COMPLETE
with Preamplifier, Equalizer and Control Section
New! 20-WATT Ultra-Linear Williamson-
type HIGH FIDELITY AMPLIFIER #HF20
KIT \$49.95. Wired \$79.95**

A low-cost, complete-facility amplifier of the highest quality that sets a new standard of performance at the price, kit or wired. Every detail, down to the etched, brushed solid brass control plate, is of the fine quality EICO is famous for.

Rated power output: 20 watts (34 w peak). 1M distortion (60 cps: 6 ke/4:1) at rated power: 1.3%. Mid-band harmonic distortion at rated power: 0.3%. Maximum harmonic distortion between 20 and 20,000 cps at 1 db under rated power: approx. 1%. Power response (20w): ± 0.5 db 20-20,000 cps; ± 1.5 db 10-40,000 cps. Frequency response ($\frac{1}{4}$ w): ± 0.5 db 13-35,000 cps; ± 1.5 db 7-50,000 cps.


5 feedback equalizations for LP's & 78's including RIAA. Variable turnover feedback tone controls do not affect volume & permit large boosts or cuts at either end of audio spectrum with mid-freqs. unaffected. Loudness control & separate level set control on front panel. Low Z output to tape recorder. 4 hi-level switched inputs: tuner, tv, tape, auxiliary (xtal/ceramic phono or 2nd tuner); 2 low-level inputs for proper loading with all leading magnetic, FM & quality xtal cartridges. Hum bal. control. Extremely fine output transformer has interleaved windings, tight coupling, careful balancing & grain-oriented steel. 8 1/2" x 15" x 10". 24 lbs.

These amazing EICO values are NOW IN STOCK at your nearest distributor. Examine them side-by-side with ANY competitor. You'll see for yourself why indeed EICO is your BEST BUY. Fill out coupon on reverse page.

TURN PAGE FOR MORE EICO VALUES...

Prices 5% higher on West Coast.

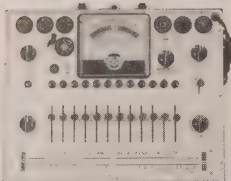**the specs are
the test that tells
who's best!**



for COLOR & Monochrome
TV servicing

**NEW! DYNAMIC
CONDUCTANCE TUBE &
TRANSISTOR TESTER #666**
KIT \$69.95 WIRED \$109.95

Unexcelled testing thoroughness & accuracy. Checks transistor collector current & Beta using internal dc power supply. Tests all receiving tubes including subminiatures (& Color & Monochrome tv pic tubes with accessory adapter). Composite indication of mutual conductance, plate conductance, & peak emission. Simultaneous sel. of any 1 of 4 combinations of 3 plate, 3 screen, & 3 ranges of control grid voltage. Grid voltage variable over 3 ranges with 5% accurate pot. New series-string voltages for 600, 450 & 300 ma types. 5 ranges meter sens. with 1% precision shunts & 5% accurate pot. 10 SIX-position lever switches for free-point connection of every tube pin or cap. Pushbuttons for rapid insert of any tube element in leakage circuit & speedy sel. of individual tube sections. Direct reading of inter-element leakage in ohms. New gear-driven rollchart. Steel case with cover & handle. Sensitive 200 ua meter.



for COLOR & Monochrome
TV servicing

**TV-FM SWEEP GENERATOR
& MARKER #368**
KIT \$69.95 WIRED \$119.95

The FINEST service instrument of this type ever offered in either kit or wired form at ANY price! Outstanding ease & accuracy in FM & TV (including Color) alignment. Entirely electronic sweep circuit with accurately biased Incredibly steep linearity on both sides of selected center freq. Newly-designed AGC circuit automatically adjusts osc. for max. output on each band with min. amplitude variations. Sweep gen. range 3-216 mc in 5 OVERLAPPING FUND. BANDS. Sweep width continuously variable from 0-3 mc lowest max. deviation to 0-30 mc highest max. deviation. Variable marker gen. range from 2-75 mc in 3 FUND. BANDS plus a calibrated harmonic band (60-225 mc). Variable marker calibrated with int. xtal marker gen. 4.5 mc xtal included. Ext. marker provision. Double pi line filter. Edge-lit hairlines eliminate parallax.

Turn page for other EICO ad



**FREE 1956
EICO CATALOG!**

Tells you how to SAVE 50% on
your test equipment costs!

TUBE TESTER #625
KIT \$34.95
Wired \$49.95

- tests 600 mil series string type tubes
- illuminated roll-chart

Pix Tube Test Adapter\$4.50

New! GEIGER COUNTER #803
KIT \$19.95 Wired \$29.95

(less batteries)
Professional, all-electronic, sensitive, rugged—at lowest cost! Indicates by neon lamp & headphone clicks.

5" PUSH-PULL OSCILLOSCOPE #425
KIT \$44.95
Wired \$79.95

7" PUSH-PULL OSCILLOSCOPE #470
KIT \$79.95
Wired \$129.50

VACUUM TUBE VOLTMETER #221
KIT \$25.95
Wired \$39.95

DELUXE VTVM #214 (7 1/2" METER)
KIT \$34.95
Wired \$54.95

RF SIGNAL GENERATOR #320
KIT \$19.95
Wired \$29.95

150 kc-34 mc, calibrated harmonics to 102 mc. Pure or mod. RF, & Colpitts osc. 400 cps sine outputs.

NEW! REDI TESTER #540
KIT \$12.95
Wired \$15.95

Multi-range ac/dc voltmeter, ammeter, ohmmeter, wattmeter, leakage checker for home & auto repairs.

#944 FLYBACK TRANSFORMER & YOKE TESTER
KIT \$23.95
Wired \$34.95

- fast check all flybacks & yokes in or out of set.
- spots even 1 shorted turn!

TV/FM SWEEP GENERATOR #360
5MC-4.5MC CRYSTAL\$3.95 ea.

Range 500 kc-228 mc on fund. Cont. sweep width control, 0-30 mc.

KIT \$34.95
Wired \$49.95

DELUXE RF SIGNAL GENERATOR #315

1% accuracy on all 7 ranges. Range 75 kc-150 mc. Volt reg.

KIT \$39.95
Wired \$59.95

Sep. volt-meter & ammeter
KIT \$29.95
Wired \$38.95

6V & 12V BATTERY ELIMINATOR & CHARGER #1050

DELUXE MULTI-SIGNAL TRACER #147

Sep. hi-gain RF & lo-gain audio inputs. Special noise locator. Calibrated wattmeter.

KIT \$24.95
Wired \$39.95

R-C BRIDGE & R-C-L COMPARATOR #950B

Reads 0.5 ohms -500 megs, 10 mmfd-5000 mfd power factor.

KIT \$19.95
Wired \$29.95

HI-FI PREAMPLIFIER #HF-61
KIT \$24.95. Wired \$37.95. With Power Supply: KIT \$29.95. Wired \$44.95

Feedback circuitry thruout! Preamp-equalizer, tone controls, scratch & rumble filters, K-follower output.

20,000 Ohms/Volt MULTIMETER #565
KIT \$24.95
Wired \$29.95

1000 Ohms/Volt MULTIMETER #536
KIT \$12.90
Wired \$14.90

VTVM PROBES KIT Wired

Peak-to-Peak	\$4.95	\$6.95
RF	\$3.75	\$4.95
High Voltage Probe-1		\$6.95
High Voltage Probe-2		\$4.95

SCOPE PROBES

Demodulator	\$3.75	\$5.75
Direct	\$2.75	\$3.95
Low Capacity	\$3.75	\$5.75

For FREE 1956 catalog, mail coupon NOW!



84 Withers St. • Brooklyn 11, N. Y.

Prices 5% higher on West coast and subject to change without notice. ©56

EICO, 84 Withers Street
Brooklyn 11, New York

Send FREE 1956 Catalog and name of neighborhood EICO jobber.

Name.....

Home Address.....

City.....Zone.....State.....

Occupation.....

1945 to 1955: a decade of Know-How & Value Leadership in Kits & Instruments—over 1/2 million sold to date!

AIRPLANE COLLISION PREVENTION

... Electronic Collision Control Is Long Overdue ...

THE tragic collision and crash of two large airplanes over Grand Canyon, in Arizona, on June 30, with the loss of 128 lives, need never have happened.

For the last few years, many of our pilots time and again have warned our authorities of *near collisions*, which occur more and more frequently, particularly in the vicinity of our airports.

During a single week, airport control towers operated by the Civil Aeronautics Administration guide an estimated 400,000 outgoing and incoming flights. This is likely to grow to around a million within 10 years.

Ground control stations which dot the land theoretically "guide" all planes by radio, keeping pilots informed along the way. The planes also report their position by "fix postings" over specified points along the route. When, however, a plane is flying blind in an overcast, it is "on visual control" and the pilot must look out for other planes—if he can. During violent thunderstorms he is likely to drift from his course and be miles away from the control point which he may think erroneously is directly underneath him. This is exactly what happened on June 30—one of the airplanes being about 25 miles off course.

It is senseless to blame the pilots, who, having their hands full in a violent storm, probably did their best to prevent their buffeted planes from being wrecked. Apparently they could not get them above the clouds, and, as for "visual control," there probably was none or very little visibility—till it was too late. With the two planes approaching each other—most likely at an angle—at 300 miles per hour each, they must have collided at a combined speed of between 400 and 500 miles per hour—much too fast even after they saw each other—to change direction in a few short seconds.

But a plane flies in a three-dimensional medium. Pilots have only a comparatively small angle within which to make visual observations. They cannot look behind them, far sideways or above, or below them at a steep angle in a heavy overcast. Hence the "visual control" is wholly academic and—under certain adverse weather conditions—absurd.

With greatly accelerated air traffic and with jet planes flying at 750 miles an hour in a few years, drastic changes must be made soon to overhaul and modernize our present archaic aviation control.

It is true that the Civil Aeronautics Administration has already under construction an Airways Plan on which \$110 million has already been expended. According to a CAA spokesman, the total cost will reach \$246 millions for the complete 5-year plan. This plan, according to CAA Administrator Charles J. Lowen, "will give the traffic controller 'radar eyes.' When the plan has been put completely into effect, we will have radar coverage of the entire airspace of the United States at high altitudes."

This would seem to be an excellent plan to keep down collisions, but in our opinion it does not go far enough. Nor can we afford to wait 5 years when we reflect that, since 1950, 65 midair collisions have occurred. Radar control from the ground cannot possibly forestall *all* collisions during thick weather, violent thunderstorms and black overcasts, particularly at night.

Yes, ground radar can warn the planes, but the pilots themselves cannot pinpoint *their own* relative positions in regard to each other. For all practical purposes, the pilots are blind now. Each can move in six directions—east, west, south, north, up, down. Which shall each choose? The distant radar—unless we have radar by triangulation, each connected to a fast radio computer—will prove of little use in such situations.

In our May, 1495, issue, we said, under "Airplane Collisions": "Radar on locomotives will prevent not only head-on collisions, but rear-end collisions with other trains as well.

Fog, thick weather and darkness, whether at night or in tunnels, do not interfere with radar. What is true of trains is equally true for airplanes, which no longer will collide with other planes in flight nor run into mountains at great loss of life, as at present."

We foresaw most of today's air complexities as far back as 1951 when, in our May issue, we stated editorially:

"The more planes we operate, the more chances of midair collisions increase. Aerial collisions are by no means a rarity nowadays. They happen right along at great cost of life and property.

"It is physically impossible for a pilot to see simultaneously in six directions: up, down, east, west, north and south. The busy pilot has all he can do to look in one direction, perhaps two at times, but that is all.

"In the not too distant future all planes will be equipped with 'television cameras' in such a manner that screen images from a number of directions will be in front of the pilot at all times. Only the great weight and cost of the equipment make this idea unworkable at present.

"It should be possible in the meanwhile, however, to use a six-way modified—or sweep—radar installation, which need not weigh too much if miniature tubes and other miniature components are used. In this case, too, there would be several miniature screens which pilot or copilot could watch and see if another plane was approaching from any direction. When finally engineered such a device will prevent many collisions. Such radar installations will be particularly advantageous during night flying and while flying in overcast weather when the visibility is extremely poor or nil."

This does not exhaust the subject even remotely, but we do maintain that we have sufficient electronic talent in this country to bring into life an Anti-Airplane Collision Crash Program, now necessary. We cannot wait 5 years for the CAA ground radar, no matter how well it is perfected. By itself it may never prevent all collisions, particularly when jet planes flying at 750 miles per hour move in on each other at 1,500 miles an hour, *25 miles in a single minute*, or over 4 miles in 10 seconds!

From this it would appear that planes soon must be required to carry their own collision alarms, *in addition* to supervision by modern ground radar devices.

We are certain that American ingenuity can devise a reasonably safe collision warning device on board all planes that will be light and noncumbersome.

A comparatively simple instrumentality comes to mind that might be evolved from means in existence now.

Let each plane be equipped with one or more automatic revolving direction finders. Every plane will have a high-frequency transmitter, which emits a special type of signal (or a plurality of signals) assigned only to planes. This signal normally should not carry farther than 100 miles. The receiver is peaked for this special signal only, which can be made to heterodyne with its own signal when another plane moves into its field. As the planes approach each other, the intensity of the received signal rapidly increases in proportion to the diminishing distance between the planes, and the pilot is alerted by visual and aural alarms.

In time it should be possible to evolve an instrumentality whereby the pilot or navigator can read not only the exact distance between two planes in miles, but he will see the vertical or horizontal angle of the approaching plane, too.

By radiophone, both pilots then take the proper steps to change course, thus avoiding collision, no matter what the weather.

If a system such as this, or a similar one is evolved, the nightmare that now continuously frays pilots' nerves and puts thousands of passengers on edge daily, will, we hope, become a bad dream of the past—soon. —H.G.

Remote Controls for TV

By HENRY O. MAXWELL

*Popular electromechanical
and electronic units
for simplified viewing*

DURING the past 7 years or so manufacturers have sporadically introduced and then discontinued remote controls in some of their TV receivers.^{1,2,3} In any one year hardly more than two or three brands had this feature. Now it looks like 1956 will be remote-controlled TV's big year. Almost every major manufacturer offers it in some form.

The control systems may be divided roughly into three basic types: electromechanical, electronic and split-chassis. The electromechanical system has a motor-driven tuner for channel selection and may or may not include remote control of volume, brightness and fine tuning. The electronic type includes those systems that permit controlling the set from a remote point without running wires or cables from the receiver. The split-chassis type has the tuner, and possibly if circuits, on the remote-control chassis along with

other controls that may be needed. The electronic and electromechanical types are described in this article. Further electromechanical, and the circuitry and novel features of several split-chassis types will be discussed in subsequent ones.

The Zenith Flash-Matic

This system enables the viewer to control the TV receiver with the beam of light from a small flashlight. Four cadmium-sulfide photocells are mounted behind bezels in the four corners on the front of the TV cabinet. A momentary flash of light on the lower-left photocell turns the power on and off, on the lower-right one mutes the sound. The cells in the upper left and right corners turn the channel selector counterclockwise and clockwise, respectively. Thus, by turning the motor to the left you can flip immediately from channel 2 to 13 or from 5 to 4 without

having to switch through all other channels. A large illuminated numeral on the manual channel selector shows the channel in use.

The circuit of the Flash-Matic is shown in Fig. 1. Its functions can be broken down into on-off and motor-control operations.

Cadmium-sulfide photocells are a resistive type in which the resistance varies inversely as the light intensity. In the absence of light the resistance may be as high as 100 megohms; in bright light it may drop to around 25,000 ohms.

The power supply in the control unit supplies 117 volts ac for the plates of the 6BX7-GT motor-control tube, 145 volts ac for the plates of the 2D21 thyratrons controlling the on-off and audio-mute circuits and -25 volts dc bias for the 6BX7-GT and 2D21's.

The basic thyatron control circuit is shown in Fig. 2. The grid of the

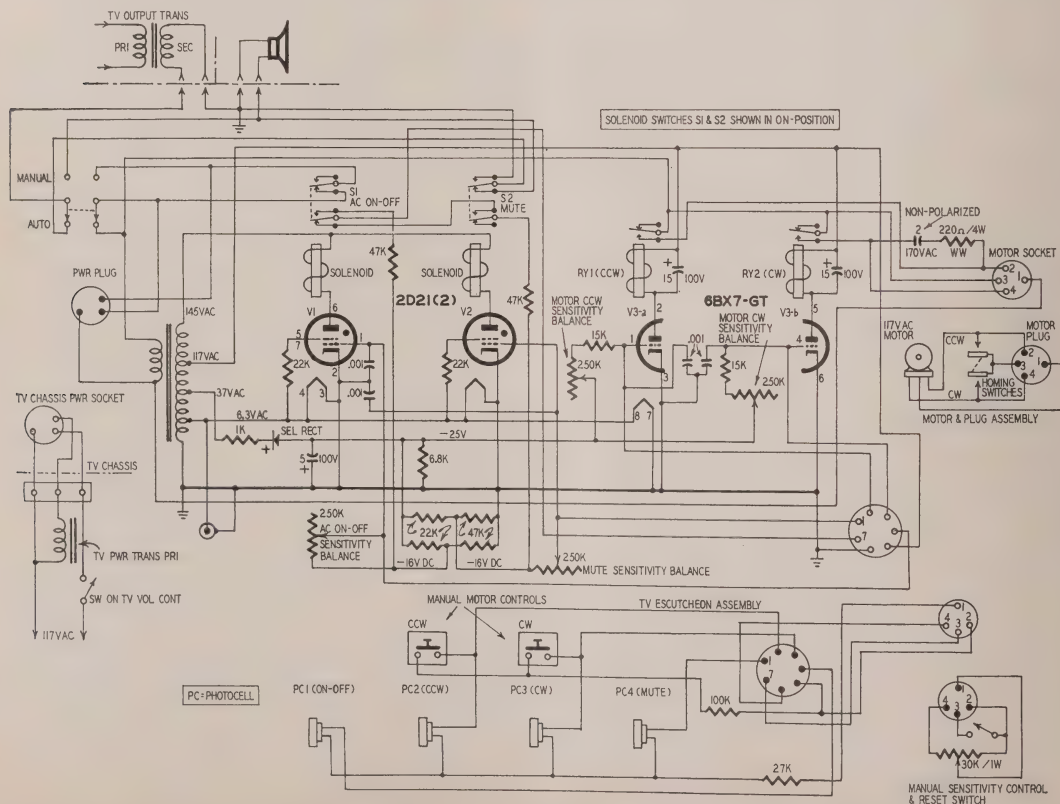


Fig. 1—Schematic diagram of Zenith's Flash-Matic remote tuner. Unit triggered by light falling on four photocells.

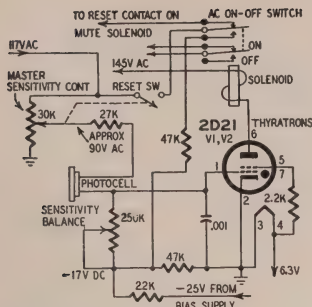


Fig. 2—The thyatron control circuit.

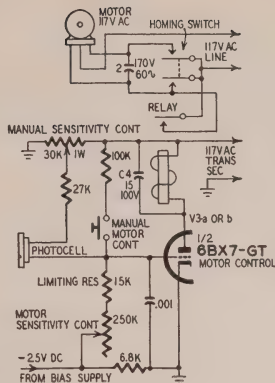


Fig. 3—Zenith motor control circuit.

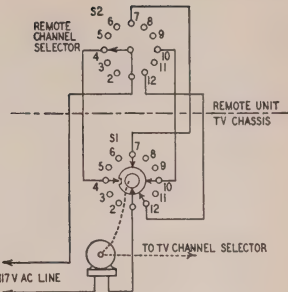


Fig. 4—Basic motor control circuit.

2D21 is biased to cutoff by a negative voltage from the power supply. The plate is supplied with 145 volts ac through the solenoid coil and the grid is supplied with ac through the photocell. The ac voltages on the plate and grid are in phase. The amplitude of the ac voltage on the photocell is determined by the setting of the MANUAL SENSITIVITY CONTROL (Fig. 1) and the ac on the grid is determined by the light on the photocell.

When light of sufficient intensity—as from the flashlight—strikes the cell, its resistance drops and applies a high ac voltage to the 2D21 grid. If the positive peaks of the ac voltage are

high enough to override the negative grid bias, the thyatron conducts and the solenoid operates the switch. This switch is a latching type. One operation of the solenoid throws it in one direction and the next operation returns it to its original position. The 2D21 cuts off on the next negative half-cycle of the line voltage after the flashlight is turned off.

When the MANUAL-AUTO switch (Fig. 1) is set to AUTO (for remote control), the switch operated by the solenoid in V2's plate circuit is in series with one side of the speaker voice coil. Similarly, S1, controlled by the solenoid in V1's plate circuit, breaks or makes one

side of the ac line to the main power transformer. The second set of contacts on S1 and S2 interlock V1 and V2 so that they fire *only* in sequence.

There is a possibility that the TV set will be turned off manually when S1 is in the off position or S2 is set to MUTE. With S1 off, the line voltage does not reach the primary of the TV power transformer and with S2 thrown to MUTE, the speaker circuit is open. To avoid having to use the flashlight to reset S1 and S2, a reset switch is ganged to the MANUAL SENSITIVITY CONTROL so that, when it is turned momentarily to its extreme counterclockwise position, the switch closes and applies a 117-volt ac pulse to the thyatron grids. This pulse overcomes the bias on the 2D21's and returns S1 or S2 to the desired position.

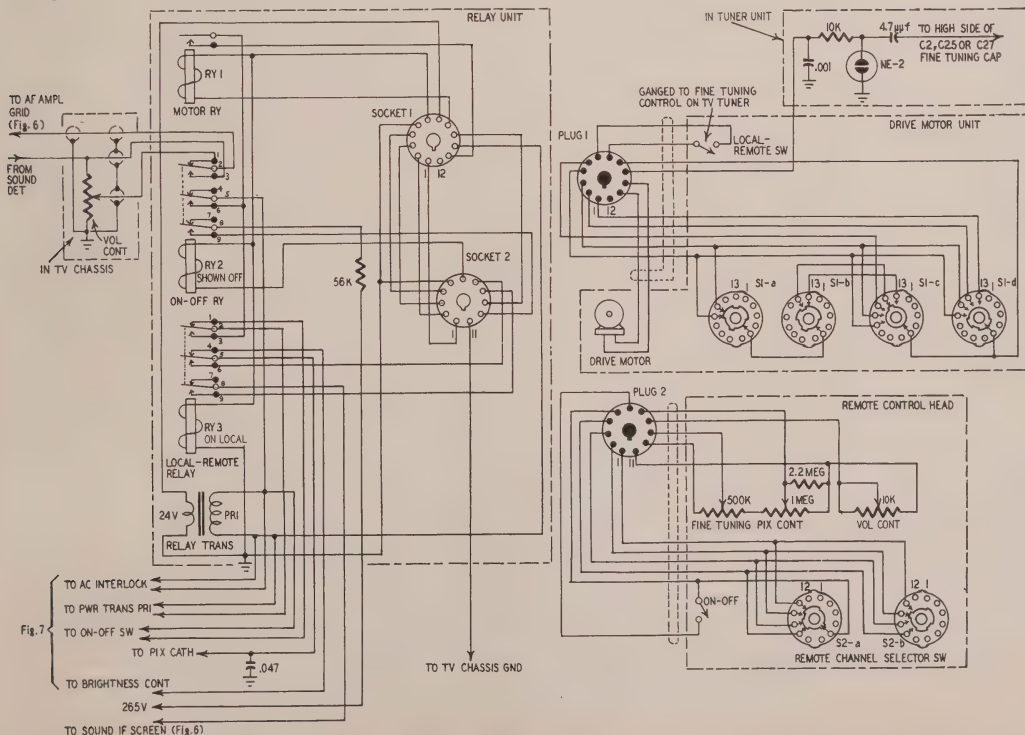


Fig. 5—Schematic diagram of the RCA Magic Brain TV control system. Unit is typical electromechanical control.

TELEVISION

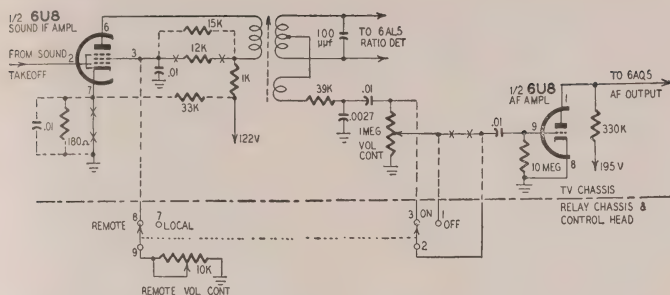


Fig. 6—Schematic of circuit for volume control from the remote panel.

The motor control circuit

A 117-volt induction type ac motor drives the channel-selector shaft of the tuner. Its direction is controlled by V3. The motor has two series-connected windings with one side of the ac line tied to the junction. The ends of the windings are connected to the other side of the ac line through the contacts of RY1 and RY2 in the plate circuits of V3-a and V3-b, respectively.

Fig. 3 is the basic motor control circuit. V3 is biased to cutoff by a voltage supplied through the MOTOR SENSITIVITY CONTROL. When light strikes the photocell, its resistance drops and applies an ac voltage to the grid, causing the tube to conduct on positive half-cycles. The relay pulls in and remains closed as long as the light beam is on the photocell.

Two cam-operated homing or interlock switches insure that the motor always stops with the tuner centered on a channel. One switch is across clockwise relay RY2 contacts, the other across counterclockwise relay RY1 contacts. The homing switches are operated by two index cams that make one revolution per channel. The cams are positioned so both switches are open when the turret is exactly on a channel. Thus, a short pulse of light will start the motor and the homing switch keeps it running until the cam breaks the circuit.

Electromechanical control

Sets with electromechanical control have the control box or head connected to the chassis through a multiconductor

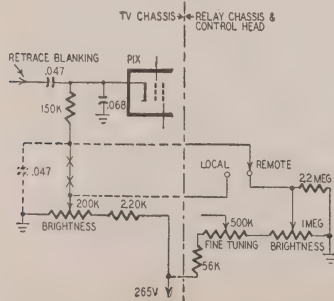


Fig. 7—Remote brightness control.

cable. Controls on the box permit the viewer to select channels and adjust volume, brightness and fine tuning. Like the Zenith, the tuner's channel selector is driven by a small motor. The circuit is shown in Fig. 4. S1 is the channel selector on the control box and S2 a switch that rotates with the tuner shaft driven by the motor.

When S1 is moved to any new position, the circuit to the motor is completed through the corresponding contact on S2. The motor runs until the wiper on S2 moves around and breaks the circuit. In this basic arrangement, the control cable would have to have 13 conductors for the channel selector alone and additional conductors for the other circuits.

In practice, the number of conductors needed for channel selection is greatly reduced by using a more complex switching system like that shown in Fig. 5 of the RCA Magic Brain TV Control. S1 is a rotary switch ganged to the tuner shaft and S2 the remote channel-selector switch on the control head. These switches are shown in the channel-2 position and the motor circuit is open.

Rotating S2 right or left to another channel completes the circuit to motor relay RY1 and starts the motor. The channel-selector shaft on the tuner rotates to the desired channel, breaking the circuit through S1 and S2 and releasing RY1 and stopping the motor.

Volume control

A simplified circuit showing the

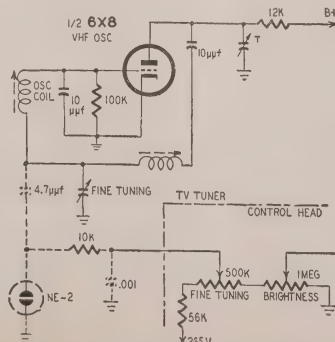


Fig. 8—Control of the vhf oscillator.

method of controlling volume from the remote panel is shown in Fig. 6. The dashed lines indicate wiring and components added to the KCS96 chassis to adapt it for remote control. The dpdt switch is actually made up of parts of RY2 and RY3 (Fig. 5). The switch section labeled ON-OFF is a part of RY2 and the REMOTE-LOCAL section is a part of RY3.

One section of this switch opens the circuit to the arm of the master or local volume control on the TV set and connects the high side directly to the grid of the first af amplifier. The other section connects the remote volume control between ground and the screen grid of the sound if amplifier.

Brightness and fine tuning

In Fig. 7 the contacts of RY3—shown as an spdt switch—transfer the cathode return of the picture tube from the arm of the local brightness control to the arm of a similar control in the remote-control head.

Fig. 8 is a simplified circuit of the vhf oscillator in the tuner and its connection to the remote fine-tuning control. Added components are shown in dashed lines. In this arrangement a 4.7- μf capacitor and NE-2 neon lamp are in series across the fine-tuning capacitor in the tuner. A positive voltage, tapped off the fine-tuning potentiometer, is applied to the neon lamp through an R-C filter network. The neon lamp acts as a capacitor whose capacitance increases as the current through it. Thus, the oscillator frequency can be controlled within limits by varying the voltage on the lamp.


The lamp may also be considered as a variable resistor in series with the fixed capacitor. When the applied voltage is low, the lamp resistance is high and the 4.7- μ mf capacitor has little or no effect on the oscillator frequency. Increasing the voltage decreases the resistance and raises the effective circuit capacitance. Regardless of the method of circuit analysis, the oscillator frequency decreases as the lamp voltage and current increase.

Power on-off circuit

When the receiver is modified for remote control, the 24-volt transformer in the relay unit floats across the ac line. To operate the receiver remotely, the local fine-tuning control is turned clockwise to throw the local-remote switch and apply 24 volts to the coil of RY3. Closing the on-off switch on the control head applies 24 volts to the coil of RY2 to switch the volume-control circuits and complete the circuit to the primary of the power transformer in the TV set.

References

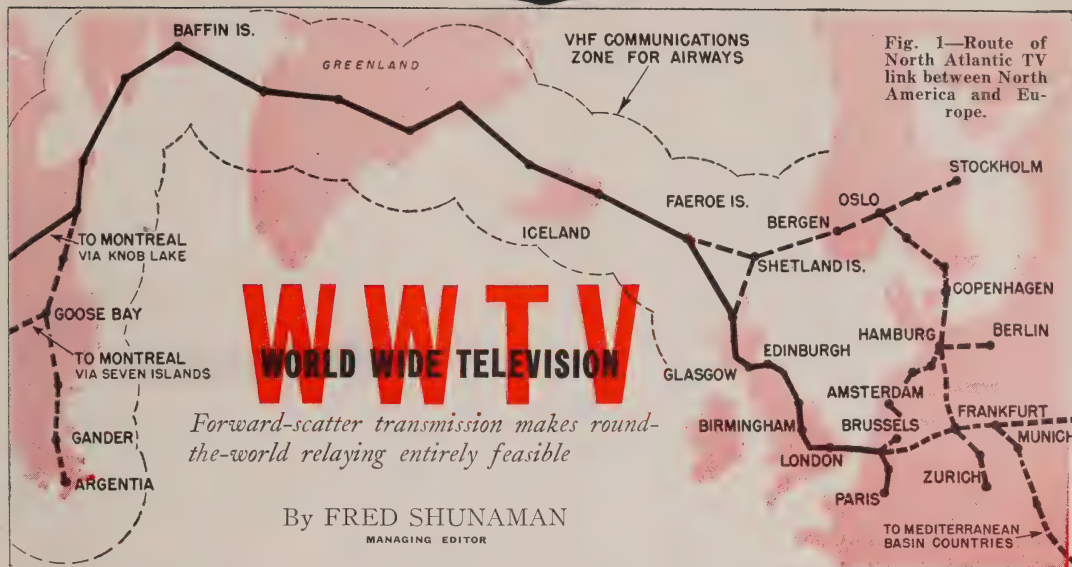- ¹ "Extension Viewers and Remote Control for TV," Radio-Electronics, March, 1949.
- ² "Remote Controls for TV Promote Viewer Comfort," Radio-Electronics, November, 1951.
- ³ "Two Remote TV Control Units," Radio-Electronics, March, 1954.



AROUND-THE-WORLD television network sounds fantastic—at first. Of course, most of us are already sophisticated enough to know that the Atlantic is a big lake only until one decides to travel via Canada, Greenland and over the edge of the world. And the occupation of Attu during World War II jolted us into the knowledge that the Pacific isn't so wide either.

But if these bodies of water don't impose an impassable barrier to TV transmissions, the question "Who will pay for the broadcasts?" does. TV stations must be sustained. More than one American TV broadcaster has had to cease operating—and the failures weren't all in the uhf band!

A TV network's economic problems would be much more serious if it had to pick up its programs on one continent and broadcast on another. True, some important events (such as the Olympic games) might pay commercial sponsors handsomely. Coronations, important diplomatic conferences or his-

toric UN sessions might also justify commercial sponsorship, if the governments concerned did not care to broadcast them. The Voice of America could no doubt use the network for some broadcasts and some governments would probably want to sponsor regular programs. But the sum total could not add up to a self-sustaining system. Here—one would think—is the impassable barrier.

Economic aspect

The plain fact is that television wouldn't have to pay for the system—any more than it pays for our transcontinental "television" microwave relay routes. These are broad-band circuits paid for and occupied mainly by telegraph and telephone services, with TV occupying only a portion of the band part of the time.


A transworld relay system would also serve for general communications as well as TV and would thereby fill a genuine need. A single broad-band trans-Atlantic service would in fact be

able to carry more traffic than the present cable and radio routes combined.

Engineering problem

Then what of that other difficulty—spanning the oceans between us and Europe on the one side and Asia on the other? The greatest single water gap—as Fig. 1 indicates—is the 290-mile jump between Iceland and the Faeroe Islands. Two other gaps—from Baffin Land to Greenland and from Greenland to Iceland—can be bridged with 275-mile jumps, and all other distances between practical station sites are shorter. The problem, then, is to maintain reliable communication over a maximum distance of 290 miles.

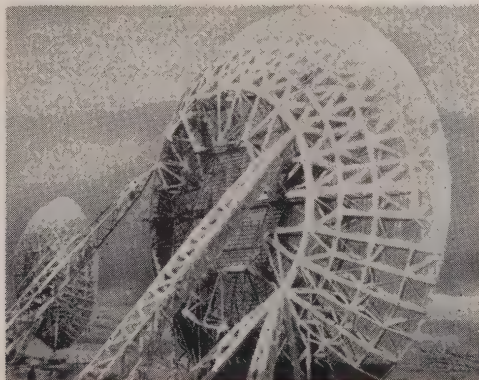Conditioned by our own experience with TV broadcast reception we may think of 290 miles as almost as bad as the whole Pacific, as far as sending and receiving TV is concerned. But we have recently been hearing more and more about *beyond-the-horizon* transmissions. The August, 1955, issue of RADIO-ELECTRONICS gave a detailed



60 - foot - diameter parabolic antenna used for scatter communications in our northern defense perimeter.

Courtesy Spencer-Kennedy Labs.

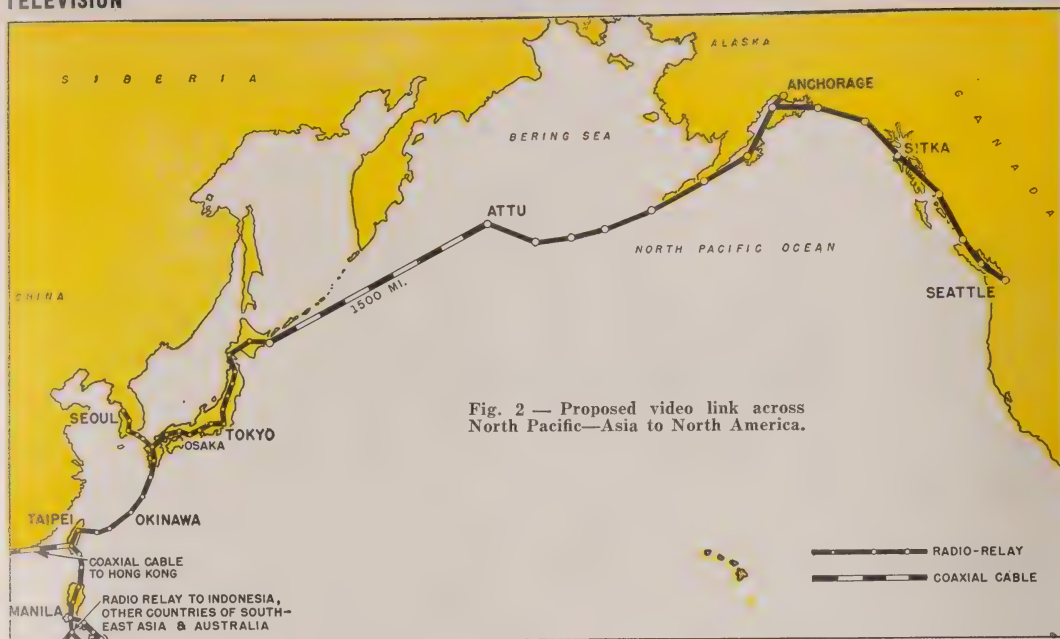


Fig. 2 — Proposed video link across North Pacific—Asia to North America.

account of experiments in which signals from the Bell experimental transmitter at Holmdel, N. J., were picked up regularly at MIT's research station at Round Hill, Mass. Experiments made in Newfoundland for a period of 5 months in 1954 (*Bell Labs Record*, February, 1956) proved that reliable communication can be maintained over a path of 290 miles (from St. Anthony to Harbour Main).

Just such long-distance communication has actually been working in commercial service for several years, though little may have been known of the underlying theory when it was first installed. The French *Compagnie Générale de TSF* has been operating a broad-band transhorizon radio link between Grasse, on the French mainland, and Calenzana in Corsica, since 1947. Frequencies are in the order of 100 mc and the distance is 127 miles. The antenna at Grasse is 1,900 feet above sea level and at Calenzana 1,050 feet.

A still longer jump is that between Mt. Cavo, near Rome, Italy, and Mt. Serpeddi, Sardinia, operated by the same company. A 48-channel telephone service is operated over a 242-mile range, with antennas approximately 3,200 feet high at both ends.

Both these systems are low-power. The French transmitters are rated at 100 watts and operate with 10-db gain antennas, and the Italian system uses 500-watt transmitters and 20-db-gain antennas. These distances could be increased enormously with the power—measured in thousands of kilowatts—used in recent American experiments.

Indeed, a number of spans are now being covered with moderate power. The antennas on our cover are proto-

types of those to be used in the Puerto Rico-Dominica system now under construction by the International Telephone & Telegraph Corp. These antennas, mounted on the roof of the Federal Telecommunication Laboratories, a division of IT&T, Nutley, N. J., have been in regular communication with Southampton, Long Island, N. Y., for the last year and a half. Distance is 91 miles; power 500 watts.

IT&T intends to use the same power for the Dorado, Puerto Rico, to Ciudad Trujillo, Dominica, link, as well as for a 240-mile span between Sardinia and the Spanish island of Minorca. Both these systems are relatively narrow-band (6 voice channels) and the Sardinia-Minorca link will use 60-foot dishes. On the other hand IT&T is using 10 kw on a system that will carry 1 TV and 120 voice channels between Florida and Cuba.

Broad-band tropospheric radio is also being used in our northern defense network—the famous DEW line. Detailed information on the number of stations and path lengths is, of course, not available, but it is understood that distances of at least 175 miles are being spanned.

Engineers have no doubt that bridging the longest gap in a world-wide communications service is simply a matter of power plus right antennas.

Beyond the horizon

What is this method of transmission that makes such distances possible? It is based on three fundamentals: recognition that a method of transmission not covered by traditional theory does exist; very high power; directional high-gain antennas.

That such a method of transmission exists has been known for some time. Shortly after the Grasse-Calenzana circuit opened, the *Annales d'Electricité* printed a report showing the fantastic spread between the calculated and actual signal strength—a spread of thousands of times. In 1950, a paper by Booker and Gordon in the *Proceedings of the IRE* announced that it was possible to communicate over greater distances with vhf and uhf than had formerly been believed possible. The paper further suggested that waves may have been reflected or scattered by discontinuities or turbulence in the troposphere or ionosphere.


The effect has been compared to that of a searchlight projecting its beams through foggy, dusty or smoky air. It is possible to see the area illuminated by the beam at distances far over the horizon, due to reflections from airborne particles, though the source itself may be well below the line of sight.

This "scatter" theory falls short in explaining a number of points and for some time other theories were sought. Recently, however, two Bureau of Standards bulletins have supported the turbulence idea very strongly, not even mentioning other possible hypotheses.

Incidentally, there are two types of beyond-the-horizon transmission—the tropospheric scatter we have been discussing, and an ionospheric type that operates best at distances of more than 600 miles. Because of multipath reflections, the ionospheric type is of greatest value for narrow-band transmissions and apparently is not applicable to broad-band systems.

All agree on two necessary factors

RADIO-ELECTRONICS

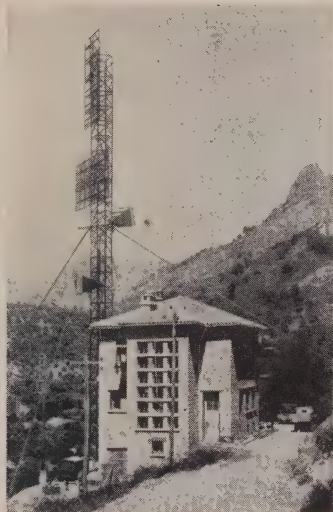

Compagnie Générale de TSF microwave installation at Calenzia in Corsica.

The microwave installation at Grasse on French mainland.



for beyond-the-horizon transmission—high power and directive antennas. The antenna on our August, 1955, cover was able to pack its 10-kw signals into a beam only 0.25° wide at 4,000 mc and broadening out to only 2.5° at 400 mc. Such quantities of power (or even greater ones) and such antennas are the solution to the engineering aspect of world-wide television.

Practical approach

Unlike many "global" projects, world-wide television is a thoroughly practical proposition. It does not depend on some stupendous combination of finance and engineering which would lay down a global system all in one piece. It can operate in pay-as-you-go stages, first from America to Europe, then to near Asia and so on to its point of origin.

Chief proponent of world-wide TV is William S. Halstead of Unitel, Inc. An old-time communications engineer, he has in the past not hesitated to depart from the more hidebound methods for a reliable communication system (See "Communication by Induction," RADIO-CRAFT, January, 1945).

Mr. Halstead has worked out a method for a feasible and practical system of communication around the world. The route would follow the course of Fig. 1 from North America to Europe, would branch off to the south and go eastward along the Mediterranean, through Turkey, the Near East, India,

Pakistan and Indonesia to the Philippines, thence north through the Japanese archipelago and on to the Aleutians by coaxial cable (Fig. 2). The connection between Asia and North America can then be made with even shorter jumps than along the Iceland-Faeroe Islands route from North America to Europe.

The plan was proposed some years ago, but has gained in interest greatly within the past year because of our increasing knowledge of beyond-the-horizon transmission, its reliability and its possibilities. Development of area networks which could form portions of the world-wide system has also helped demonstrate the idea's feasibility. Notable among these are the Mediterranean net, of which the French and Italian stations already mentioned form a part, and a Japanese system, in the design and installation of which Halstead played a prominent part.

We will not be at all surprised to see instantaneous TV from Europe within the next 4 or 5 years. And—since partial success breeds greater success—it may not be many more years before our screens show a presidential inauguration in Manila or a person-to-person visit to the home of the Emperor of Japan.

END

The writer wishes to express his appreciation for the assistance given him by William Halstead of Unitel, Arnold Goldburger of Intercontinental Electronics Corp. (U. S. associate of the Compagnie Générale de TSF), Ed. Felesina of Federal Telecommunication Laboratories and C. W. Creaser of D. S. Kennedy & Co.

Did You Ever? . . .

By H. A. HIGHSTONE

... **G**ET confused over which tubes belonged to the customer and which were yours, after solving a case of TV trouble by mass tube substitution? A 15c bottle of nail polish will help end such snafus. Use it to color sealoff tips of seven- and nine-pin miniatures. In the case of octals, color the bottom of the key.

... groan when some thrifty customer confronted you with a shopping bag filled with small tubes to be tested? Next time, after inserting a tube in its test socket, briefly jump the heater voltage to the next higher setting on the tester. With only a little practice you can check tubes about as fast as they can be popped in and out of the tester.


... get beaten on a poor-sound complaint? I nearly did a while back. A last-ditch hunch saved me when I investigated the speaker itself. Everything was OK after removing half a teaspoon of iron filings lodged between the voice coil and magnet pole-piece. (If it's a direct-coupled amplifier you're fighting, a variation as small as 0.75 volt in the first-audio cathode voltage can be the difference between crisp, clean sound and an effect reminiscent of a loudspeaker filled with mush.)

... forget to discharge a picture tube and get a sharp bite while rassing it around, removing it from a chassis? Then visualize yourself getting such a bite while the tube is suspended in midair, and dropping it. I used to forget and get bitten at intervals, but never after setting up my foolproof double-check system, like this: Discharge tube. Tape triple thickness of cardboard over second-anode connection, using Scotch Brand Tape No. 33 (10-kv insulation). I probably still occasionally forget to discharge tubes, but it doesn't matter any more. Might have already saved me the price of a glass eye.

... give up on a case of vertical jitter? Before you do, give the gain (contrast) control a short snort of standard cleaner-lubricant first. That's all a Mercury chassis recently required, although I got stuck for a callback in discovering the cure. The control was glazed; extremely loud bursts of sound from the speaker jarred it open momentarily, causing jitter which sometimes went to the point of frame-jumping. It never showed up in the shop where speakers ordinarily run in low gear, but in customer's home only, intermittently.

... blister your thumb and/or forefinger pulling some superheated rectifier or short-circuited small tube? Buy a few 10c hotpads next time you're in a dime store. Not even a slight scorch around here since thinking up this uncomplicated trick.

END

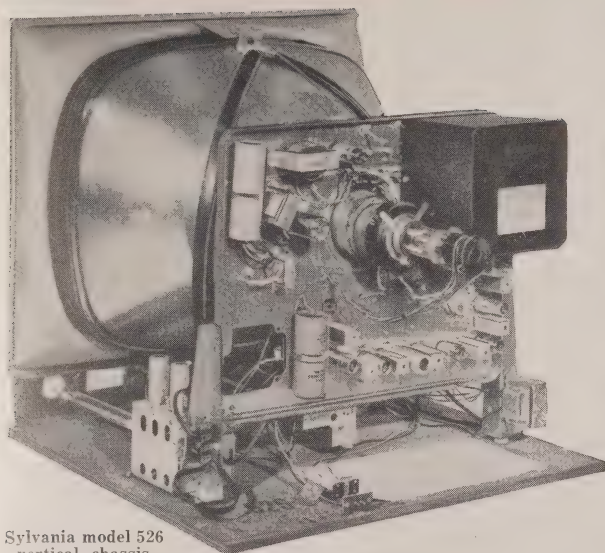

Sylvania model 526
vertical chassis.

EVER wonder why transformerless power supplies rarely use the once popular (and much-to-be-desired) full-wave doubler circuit? I say "rarely" because now and then an equipment manufacturer will take a chance on it—usually to his subsequent sorrow. True, some trade literature still displays the full-wave doubler along with series heaters. But today no tube manufacturer will honor a warranty when such a circuit is used.

Fig. 1 shows a conventional full-wave voltage doubler as used until a few years ago. It can be seen that point A rides at a positive potential of 150 volts with respect to chassis ground. Since one end of the heater string connects to point A and since all cathodes are effectively tied to the chassis, a sizable heater-cathode strain will appear along the entire string.

Because this dc potential on the heaters is a static thing, unflowing, there can be no voltage drop. Consequently, 150 volts will appear across the heater and cathode of every tube. The stress or strain will not diminish as you go down the series string.

This force, incidentally, is in addition to that exerted because of the ac potential which also appears across the cathodes and their respective heaters. The ac strain, however, does diminish as you go down the string since ac flows through the heaters.

Thumb through any tube manual now and observe the bad news. Most tubes are rated at only 90 to 100 volts, heater positive with respect to cathode. And that, precisely, is what killed the full-wave doubler circuit for use in transformerless power supplies.

* Senior liaison engineer, television design, Sylvania Electric Products.

*New circuit permits
transformerless design*

Heater— Cathode Stress in

FULL-WAVE DOUBLERS

By GEORGE C. CHERNISH*

It took some time for tube engineers to catch up with this one. Sylvania was one of the first to recognize the necessity for placing the present ratings on heater-cathode stress. However, shortly after these became standard in the tube industry, abnormal failures ceased.

Then the trend back to half-wave doublers began with, of necessity, larger filter chokes and electrolytics. Some manufacturers even returned to the transformer type chassis rather than contend with the lower ripple frequency of the half-wave doubler.

In Canada, where 25-cycle power is found in large sections of Ontario, the bad news hit hard. A ripple frequency that low is murder to filter out. With the now-condemned full-wave doubler, the resultant 50-cycle ripple had been

difficult enough to smooth. It meant a switch to "brute" filtering—or the transformer type chassis.

When management abruptly announced that we were about to enter the Canadian television market, this problem of heater-cathode strain became a pressing one. Among our various chassis requirements was a 25-cycle vertical model (see photo) employing a doubler circuit and series heaters. True, we could have used an isolation transformer to block the dc from the heater string, but that would have lifted the chassis out of the "transformerless" classification—not to mention the fact that there was no room to mount a big 25-cycle transformer on the little chassis. Unless it were well shielded and kept an appreciable distance from the picture tube, its 25-

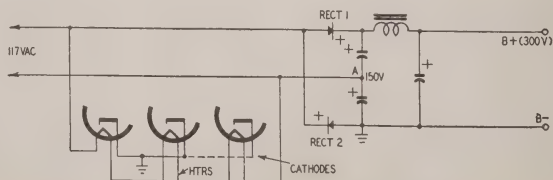


Fig 1—A full-wave voltage doubler.

cycle magnetic field would play havoc with the beam.

It appeared, therefore, that we were forced to turn to the half-wave doubler and brute filter. Using such a circuit, it soon became obvious that to obtain a high-quality picture, very large filter chokes would be required for 25-cycle operation. Even so, there was also the problem of wobbly interlace caused by the proximity of heater wiring to the neck of the picture tube—passing as it did through a hole in the chassis.

Fig. 2 shows a circuit developed by the author to overcome this problem of heater-cathode stress in full-wave doublers. Born of sheer necessity, it has been used for some time in the vertical chassis manufactured by Sylvania in Canada. It makes possible, for

the desired reduction of the injurious potential at C.

Capacitor C1 also plays a dual role. In addition to providing a constant opposition voltage at B, it acts as a dc filter for the pulsating current supplying the series string. Its value depends on the total voltage required by the heaters and the level to which it is required to reduce the damaging potential at B.

As for RECT 3, conventional radio-television stacks may be used. There is nothing special or off-standard about any of the components. RECT 1 and RECT 2 are the same as in Fig. 1. In both cases, these may be vacuum tubes.

Two other important advantages are gained with this circuit: heater-induced hum is drastically minimized; in tele-

Next, determine the value of electrolytic capacitor required for C1. After the rectifier has been wired in, start with 40 μ f, shunting with other capacitors until rated current flows through the string at normal line voltage. Then a single unit may be selected and installed permanently.

If no dropping resistor is presently used in the series string, one must be inserted. However, when the first tube in the string is, say, a 25Z5, which has a high heater-to-cathode rating, R1 may not be necessary. The trick in any event is to make sure there is enough resistance between the first tube of low heater-cathode rating (less than 150 volts) and the line at X, so that R1 will function as explained earlier. The greater the resistance required, the larger the value of C1.

Measure heater-to-cathode voltage on a vtvm. The reading will be an approximation only, particularly in TV receivers where pulses on the cathode of the damper tube influence polarity at its end of the heater string. However, unless checking a new design in the lab, more elaborate equipment and test procedures are not needed for checking.

Circuits have a peculiar way of growing on us. Sometimes, while designing a conventional series string, we run out of line voltage. Perhaps we would like to use five 25-volt tubes. Or maybe a proposed tube complement in a TV chassis requires more than 117 volts for its heaters. In either case, we have, as it were, too much voltage for a split string—yet not enough for a single string. This problem is quickly eliminated with the circuit of Fig. 2 since, by merely increasing C1, we can obtain an effective dc potential higher than the rms value of the ac line.

Because it lends itself so readily to miniaturization, this new circuit is currently finding favor with manufacturers of airborne and other portable communications equipment. Although it was developed to fill a specific need here at Sylvania, the reader may think of many applications undreamed of by the inventor.

END

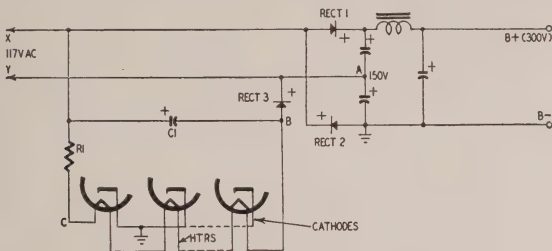


Fig. 2—Circuit developed by author.

the first time, a high level of picture quality in 25-cycle television receivers employing series heaters. Here at home, it also imparts a higher degree of quality to those sets using a series string.

During that half of the input cycle when X is positive with respect to Y current will flow through the selenium rectifier RECT 3 charging capacitor C1. One end of the heater string, point B, will assume a polarity which opposes the 150 volts at A. The net positive potential (with respect to chassis ground) depends on the value of C1, and can be made very small. In the Canadian design, point B measured +9 volts.

During the next half of the input cycle, while X is negative with respect to Y, RECT 3 does not conduct, thereby effectively blocking the 150 volts at A. However, X also carries this static dc potential developed at A, for somewhere, either on a pole outside or in a near-by substation, there is a distribution transformer winding linking X and Y. We.e it not for dropping resistor R1, we would be back where we started on this problem of heater-cathode stress.

Resistor R1 performs two functions. First, it serves in its conventional role as a current-limiting resistor to protect the heater string. Second, it reduces the injurious static potential developed at A which now must flow, because of this special circuit, and dissipate itself to some harmless level through extraneous circuitry linking X and Y. The value of R1 will depend, therefore, not only on the amount of current limiting required, but also on

vision receivers whose supply frequency is less than 100% stable, where heater wiring runs near the picture tube—as in vertical chassis—there is far less likelihood of trouble from asynchronous operation.

Anyone owning a transformerless radio or television set manufactured prior to the clampdown on heater-cathode ratings may greatly prolong tube life with this protective circuit. The first step would be to verify that the full-wave doubler is used therein. Then, a rectifier one size larger than normal heater current calls for should be selected for RECT 1. For example, if the series string draws 300 ma, choose the 350-ma size. This is to allow for possible increase in line voltage from time to time.

In **RADIO - ELECTRONICS** October issue—

UNDERGROUND ANTENNA

A TV signal distribution system that gets away from disadvantages of aerial cables

TV ANTENNA ADJUSTMENTS FOR ELIMINATING INTERFERENCE

LONG-TAILED CASCODE PAIR AMPLIFIER

FLEA-POWER TRANSISTOR TRANSMITTER

Order your copy NOW!



WHEN picture and raster are normal, any defect in the sound that cannot be corrected by replacing audio tubes or checking voltages and the audio amplifier calls for alignment of the sound if section. This includes all circuitry from the sound takeoff point to the output of the ratio detector. The defeat can include anything from weak or no sound to drift, distortion and oscillations. Sometimes oscillation causes patterns to appear on the screen.

Sound if alignment is comparatively simple because only one frequency is involved—4.5 mc. Test equipment requirements are few and the basic work consists of peaking the sound if stages for maximum output and balancing the ratio detector for zero output at 4.5 mc.

A highly accurate 4.5-mc signal generator is necessary. The best source is a television signal where the video and sound carriers are transmitted precisely (crystal-controlled) 4.5 mc apart. When a TV signal is not available, a signal generator—checked against a crystal calibrator or some other frequency standard—may be used. Accuracy should be within 1 kc at 4.5 mc.

In general, it is a good idea to check the alignment of the video if stages before going on to the 4.5-mc sound. This is especially true where the picture appears degraded. However, where trouble appears limited to the sound section only, with the picture strong and sharp on all channels, video if alignment may be bypassed.

While the circuitry of the ratio detector will vary slightly from set to set, the fundamental operation remains the same. Thus, while space permits a discussion of a limited number of circuits only, the alignment procedure may be applied to virtually all ratio detectors used in today's television receivers.

Fig. 1 shows the sound if section of the Motorola TS-402 chassis. When aligning with a TV signal, use the fine-tuning control and detune the signal slightly until you can measure from about 5 to 8 volts from the positive side of stabilizing capacitor C56-b to chassis. This procedure will permit

operation below the limiting level of the FM driver tube and provide sharp alignment.

If a signal generator is used, tune it exactly to 4.5 mc, adjust its output to approximately 5,000 microvolts and short the antenna input terminals or remove the antenna lead-in. Connect the hot side of the unmodulated AM signal generator output to pin 2 of the third if transformer T3; the cold side goes to chassis. From this point on, the alignment procedure is the same whether a TV signal or generator is used.

From the positive side of C56-b, a 10- μ f electrolytic capacitor, connect a dc vtvm or other high-impedance voltmeter (at least 20,000 ohms per volt) to chassis through a decoupling resistor of about 10,000 ohms. The first tuned circuit after the point of sound takeoff is C62-L33; tune L33 for maximum reading on the voltmeter (parallel resonance). Interstage trimmer C66 should also be tuned for maximum reading.

During alignment, as adjustments are tuned to resonance and the 4.5-mc signal strength is increased, reduce the signal generator output or TV signal input to the receiver to prevent overloading and to get sharper peaks and nulls. It is often advisable to insert an attenuation pad at the antenna input.

The ratio detector primary (top core in this chassis) is now tuned for maximum reading on the meter. In tuning this and the secondary circuits of the ratio detector there will usually be two tuning points. Only one is correct—the point at which the cores are farthest out of their windings (minimum inductance). The inner position produces improper bandpass.

For balancing the secondary, connect a matched (1%) pair of 100,000-ohm resistors across the ratio detector load resistor R62 and connect the ground side of the meter between the resistors. The high side of the meter is connected to the output of the de-emphasis network (junction of R63 and C74).

Now vary the ratio detector secondary for zero response on the lowest range of the meter. Make sure the slug is tuned to the outside of the coil winding—this corresponds to the crossover point of the detector curve. The symmetry of the curve may now be checked by tuning the signal generator 25 kc above and below 4.5 mc and observing the plus and minus voltages obtained, reversing the meter connections as necessary. The voltages should be approximately equal. If not, repeat the entire procedure and try replacing the ratio detector tube. Repeat the process for maximum accuracy.

Fig. 2 shows the sound if system of the Admiral 20Y4H chassis. Here again, either a TV signal or generator may be used. Tune to a strong station or connect the high side of the generator to the junction of L304-L305 (in series with an isolating resistor or, better still, a .01- μ f capacitor); the

generator cold lead goes to ground. Connect the vtvm from the negative side of C206 (4 μ f) to chassis.

With the vtvm set on a low dc scale and the generator tuned to exactly 4.5 mc, vary L201 and the primary of the ratio detector transformer for maximum indication on the meter. Keep reducing generator or signal strength so the meter reading does not exceed a few volts.

To adjust the ratio detector secondary, move the ungrounded lead of the vtvm to point A and vary the secondary core for zero reading on the meter. It will be between a positive and negative maximum. If available, use a vtvm having a zero-center scale.

To touch up the ratio detector secondary using a TV signal, vary the core for best sound with minimum buzz. Make this adjustment carefully since only a very slight rotation will usually be necessary. The correct alignment point is between the two maximum buzz peaks that are generally obtained by turning the slug back and forth about one-half turn.

While manufacturers' alignment instructions vary slightly, the above indicates the general process; align all sound if circuits up to and including the ratio detector primary for maximum output across part of or the entire stabilizing capacitor (the voltage developed here acts as sort of an avc indicator or signal strength). Align the ratio detector secondary for zero output (balance) at 4.5 mc with the vtvm connected between the electrical center of the secondary and the output of the de-emphasis network.


Sound buzz and oscillation

A peculiar condition occurs in an RCA KCS83 chassis. An intermittent oscillation can be clearly seen on the screen. At other times this trouble disappears and there is a strong buzz in the sound with an accompanying beat pattern on the screen. The customer said both defects occurred about the same time, but it seems unlikely that one component would cause both symptoms.

I have replaced all rf and if tubes, both video and audio, without improvement. All voltages appear as per RCA schematic and, while I have noted changes in the sound signal during the trouble, I have been unable to clear up the defects.—T. L., Richmond, Va.

Ordinarily, from the information furnished, I could only suggest a thorough check of all components in the sound if section together with alignment. However, in this chassis the probability is very great that the trouble is due to a defective dual capacitor Cl-a and Cl-b (Fig. 3). It is used as a screen and cathode bypass capacitor in the first sound if amplifier.

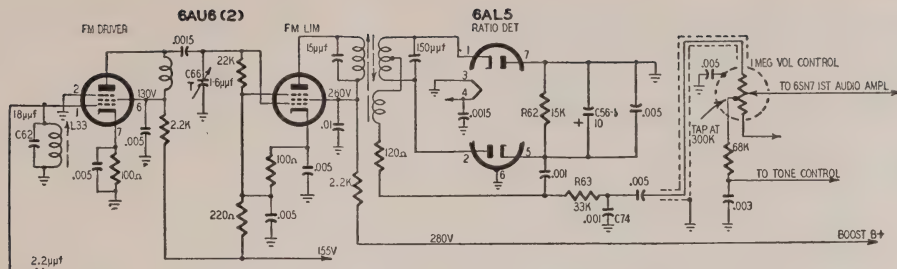When Cl-b decreases in capacitance, as it often does, this stage oscillates at about 2 mc or so and will generally produce the buzz and beat pattern you





describe. Replace this capacitor with two separate units. The cathode bypass should be a .01- μ f capacitor, with the screen bypass preferably a smaller unit of about .001 μ f. Both capacitors should have a positive temperature coefficient. Try to maintain as closely as possible the original lead dress, keeping the leads short and to the same points on the chassis.

Line fuse blows

Back in the shop for the third time is a Sentinel 443 set with a blown fuse in the primary circuit of the power transformer. Every tube has been checked and the wiring carefully inspected. What makes this all the more puzzling is that there is a ½-ampere fuse in the secondary circuit of the power transformer which does not blow. On this basis I assume that the trouble must be in one of the filament circuits but have drawn a complete blank.—P. R. Waco. Tex.

The fact that the ½-ampere secondary fuse does not blow is important. And since you have checked all tubes and filament wiring without finding any faults, the fuse blowing is probably due to a defect that was very common about 5 years ago when this particular chassis was produced.

There is a 1-inch self-tapping back mounting screw that holds the back to the chassis near the interlock plug. This places it very close to one of the filament pins of either the 6W4-GT or 6BY5-G rectifiers and occasional vibrations will produce contact and blow the primary fuse. This can be corrected by placing a heavy washer under the head of the screw, thus shortening it. On the possibility that the fuse is blowing due to transients, replace it with a 3-ampere Slow-Blo unit.

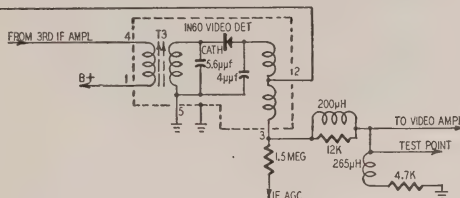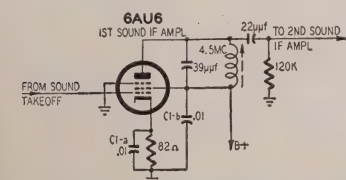

Phase reversal in picture

The picture on a General Electric has practically no contrast range and could be considered a monotone. The set, model 810, shows very little change when the contrast control is varied. In fact, it would be correct to say that the picture is reversed—whites where the blacks should be and vice versa.

At first I took it to be the picture tube, but a new tube had no effect. I also noted that synchronization was very poor. The trouble could not be weak signal because there is no snow in the picture. I then aligned the video if amplifier. This produces a slight change, but not very much. All if and video amplifier tubes have been replaced with no luck.—B. S., Houston, Tex.

From your description, the trouble seems almost surely to be in the video amplifier section. Often many effects are mistakenly called a phase reversal.

However, if you clearly see a black-white reversal of tones, accompanied by very little contrast and a faint signal, the cause is an inoperative video amplifier stage. With this the video signal could feed through the internal grid-to-plate capacitance of the 12AU7 (Fig. 4). The usual 180° phase reversal would be missing, causing the black-white reversal. In addition, with sync pulses of the wrong polarity, synchronization would be virtually destroyed, depending on how close to 180° the phase reversal was.

So check for plate voltage on the first and second video amplifier stages. Watch out especially for R39, as unreliable a resistor as any. It often opens and cuts off that stage. Also replace C27 regardless of what your checker indicates. If this does not help, check all components shown in Fig. 4. Most likely, the trouble will be, not an off-value part, but one completely open or shorted. END


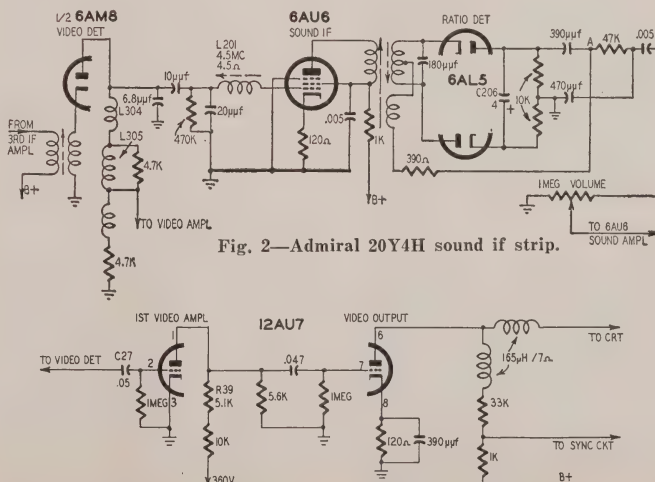


Fig. 3—The first sound if amplifier stage in the RCA type KCS83 chassis.

Fig. 4—Video amplifier in G-E 810.

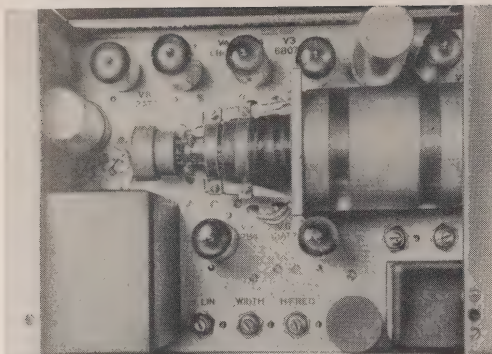

Dage television camera—controls are easily accessible.

ITV PULSE-GENERATOR TECHNIQUES

By EDWARD M. NOLL*

*Part II—The noninterlaced sweep
system for closed-circuit TV*

THE noninterlaced pulse generator of a closed-circuit television system forms line-rate (horizontal) and field-rate (vertical) timing pulses. These two pulse-generating circuits are not locked together, as they must be in an interlaced system, but run freely with respect to each other. Consequently, the noninterlaced pulse generator forms a sequential line structure instead of an interlaced one. When a standard television receiver is synchronized by the pulses from a closed-circuit camera using a noninterlaced pulse generator, a 60-frame raster is formed having some 250 scanning lines. If the pulse generator were of an interlaced type, a 30-frame raster with some 500 lines would result.

The noninterlaced generator is frequently used in closed-circuit cameras because of its circuit simplicity—it requires no counter chain nor phase-comparison circuit.

The pulse and sweep systems of the Dage 60-B closed-circuit camera are shown in Fig. 1. The frame-rate 60-cycle pulse is derived directly from the 60-cycle power line. A 60-cycle high-voltage sine wave is taken from a winding on the power transformer and applied through resistor R1 to a rectifier diode and the grid of V1.

The sine wave is clipped by the selenium rectifier and then fed to a differentiating or sharpening circuit consisting of C1 and R2. This circuit shapes the clipped sine wave which must excite the discharge tube grid.

The shaped 60-cycle wave applied to the grid has a very high amplitude and drives the tube between cutoff and grid conduction. In fact a major portion of the applied grid waveform is below cutoff and therefore holds the tube cut off for a long interval. During this time a sawtooth trace is formed across capacitor C4. As this capacitor charges toward B plus through resistor R3, a sharp positive swing of the grid waveform causes the discharge tube to conduct for a short interval. Now the C4 voltage is discharged because of the shunting of the conducting tube.

This portion of the cycle on the

capacitor constitutes the retrace segment of the generated sawtooth wave. Hence the sawtooth wave generated in the plate circuit of the discharge tube can be used as a driving sawtooth for application to the grid of the camera vertical output tube. The output tube develops the deflection energy for the vertical deflection coil of the Vidicon camera tube.

Actually, the grid of the discharge tube is driven so far positive that it draws grid current and charges capacitors C2 and C3 to a high negative value. This action limits the extent to which the grid can be driven positive and prevents excessive plate current flow. The negative capacitor charge and the now-swinging negative portion of the grid waveform carry the tube way beyond cutoff. Once again capacitor C4 charges to begin another frame scanning cycle.

Note that the discharge tube conducts for only the short interval that the grid waveform (Fig. 2) swings positive. However, during this time the cathode-plate current is high and develops a sharp positive voltage across cathode resistor R4. This positive voltage is in the form of a pulse because, as soon as the tube is driven quickly to cutoff, the plate current ceases and no voltage is developed across the cathode resistor. The pulse developed across R4 coincides in time with the discharge period of the sawtooth wave developed across capacitor C4. The retrace time of the sawtooth constitutes the synchronizing and blanking periods of a television system. Hence the pulse developed across the cathode resistor can be used for synchronizing and blanking functions because it does coincide with the retrace period of the deflection waveform.

This is an important fact in understanding the operation of a closed-circuit system. During the retrace interval of the deflection waveform the scanning beam of the Vidicon is in retrace. Thus the camera itself must be blanked during this period. The blanking pulse is, in fact, the pulse developed in the cathode circuit of the discharge tube. Furthermore this very same sync-blanking pulse is also in-

serted into the video signal and, at each television viewer, will cause the picture-tube beam to be blanked during vertical retrace.

This very same pulse in a closed-circuit system can be used for synchronization. At the viewer the pulse is also applied to the vertical synchronization and sawtooth-generating circuits. As with standard TV receivers the synchronizing pulses start the retrace periods of the sweep waveforms. In other words, the retrace period of the viewer vertical sweep waveform has been made to coincide with the retrace period of the camera vertical-deflection waveform. In effect the vertical motion of the viewer picture-tube scanning beam corresponds with the similar motion of the Vidicon camera beam.

The frame rate is set at 60 cycles and framing thus follows in frequency and phase the variations of the power-line frequency. The close lock-in between frame rate and power-line frequency minimizes many of the hum and synchronizing disturbances to which a television system can be subject. It does so because any 60- or 120-cycle hum field produces a stationary disturbance on the scanning raster because the scanning rate itself follows in frequency and phase the troublesome hum activities.

The sawtooth wave developed across capacitor C4 is properly spiked by resistor R5 before application to the grid of the Vidicon vertical output tube. This step insures a linear change of current in the vertical deflection coil. A low-impedance coil is used and, consequently, it can be driven by a cathode-follower output stage. During the trace portion of the sawtooth wave applied to the grid of the vertical output tube the current rises linearly in the vertical deflection coil to produce a linear motion of the scanning beam. The cathode potentiometer permits linearity control by setting the output tube bias at a correct point.

Horizontal pulse formation

The horizontal pulse generator is a combined horizontal output tube and cathode-coupled multivibrator. To in-

* Author, *Closed-Circuit and Industrial Television* (Macmillan).

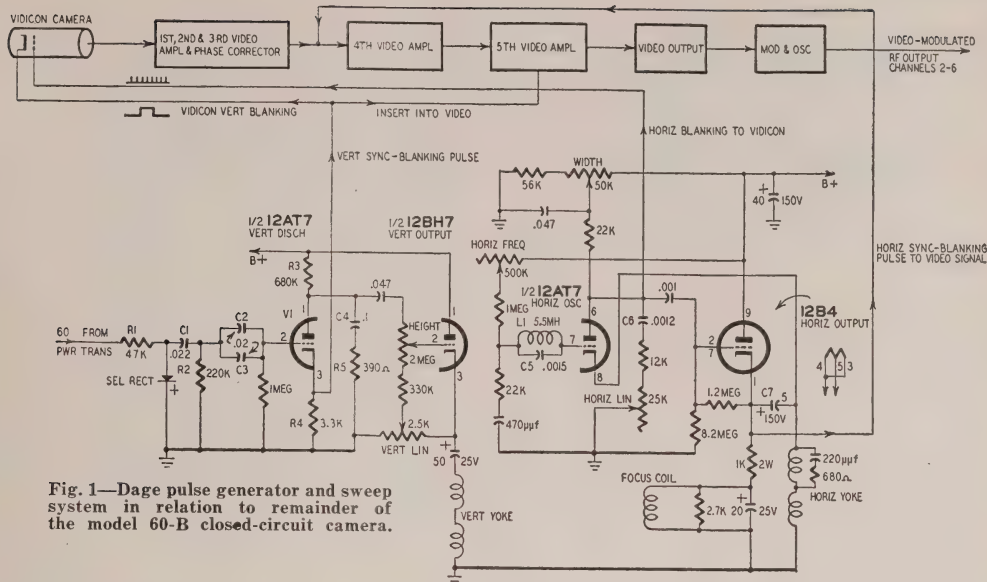


Fig. 1—Dage pulse generator and sweep system in relation to remainder of the model 60-B closed-circuit camera.

sure stable operation of the multivibrator at the high horizontal frequency, a stabilizing tuned circuit consisting of inductor L1 and capacitor C5 is inserted in the grid circuit of the first section. The multivibrator frequency is also controlled in this grid circuit by regulating the B-plus value toward which the grid circuit discharges during the nonconducting period of the first section. During a long cutoff period of this tube, capacitor C6 charges toward B plus to form the trace portion of the deflection waveform. When the feedback cycle drives the first section into conduction for a short interval, this capacitor discharges quickly because of the shunting influence of the tube, forming the retrace period of the horizontal deflection waveform.

The horizontal sweep waveform excites the grid of the horizontal output tube. In so doing it produces a sawtooth current in the horizontal deflection coil located in the cathode circuit. Inasmuch as the second section conducts for a longer period than the first, the current in the deflection coil rises linearly to produce the horizontal trace portion of one line.

The dc required by the focus coil also flows in the horizontal-output cathode circuit. The cathode of the first section is linked through capacitor C7 to the cathode of the second section to form the necessary cathode-coupled feedback link to sustain relaxation oscillations.

The width control is in the plate circuit of the first section. It regulates the B plus toward which capacitor C6 charges during the trace interval. Therefore it regulates the amplitude of the deflection waveform applied to the grid of the second section.

The second section of the horizontal cathode-coupled multivibrator conducts

for a long interval. Consequently, a long positive pulse is developed at the cathode during this period. When the tube is nonconducting, the cathode waveform drops to zero. However, if we notice the cathode waveform closely (Fig. 3) we can see that in effect it can be considered a short-duration negative pulse. This negative pulse coincides with the horizontal retrace period. Again we have developed a useful pulse output that coincides exactly with the timing of a horizontal retrace interval. Thus we can use this pulse as a combined horizontal sync-blanking pulse for synchronizing the horizontal sawtooth-forming circuits of the viewer and to supply blanking for the picture-tube scanning beam of the viewer.

The functional block diagram of Fig. 1 demonstrates the simplicity of the synchronizing methods employed in closed-circuit television. The pulse generator is really a combined pulse and deflection waveform generator. By proper choice of circuits the sync-blanking pulses, as formed, can be made to coincide with the retrace intervals of the camera-tube vertical and horizontal deflection waveforms. Therefore the system can be synchronized and viewer and camera tubes blanked coincidentally with only a few tubes.

The number of pulse-generator controls is surprisingly few. The vertical circuit contains linearity and height controls only. No vertical frequency control is necessary because of the direct link with the 60-cycle power frequency. The horizontal circuit contains frequency, width and linearity controls.

The horizontal frequency control is adjusted to lock in the picture on the viewer. In many cases the viewer is a standard television receiver which has been adjusted previously to the correct

horizontal frequency by tuning in a standard telecast station. The horizontal frequency of the camera is then adjusted until it too produces a locked-in picture on the receiver screen.

The linearity and size adjustments are generally set correctly at the factory. However, if adjustments are necessary a standard test chart is provided by the manufacturer. The chart is placed in position in front of the camera at a prescribed distance and the linearity and size controls are set to produce a linear and full-size picture on the viewer screen.

The next article will be on an interlaced pulse generator for closed-circuit television.

TO BE CONTINUED

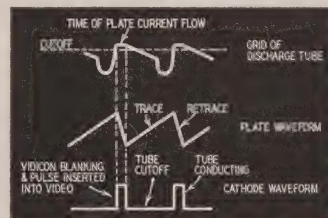


Fig. 2—Waveforms of the vertical pulse and sawtooth-forming circuits.

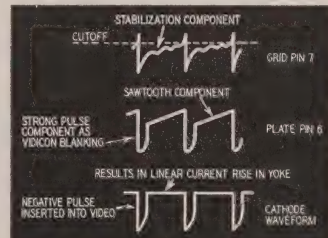


Fig. 3—Horizontal multivibrator action.

VTVM

servicing is not so simple!

Recognize the limitations when servicing with this instrument

By ROBERT G. MIDDLETON *

THE vtvm appears to be an easy-to-use service instrument and, in general, this is so. Nevertheless, perplexing situations arise in practice. Some of these are discussed and analyzed here.

A good vtvm will always indicate the same resistance value, no matter which range is used, provided the resistor under test is linear. However, not all resistors are linear. Consider, for example, the filament of a small receiving tube. It has a higher resistance when hot than when cold (Fig. 1) and hence exhibits rated resistance only when rated voltage is applied to the terminals. But the voltage applied to the filament varies with the range which is used.

Consider, for example, a vtvm with a 1.5-volt ohmmeter battery (see photo) used to measure the filament resistance

of a 1R5:

1R5 TUBE		
Range		Ohms
R×1		24
R×10		10

Since the 1R5 is rated to draw .05 amp at 1.4 volts, its rated filament resistance is 28 ohms. Hence it appears that the rated resistance was approached on the R×1 range, but was not approached on the R×10 range.

Consider a picture-detector crystal diode. The diode has a nonlinear characteristic, like a tube filament. Fig. 2 shows the difference between a linear and a nonlinear detector. The apparent resistance of a crystal diode on various vtvm ranges is as follows:

1N34A CRYSTAL

Range	Resistance (ohms)	
	Forward	Backward
R×1	120	unreadable
R×10	150	unreadable
R×100	295	800,000
R×1,000	1,000	250,000
R×10,000	4,000	140,000
R×100,000	20,000	unreadable

The varying resistance values are easy to understand by observing Fig. 2. The varying E/I ratio implies a different resistance value at different applied voltages. Thus, a rated front-




The Simpson model 303 vacuum-tube voltmeter — uses 1.5-volt ohmmeter battery.

to-back ratio for a crystal diode is meaningless, except at a specified voltage.

High-frequency measurements

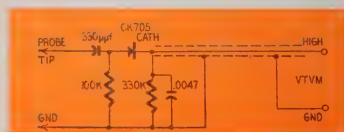To measure high-frequency voltages, a detector type probe, such as shown in Fig. 3, is often used. This probe provides an indication of the peak values of unmodulated high-frequency voltages when the output from the probe is applied to the dc input terminals of a vtvm. It also indicates the peak value of the carrier voltage in a modulated



Courtesy Simpson Electric Co.

Fig. 3—Circuit of detector probe—measures peak of high-frequency voltages.

wave. The probe indicates the rms value of the modulating voltage in a modulated high-frequency voltage when its output is applied to the ac input terminals of a vtvm. Indication of the rms value is the result of passing the modulating voltage as an unrectified and unfiltered component in the probe output voltage, and the calibration of the ac ranges of the vtvm in rms values.

Just as the crystal diode is a nonlinear device, so is the demodulator probe. The practical result of this nonlinearity is that when voltage values of less than 1 are measured, the scale indication is somewhat less than the actual value of the voltage. And as

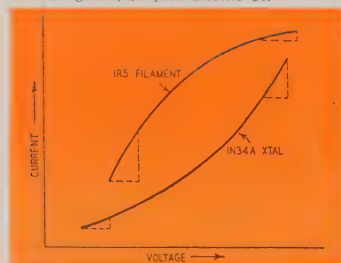


Fig. 1—Voltage-current characteristics of crystal diode and tube filament. Dashed lines indicate voltage-current ratio at opposite ends of the curves.

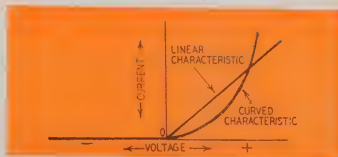


Fig. 2—Detector characteristic types.

smaller and smaller voltages are applied, the error becomes proportionately greater. To avoid this difficulty it is necessary to provide an auxiliary scale for the probe when small voltages are to be indicated. The probe scale is cramped at the low-voltage end, as is required by the diode characteristic.

Some care must be taken when applying the output from a high-frequency probe to the ac voltage ranges of a vtm because some service vtm's do not have a high-impedance input for ac, but provide only a copper-oxide or selenium type ac circuit which has a low input impedance of 1,000 or 5,000 ohms per volt. Unless the input impedance is much higher, the probe will not operate satisfactorily. The input resistance of the instrument shown in the photo is 270,000 ohms on the ac-volts range.

Test points must be avoided which apply excessive input voltage to the crystal probe, as loss of sensitivity or complete burnout will result. If a 1N34 crystal is used, probe manufacturers usually rate the maximum input voltage as approximately 20. Test points which have a high impedance must also be avoided, since the loading effect of a demodulator probe is appreciable.

Thus, signal tracing in the if circuits of a TV receiver with a vtm and demodulator probe is a questionable procedure because the input capacitance of the probe detunes the circuit under test and impairs the measurement. Sometimes the indication is only attenuated, but sometimes the shunt capacitance throws the circuit into oscillation and the indication is enormously increased. Since the lower voltages which can be read on a vtm scale are useful only at the last if stages, signal tracing by this means is largely impractical.

Testing with weak batteries

A linear resistance will appear to be nonlinear when tested with a vtm which has weak batteries in the ohmmeter circuit. For example, a 100-ohm composition resistor gave the following apparent readings when tested under this condition:

Range	Ohms
R×1	50
R×10	90
R×100	100

The variation in apparent resistance is caused by the varying current drain in the ohmmeter circuit on the various ranges and the great increase in internal resistance of the ohmmeter battery on the heavy-current ranges. A fresh battery has a practically constant internal resistance in the ohmmeter circuit. It gives correct indications on all ranges.

Tracing ac signals on dc range

It is sometimes not clearly understood how an ac signal can be traced through some sync circuits; for example, using the dc voltage ranges of a vtm. How

this is possible is shown in Fig. 4. The applied sync pulse is an ac voltage waveform which is partly positive and partly negative. There is just as much positive electricity in the waveform as there is negative, so that the zero-volt level in the waveform exists at the point which divides the waveform into equal positive and negative areas. ("As much" electricity means $\text{current} \times \text{time}$. Zero-volt line is a time axis.)

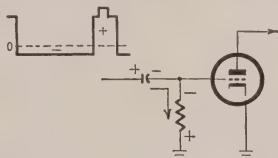


Fig. 4—Developing grid-leak bias.

The positive excursion drives the tube to grid current flow in a circuit using signal-developed bias. The grid current flow traps electrons on the grid coupling capacitor, which then have a limited rate of escape through the grid leak. The end result is the buildup of a negative dc voltage on the grid when a signal is present. This dc voltage from grid to ground can of course be measured on the dc ranges of a vtm.

To obtain a clearer understanding of the voltages in a capacitively coupled circuit, refer to Fig. 5. Here the sync pulse is superimposed on the dc plate voltage on the plate side of the coupling capacitor; the voltage here is pul-

sating dc (which never goes negative) and consists of an ac voltage superimposed on dc. The capacitor will "conduct" the ac voltage but blocks the dc.

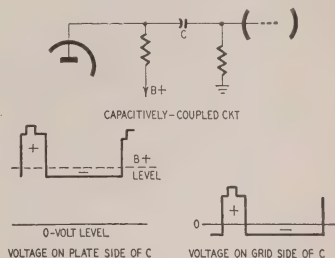


Fig. 5—Voltage relationships on plate and grid sides of coupling capacitor.

When the ac function of a vtm is used to check the voltage on either side of C, the same value is indicated. This equality results because the ac function of the vtm itself utilizes a blocking capacitor whereby only the ac component of the voltage is passed into the meter circuit.

When the dc function is used to check the voltage on either side of C, different values are indicated. This inequality results because the dc voltage on the plate side of C is determined by the value of B plus; the dc voltage on the grid side of C is determined by the amount of grid current drawn by the tube in response to the applied ac signal.

END

DAUGHTER OF NECESSITY

FORCED to do a minimum amount of lifting due to a bad back, I constructed what I believe to be an interesting and unusual workbench arrangement. This setup (see photo) has been in use some 4 years with no changes except the addition of antenna outlets. For these, I installed Blonder-Tongue equipment composed of channel strip amplifiers for channels 3, 4, 12 and 13, using an eight-outlet distribution amplifier to feed my workbench.

The bench is approximately 40 feet

long, with National Trolley rail mounted overhead. From this I have all my test equipment, as well as the telephone, suspended on rollers so that it can be rolled to any location on the work bench. The telephone line travels on pulleys from one side of the rack with the ac power (to test equipment) traveling on the opposite side.

This arrangement permits me to work my entire bench with one set of test equipment by rolling the instruments to any position.—Jack Wise



AUDIO SIGNAL GENERATOR

Resistance-tuned instrument is small, light, safe and versatile

By LYMAN E. GREENLEE

A SIGNAL source was needed for checking audio equipment. The basic requirements were: small size, light weight, adequate isolation from power lines, complete frequency coverage, provision for monitoring the signal with a scope and enough power output to check loudspeakers without additional amplification. No low-priced commercial equipment available met all the above requirements, so I designed and built my own audio signal generator. It is rugged and reliable, and anyone interested in working with sound equipment may find it a tool well worth the time and cost of construction.

No chassis is used or needed—all parts are mounted directly on the front and back covers of a standard 6 x 6 x 6-inch utility cabinet (see photo). Although the front and back panels are permanently wired together, they can be easily removed from the cabinet for service by turning the back panel at an angle so it will slip through along the diagonal.

The power supply, which is built on the back panel, uses a small filament transformer combined with an output transformer for isolation from the power lines, a necessity for successful operation of test equipment. This power supply has proved very satisfactory. Since the normal plate drain of the two tubes is about 5 ma, the small transformers do not even get warm. This power supply is easily adapted to other test equipment and is much lighter than most supplies using conventional power transformers.

A 12AU7 miniature dual triode is used as a resistance-tuned audio oscillator. With the values shown in Fig. 1

the tuning range should be from about 75 to more than 30,000 cycles; the upper range extends well beyond the limits of the human ear. The output voltage is uniform through the audible range but will fall off rapidly as the ultrasonic limit is approached. The top and bottom frequency limits will depend somewhat on the characteristics of individual tubes and the tolerances of the various parts.

The values of C1 and C2 have a considerable effect on the frequency coverage of this generator. The combination of .002 and .005 μ f, respectively, provides a usable range from 75 to 35,000 cycles. Using .007 and .01 μ f, the range goes from 50 to 25,000 cycles; .012 and .015 permit a range from 25 to 15,000 cycles. Thus, increasing the values of C1 and C2 gives a lower frequency response at the expense of reducing the high-frequency coverage.

There is a slight shift in frequency as the feedback control is varied. To calibrate the dial accurately, a fixed setting of this control must be marked on the front panel. This point may be ignored for most applications since we are not always too concerned about the exact frequency when checking speakers or audio amplifiers.

The feedback control should always be set at the lowest point which will produce satisfactory oscillation. This adjustment should be made while observing the waveform on an oscilloscope so that the waveform will have minimum distortion. If excessive feedback is used, the output will contain highly distorted pulses. Actually, owing to the stabilizing effect of the 3-watt bulb in the cathode of the 12AU7, very little change in the feedback control is neces-


sary while tuning from one end of the dial to the other. By monitoring the output on a scope, the distortion can be held to a minimum and a very pure sine wave will result. The waveform is of little concern unless checks for distortion are being made.

The signal generator is useful for making distortion checks when used with an electronic switch and scope so that input and output waveforms can be viewed simultaneously. I found it convenient to monitor the output on a small scope, using a larger scope as a signal tracer to observe the waveform at various points in the amplifier being checked. This method is faster and involves no difficulties in the way of feedback, crossed wires and haywire hookups, bound to occur if a single scope is used with the electronic switch for signal tracing. For an overall check the electronic switch may be preferred because a direct comparison of waveforms can be made on the same screen.

The 12AU7 feeds a 6C4 miniature triode used as the output amplifier. A low-voltage high-current signal is thus available for checking speaker voice coils. However, since some distortion is introduced by the small output transformer, a direct output connection from the 6C4 plate is also provided. This connection may be used when making checks with the scope for distortion or for any application where higher voltage output is needed. Although the distortion from the output transformer cannot be detected by ear, it is easily visible on a scope.

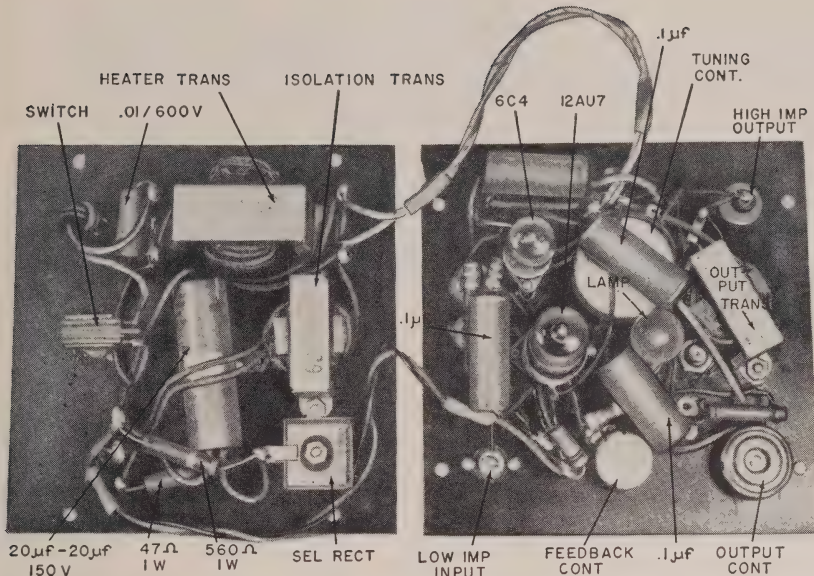Provision is made for connection to the 6C4 grid through a pin jack and 0.1- μ f capacitor. This input connection may be used to mix another audio sig-





All components are mounted on the front and back covers of the utility box.

nal into the 6C4 grid while calibrating the instrument or it may be used for low-amplitude audio output directly from the 12AU7. A calibration chart should be made for the signal generator. The most convenient way to do this is to use another audio generator as a reference source. Couple them together and tune to zero beat to locate fundamentals or harmonics. A cathode-ray oscilloscope is a useful zero-beat or null indicator.

A cathode connection to the 6C4 provides a signal 180° out of phase, useful whenever a phase inverter is called for (checking push-pull amplifiers, etc.). The cathode connection may also be used to monitor the waveform on a scope. These features are extremely worth while when a critical analysis of amplifier performance must be made, yet they are missing from most commercially built instruments.

Generator construction

The two miniature tube sockets should be fully wired before they are fastened to the panel. They are slipped over 1-inch 6-32 screws and soldered fast. Very little actual wiring is required, as most connections are made with the capacitor and resistor leads. The 3-watt lamp in series with the 750-ohm cathode resistor is mounted in a socket salvaged from a candelabra panel-light assembly. Since one side of the lamp (G-E 3S6) is grounded, the socket can be bolted directly to the front panel, the bolt making the center contact.

Different transformers from the ones specified may give an unsatisfactory dc voltage, so a preliminary check should be made to make sure the voltage is

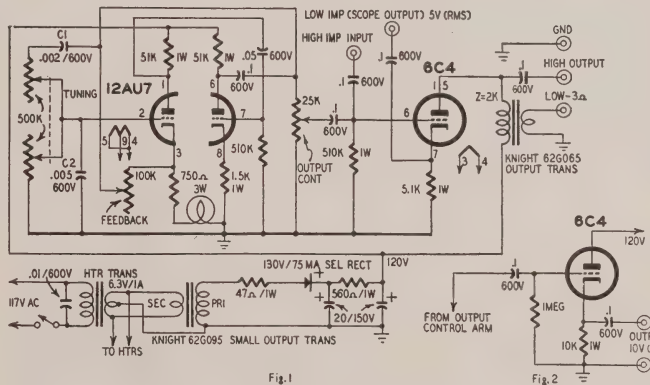


Fig. 1—Schematic of the resistance-tuned af signal generator with three output terminals. Fig. 2—Alternate output circuit eliminates transformer.

Parts for audio generator

Resistors: 2-510,000 ohms, 1/2 watt, 5%; 1-47, 1-560, 1-750, 1-1,500, 1-5,100, 2-51,000, 1 watt, 5%; 1-25,000-ohm carbon potentiometer (Ohmite CU2531 or equivalent); 1-500,000-ohm dual potentiometer (Ohmite CCV5041 or equivalent); 1-100,000-ohm potentiometer (Ohmite CU1041 or equivalent).

Capacitors: 1-C1 and C2 (see text); 1-.01, 1-.05, 5-.01 µf, 600 volts; 1-20-20 µf, 150 volts, electrolytic.

Miscellaneous: 1-12AU7; 1-6C4; 1-7-pin, 1-9-pin

miniature socket; 1-75-ma selenium rectifier; 1-6.3-volt 1-amp filament transformer; 1-small output transformer, primary impedance 2,000 ohms at 50 ma, secondary 3-4 ohms (Knight 62 G 065 or equivalent); 1-small output transformer, primary impedance 5,000 ohms at 40 ma, secondary 3-4 ohms (Knight 62 G 095 or equivalent); 1-line cord; 1-3-watt lamp (G-E 3S6) and candelabra socket; 1-6 x 6 x 6-inch cabinet; 1-tuning dial; 1-spst switch; 4-phone tip jacks; 1-connector for cable; 1-3-foot length of microphone cable; 2-alligator clips for cable; 1-handle for cabinet.

within the 120-150 range. (Up to 250 volts could be used on the plates of the tubes, but this is too high for the filters and selenium rectifier in the power supply.) To operate the 12AU7 on 6 volts it is necessary to connect its two heaters in parallel by joining pins 4 and 5 together at the socket. Total heater drain for the two tubes will be 450 ma. Certain parts have been specified by manufacturer's name and part number to enable the constructor to duplicate the

generator more easily. Other items are standard and require no particular care in their selection.

Fig. 2 shows an alternate output circuit that may be used when an output transformer is not used in the plate circuit of the 6C4. The circuit is a cathode follower and delivers a surprisingly uniform output voltage over the usable range of frequencies. The output voltage shown is the minimum average over the entire range.

END

DELAY and TIMING GENERATOR

By TOM JASKI

FOR the great majority of service tasks and the most frequently encountered experimental work commercial oscilloscopes in the low- and medium-price ranges are adequate. A compromise between versatility and economy, they are designed for a specific and, in some respects, limited field of work.

With new high-speed films generally available and with a greater interest in pulse techniques applicable to the growing uses of electronic control, the prospects of observing and photographing cathode-ray tube patterns become more feasible and attractive.

However, this type of work brings with it certain demands not readily met in the average oscilloscope. Observing transients, for example, requires close control of the scope sweep so that the trigger producing the transient can be made also to place the transient waveform in the proper position on the screen. Or, it may happen that a cer-

tain sequence of events has to take place ahead of the desired trace observation. Fairly long delays may be needed; relay sequences could be such a case.

It is possible to use a camera with shutter-operated flash contacts, allowing these contacts to trigger the event. This places a somewhat serious limitation on the delay, generally fixed at some convenient values such as 5 or 20 milliseconds. In photography these delays are short, but in oscillography we work in *microseconds* and delays measurable in milliseconds are enough to waste a good deal of film and effort.

There is another class of work not readily performed with standard oscilloscopes, excluding again those in the higher price bracket: the observation of very slow or very fast voltage variations. The very fast phenomena put another demand to the scope, generally requiring special vertical deflection amplifiers which are connected direct-

ly to the vertical deflection plates.

The limitation of the scope amplifier is not so much the frequency response, as often advertised, but the rise time, not so much emphasized. A real problem in industry, the requirements are rarely as severe for the average experimenter. No such limitation is encountered at the other end of the scale—the low-frequency waveforms. Virtually all scope amplifiers are usable to 1 cycle or lower, and all we need then is a slow enough sweep to scribe our pattern.

To solve my problems of observing and photographing transients and low-frequency waveforms, a separate sweep generator was built to supply a sawtooth waveform of excellent linearity, as slow as 1 cycle and up to almost 1 megacycle. For a 4-inch deflection this works out from 0.25 second per inch to 0.25 microsecond per inch (if the horizontal amplifier will permit). The generator also furnishes sweep



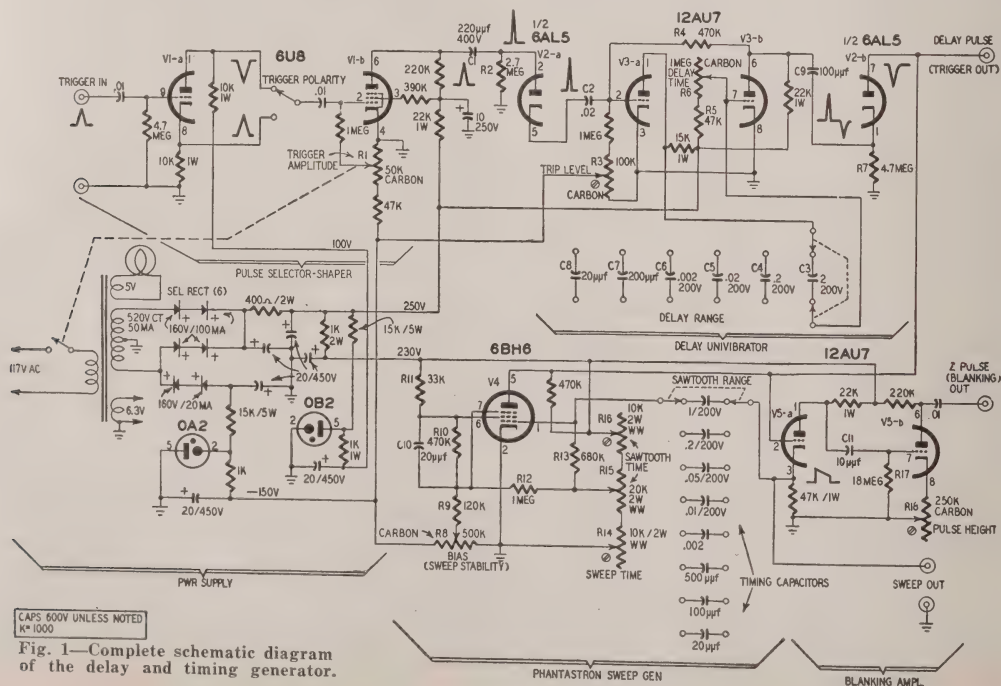
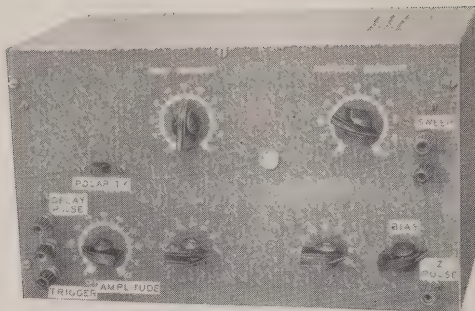


Fig. 1—Complete schematic diagram of the delay and timing generator.

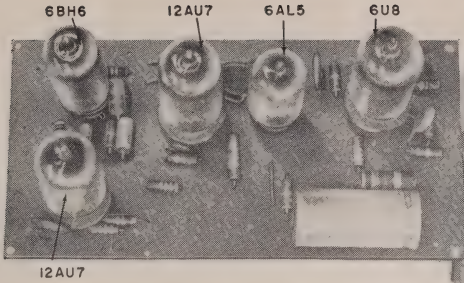


Top view of the generator circuits.

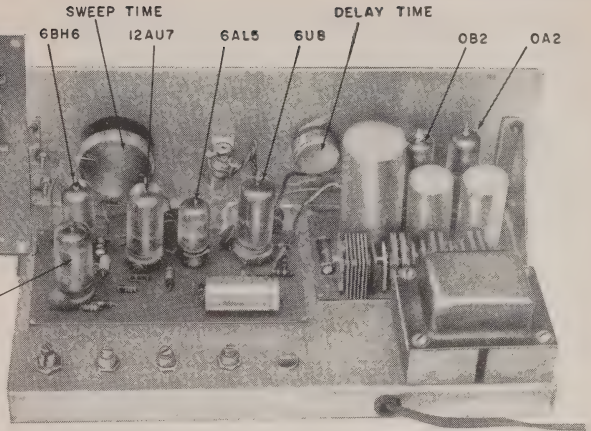


Rear top view shows the mounting of major components and circuit boards.


The power supply circuit board.

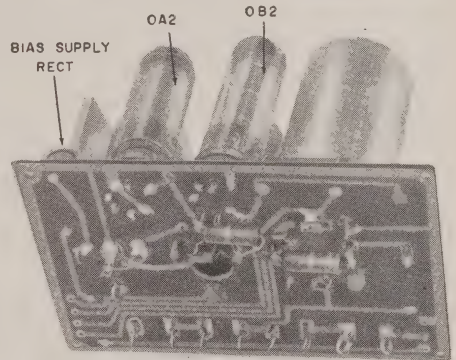

Generators and pulse shaper board.

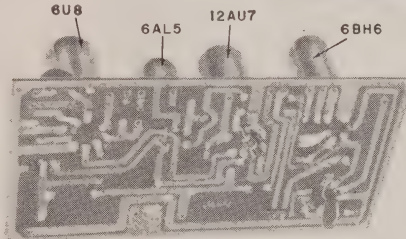

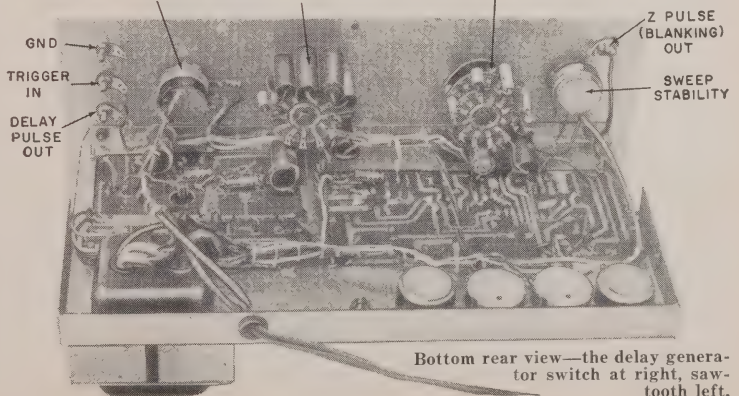TRIGGER AMPLITUDE DELAY RANGE SWITCH SAWTOOTH RANGE SWITCH ↑



Bottom rear view—the delay generator switch at right, sawtooth left.

delays from 2 seconds to 1 microsecond and supplies externally a delayed pulse and a blanking pulse at the end of the sweep. The sawtooth wave can be repetitive or triggered. The repetitive sawtooth can be synchronized with an external input.

Fig. 1 shows the complete circuit diagram of the generator. This can be divided, for discussion, into four parts: the power supply, the pulse selector and shaper, the delay univibrator and the phantatron sawtooth oscillator with blanking pulse discriminator. The power supply needs no discussion, except that the better the regulation, the greater the accuracy of the sweeps and the greater the stability. If very high accuracy is required, more effective regulation should be considered. Excellent voltage-regulated power supplies have been described in *RADIO-ELECTRONICS* (August, 1952, page 47; April, 1952, page 66).

Pulse selector and shaper

The function of the selector and shaper is as follows: A signal of any waveform or a pulse of any polarity is applied to the grid of the triode half of the 6U8 through the .01- μ f capacitor. The signal then appears at the cathode of the triode in the same polarity as the input and at the plate with opposite polarity. The trigger polarity switch is used to select the negative polarity trigger always. Thus at the plate of the pentode a positive signal appears. The pentode always conducts, but conducts less when the trigger signal is impressed on the grid. The amplitude (and with certain waveforms, the pulse shape) is regulated by R1, which alters the bias on the pentode. If the trigger is a sine wave, the signal from the pentode will contain both a negative and a positive peak. Since a positive peak only is required to trigger the delay univibrator, the trigger is next sent through a diode, one half of a 6AL5, which effectively eliminates the negative peaks. The 6U8 is coupled to the diode through differentiating network C1-R2, which further sharpens the pulses. The positive trigger is applied through coupling capacitor C2 to the univibrator. The coupling capacitor is needed since otherwise the cathode of the diode would be biased and the signal would be blocked.

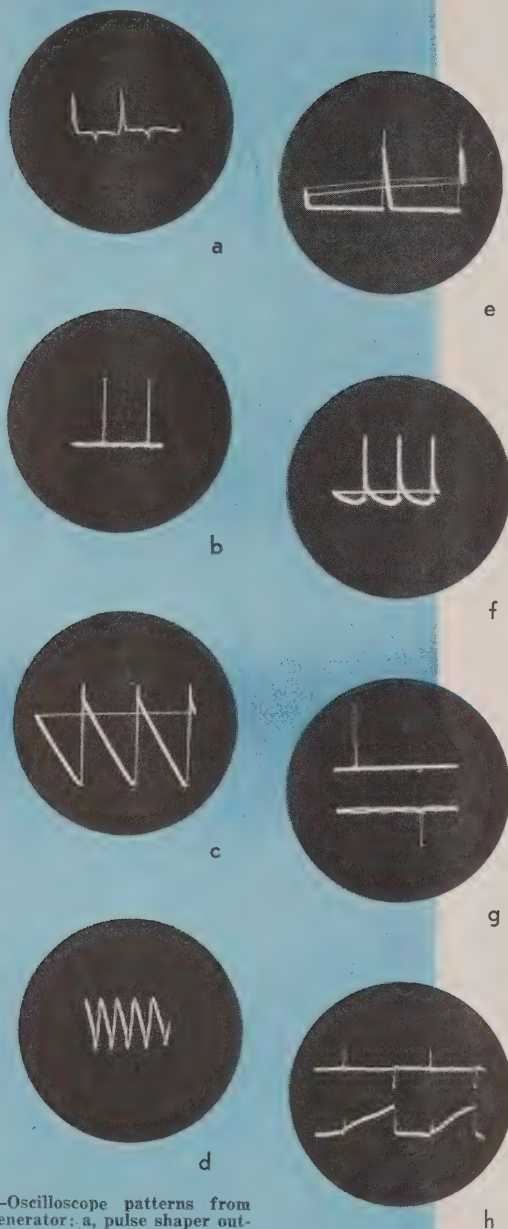


Fig. 2—Oscilloscope patterns from sweep generator: a, pulse shaper output with sine-wave input; b, delay univibrator output pulses; c, free-running sawtooth—1 kc; d, free-running sawtooth—500 kc; e, triggered at 200 cycles, sweep at 0.25 millisecond per inch; f, blanking pulse at 200 kc; g, trigger pulse (top) produces delay output pulse; h, trigger pulse (top, up), blanking pulse (top, down) and resulting sweep (bottom) near zero delay.

Fig. 2-a shows the resultant pulse when a sine wave is applied to the pulse shaping circuit.

Delay univibrator

There are many circuits which can provide a variable delay. For example, a phantastron similar to the one described here as sawtooth and blanking generator is frequently used. All that is required, basically, is a monostable circuit which after a period of time returns to the rest condition. However, the univibrator has certain advantages: the pulse output varies only very little with different delays; it is a relatively simple circuit and very easily controllable over a very wide range. The univibrator was described in the October, 1954, issue of *RADIO-ELECTRONICS*.

The first triode is normally cut off; the second triode conducts. A predetermined bias is placed on the grid of V3-a, set by potentiometer R3. When a positive pulse arrives from diode V2-a, V3-a conducts and charges capacitors C3-C8, selected by the delay time switch.

The current of V3-a lowers the voltage at the plate and also the grid potential of V3-b until it is cut off. This causes a sharp rise in potential at the plate of V3-b (see Fig. 2-b) and the grid of V3-a coupled to it through resistor R4. Triode V3-a conducts more vigorously, charging the delay capacitor through R5 and R6 and finally reaching the point where the grid of V3-b has sufficient voltage on it to once more make it conduct. The resultant drop of V3-b plate voltage coupled back to V3-a cuts off the latter and the original condition is restored. The off period of V3-b corresponds to the delay time, forming a square wave of that length. Through differentiating network C9-R7 this appears as a pair of pulses, one negative and one positive. The negative pulse only is passed on through diode V2-b to the phantastron. Potentiometer R8 is adjusted to prevent the univibrator from running free without a trigger. With trigger applied and trigger amplitude full on, set R8 to allow the univibrator to trip at the trigger frequency.

The phantastron

For the sweep oscillator the phantastron circuit was selected because of excellent linearity and wide frequency range. It is also suitable for repetitive (free) running (Figs. 2-c, d) and for trigger operation (Fig. 2-e) and can be changed from one type of operation to the other by merely changing the bias with potentiometer R8.

The phantastron is made up of two tubes: a 6BH6 (V4) and a cathode follower which is one half of a 12AU7 (V5-a). Basically the phantastron is a transitron type of oscillator. But when triggered, the transitron characteristics are not used as the circuit operates here. The plate resistor in the V5-a plate circuit can be ignored in the

discussion of function for it was put there only to provide a takeoff point for the blanking pulse amplifier.

At rest position the voltages at the tube elements are:

Pentode	Cathode Follower
plate 180	plate 230
screen grid 80	control grid 180
suppressor -20	cathode 185
cathode 0	
control grid -0.5	

The apparently lowered plate voltage on the plate of V4 reaches 180 because V5-a is drawing grid current through the 470,000-ohm plate resistor.

At rest position the plate of V4 is cut off by the negative voltage on the suppressor grid. The triode conducts heavily and keeps the timing capacitor charged. The screen of V4 also draws current. When a negative pulse arrives on the plate of V4 and grid of V5-a, grid current drops and the plate will momentarily conduct a part of the total cathode current. Since the control grid remains at equilibrium, the total cathode current will be the same. The screen will draw less current, allowing the screen voltage to rise sharply.

Through voltage divider R9-R10-R11 the suppressor will be brought up to almost 0 and the plate continues to conduct, lowering still further the plate voltage on V4. This eventually falls to about 15. The lowering plate voltage on V4 drops the grid voltage of V5-a also, considerably below the cathode voltage, and cuts off V5-a for the time being.

The timing capacitor selected discharges the so-called "rundown" at a rate determined by the values of divider network R9-R12-R13 and also by the position of sweep-time potentiometer R14, which determines the equilibrium point for the grid. These resistors are so arranged that with increasing plate current the grid becomes more rapidly less positive, thus restoring equilibrium and assuring a linear rundown.

When the capacitor contains no further charge, V4 is very near cutoff for the very low plate voltage then present. At this point the energy stored in capacitor C10 is sufficient to kick the suppressor grid negative and cut off V4. It remains cut off until another negative pulse arrives on the plate. The sudden jump in plate voltage resulting from the plate cutoff allows V5-a to conduct heavily and rapidly recharge the timing capacitor. When continuous operation is desired, the bias on the suppressor grid is so arranged that, when the timing capacitor contains no further charge, there is not sufficient energy to restore the plate-cutoff condition and the cycle repeats itself—when V4 momentarily cuts off altogether and allows V5-a to recharge the capacitor.

Blanking amplifier

The frequency range of the sweep generator is determined by three factors: potentiometers R8, R14 and R16.

Potentiometer R16 sets the upper limit, R14 the lower. These pots interact to a certain extent since changing either affects the relative value of R15 and the other. The following shows the approximate range in each position:

1 1-5 cycles	5 0.5-4 kc
2 3-25 cycles	6 3.6-30 kc
3 12-100 cycles	7 25-200 kc
4 80-650 cycles	8 180 kc-1 mc

The above cover about a 1-to-8 frequency range. By resetting R8 a frequency ratio of 1 to 10 can be obtained with a minimum frequency down to ½ cycle. Thus, if a calibration scale is desired, it must be made with R8 in one certain, resettable position.

The blanking amplifier is supplied with a sawtooth signal from the plate of the phantastron cathode follower through differentiating network C11-R17. The small capacitance and the high bias on the tube (V5-b) allow only the very highest peaks of the sawtooth wave to be amplified, resulting in a sharp negative pulse (Fig. 2-h). These pulses are of the correct polarity for direct connection to the grid of a cathode-ray tube. The blanking pulse (Fig. 2-f) voltage obtained is about 15 volts peak, depending on the setting of the cathode bias on the blanking amplifier triode. This is usually sufficient to do an adequate blanking job. Potentiometer R18 varies the shape of the blanking pulse, generally close to tube cutoff.

The output voltage of the sawtooth oscillator is approximately 40 volts peak in the free-running condition. This again depends on the bias setting in this case of the suppressor grid bias. The output voltage in the triggered operation is somewhat less, primarily because a greater bias must be applied to prevent free running. The output voltage of the delayed pulse (Fig. 2-g) is approximately 25 volts peak. This pulse is always of very short duration. Any device to be operated by the delayed pulse will generally require some intermediate amplifier or triggered relay, such as a 5823. The narrow pulses have been used successfully to trip a 5823 cold-cathode relay tube.

Construction

A compromise between etched circuits and wiring has been used. See chassis photos. It would have been possible to use a larger printed circuit which could contain the screwdriver-adjusted potentiometers, or even the capacitors mounted on the range switches. Or a single circuit board could contain both power supply and generator chassis. For those who wish to use etched-circuit techniques to build this generator, see "Making Printed Circuits Is Easy," September, 1955, and "Making Photoetched Circuits," December, 1955, and January, 1956. The boards in the photos can be used as guides, but it would not be practical to copy them exactly unless it is first established that parts of exactly the

same dimensions are available. I had some thick, short 15,000-ohm 5-watt resistors and designed the power supply board accordingly. More length may well be required, unless a miniature 5-watt type is available. The generator board, however, is designed with entirely standard parts.

Those desiring to use wired construction will find the wiring not particularly critical. The univibrator will not trigger on anything but a positive signal, and the phantastron must have a negative signal. However, it would do well to keep the input trigger circuit wires away from those connected to the univibrator input and the phantastron trigger input to prevent false triggering. The phantastron sockets and connections must be kept clean and the tubes used of good quality for leakage discharge of the capacitor might start a rundown without a trigger, no matter what the bias setting is.

Operation

If a repetitive trigger is supplied to the univibrator delay circuit, the delay setting must be less than the space between triggers. If this is not observed, triggers will be missed and the operation will become erratic. Similarly it is not possible to operate with a sweep time greater than the space between triggers. If such a setting is made, the phantastron will simply trigger on alternate pulses or will operate on some other multiple or submultiple of the trigger repetition rate.

Parts for delay and timing generator

Resistors: 1-1,000, 1-33,000, 2-47,000, 1-120,000, 2-220,000, 1-390,000, 3-470,000, 1-680,000 ohms, 3-1,000, 1-2.7, 2-4.7, 1-10, 1-15, 1-20, 1-30, 1-50, 1-100, 1-150, 1-200, 1-300, 1-500, 1-1,000, 3-22,000, 1-1,000 ohms, 1 watt; 1-400, 1-1,000 ohms, 2 watts; 2-15,000 ohms, 5 watts.

Potentiometers: 1-50,000 (with switch), 1-100,000, 1-250,000, 1-500,000 ohms, 1-1 megohm, carbon; 1-10,000, 1-20,000 ohms, wirewound, 2 watts.

Capacitors: 1-10, 3-20, 1-100, 1-200, 1-220, 1-500 µf, 600 volts, ceramic; 1-.002, 1-.01, 1-.02, 1-.05, 2-.02, 1-1, 1-2 µf, 200 volts; 1-.002, 3-.01, 1-.02 µf, 600 volts, ceramic; 1-10 µf, 250 volts, electrolytic; 6-20 µf, 450 volts, electrolytic.

Miscellaneous: 1-power transformer, 570 volts ct at 50 ma, 6.3 volts at 1.2 amps; 4-100-ma selenium rectifiers; 2-20-ma selenium rectifiers; 1-spst switch; 1-2-circuit 6-position switch; 1-2-circuit 8-position switch; 1-6A8; 1-6AL5; 2-12AU7's; 1-6BH6; 1-QA2; 1-0B2; 1-pilot light and assembly; 3-9-pin, 4-7-pin miniature sockets; 1-chassis; 1-cabinet; 6-output terminals; line cord; printed wiring materials (optional).

To calibrate the delay time, an electronic switch can be used. Two traces are displayed on the C-R tube, one containing at least two pulses at the trigger rate (Fig. 2-g, the end of the trace is at a trigger mark). This can be a calibrated frequency from a signal generator or other source. With the delay range switch and the delay potentiometer, the delay-output pulse can be made to walk the other trace from trigger to trigger. The desired delay can be measured with a scale as a portion of the trigger spacing. The univibrator is reasonably accurate, but for very accurate work it is best to calibrate the delay time for each setting used. Minimum trigger voltage required is about five volts peak and pulses are preferable as triggers.

END

Setting Your Checker For New Type Tubes

*Checking the latest tubes,
or, what to do until the new
roll chart arrives*

By BASIL C. BARBEE

NEW tube types are appearing at the most rapid rate in electronic history, making it quite a problem to keep tube-tester data up to date. A new type need not be any better than its predecessor; all that is required is that it be *different*, if only in some minor respect such as a slight change in basing. How can the technician test a new type he has never even heard of and cannot find listed on the roll chart of anybody's tube tester? Here is the procedure I developed during the testing of some hundreds of thousands of tubes over a period of years. It may not be the *best*

approach, but it is one that has worked for me.

The oldest and simplest way of determining whether a tube is defective is to substitute a known good one of the same type and note whether the performance of the set is improved. This method is sometimes useful even when a tube tester and up-to-date chart of settings are available. For instance:

A tube may test *good* yet may oscillate in its circuit due to an open screen or other internal shielding.

A tube may test *good* yet may fail to perform in a high-frequency oscillator circuit due to small changes in


interelectrode capacitance as a result of misalignment of the tube elements.

A tube may test *good* yet not work satisfactorily in a TV horizontal oscillator or sync-clipper circuit due to its being used in the circuit under conditions other than those for which it was designed and tested.

The substitution method fails under certain conditions:

When no known-good tube of the same type is available for substitution. Having a new tube on the shelf is no guarantee that a good tube is available; new tubes, particularly of a new type, may be defective, usually due to interelectrode shorts. A tube which has performed daily for a year is a far better bet than a new one fresh from the distributor.

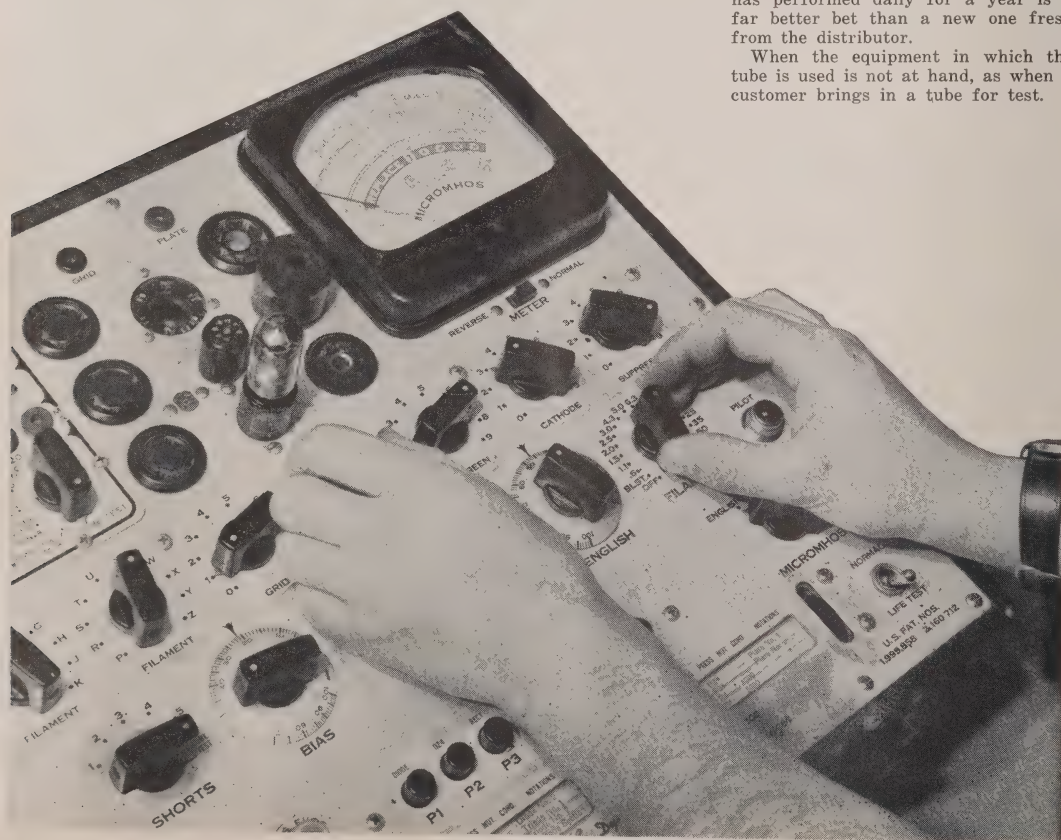When the equipment in which the tube is used is not at hand, as when a customer brings in a tube for test.



When there are one or more faults in the set in addition to the suspected tube.

Data-compilation method

The first step in this method is to understand your tube tester. Read the instruction book thoroughly and find out just what each of the controls on the panel is for and how it works. Study the schematic so that every time you turn a switch or dial and push a button you visualize what is happening inside the instrument.

The second step is to accumulate every scrap of information on the characteristics and base connections of every new tube type that comes out. A subscription to one of the looseleaf tube-data services offered by the leading tube manufacturers will pay for itself several times in a year in time saved. Better still, subscribe to two or more such services since a new type will sometimes be announced first by one company, sometimes by another.

Take sample sheets from each looseleaf tube manual to your stationer and buy a sheaf of blank sheets to match one of them. Then order an extra looseleaf binder from the tube manufacturer (if you want it to match the others) and make up a volume of new and unusual types from clippings from RADIO-ELECTRONICS and other magazines by pasting the clippings to the blank sheets. When these types are covered by the printed supplements issued for the looseleaf manuals, the homemade sheets may be thrown away.

The third step is to identify the new tube with a similar type which appears on the roll chart of the tube tester or to make up the test settings for a unique type. A complete and up-to-date interchangeability chart will frequently be of value in determining kinship of tube types.

"There is nothing new under the sun" is almost always true in new tube types. Usually a new type will be simply a well-known one with different base connections or heater ratings or a combination of two or more single-purpose tubes in one envelope. If the electrical characteristics and base connections of the new type are at hand, it is an easy matter to find a similar type whose test settings are given on the chart of the tester—unless the new one has unusual base connections, in which case a knowledge of the workings of the tube tester, as recommended above, will be necessary.

When comparing published characteristics, the interelectrode capacitances are of no importance and may be neglected since the testing will be done at 60 cycles.

In most tube testers one heater pin, the cathode, the suppressor (if any) and any other elements other than grid, plate and screen of the section of the tube being tested are grounded. (In emission type testers, suppressors are not necessarily grounded; with triodes, of course, there is no screen.)

Which pin goes to the heater supply is selected by a switch or by plugging the tube into the proper one of two or more sockets. The heater voltage is selected by another switch which may or may not be calibrated in volts. If it is simply labeled with consecutive numbers, the meaning of each number in terms of voltage may be determined by referring to the settings on the chart for tube types of known heater voltage. If the tube has a tapped heater, it is essential that the tap be ungrounded. Some of the more flexible tube testers make it possible to test centertapped heater tubes with the two halves in either series or parallel. In the parallel case, both ends of the heater are left grounded, with heater voltage applied to the tap.

A third switch usually selects the plate load resistance for the tube under test. One position will be for all ordinary amplifier tubes, another for rectifiers, a third for diode detectors and perhaps other positions will be provided for pentagrid converters, triodes of unusually low or high transconductance and other tubes of special characteristics. This switch may take the form of a series of pushbuttons.

Grid, plate and screen pins are selected by other switches or pushbuttons. (In emission testers, usually all elements except the cathode are connected together and tested as a diode plate.) A variable resistor is used as a fine adjustment of plate load resistance or as a sensitivity control in the meter circuit. The setting of this control will vary roughly as the plate resistance of the tube type under test and may be estimated fairly closely for a new type of known characteristics from a knowledge of the characteristics of tube types listed on the chart.

Another variable resistance (except in emission testers) is used to adjust the ac excitation applied to the control grid. Settings of this control will vary roughly inversely as the amplification factor of the tube and may be estimated by comparing characteristics as in the case of the plate load or sensitivity control. On a transconductance tester, sharp-cutoff tubes may be differentiated from remote-cutoff (variable- μ) types by noting the manner in which the meter reading varies as the grid excitation control is varied.

Inspection method

Suppose the questionable tube is so new that no published data are available, either in the tube manuals or in the magazine clippings? Most new types are glass miniatures and with the aid of a magnifying glass the base connections may be determined by visual inspection, particularly if you have ever dissected discarded tubes and studied their structure.

In drawing your diagram of base connections, don't forget that the pins are numbered clockwise looking at the base of the tube, whereas you will be looking from the opposite direction

since the button of a miniature tube is not very transparent. Be sure also not to overlook any "built-in shorts" (where two or more pins are connected together internally) as frequently found in high-frequency tubes. Otherwise, you may discard a perfectly good tube as being "shorted." An easier method of determining the base connections is by noting the small numbers around the tube symbol on a schematic, if one is available, or by inspecting the connections to the socket underneath the chassis in which the tube is used.

Electrical characteristics other than heater ratings may be estimated by the experienced eye from the tube geometry (relative spacing of elements, pitch of grid windings, cathode area, etc.) and by comparison with types of known characteristics.

Heater ratings may be estimated by inserting the tube in the tester (after having first identified the heater pins) and slowly raising the heater voltage from the lowest tap until the color of the cathode corresponds with that of a similar-looking tube operated at normal heater voltage. If desired, the heater current may now be determined with an ammeter (with normal voltage, as determined above, applied to the heater). When working with tubes taken from a series-string set, it may be simpler and quicker to adjust the heater voltage till the ammeter reads the correct heater current. Then it should be operating at the nominal voltage and the heater should look normal. If the tube is in series with others of known characteristics, its correct heater current is known. Similarly if a tube is in parallel with others which are known, its heater should appear normal at the heater voltage which the others are getting.

A knowledge of the heater current is useful in estimating the other characteristics of the tube inasmuch as the transconductance is roughly proportional, all else being equal, to the heater power (voltage times current).

Characteristics estimated in the manner described, while not highly accurate, are sufficiently so for all practical purposes in tube testing. In combination with a thorough short check, a tube-quality test conducted on the basis of data arrived at by inspection will tell whether or not a given tube could have caused the operational fault of which it is suspected. These data are therefore valuable enough that it is worth while to record them on a looseleaf sheet to be filed in the extra tube-manual binder until the manufacturer's data arrive, and to add the test settings derived from them to the supplementary test data chart.

Even though the type number on a tube may be illegible, the inspection method will still yield the approximate data. If the tube tests *bad*, you have the data to help in finding a replacement for it; if it tests *good*, all you have to worry about is how to file the data sheet. END

THE LABORATORY

Part II—Adding variable damping; construction and adjustment

Neither schematic nor photo is therefore intended as a model for exact duplication. They are offered as basic ideas to be modified to suit the requirements of the advanced audiophile. The amplifier portion can be built on a 7 x 12 x 3-inch chassis with room to spare. I recommend a separate chassis for the power supply; hum is minimized and low-level intermodulation held down to the vanishing point. Aluminum chassis material is recommended.

Run a common bus bar of No. 18 or larger wire from the input jack to the center terminals of all turrets, or the turret deck, and return all circuit

The power supply (Fig. 3) uses readily available components. If the amplifier is to use a single pair of KT66's, a simpler and cheaper supply with a single 5U4-G and capacitor-input filter can be used (see parts list). With two tubes the no-signal current will be less than 125 ma and maximum-signal current about 175 ma. With four tubes the no-signal current is around 225 ma and maximum under 300.

This amplifier was designed primarily, as its name implies, to serve as a laboratory-grade piece of equipment that can be used for measurements. For this reason, variable damping was not included in the original. However, due to the current popularity of this feature, I did some experimenting with variable-damping circuits and

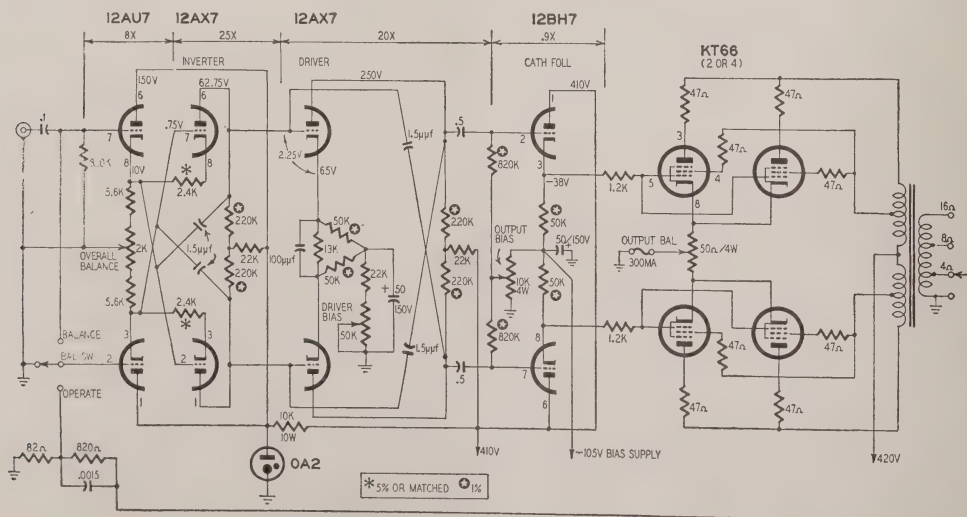


Fig. 1—Schematic diagram of the Laboratory Golden Ear—less power supply.

came up with a modification (Fig. 2) that works well. The feedback circuit now includes switching so the variable-damping feature can be put out of action when using the amplifier for measurements.

The variable-damping arrangement follows the principle used in Bogen's amplifiers. Due to the choice of values, the adjustable current feedback is effective only at frequencies below about 200 cycles. Adjusting the 25-ohm pot provides a choice of either positive current feedback for increased damping or negative current feedback for decreased damping. When the 1-ohm 1-watt variable resistor is correctly set, the 25-ohm unit provides continuous adjustment over a range of about ± 10 db. The 100- μ f electrolytic capacitor restricts the current feedback to the low frequencies. The 1-ohm resistor will rob the speakers of some power, but audibly the loss is insignificant.

Adjustment

When the amplifier is finished, check for continuity and shorts with an ohmmeter. When you are sure all is well, adjust as follows:

1. Insert only the 12BH7 with the output bias pot about half on. Connect a vtvm from one cathode to ground and adjust for a reading of minus 38 to 40 volts. (It is possible to obtain positive bias, so be sure the polarity of the vtvm is right.)

2. Insert the KT66's and readjust the bias to obtain a total cathode current of about 100 ma for a pair and 200 ma for four KT66's.

3. Balance the output tubes with the output balance control in the cathode leg of the output tubes. Use a voltmeter connected from plate to plate and adjust for zero voltage difference.

4. Insert the other tubes (with power off). Connect the vtvm from cathode to grid of one section of the 12AX7 driver tube. (Be sure it is the same section.) Adjust the driver bias pot for a bias of -2.25 volts.

5. Throw the balance switch to BALANCE (which ties both input grids together and disconnects the feedback loop). Feed in any signal and adjust OVERALL BALANCE in the input tube circuit for a null or minimum output.

6. Set the balancing switch in its center position and feed in a sine-wave signal; adjust the input to provide an output reading of 1 volt.

7. Throw the balance switch to OPERATE. If variable damping is used, inactivate it by throwing its switch to OFF (contacts closed). Observe the reading on an output meter. It should be about 18 to 20 db down from the 1-volt reading (between 0.1 and 0.11 volt). If the reading is higher, reduce the value of feedback resistor R1 (Fig. 2) slightly; if lower, increase the value slightly. If you have a scope and square-wave generator, check the appearance of a 20- or 30-kc square wave; it should be quite vertical and with little or no trace of ringing. If the ringing is

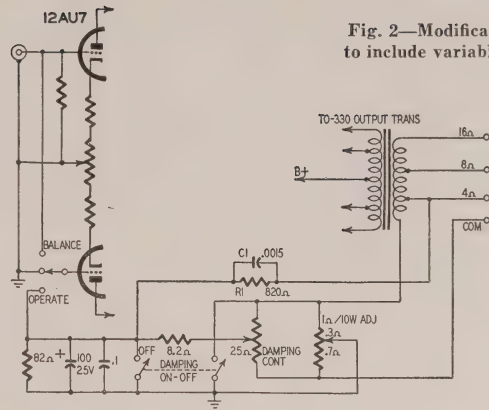


Fig. 2—Modification in feedback line to include variable damping feature.

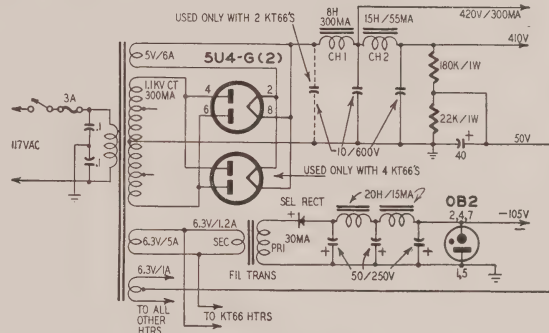


Fig. 3—Schematic diagram of power supply for use with the amplifier.

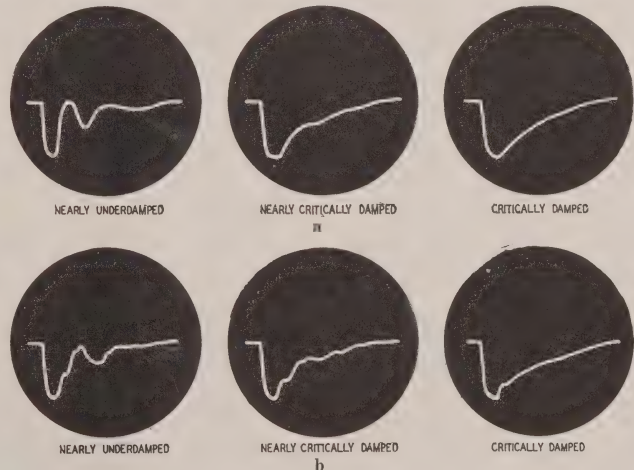


Fig. 4—Effect of the damping control on the keyed step-transient response.

excessive, add small capacitances in parallel with phase-shifting capacitor C1 which shunts the feedback resistor. If there is rounding of the leading edge, replace C1 with a smaller capacitance. The values given should be sat-

isfactory unless the capacitor used is way off its rated value.

8. If using variable damping, throw the damping switch to the ON position. If you have a square-wave generator and a scope, set the generator for 200

AUDIO—HIGH FIDELITY

cycles and turn the damping control until you get the flattest and squarest top on the scope trace. This indicates the neutral position of the damping control. If you have no square-wave generator and scope, set the control about half on. Now, with the speaker you are going to use with the amplifier, adjust the damping control for critical damping. The best way to do this is with a step-transient input and a scope across the speaker line. A 1.5-volt cell keyed momentarily into the amplifier input will provide the step transient. For best results the scope should have a triggered sweep. Set the sweep for its lowest rate. Key the 1.5-volt cell and observe the trace. What you want is the nearest approximation to traces indicating critical damping. The traces at *a* in Fig. 4 are those obtained by Tomcik (RADIO-ELECTRONICS, January, 1955) with the speaker in an infinite baffle and those at *b* were obtained with the speaker in a large bass-reflex enclosure. You will probably get a slight bounce or hang-over but in any case adjust the control for the smallest bounce or the straightest line.

The adjustment can also be made with the square-wave generator. Again set the generator for 200-cycle square wave and adjust the damping control for flattest top and squarest wave, an indication that the voltage developed across the speaker voice coil is as flat as possible. The adjustment can also be made by ear. Alternately feed 500- and 50-cycle notes to the amplifier and adjust the damping control so both are

about the same volume. When adjusting by ear keep the volume as loud as you can stand without endangering the speakers, to make the adjustment at a point where your ear is fairly flat; if you adjust at low volume levels, you will underdamp. The damping control should not be used to obtain a bass boost; it should be used merely to flatten out the speaker peak and to damp speaker hangover. The critically damped point is *not* the point of maximum bass response. If the constants in the feedback loop are adhered to rigidly, adjustment of damping will have only the slightest effect on distortion (raising it from 0.3% to perhaps 0.35% at the most). It is possible for the damping control to produce subsonic oscillation at one extreme or the other with some speakers. This can be verified by watching the inside of the KT66's through the top of the envelope; oscillation will produce periodic ionization. It may also cause the speaker cone to move slowly, and can be measured by meters with good response below 20 cycles.

If you have an IM meter, the final touching up can be done with extreme accuracy. Take an IM reading at a level of about 10 watts. Leave the IM meter on and adjust OVERALL BALANCE for minimum IM. If you like, you can increase the level to just under maximum output and readjust the driver bias control slightly for lowest IM. When adjusting be careful to obtain minimum IM without reducing output more than a fraction of a watt. The OUTPUT BALANCE can be used as a vernier for OVERALL BALANCE. It is possible that using it this way you may sacrifice a watt or so of maximum output, but you can obtain a more complete balance at lower outputs.

There will be some tendency for the adjustments to drift until the tubes are aged. In the early period OVERALL BALANCE can be reset about once a

month by the null-output method. After tubes are aged, the adjustments will hold good for long periods.

Listenability

An amplifier such as this could be expected to produce good listening and the expectation is realized. The reserve power is reflected in unusual cleanliness in peaks. The definition is exceptional and actually is limited almost entirely by the speaker system. The most notable difference from home type amplifiers is the remarkable ability to handle low frequencies. Given a preamplifier with sufficient stability, the low end can be brought up by bass boosting to provide startlingly realistic reproduction of high-level bass—especially bass drums and tympani. With a smooth bass boost and speakers capable of taking and dishing it out, it is possible to bring these instruments up to true concert-hall level with all their floor-shaking awesomeness. Similarly, the crash of cymbals can be reproduced cleanly, assuming they are recorded with anything like proper dynamic balance. There is never any sense of strain. I have applied as much as 80 db of boost at 20 or 30 cycles (including equalizer boost) and the amplifier takes the bass peaks in stride and with no tendency to break up.

At ordinary home listening levels, however, the improvement over Milady's Golden Ear is so slight that except for record reviewers and others requiring the most complete definition, the much higher cost would probably not be justified. Moreover, the full capabilities are realized only with the very finest speaker systems. But for those who, like myself, chase the phantom of perfection, whether or not it has any practical worth when caught, the Laboratory Golden Ear may satisfy far beyond the added money and time expended. END

Parts for Lab Golden Ear (Fig. 1)

Resistors: 8-47, 1-82, 1-820, 2-1,200, 2-2,400 (5%), 2-5,600, 1-13,000 (5%), 3-22,000, 1-820,000 ohms; 1/2 watt; 4-50,000, 4-220,000, 2-820,000 ohms, 1%, 1/2 watt; 1-10,000 ohms, 10 watts; 1-50 (4 watts), 1-2,000, 1-10,000, 1-50,000 ohms, potentiometers. **Capacitors:** 4-15 (NPO) 1-100 μ f, 1-.0015, 1-.01, 1-.05 μ f; 2-50 μ f, 150 volts, electrolytic. **Tubes:** 2-12AX7, 1-12AU7, 1-12BH7, 2 (or 4) KT66, 1-6A2.

Miscellaneous: 1-7-pin, 4-9-pin miniatures, 2 (or 4) octal sockets; 1-TO-330 Acrosound output transformer; 4-Vector turret sockets, novel, or No. 8-4N-64-2 turret deck; 1-300-ma fuse and holder; 1-1-pole 3-throw switch; 1-chassis, approximately 7 x 12 x 8 inches, aluminum. (For triode operation use either Chicago BO-11 or Stancor 8052 output transformers.)

Components for variable damping

1-8.2-ohm resistor; 1-1-ohm resistor, with slider, 10 watts; 1-25-ohm potentiometer; 1-0.1- μ f capacitor; 1-100- μ f 25-volt electrolytic capacitor; 1-dpst switch.

Parts for power supply

1-22,000, 1-180,000 ohms, 1 watt, resistors; 2-0.1- μ f 400-volt capacitors; 2 (or 3 for 2 KT66's)—10 μ f, 600 volts, electrolytic; 1-40- μ f 450-volt, 3-50- μ f 250-volt electrolytic; 1 (or 2)—5U4-G, 1-OB2; 2-octal sockets; 1-7-pin miniature socket; 1-3-ampere fuse and holder; 1-selenium rectifier, 30 ma; 2-20-henry filter chokes, 900 ohms (Stancor C1515 or equivalent); 1-filament transformer, 6.3 volts at 1.2 amperes (Stancor P-4134 or equivalent); 1-choke (CH2), 15 henries, 55 ma, 420 ohms (Chicago RC-1555 or equivalent).

For 2 KT66's:

1-power transformer, 800 volts ct at 200 ma, 5 volts at 4 amps, 6.3 volts ct at 5.5 amps (Chicago PV-200 or equivalent); 1-choke (CH1), 8 henries, 200 ma, 125 ohms (Chicago R-7200 or equivalent).


For 4 KT66's

1-power transformer, 1,100 volts ct at 300 ma, 5 volts at 6 amperes, 6.3 volts ct at 5 amps, 6.3 volts ct at 1 amp (Chicago PCR-300 or equivalent); 1-choke (CH1), 8 henries, 300 ma, 60 ohms (Chicago RC-8300 or equivalent).

TRANSISTORIZED EXECUTIVE DESK SET

OLD-TIME readers may remember a construction article on "The Executive" radio-clock desk set. That set, which included a clock radio almost a foot long, 8 inches high and about as deep, remained on Hugo Gernsback's desk for some years. It has now been replaced by this set, which occupies a

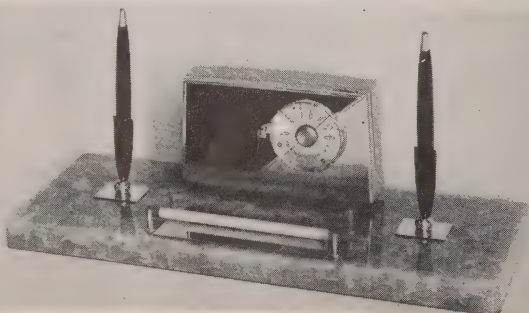fraction of the space and has styling far more in keeping with the transistor age. The portable radio is bolted to the desk-set base. There is a hint here for the office-supply manufacturer or even the technician with the right kind of clientele—more than one businessman might like a similar desk set.



HI-FI

preamp for easy listening...

Transistorized unit features very low hum and distortion, and no microphonics

By J. H. OWENS

HI FI doesn't have to be loud! It can be soft and sweet—just like “Lo Fi” or “Mid Fi”—provided the distortion is low, the overall response smooth and pleasantly balanced at low levels. Of course, the reproduction must not be marred by buzz, hum, rumble, hiss, pops, ticks and other inharmonic, nonrhythmic, attention-attracting extraneous sounds which jar the listener's nerves and callous his senses.

One of the important links in the chain of hi-fi components is the preamp, a link which often becomes the limiting factor in the quest for low distortion, low hum and freedom from microphonics. Insofar as balance is concerned, the preamp-equalizer is almost always the sole controlling element.

So the preamp is worthy of review, especially in view of components available today which promise to make performance improvements possible. Transistors alone offer freedom from certain hum sources and microphonics common to tubes. Generally speaking, transistors are more linear than tubes.

But enough about transistors. This is a story of a hi-fi preamp which features low distortion, low hum and low noise, plus the advantages of continuously variable tone controls. With a bass boost ranging from flat to 20 db up and a treble-control range of 10 db up to 10 down, more or less, lows and highs can be balanced as well for low-level relaxation music as they can for high-level exhilaration sound.

Take the output stage (see diagram), for example. Here a 2N109 is used in a common-emitter circuit which is analogous to a grounded-cathode tube hookup. The signal from the preceding stage is fed to the base; there is collector load

resistor R21; an emitter resistor R22 and a base-bias network R18 and R20.

The emitter resistor provides a degree of degeneration which reduces distortion and—of equal importance—stabilizes against the effects of temperature changes. It also helps the circuit accept a range of transistors with considerably different characteristics. However, at this stage of the art (or science) some transistors may still require individual circuit adjustments—and this can be done by increasing or decreasing the value of either or both of the resistors in the bias network. The bias adjustment is for obtaining a voltage at the collector which is about 40 to 50% of the collector supply voltage. Thus the collector voltage should be about 6 to 7 for a 15-volt collector supply. This principle applies to the first and second stages (both of which use 2N109's) although only one 2N109 out of a dozen tested required a change in the bias network.

The first stage will be recognized as either a common-emitter or common-base circuit. Actually, it is either, as desired—the switch not only selects the input but applies it to either the base or the emitter. The selector switch has two other functions: it connects or disconnects the components which convert a constant-velocity to a constant-amplitude characteristic (R6 and C13); it inserts series load resistors (R23 and R24) where needed to match the input impedance to a particular source.

Sound-source positions

The MIKE position connects a low-impedance microphone to the emitter of the transistor in a common-base circuit. The output of the transistor is attenuated by R6, R25 and C12, but in


a nonfrequency-selective manner. This input circuit is for sources with output impedances of approximately 12–200 ohms and may be used with low-level lines as well as mikes.

The RADIO position connects the output of an AM-FM tuner to the base of the transistor in a common-emitter circuit. The input signal goes through R23 which attenuates it to the level of a phono pickup and at the same time increases the input impedance of the preamp as “seen” by the tuner. The output of the transistor is attenuated the same as for mike input.


The TAPE-PHONO position connects the output of a tape reproducer head or a low-impedance phono pickup (like Fairchild or Elector-Sonic) to the emitter of the transistor in a common-base circuit. The output circuit of the transistor (R6 and C3) converts the velocity curve to an amplitude curve.

The PHONO (Hi-Z) position connects the output of a high-impedance magnetic pickup (G-E variable reluctance) to the base of the transistor in a common-emitter circuit. R24 is a series load resistor—a higher value will accentuate highs, a lower value lows. The transistor output is converted from a velocity to an amplitude characteristic as in the tape-phono position.

Many variations are possible. For example, high frequencies can be further accentuated in the radio and phono positions by connecting small capacitors (in series with resistors of 1,000 ohms or so) between the unused contacts of the middle switch section and ground. Or a dynamic microphone with a high-impedance transformer can be connected to the radio position (series resistor R23 might have to be reduced to about 50,000 ohms or so for

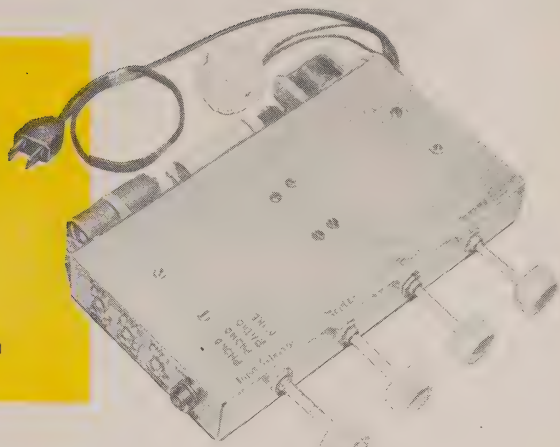

Preamp power supply is at the rear.

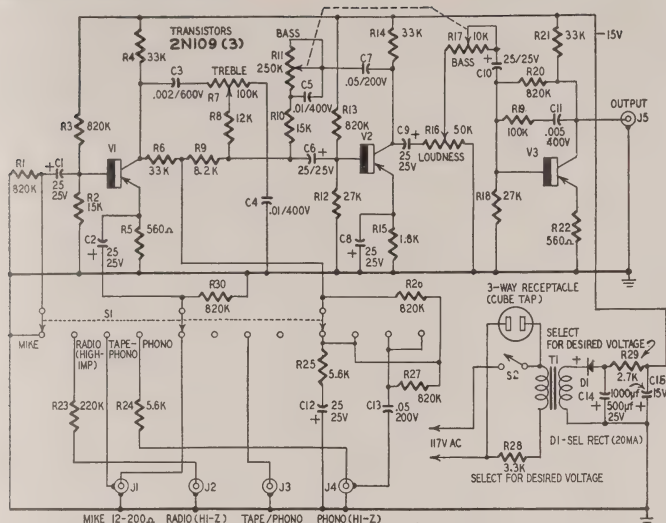

Schematic diagram of high-fidelity preamp—unit uses three 2N109 transistors.

maximum gain to be developed).

Resistors R1, R30, R26 and R27 simply maintain capacitors charged at proper levels so that there will be no switching "plops." Should there be a switching plop when going to RADIO position, it will probably be due to a

capacitor with no ground return in the tuner. Correction can be made by connecting an 820,000-ohm resistor between the capacitor and ground, either in the tuner or the preamp.

Looking now at the treble control

stands out as a very simple but effective circuit. Highs are picked off the collector by C3 and adjusted in level by R7. At the other end of R7, highs are bypassed to ground by C4. R8 and R9 are simply isolating resistors which prevent objectionable circuit interaction.

The second stage is the bass booster. In the position where R11 is shorted out, C5 is also short-circuited. Thus, there is negative feedback at all frequencies between the collector and the base, by way of C7 (a dc blocking capacitor) and R10. But when R11 is rotated clockwise, the negative feedback is removed for the lower frequencies which cannot "get through" C5, and a bass boost results. R17 is ganged with R11 as a complementary control. In its maximum-resistance position it increases the effectiveness of the C11-R19 feedback circuit and reduces the gain of the amplifier except at the bass-note frequencies. It works in conjunction with R16, the result being a fair degree of self-compensation with changes in the loudness-control setting.

Finally, the power supply. After long seeking, a suitable power transformer was located—a familiar TV vertical blocking oscillator transformer, readily available at low cost. Hooked up "backward," it provides the necessary step-down ratio for a transistor power supply.


Preamp construction

The entire preamp is built on a 1½ x 9 x 5½-inch chassis with a bottom plate. The power supply is mounted on the rear apron (see photos) to simplify the assembly and guard against hum pickup. This leaves more than enough space inside to mount the resistors, capacitors and transistors, point-to-point, on four eight-point terminal strips.

Electrically, a ground bus is used and connections to it are made progressively from the output stage to the input stage to the input end where the bus goes to chassis ground. The ac line enters the case at the "output end" of the chassis, going to the power switch. A point of novelty is the three-way ac receptacle to which other components in the system may be plugged. Thus the preamp power switch may be used to turn the entire system on and off.

Tests on the model produced very gratifying results. Distortion was measured at 0.25%. Maximum voltage output was over 3 rms. Hum was inaudible at normal levels, as was noise (hiss) produced by the transistors. There was plenty of gain, with adequate reserve for all the sound sources listed.

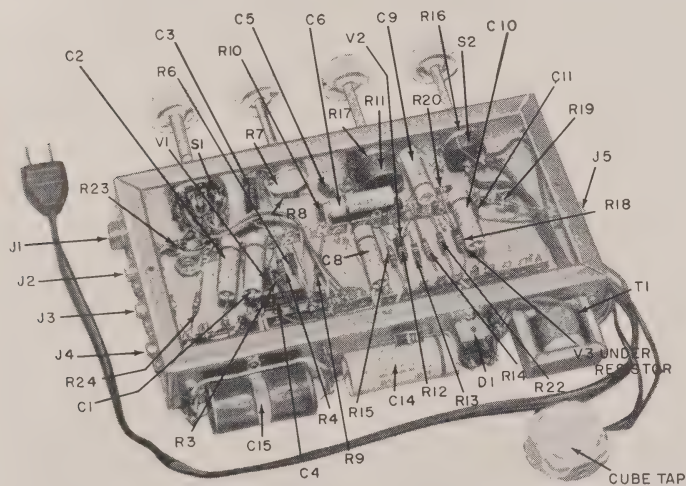Consideration was given to provision for compensation (turnover and roll-off) to match the several recording characteristics. This complication was abandoned, however, when experienced ears failed to recognize an improvement over results obtained by adjustment of the bass and treble controls for most pleasing reproduction. END



FOR GOLDEN EARS ONLY

Shure WC10 ceramic cartridge;

Elac Miratwin cartridge

By MONITOR

THE Shure WC10 ceramic cartridge is intended as a universal replacement for various crystal, ceramic and even magnetic cartridges. Shure makes no extravagant claims for it and it is highly probable that its excellent performance has been overlooked.

As indicated by Fig. 1, taken directly off the cartridge into the 1-megohm load of a Heathkit ac vtm, it has a reasonably smooth response under this relatively low load. The response at 8,000 cycles is only 1 db down from that at 1,000 and at 10,000 cycles only 5 db down. Response rolls off pretty sharply beyond that.

The most gratifying thing is the low-frequency response, which is plus 2 db at 50 cycles and 0 db at 30. Most crystal and ceramic cartridges require a much higher load to achieve such a bass response. Indeed, the WC10 delivers an excellent response even into the normal 500,000-ohm input of most amplifiers. The 4-db dip between 1,000 and 6,000 cycles is much less serious to the ear than it looks to the eye. As a matter of fact, the WC10 produces a highly pleasing sound with most of

resistance input of magnetic preamps and works acceptably well with magnetic equalizers—though there is some possibility of overloading modern high-gain preamps. Distortion is very low. All in all, this is one of the best of the piezo cartridges. While it does not come up to the finest (and most expensive) of today's magnetics, I am confident that most people will be hard put to tell it from some of the magnetics. Its higher output, lower susceptibility to hum and low price are advantages which should give it wider application in the high-fidelity field.

Elac Miratwin cartridge

The Miratwin, the product of the same mechanical ingenuity which produced the Miracord changer, presents along with first-class performance several innovations.

Performancewise the Miratwin ranks with the finest available cartridges. Under optimum conditions my sample delivered a response (Fig. 2-a) flat within 2 db to 19,000 cycles at 33 rpm, to 22 kc at 78 rpm (into a pentode preamp, very low-capacitance input, short three-wire cable). Fed into a good equalizer with a 50,000-ohm triode input, through 3 feet of shielded cable, it delivered the response of Fig. 2-b. It is notably indifferent to load, both resistive and capacitive. Decreasing load resistance or increasing capacitance produces a quicker rolloff at the high end, but the capacitance has to be very high to produce a peak and even then it is broad and results in no serious deterioration of audible quality.

The response to the square waves (Fig. 3) on the Folkways test record is very good. The distortion with a

pressure of 8 grams is among the lowest I have registered. The tracking ability is very fine, even when the cartridge is used in a changer rather than an expensive independent arm. The output is among the highest but not high enough to overload a good preamp. The cartridge is very well shielded and this, along with its low impedance and high output, results in an extremely good hum figure when used with low-hum turntables.



Fig. 3—Miratwin square-wave response.

The listening quality is very satisfying; the highs especially are clean and sweet. Furthermore, the needle chatter is phenomenally low—almost nonexistent on the best modern classical records—and this seems to make the highs even cleaner. It is one of the two or three wide-range cartridges I have used which seldom requires any rolloff and can, in fact, stand considerable boost above 10 kc. Its wide response therefore, is really useful.

One innovation, long overdue, is that every Miratwin is numbered and tested for response by an independent laboratory and comes with a pen recorder chart of response at 10 frequencies. The frequencies are not specified but the overall curve can be inferred easily.

The mechanical design also has some very commendable points. The cartridge consists of two independent movements (similar in appearance to the Pickering 240 series) fastened back to back in a turnover mount. The cartridges can be removed from the mount without any tools and the mount can therefore be used in even the most cramped arm with a minimum of inconvenience. The mount has a grounding lug so that it and the arm to which it is attached can be grounded—if they are not already grounded on the turntable.

An admirable feature is the needle. It can be changed in seconds with only the fingers; this should encourage more frequent change. There is no gap in which dust can clog and spoil compliance. The needle can be wiped of dust with a brush without any danger of removing damping material. The price is moderate—under \$25 with sapphire needles.

END



Fig. 1—Response of Shure WC10 cartridge with Dubbing D-101—RIA curve.

today's recordings. Because of the sharp rolloff beyond 8,000 cycles, it actually sounds cleaner on most pop records than magnetic cartridges of flatter response because most pop records are still much overcut and the spectrum above 8,000 cycles has more distortion than worth-while high highs.

The cartridge is particularly felicitous at 78 rpm on old shellac recordings, which it reproduces with very low scratch and—given a little judicious bass boost—surprisingly good tonal quality. It can also be fed into the low-



The Shure WC10 ceramic cartridge.

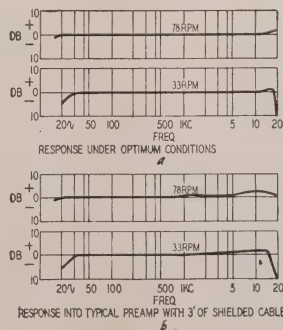


Fig. 2—Miratwin cartridge response.

A commercial killer that works!

SPEECH-MUSIC DISCRIMINATOR

By EDWARD E. PREDMORE



Device is built in old radio cabinet

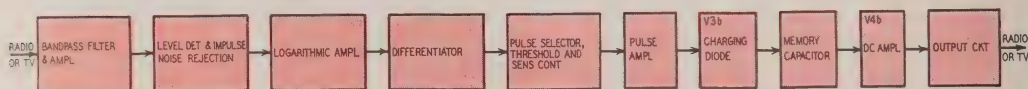


Fig. 1—Block diagram shows sequence of circuits in speech-music discriminator—unit is highly selective.

AN electronic device to discriminate between speech and music (Fig. 1) was described in the August, 1955, issue of *RADIO-ELECTRONICS*. Unfortunately, the unit fell considerably short of my expectations. After spending considerable time on the circuit, as explained in my letter of January, 1956 (Correspondence, page 16), I was able to obtain excellent results.

The device can be made to work in 1 minute by changing tubes V3 and V4 to type 12AX7. As soon as I did this, it differentiated between a singing commercial and Jimmy Durante "singing" a song. It let 100% of Durante through and rejected 80% of the singing commercial. I believe these are the tubes for which the gadget was originally designed, as the 10,000-ohm threshold resistor is then the optimum value if operated as a fixed resistor.

I now wish to apologize to Genius R. C. Jones, who invented this, for the doubts concerning him expressed in my letter in the January, 1956, issue. It would be very interesting to have Mr. Jones tell how the difference between

speech and music was discovered, if he happens to read these lines.

The block diagram shown is the same as the original circuit, made by the Vocatrol Corp., Cambridge, Mass. The circuit (Fig. 2) is the revised one. I used Music Appreciation Record MR18A *Analysis of Beethoven's Fifth Symphony* as a convenient controlled repetitive source of alternate speech and music. It gives an excellent speech-music ratio as measured by the voltages across the 2- μ f integrating capacitor C1.

10K and threshold	Sensitivity	Voltage on C1	
		speech	music (max.)
30K	maximum	-5 to -8	-1.0
15K	reduced	-5 to -8	-1.3
15K	maximum	-12 min.	-1.9
10K	reduced	-5 to -8	-2.4

Adding the .001- μ f capacitor from the cathode of V2-a to ground improves the speech-music ratio about 10%. This ratio is further improved by having the threshold resistor as a variable control, as shown. The threshold bias

rejects pulses whose peak is below the selected voltage and clips the base off larger pulses. The table shows the performance of the device with various threshold control settings, using miniature tubes. The output is flipped when the voltage across integrating capacitor C1 passes -2.8 volts.

Thus, using maximum possible threshold and full sensitivity gives the best speech-to-music ratio. For the 10,000-ohm setting it works but barely. For 15,000 ohms the speech voltage is too high and takes too long to die out after voice ceases, thus losing too much of the following music. Reducing the sensitivity corrects this but raising the threshold to 30,000 ohms does likewise and gives a greater margin for error. This margin is greatly desired for speakers who do not talk crisply and for singers. The performance using 15,000 ohms corresponds to that of about 12,000 ohms using the slightly lower-gain 6SL7 tubes.

Unfortunately, although these changes improve the ratio of voltages developed between speech and music, they do not improve the gadget's IQ very much, for it still has some trou-

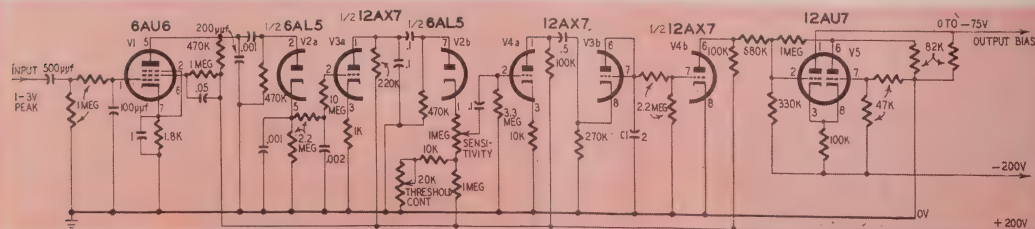


Fig. 2—Schematic diagram of the speech-music discriminator. Device is automatic and contains threshold control.

ble distinguishing between some girl "pop" singers and a singing commercial. Also, I ran across one cornet solo which the gadget insisted was speech, or to put it more correctly, the envelope of this music contained a 10-cycle component large enough to activate the gadget.

Circuit description

The theory of operation given in the August, 1955, issue seems correct and complete. I'll go through the discriminator, making operational and adjustment comments.

The input should have peaks between 1 and 3 volts. This is what the detector of my Craftsman RC10 tuner puts out on both AM and FM, so this is convenient.


Input stage VI is a bandpass amplifier, rolling off at 300 and 1,500 cycles. V2-a is a simple detector or half-wave rectifier giving the positive half envelope of the audio-frequency voltage.

V3-a, the logarithmic amplifier, can be explained as follows (with the help of Vocatrol Corp.): Consider just the grid and cathode as a diode. A positive pulse from the detector V2-a causes the grid to draw current. The positive pulse is then divided between the series grid resistors and the dynamic grid resistance of the tube, the resultant grid voltage being approximately proportional to the log of the applied positive voltage. This is amplified by V3-a as a triode. It certainly needs amplifying at this point, for the grid attenuates the peaks several hundred to one.


The plate circuit of V3-a is a low-pass filter rolling off at 8 cycles. The coupling to the next stage passes above 3 cycles as do the following coupling circuits. The 0.1- μ f coupling capacitor in the plate circuit of V3-a differentiates each word pulse, giving a short negative pulse for the start and a short positive pulse for the end of the word pulse. This capacitor seems a bit large for this job but I have not been able to show that a smaller one (.03 or .05 μ f) works any better; less works worse.

V2-b is another rectifier used to select only pulses due to the stopping of speech syllables. Positive pulses applied to the plate of V2-b cause the diode to draw current and thus pass these positive pulses. The negative pulses simply cut the tube off further and are lost completely. The threshold resistors—the 10,000-ohm resistor and the 20,000-ohm pot—act as a voltage divider along with the 1-megohm fixed resistor to apply a positive bias on the cathode of V2-b. The positive pulse must rise above this bias (plus contact potential) before it causes the tube to conduct and thus pass the pulse. In this way the bias cuts off the base of a large pulse and eliminates small positive pulses.

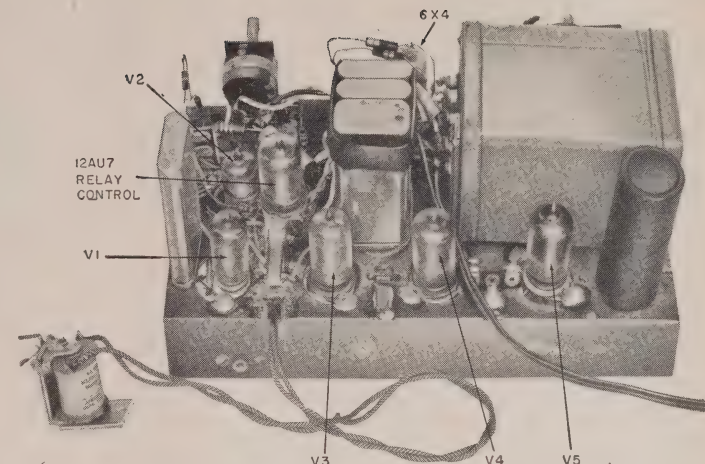Speech generates large pulses and noise and music generate small pulses. I find that for orchestral music I keep the threshold at 25,000 ohms and sensitivity at maximum. This works prac-



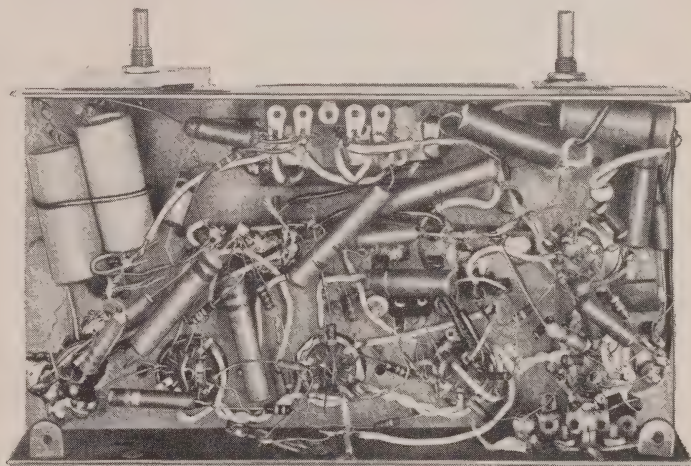Unit is built on a radio chassis, using components author had on hand.



Underchassis layout of discriminator.

tically perfectly . . . but some popular female vocalist will flip it at this value (and some announcers who slur their speech will not). Announcers connected with classical music seem to talk crisply, and on a classical music program the speech-music discriminator can be set and forgotten. On a popular music program the controls require adjustment to match the music and the announcer.

V4-a is a simple amplifier which inverts the pulse. This negative pulse applied to diode-connected V3-b causes it to draw current, producing a negative voltage on the 2- μ f integrating capacitor. This voltage builds up sharply with each pulse as it is charged through the relatively low-impedance path of V3-b and V4-a. It discharges slowly between pulses as it can only discharge through the two 2-megohm resistors in series, and takes 8 seconds to lose 63% of any voltage left on it. This voltage is direct-connected to

and amplified by V4-b, whose plate is direct-connected to V5, the flip-flop stage. As the plate of V4-b goes more positive, due to the negative voltage on C1, it causes the left side of V5 to conduct and the right side to cut off. The 1-megohm resistor from the grid to plate helps this action to be more abrupt.

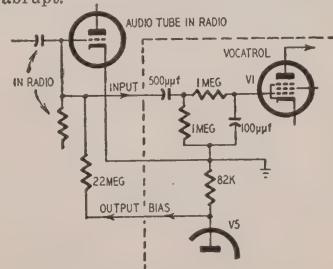


Fig. 3—Circuitry for receiver connection—relay control stage may be used.

New



MODEL O-11
Shpg. Wt.
21 lbs.

\$69⁵⁰

- * *An improved model of what was already an outstanding instrument.*
- * *Performance is unmatched in this price range.*
- * *Incorporates the extra features required for color TV servicing.*

Extra!

A FULL YEAR TO PAY

SEND FOR DETAILS OF HEATH
TIME-PAYMENT PLAN.

**5
BIG
REASONS
WHY**



**HEATH
COMPANY**

A SUBSIDIARY OF DAYSTROM, INC.

BENTON HARBOR 20, MICH.

HEATHKIT ETCHED CIRCUIT, PUSH-PULL

5" Oscilloscope Kit COLOR TV

The previous Heathkit oscilloscope (Model O-10) which was already a most remarkable instrument, has been improved even further with the release of the Heathkit Model O-11. It incorporates all the outstanding features of the preceding-model, *plus* improved vertical linearity, better sync stability, especially at low frequencies, and much-improved over-all stability of operation, including less vertical bounce with changes in level. These improvements in the Model O-11 circuit make it even more ideally suited for color TV servicing, and for critical observations in the electronic laboratory. Vertical response extends from 2 CPS to 5 MC without extra switching. Response only down 1½ DB at 3.58 MC. The 11-tube circuit features a 5UP1 cathode-ray tube. Sync circuit functions effectively from 20 CPS to better than 500 kc in five steps. Modern etched circuit boards employed in the oscilloscope circuit cut assembly time almost in half, permit a level of circuit stability never before achieved in an oscilloscope of this type, and insure against errors in assembly. Both vertical and horizontal output amplifiers are push-pull. Built-in peak-to-peak calibrating source — step-attenuated input — plastic molded capacitors and top-quality parts throughout — pre-formed and cabled wiring harness — and numerous other "extra" features. A professional instrument for the serveshop or laboratory. Compare its specifications with those of scopes selling in much higher price brackets. You can't beat it!

1 FEWER DOLLARS BRING MORE REAL QUALITY.

- Factory-to-you sales eliminate extra profit margin.
- "Build-it-yourself" eliminates labor charge.
- Heath purchasing power cuts component costs.

2 PERSONAL SERVICE ASSURES CUSTOMER SATISFACTION.

- You deal directly with the manufacturer.
- We are interested in you before and after sale.

Heathkits®

ARE YOUR BEST BUY...

3 PROVEN DESIGNS MEAN RELIABLE PERFORMANCE.

- Research and development efforts concentrated on kits only.
- All kits guaranteed to meet advertised specifications.

4 EVERY KIT BACKED BY WORLD-WIDE REPUTATION.

- The world's largest manufacturer of electronic equipment in kit form.
- Producer of more than a million electronic kits for the home workshop and industry.

5 EASY TIME-PAYMENT PLAN TO FIT YOUR BUDGET.


GREATEST SELECTION . . .

Whether your particular special interest is in servicing, ham-radio, high-fidelity, or just experimenting—there are Heathkits to fill your needs. You can equip an entire service shop or lab, buy a complete ham station or high-fidelity system, or set up a really deluxe home workshop, by choosing from the more than 70 different "do-it-yourself" electronic kits by Heath. Just glance through the kits displayed in this ad, and you will get some idea of the tremendous array of low-priced, high-quality electronic equipment available.

This new and improved oscilloscope retains all the outstanding features of the preceding model, but provides wider vertical frequency response, extended sweep-generator coverage, and increased stability. A new tube complement and improvements in the circuit make these new features possible. Vertical frequency response is essentially flat to over 1 mc, and down only 1½ DB at 500 kc. The sweep generator multivibrator functions reliably from 30 to 200,000 CPS, almost twice the coverage provided by the previous model. Deflection amplifiers are push-pull, and modern etched circuits are employed in critical parts of the design. A 5BP1 cathode-ray tube is used. The scope features external or internal sweep and sync, one volt peak-to-peak reference voltage, 3-position step-attenuated input, adjustable spot-shape control, and many other "extras" not expected at this price level. A calibrated grid screen is also provided for the face of the CRT, allowing more precise observation of wave shapes displayed. The new Model OM-2 is designed for general application wherever a reliable instrument with good response characteristics may be required. Complete step-by-step instructions and large pictorial diagrams assure easy assembly.

New HEATHKIT ETCHED CIRCUIT 5" Oscilloscope Kit

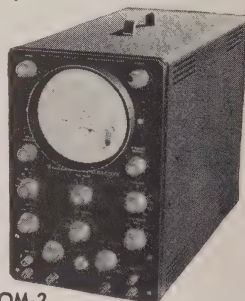- * Brand new model with improved performance specifications.
- * Full 5" scope for service work at a remarkably low price.
- * Attractively styled front panel in charcoal gray with sharp white lettering.
- * Easy to build from step-by-step instructions and large pictorials. Not necessary to read schematic.



MODEL OM-2

\$42⁵⁰

Shpg. Wt.
21 Lbs.

HEATHKIT LOW CAPACITY PROBE KIT

Oscilloscope investigation of high frequency, high impedance, or broad bandwidth circuits encountered in television requires the use of a low-capacity probe to prevent loss of gain, circuit loading, or waveform distortion. The Heathkit low-capacity probe may be used with your oscilloscope to eliminate these effects. It features a variable capacitor, to provide correct instrument impedance match. Also, the ratio of attenuation can be varied.

No. 342

\$3⁵⁰

Shpg. Wt. 1 Lb.

HEATHKIT ELECTRONIC SWITCH KIT

This handy device allows simultaneous oscilloscope observation of two signals by producing both signals, alternately, at its output. It features an all-electronic switching circuit, with no moving parts. Four switching rates are selected by a panel switch. Provides actual gain for input signals, and has a frequency response of ± 1 DB from 0 to 100 kc. Sync output provided to control and stabilize scope sweep. Will function at signal levels as low as 0.1 volt. This modern device finds many applications in the laboratory and service shop. It employs an entirely new circuit, and yet is priced lower than its predecessor.

MODEL S-3

\$21⁹⁵

Shpg. Wt. 8 Lbs.

HEATHKIT SCOPE DEMODULATOR PROBE KIT

Extend the usefulness of your oscilloscope by employing this probe. Makes it possible to observe modulation of RF or IF carriers found in TV and radio receivers. Functions much like an AM detector to pass only modulation of signal, and not the signal itself. Among other uses, it will be helpful in alignment work, as a signal tracer, and for determining relative gain. Applied voltage limits are 30 volts (RMS) and 500 volts DC. It uses an etched circuit board to simplify assembly.

NO. 337-C

\$3⁵⁰

Shpg. Wt. 1 Lb.


HEATHKIT VOLTAGE CALIBRATOR KIT

This entirely new voltage calibrator produces near-perfect square wave signals of known amplitude. Precision 1% attenuator resistors assure accurate output amplitude, and multivibrator circuit guarantees good, sharp square waves, as distinguished from clipped sine waves. Output frequency is approximately 1000 CPS. Fixed outputs selected by panel switch are: .03, 0.1, 0.3, 1.0, 3.0, 10, 30, and 100 volts peak-to-peak. Allows measurement of unknown signal amplitudes by comparing to known peak-to-peak output of VC-3 on an oscilloscope. Will also double as a square wave generator at 1000 cycles for determining gain, frequency response, or phase-shift characteristics of audio amplifiers. Equally valuable in the laboratory or in radio and TV service shops.


MODEL VC-3

\$12⁵⁰

Shpg. Wt. 4 Lbs.

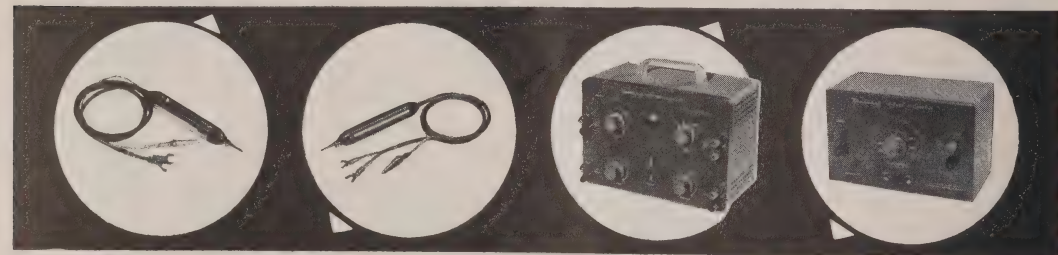

HEATHKIT ETCHED CIRCUIT VACUUM TUBE

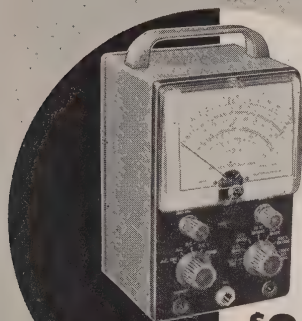

MODEL
V-7A

\$24⁵⁰

Shpg. Wt.
7 lbs.

- * Easy to build — a pleasure to use.
- * 1% precision resistors employed for high accuracy.
- * Etched circuit board cuts assembly time in half.

Voltmeter Kit

The fact that this instrument is the world's largest-selling VTVM says a great deal about its accuracy, reliability, and overall quality. The V-7A is equally popular in the laboratory or service shop, and represents an unbelievable test equipment bargain, without a corresponding sacrifice in quality. Its appearance reflects the performance of which it is capable. A large 4½" panel meter is used for indication, with clear, sharp calibrations for all ranges. Front panel controls consist of a rotary function switch and a rotary range selector switch, zero-adjust, and ohms-adjust controls. Precision 1% resistors are used in the voltage divider circuits and etched circuits are employed for most of the circuitry. This makes the kit much easier to build, eliminates the possibility of wiring errors, and assures duplication of laboratory instrument performance. This multi-function VTVM will measure AC voltage (rms), AC voltage (peak-to-peak), DC voltage, and resistance. There are 7 AC (rms) and DC voltage ranges of 0-1.5, 5, 15, 50, 150, 500, and 1500. In addition, there are 7 peak-to-peak AC ranges of 0-4, 14, 40, 140, 400, 1400, and 4000. 7 ohmmeter ranges provide multiplying factors of X1, X10, X100, X1000, X10K, X100K, and X1 megohm. Center-scale resistance readings are 10, 100, 1000, 10K, 100K ohms, 1 megohm, and 10 megohms. A DB scale is also provided. The precision and quality of the components used in this VTVM cannot be duplicated at this price through any other source. Model V-7A is the kind of instrument you will be proud to own and use.

HEATHKIT Etched Circuit RF PROBE KIT

This RF probe extends the frequency response of any 11-megohm VTVM so that it will measure RF up to 250 megacycles within ± 10%. Employs printed circuits for increased stability and ease of assembly. Ideal for extending service and laboratory applications of your Heathkit VTVM.

No. 309-C

\$3⁵⁰

Shpg. Wt. 1 lb.

HEATHKIT SCOPE DEMODULATOR PROBE KIT

This probe functions like an AM detector to pass only modulation of signal and not signal itself. Permits observation of modulation from RF or IF carriers in TV and radio receivers. Extends usefulness of your oscilloscope. Voltage limits are 30 V. rms, and 500 V. DC. Very valuable in service or laboratory applications.

No. 337-C

\$3⁵⁰

Shpg. Wt. 1 lb.


HEATHKIT 20,000 OHMS/VOLT VOM KIT

Sensitivity of this instrument is 20,000 ohms-per-volt DC and 5,000 ohms-per-volt AC. Measuring ranges are 0-1.5, 5, 50, 150, 500, 1500, and 5000 volts for both AC and DC. Also measures current in the ranges of 0-150 microamperes, 15 ma, 150 ma, 500 ma, and 15 a. Resistance ranges provide multipliers of X1, X100, and X10,000, resulting in center scale readings of 15, 15,000, and 150,000 ohms. DB ranges cover from -10 db to +65 db. Housed in attractive black bakelite case with plastic carrying handle, this fine instrument provides a total of 25 meter ranges on its two-color scale. It employs a sensitive 50 microampere, 4½" meter and features all 1% precision multiplier resistors. Requires no external power, and is, therefore, valuable in portable applications where no AC power is available.

MODEL MM-1

\$29⁵⁰

Shpg. Wt. 6 lbs.

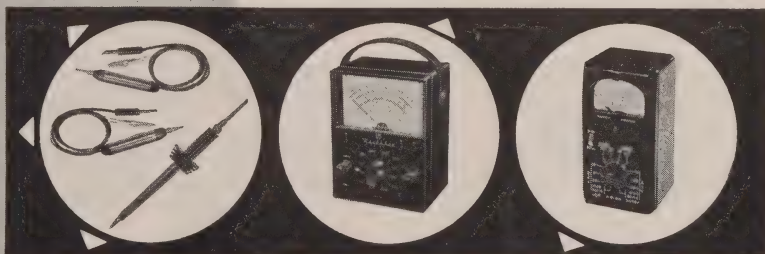

HEATHKIT 30,000-VOLT DC HIGH VOLTAGE PROBE KIT

This probe provides a multiplication factor of 100 on the DC ranges of the Heathkit 11-megohm VTVM. Precision multiplier resistor mounted inside the two-color plastic probe body. Plenty of insulation for completely safe operation, even at highest TV potentials. Designed especially for TV service work.

No. 336

\$4⁵⁰

Shpg. Wt. 2 lbs.

HEATHKIT HANDITESTER KIT

The Model M-1 measures AC or DC voltage at 0-10, 30, 300, 1000, and 5000 volts. Direct current ranges are 0-10 ma, and 0-100 ma. Ohmmeter ranges are 0-3000 (30 ohm center scale) and 0-300,000 ohms (3,000 ohms center scale). Uses a 400 microampere meter for sensitivity of 1000 ohms-per-volt. A very popular test device for the home experimenter, electricians, and appliance repairmen, and for use as an "extra" instrument in the service shop. Its small size and rugged construction make it perfect for any portable application. Easily slips into your tool box, glove compartment, coat pocket, or desk drawer. Top quality, precision components employed throughout.

MODEL M-1

\$14⁵⁰

Shpg. Wt. 3 lbs.



HEATH COMPANY

A Subsidiary of Daystrom, Inc.

BENTON HARBOR 20, MICH.

CONTROLLED QUALITY...

Incoming parts inspection, and inspection of material coming off of our own production line assures you of the finest "build-it-yourself" kit that money can buy. Each kit contains all the components you need for assembly—and you can have confidence in the quality of the parts themselves. In addition to this inspection procedure, an extensive proof-building program for each new kit guarantees easy-to-follow instructions and reliable performance.


This brand new AC vacuum tube voltmeter emphasizes stability, broad frequency response, and sensitivity. It is designed especially for audio measurements, and low-level AC measurements in power supply filters, etc. Employs a cascode amplifier circuit with cathode-follower isolation between the input and the amplifier, and between the output stage and the preceding stages. An extremely stable circuit with high input impedance (1 megohm at 1000 CPS). Response of the AV-3 is essentially flat from 10 CPS to 200 kc, and is usable for tests even beyond these frequency limits. Increased damping in the meter circuit stabilizes the meter for low frequency tests. Nylon insulating bushings at the input terminals reduce leakage, and permit the use of the 5-way Heath binding post.

The extremely wide voltage range covered by the AV-3 makes it especially valuable not only in high-fidelity and service work, but also in experimental laboratories. AC (RMS) voltage ranges are 0-.01, .03, .1, .3, 1, 3, 10, 30, 100, and 300 V. Decibel ranges cover -52 DB to +52 DB. An entirely new circuit as compared to the previous model. Employs 1% precision multiplier resistors for maximum accuracy. Handles AC measurements from a low value of one millivolt to a maximum of 300 volts.

HEATHKIT NEW AUDIO VACUUM TUBE

Voltmeter Kit

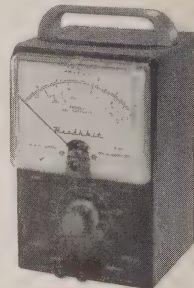- * Brand new circuit for extended frequency response and added stability.
- * Ten accurate ranges from 0-.01 to 0-300 volts.
- * Modern, functional panel styling. "On-off" switch at both extreme ends of range switch.



MODEL AV-3

\$29.50

Shpg. Wt. 5 Lbs.

HEATHKIT AUDIO WATTMETER KIT

This instrument measures audio power directly at 4, 8, 16, or 600 ohms. Load resistors are built in. Covers 0-5 MW, 50 MW, 500 MW, 5 W, and 50 W full scale. Provides 5 switch-selected DB ranges covering from -10 DB to +30 DB. Large 4½" 200 microampere meter and precision multiplier resistors insure accuracy. Frequency response is ± 1 DB from 10 CPS to 250 kc. Functions from AC power line. Use in the audio laboratory or in home workshop.

MODEL AW-1

\$29.50

Shpg. Wt. 6 Lbs.




HEATHKIT AUDIO ANALYZER KIT

This multi-function instrument combines an AC VTVM, an audio wattmeter, and an intermodulation analyzer into one case, with combined input and output terminals and built-in high and low frequency oscillators. The VTVM ranges are .01, .03, .1, .3, 1, 3, 10, 30, 100, and 300 volts (RMS). Wattmeter ranges are .15 MW, 1.5 MW, 15 MW, 150 MW, 1.5 W, 15 W, 150 W. IM scales are 1%, 3%, 10%, 30%, and 100%. Provides internal load resistors of 4, 8, 16, or 600 ohms. A valuable instrument for the engineer or serious audiophile.

MODEL AA-1

\$59.50

Shpg. Wt. 13 Lbs.

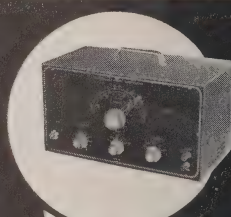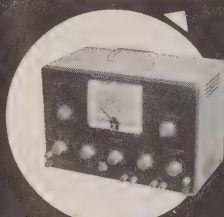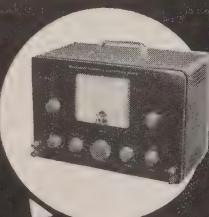

HEATHKIT HARMONIC DISTORTION METER KIT

The HD-1 is equally valuable for the audio engineer or the serious audiophile. Used with a low-distortion audio signal generator, this instrument will measure the harmonic content of various amplifiers under a variety of conditions. Functions between 20 and 20,000 CPS, and reads distortion directly on the panel meter in ranges of 0-1, 3, 10, 30, and 100 percent full scale. Built-in VTVM for initial reference settings and final distortion readings has voltage ranges of 0-1, 3, 10, and 30 volts. 1% precision resistors employed for maximum accuracy. Features voltage regulation and other "extras". Meter calibrated in volts (RMS), percent distortion, and DB.

MODEL HD-1

\$49.50

Shpg. Wt. 13 Lbs.

HEATHKIT AUDIO OSCILLATOR KIT

Producing both sine waves and square waves, the Model AO-1 covers a frequency range of 20 to 20,000 CPS in three ranges. An extra feature is thermistor regulation of output for flat response through the entire frequency range. AF output is provided at low impedance, and with low distortion. Produces good sine waves, and good, clean square waves with a rise time of only two micro-seconds for checking square wave response of audio amplifiers, etc. Designed especially for the serviceman and high-fidelity enthusiast. A real dollar value in test equipment.


MODEL AO-1

\$24.50

Shpg. Wt. 10 Lbs.

HEATHKIT

Audio Generator Kit

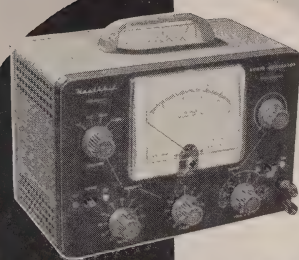

**MODEL
AG-9**

\$34⁵⁰

Shpg. Wt.
8 Lbs.

- * Less than 0.1% distortion — ideal for hi fi work.
- * Large 4½" meter indicates output.
- * Step-type tuning for maximum convenience.

This particular audio generator is "made to order" for high fidelity applications. It provides quick and accurate selection of low-distortion signals throughout the audio range. Three rotary selector switches on the front panel allow selection of two significant figures and a multiplier for determining audio frequency. In addition, it incorporates a step-type output attenuator and a continuously variable attenuator. Output is indicated on a large 4½" panel meter calibrated in volts and in db. Attenuator system operates in steps of 10 db, corresponding with the meter calibration. Output ranges are 0-.003, .01, .03, .1, .3, 1, 3, and 10 volts rms. A "load" switch provides for the use of a built-in 600 ohm load or an external load of higher impedance when required. Output and frequency indicators accurate to within $\pm 5\%$. Distortion is less than .1 of 1% between 20 cps and 20,000 cps. Total range is 10 cps to 100 kc. New engineering details combine to provide the user with an unusually high degree of operating efficiency. Oscillator frequency selected entirely by the switch method means that accurate resetability is provided. Comparable to units costing many dollars more, and ideal for use in critical high fidelity applications. Shop and compare, and you will appreciate the genuine value of this professional instrument.

HEATHKIT RESISTANCE SUBSTITUTION BOX KIT

The RS-1 contains 36 10% 1-watt resistors ranging from 15 ohms to 10 megohms in standard RETMA values. All values are switch-selected for use in determining desirable resistance values in experimental circuits. Many applications in radio and TV service work.

MODEL RS-1
\$5⁵⁰

Shpg. Wt. 2 Lbs.

HEATHKIT CONDENSER SUBSTITUTION BOX KIT

This kit contains 18 RETMA standard condenser values that can be selected by a rotary switch. Values range from 0.00001 mfd to 0.22 mfd. All capacitors rated at 400 volts or higher. Capacitors are either silver-mica, or plastic molded.

MODEL CS-1
\$5⁵⁰

Shpg. Wt. 2 Lbs.

HEATHKIT AUDIO GENERATOR KIT

The Model AG-8 is a low cost, high performance unit for use in service shop, or home workshop. It covers the frequency range of 20 cps to 1 mc in five ranges. Output is 600 ohms, and overall distortion will be less than .4 of 1% from 100 cps through the audible range. Output is available up to 10 volts, under no load conditions, and output remains constant within ± 1 db from 20 cps to 400 kc. A five-step attenuator provides control of the output. Precision resistors are employed in the frequency determining network.

MODEL AG-8
\$29⁵⁰


Shpg. Wt. 11 Lbs.

HEATHKIT DECADE CONDENSER KIT

Precision, 1% silver-mica capacitors are employed in the Model DC-1 in such a way that a selection of precision capacitor values is provided ranging from 100 mmf (.0001 mfd) to 0.11 mfd (110,000 mmf) in 100 mmf steps. Extremely valuable in all types of design and development work. Switches are ceramic wafer types.

MODEL DC-1
\$16⁵⁰

Shpg. Wt. 3 Lbs.

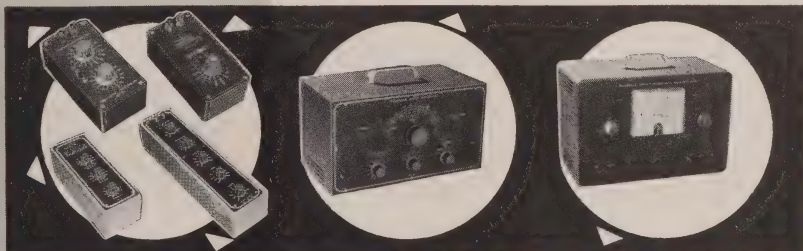

HEATHKIT DECADE RESISTANCE KIT

The Model DR-1 incorporates twenty 1% precision resistors arranged around five rugged switches so that various combinations of switch positions will provide a total range of 1 ohm to 99,999 ohms in 1-ohm steps. Switches are labeled "units," "tens," "hundreds," "thousands," and "ten thousands." Use it for ohm-meter calibration in bridge circuits as test values in multiplier circuits, etc.

MODEL DR-1
\$19⁵⁰

Shpg. Wt. 4 Lbs.

HEATHKIT VARIABLE VOLTAGE REGULATED POWER SUPPLY KIT

This power supply is regulated for stability, and the amount of DC output available from the power supply can be controlled manually from zero to 500 volts. Will provide regulated output at 450 volts up to 10 ma, or up to 130 ma at 200 volts output. In addition to furnishing B-plus, the power supply provides 6 volts AC at 4 amperes for filaments. Both the B-plus output and the filament output are isolated from ground. Ideal power supply for use in experimental work in the laboratory, the home workshop, or the ham shack. Large 4½" panel meter indicates output voltage or current.

MODEL PS-3
\$35⁵⁰

Shpg. Wt. 17 Lbs.



HEATH COMPANY
A Subsidiary of Daystrom, Inc.
BENTON HARBOR 20, MICH.


BONUS PERFORMANCE . . .

If a single word had to be selected to describe Heath Company advertising policy, it would be "conservative." By this we mean that the performance specifications and features are not exaggerated, and that the descriptions are accurate. We specify performance on the conservative side so you can be sure of equaling or exceeding our specifications. In almost every instance our kits will do more than we claim. Extra care in construction, and calibration against an accurate standard can extend performance well beyond advertised levels.

HEATHKIT

Signal Generator Kit

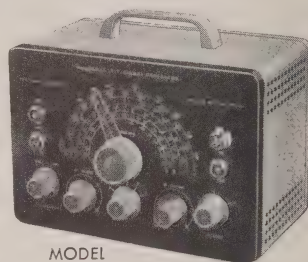- * No calibration required with pre-aligned coils.
- * Modulated or unmodulated RF output.
- * 110 mc to 220 mc frequency coverage.



MODEL
SG-8

\$19⁵⁰

Shpg. Wt.
8 Lbs.

Here is an RF signal generator for alignment applications in the service shop or the home workshop. Thousands of these units are in use in service shops all over the country. Produces RF signals from 160 kc to 110 mc on fundamentals on five bands. Also covers from 110 mc to 220 mc on calibrated harmonics. RF output is in excess of 100,000 microvolts at low impedance. Output is controllable with a step-type and a continuously variable attenuator. Front panel controls provide selection of either unmodulated RF output or RF modulated at 400 cps. In addition, two to three volts of audio at approximately 400 cps are available at the output terminals for testing AF circuits. Employs a 12AU7 and a 6C4 tube. Built-in power supply uses a selenium rectifier.

One of the most outstanding features about the Model SG-8 is the fact that it can be built in just a few hours, even by one not thoroughly experienced in electronics work. Complete step-by-step instructions combined with large pictorial diagrams assure successful assembly. Pre-aligned coils make calibration from an external source unnecessary.

HEATHKIT LABORATORY GENERATOR KIT

This laboratory RF signal generator covers from 100 kc to 30 mc on fundamentals in five bands. The output signal may be pure RF, or may be modulated at 400 cycles from 0 to 50%. Provision for external modulation has been made. RF output available up to 100,000 microvolts. Output controlled by a fixed step and a variable attenuator. Output impedance is 50 ohms. Panel meter reads RF output or percentage of modulation. Incorporates voltage regulated B+ supply, double shielding of oscillator circuits, copper plated chassis, and other "extras."

MODEL LG-1

\$39⁵⁰

Shpg. Wt. 16 Lbs.


HEATHKIT TV ALIGNMENT GENERATOR KIT

This improved sweep generator model provides essential stability and flexibility for work on FM, monochrome TV, or color TV sets. Covers 3.6 mc to 220 mc in four bands. Provides usable output even on harmonics. Sweep deviation from 0-42 mc, depending on base frequency. All-electronic sweep circuit eliminates unwieldy mechanical arrangements. Includes built-in crystal marker generator providing output at 4.5 mc and multiples thereof, and variable marker covering 19 to 60 mc on fundamentals and from 57 to 180 mc on harmonics. Effective two-way blanking.

MODEL TS-4A

\$49⁵⁰

Shpg. Wt. 16 Lbs.

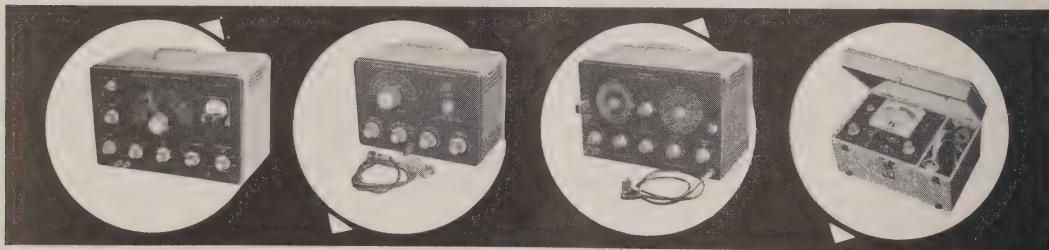

HEATHKIT LINEARITY PATTERN GENERATOR KIT

This instrument supplies information for white dots, cross-hatch pattern, horizontal bar pattern, or vertical bar pattern. It feeds video and sync signals to the set under test, with completely controlled gain, and unusual stability. Covering channels 2 to 13, the LP-2 will produce 5 to 6 vertical bars and 4 to 5 horizontal bars. The dot pattern presentation is a must for the setting of color convergence controls in the color TV set. Panel provision made for external sync if desired. Use for adjustment of vertical and horizontal linearity, picture size, aspect ratio, and focus. Power supply is regulated for added stability. Essential in the up-to-date TV service shop.

MODEL LP-2

\$22⁵⁰

Shpg. Wt. 7 Lbs.

HEATHKIT CATHODE RAY TUBE CHECKER KIT


This instrument checks cathode emission, beam current, shorted elements, and leakage between elements in electro-magnetic picture tube types. It eliminates all doubt for the TV serviceman, and even more important, for the customer. Features its own self-contained power supply, transformer operated to furnish normal test voltages for the CRT. Employs spring-loaded switches for maximum operator protection. Large 4 1/2" meter indicates CRT condition on "good-bad" scale. Luggage-type portable case ideal for home service calls. Special "shadowgraph" test permits projection of light spot on screen. Also gives relative check of picture tube screen coating.

MODEL CC-1

\$22⁵⁰

Shpg. Wt. 10 Lbs.

HEATHKIT

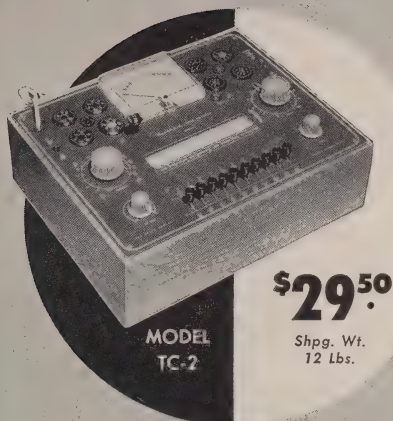

MODEL
TC-2


\$29⁵⁰

Shpg. Wt.
12 Lbs.

- * Attractive counter-style cabinet.
- * Wiring-harness simplifies assembly.
- * Large 4½" meter with two-color "good-bad" scale.
- * Separate tube element switches prevent obsolescence.

HEATHKIT PORTABLE TUBE CHECKER KIT

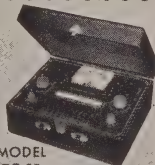This portable tube checker is identical, electrically, with the Model TC-2. However, it is housed in an attractive and practical carrying case, finished in proxilin impregnated material. The cover is detachable, and the hardware is brass plated. This rugged unit is ideal for home service calls or any portable application.



MODEL
TC-2P

\$34⁵⁰ Shpg. Wt.
15 Lbs.

HEATHKIT DIRECT READING CAPACITY METER KIT

Operation of this instrument is simplicity itself. One has only to connect a capacitor to the terminals, select the proper range, and read the capacity value directly on the large 4½" meter calibrated in mmf and mfd. Ranges are 0 to 100 mmf, 1,000 mmf, 0.01 mfd, and 0.1 mfd full scale. Precision calibrating capacitors supplied. Not susceptible to hand capacity effects. Residual capacity less than 1 mmf. Especially valuable in production line checking, or in quality control.



MODEL CM-1

\$29⁵⁰

Shpg. Wt.
7 Lbs.

HEATH COMPANY

A Subsidiary of Daystrom, Inc.
BENTON HARBOR 20, MICH.

Tube Checker Kit

This fine piece of test gear checks tubes for quality, emission, shorted elements, open elements, and filament continuity. Will test all tube types normally encountered in radio and TV service work. Sockets provided for 4, 5, 6, and 7-pin large, rectangular, and miniature types, octal and locat types, the Hytron 9-pin miniatures, and pilot lamps. Condition of tubes indicated on a large 4½" meter with multi-color "good-bad" scale. An illuminated roll chart is built right in, providing test data for various tube types. This tester provides switch selection of 14 different filament voltage values from 0.75 volts to 117 volts. Individual switches control each tube element. Close tolerance resistors employed in critical test circuits for maximum accuracy. A professional instrument both in appearance and performance.

The Model TC-2 is very simple to build, even for a beginner. It employs a color-coded cable harness for neat, professional under-chassis wiring. Comes with attractive counter style cabinet, and portable cabinet is available separately. At this price, even the part-time serviceman can afford his own tube checker for maximum efficiency in service work.

HEATHKIT TV PICTURE TUBE TEST ADAPTER

Designed especially for use with the Model TC-2 tube checker. Use it to test TV picture tubes for emission, shorts, etc. Consists of 12-pin TV tube socket, 4 ft. cable, octal connector, and necessary technical data. Not a kit.



MODEL 355

\$4⁵⁰

Shpg. Wt.
1 Lb.

HEATHKIT VISUAL-AURAL SIGNAL TRACER KIT

Although designed primarily for radio receiver work, this valuable instrument finds extensive application in FM and TV servicing as well. Features a high-gain channel with demodulator probe, and a low-gain channel with audio probe. Will trace signals in all sections of a radio receiver and in many sections of a FM set or TV receiver. Uses built-in speaker and electron beam eye tube for indication. Also features built-in wattmeter and a noise locator circuit. Provision for patching speaker and/or output transformer into external set.

MODEL T-3

\$23⁵⁰

Shpg. Wt. 9 Lbs.

HEATHKIT CONDENSER CHECKER KIT

The Model C-3 consists of an AC powered bridge for both capacitive and resistive measurements. Bridge balance is indicated on electron beam eye tube, and capacity or resistance value is indicated on front panel calibrations. Measures capacity in four ranges from .00001 mfd to .005 mfd, .001 mfd to .5 mfd, .1 mfd to 50 mfd, and 20 mfd to 1000 mfd. Measures resistance in two ranges, from 100 ohms to 50,000 ohms, and from 10,000 ohms to 5 megohms. Selection of five different polarizing voltages for checking capacitors, from 25 volts DC to 450 volts DC. Checks paper, mica, ceramic, and electrolytic capacitors. Indicates power factor of electrolytic condensers.

MODEL C-3

\$19⁵⁰

Shpg. Wt. 7 Lbs.

PIONEER DESIGN . . .


New and unique approaches to instrument and equipment designs are a Heath Company tradition. We concentrate all our development efforts on kit projects, since this is our prime activity—and not just a sideline. This logically results in more efficient, more reliable circuit designs—and you benefit from this constant engineering progress. Buying from the undisputed leader in the electronic kit field assures you of completely modern equipment, with outstanding advanced design features.

The Model IB-2 is a completely self-contained unit. It has a built-in power supply, a built-in 1000 cycle generator, and a built-in vacuum tube detector. Provision has been made on the panel for connection to an external detector, an external signal generator, or an external power supply. A 100-0-100 micro-ampere meter on the front panel provides for null indications. Measures resistance from 0.1 ohm to 10 megohms, capacitance from 10 mmf to 100 mfd, inductance from 10 mh to 100 h, dissipation factor (D) from 0.002 to 1, and storage factor (Q) from 0.1 to 1000. $\frac{1}{2}$ of 1% decade resistors employed for maximum accuracy. Typical accuracy figures are: resistance, $\pm 3\%$; capacitance $\pm 3\%$; inductance, $\pm 10\%$; dissipation factor, $\pm 20\%$; storage factor, $\pm 20\%$. Employs a Wheatstone bridge, a Capacity Comparison bridge, a Maxwell bridge, and a Hay bridge. Special two-section CRL dial provides maximum convenience in operation. Use the Model IB-2 for determining values of unmarked components, checking production or design samples, etc. A real professional instrument.

HEATHKIT

Impedance Bridge Kit

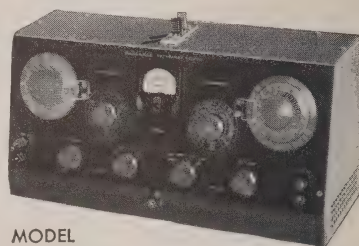- * $\frac{1}{2}\%$ precision resistors and silver-mica capacitors.
- * Battery-type tubes, no warm-up required.
- * Built-in phase shift generator and amplifier.



MODEL
IB-2

\$59⁵⁰ Shpg. Wt.
12 Lbs.

HEATHKIT "Q" METER KIT

The Q Meter permits measurement of inductance from 1 microhenry to 10 millihenries, "W" on a scale calibrated up to 250 full scale, with multiplying factors of 1 or 2, and capacitance from 40 mmf to 450 mmf, ± 3 mmf. Built-in variable oscillator permits testing components from 150 kc to 18 mc. Large $4\frac{1}{2}$ " panel-mounted meter is features. Very handy for checking peaking coils, chokes, etc. Use to determine values of unknown condensers, both variable and fixed. Compile data for coil winding purposes, or measure RF resistance. Distributed capacity, and Q of coils.

MODEL QM-1

\$44⁵⁰

Shpg. Wt. 14 Lbs.


HEATHKIT ISOLATION TRANSFORMER KIT

This device isolates equipment under test from the power line. It is rated at 100 volt-amperes continuously, or 200 volt-amperes intermittently. AC-DC sets may be plugged directly into the IT-1 without the chassis becoming "hot." Additionally, since the IT-1 is fused, it is ideal for use as a buffer between the power line and a questionable receiver, or a new piece of equipment. Protects main fuses. Features voltage control, allowing control of the output from 90 volts to 130 volts. Panel meter monitors output voltage. A very handy device at an extremely low price.

MODEL IT-1

\$16⁵⁰

Shpg. Wt. 9 Lbs.

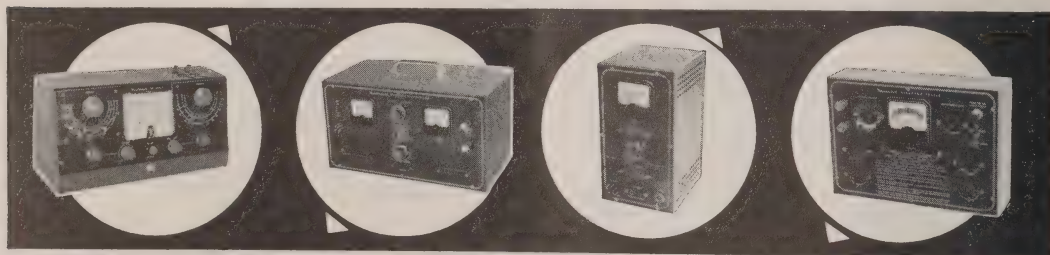

HEATHKIT 6-12 VOLT BATTERY ELIMINATOR KIT

This completely modern battery eliminator will supply DC output in two ranges for both 6-volt and 12-volt automobile radios. The output is variable for each range, so that operating voltage can be raised or lowered to determine how the receiver functions under adverse conditions. Range is 0-8 volts DC or 0-16 volts DC. Will supply up to 15 amperes on the 6-volt range, or up to 7 amperes on the 12-volt range. Two 10,000 microfarad output filter capacitors insure smooth DC output. Two separate panel meters indicate output voltage or output current. Makes it possible to test automobile radios inside at the workbench. Will also double as a battery charger.

MODEL BE-4

\$31⁵⁰

Shpg. Wt. 17 Lbs.

HEATHKIT 6-VOLT VIBRATOR TESTER KIT

This instrument functions very much like a tube checker, to test auto radio vibrators. Vibrator condition is indicated on a simple "good-bad" scale. Tests for proper starting and overall quality of operation, of both interrupter and self-rectifier types of 6-volt vibrators. The Model VT-1 is designed to operate from any battery eliminator capable of delivering continuously variable output from 4 to 6 volts DC at 4 amperes or more. It is an ideal companion unit for the Heathkit Model BE-4 battery eliminator. The construction book for the VT-1 contains vibrator test chart for popular 6-volt vibrator types. A real time saver!

MODEL VT-1

\$14⁵⁰

Shpg. Wt. 6 Lbs.

HEATHKIT DX-100 PHONE AND CW



**MODEL
DX-100**

Shpg. Wt.
107 Lbs.

\$189⁵⁰

Shipped motor freight unless
otherwise specified.
\$50.00 deposit required
on c.o.d. orders.

- * Phone or CW on 160, 80, 40, 20, 15, 11 and 10 meters.
- * Built-in VFO, modulator, and power supplies.
- * High quality components used throughout for reliable performance.
- * Features 5-point TVI suppression.

HEATHKIT COMMUNICATIONS TYPE ALL BAND RECEIVER KIT

This receiver covers 550 kc to 30 mc in four bands, and is ideal for the short-wave listener or beginning amateur. It provides good sensitivity and selectivity, combined with good image rejection. Amateur bands clearly marked on illuminated dial scale. Employs transformer type power supply—electrical bandspread—antenna trimmer—separate RF and AF gain controls—noise limiter—headphone jacks—and automatic gain control. Has built-in VFO for CW reception.

CABINET: Fabric covered cabinet with aluminum panel as shown. Part 91-15A. Shipping weight 5 lbs. \$4.95+

MODEL AR-3

\$307⁵

INCLUDING NEW
EXCISE TAX*
(Less Cabinet)
Shpg. Wt. 12 Lbs.

Transmitter Kit

The Heathkit DX-100 transmitter is in a class by itself in that it offers features far beyond those normally received at this price level. It takes very little listening on the bands to discover how many of these transmitters are in operation today. A truly amazing piece of amateur gear. The DX-100 features a built-in VFO and a built-in modulator. It is TVI suppressed, and uses pi network interstage coupling and output coupling. Will match antenna impedances from approximately 50 to 600 ohms. Extensive shielding is employed, and all incoming and outgoing circuits are filtered. The cabinet features interlocking seams for simplified assembly and minimum RF radiation outside of the cabinet. Provides a clean strong signal on either phone or CW, with RF output in excess of 100 watts on phone, and 120 watts on CW. Completely bandswitching from 160 through 10 meters. A pair of 1625 tubes are used in push-pull for the modulator, and the final consists of a pair of 6146 tubes in parallel. The VFO dial and meter face are illuminated, and all front panel controls are located for maximum convenience. Panel meter reads driver plate I, final grid I, final plate I, final plate voltage, and modulator current. The chassis is constructed of heavy #16 gauge copper-plated steel. Other high-quality components include potted transformers, ceramic switch and variable capacitor insulation, silver-plated or solid-silver switch terminals, etc. All coils are pre-wound, and the main wiring cable is pre-harnessed. The kit can be built by a beginner from the comprehensive step-by-step instructions supplied. It is a proven, trouble-free rig, that will insure many hours of "on-the-air" enjoyment in your ham shack.


HEATHKIT VFO KIT

You can go VFO for less than you might expect. Here is a variable frequency oscillator that covers 160, 80, 40, 20, 15, 11, and 10 meters with three basic oscillator frequencies, that sells for less than \$20. Provides better than 10 volt average RF output on fundamentals. Plenty of drive for most modern transmitters. Requires a power source of only 250 VDC at 15 to 20 ma. and 6.3 VAC at 0.45A. Incorporates a regulator tube for stability. Illuminated frequency dial reads frequency directly on the band being employed. Temperature-compensated capacitors offset coil heating.

MODEL VF-1

\$19⁵⁰

Shpg. Wt. 7 Lbs.

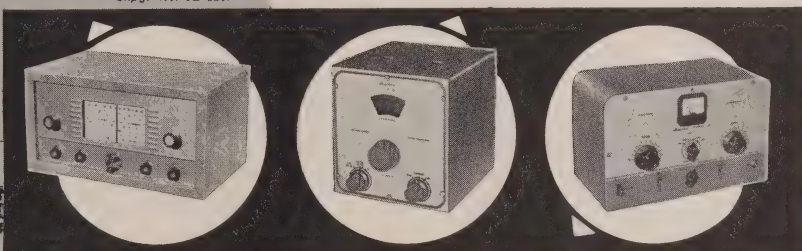

EASY ON THE BUDGET!

You can buy Heathkits on an easy time-payment plan that provides a full year to pay. Write for complete details and special order blank.



HEATH COMPANY

A Subsidiary of Daystrom, Inc.

BENTON HARBOR 20, MICH.

HEATHKIT CW TRANSMITTER KIT

This is the original low-priced Heathkit CW transmitter. Its reliable performance has been proven time and time again on the CW bands. Designed for crystal control, the Model AT-1 covers 80, 40, 20, 15, 11, and 10 meters. May be excited from external VFO. Plate power input up to 30 watts. Power supply built in. Panel meter indicates grid current or plate current for final. Incorporates pre-wound coils, copper-plated chassis, built-in line filter, profuse shielding, and top-quality parts throughout. Crystal socket and key jack on front panel. Built-in key-click filter, and single-knob bandswitching. 52-ohm coaxial output. Uses 6AG7 oscillator-multiplier, 6L6 power amplifier-doubler, and 5U4G rectifier.

MODEL AT-1

\$29⁵⁰

Shpg. Wt. 15 Lbs.

DOLLAR-SAVING ECONOMY...

There would be no particular achievement in selling inexpensive merchandise at a low price—although it is being done every day. However, there is something to crow about when, through tremendous purchasing power and factory-to-you distribution, Heath Company can offer top-quality equipment, using name-brand components, at such low prices. This is real economy, as opposed to the so-called "bargains". Needless to say, there is a big difference.

The DX-35 features a 6146 final amplifier to provide 65 watts plate power input on CW, with controlled carrier modulation peaks up to 50 watts on phone. In addition, it is a most attractive transmitter. Modulator and power supplies are built-in, and the rig covers 80, 40, 20, 15, 11, and 10 meters with a single band-change switch. Pi network output coupling provided for matching various antenna impedances. A 12BY7 buffer stage provided ahead of the final amplifier for plenty of drive on all bands. 12BY7 oscillator and 12AU7 modulator. Provision for switch selection of three different crystals. Crystals reached through access door at rear. Front panel controls marked "off—CW—stand-by—phone", "final tuning", "antenna coupling", "drive level control", and "band change switch". Panel meter indicates final grid current or final plate current. A perfect low-power transmitter both for the novice, and for the more experienced operator. A remarkable power package for the price. Incidentally, the price includes tubes, and all other components necessary for assembly. As with all Heathkits, comprehensive instruction manual assures successful assembly.

HEATHKIT PHONE AND CW

Transmitter Kit

- * 6146 final amplifier for full 65-watt plate power input.
- * Phone and CW operation on 80, 40, 20, 15, 11, and 10 meters. Pi network output coupling.
- * Switch selection of three crystals — provision for external VFO excitation.



MODEL DX-35

\$56⁹⁵ Shpg. Wt. 24 Lbs.

HEATHKIT ANTENNA IMPEDANCE METER KIT

This instrument employs a 100 microampere panel meter and covers the impedance range of 0-600 ohms for RF tests. Functions up to 150 mc. Used in conjunction with signal source, such as the Heathkit Model GD-1B grid dip meter, the Model AM-1 will determine antenna resistance and resonance, match transmission lines for minimum standing wave ratio, determine receiver input impedance, etc. Will also double as a phone monitor. A very valuable device for many uses in the ham shack.

MODEL AM-1

\$14⁵⁰

Shpg. Wt. 2 Lbs.


HEATHKIT "Q" MULTIPLIER KIT

The QF-1 functions with any receiver with an IF frequency between 450 and 460 kc that is not AC-DC type. Operates from the receiver power supply, requiring only 6.3 VAC at 300 ma. and 150 to 250 VDC at 2 ma. Simple to connect with cable and plugs supplied. Provides additional selectivity for separating two signals, or will reject one signal and eliminate heterodyne. A big help on crowded bands. Provides an effective Q of approximately 4,000 for sharp "peak" or "null". Tunes to any signal within the IF bandpass of the receiver, without changing main receiver tuning dial.

MODEL QF-1

\$9⁹⁵

Shpg. Wt. 3 Lbs.

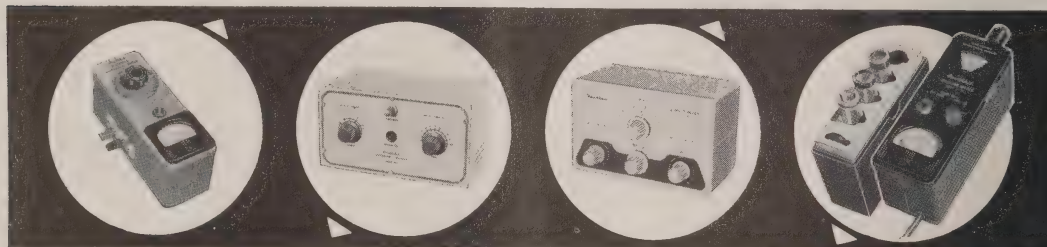

HEATHKIT ANTENNA COUPLER KIT

This device is designed to match the Model AT-1 transmitter to a long-wire antenna. In addition to impedance matching, this unit incorporates an L-type filter which attenuates signals above 36 megacycles, thereby reducing TVI. Designed for 52 ohm coaxial input. Handles power up to 75 watts, 10 through 80 meters. Uses a tapped inductor and variable capacitor. Neon RF indicator on front panel. Copper-plated chassis—high quality components throughout—simple to build. Eliminates waste of valuable communications power due to improper matching. A "natural" for all AT-1 transmitter owners.

MODEL AC-1

\$14⁵⁰

Shpg. Wt. 4 Lbs.

HEATHKIT GRID DIP METER KIT


The grid dip meter was originally designed for the ham shack. However, its use has been extended into the service shop and laboratory. Continuous frequency coverage from 2 mc to 250 mc with pre-wound coils. 500 microampere panel meter employed for indication. Use for locating parasites, neutralizing, determining RF circuit resonant frequencies, etc. Coils are included with kit, as is a coil rack. Front panel controls include sensitivity control for meter, and phone jack for listening to zero-beat. Will also double as an absorption-type wavemeter.

MODEL GB-1B

\$19⁵⁰

Shpg. Wt. 4 Lbs.

HEATHKIT BROADCAST BAND

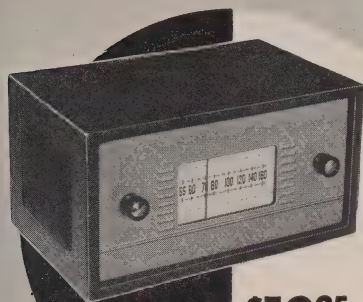

MODEL BR-2

(Less Cabinet)

Shpg. Wt. 10 Lbs.

\$19²⁵

INCLUDING NEW
EXCISE TAX*

ATTENTION BEGINNERS . . .

This kit is an ideal "first project" if you have never built a Heathkit before. A good chance to "learn by doing."

- * Miniature tubes and high-gain IF transformer.
- * Rod-type built-in antenna. Good sensitivity and selectivity.
- * 5½-inch PM speaker.
- * Provision for phono jack.
- * Transformer-operated power supply.


HEATHKIT PROFESSIONAL RADIATION COUNTER KIT

This sensitive and reliable instrument has already found extensive application in prospecting, and also in medical and industrial laboratories. It offers outstanding performance at a reasonable price. Front-panel meter indicates radiation level, and oral indication produced by panel-mounted speaker. Meter ranges are 0-100, 600, 6,000 and 60,000 counts per minute, and 0—.02, .1, 1 and 10 milliroentgens per hour. The probe, with expansion cord, employs type 6306 bismuth counter tube, sensitive to both beta and gamma radiation. It is simple to build, even for a beginner.

MODEL RC-1

\$79⁹⁵

Shpg. Wt. 8 Lbs.

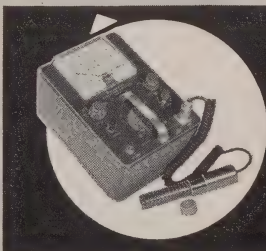

- * Amazing new circuit for high efficiency.

- * Compact, portable and rugged.
- * Stable circuit requires only one 67½ volt "B" battery and two 1½ volt "A" batteries.



HEATH COMPANY

A Subsidiary of Daystrom, Inc.

BENTON HARBOR 20, MICH.

Receiver Kit

You need no previous experience in electronics to build this table-model radio. The Model BR-2 receiver covers 550 kc to 1620 kc and features good sensitivity and selectivity over the entire band. A 5½" PM speaker is employed, along with high gain miniature tubes and a new rod-type built-in antenna. Provision has been made in the design of this receiver for its use as a phonograph amplifier. The phono jack is located on the back chassis apron. A transformer operated power supply is featured for safety of operation, as opposed to the usual AC-DC supply commonly found in "economy radio kits." Don't let the low Heathkit price deceive you. This is the kind of set you will want to show off to your family and friends after you have finished building it.

Construction of this radio kit is very simple. Giant size pictorial diagrams and detailed step-by-step instructions assure your success. The construction manual also includes an explanation of basic receiver circuit theory so you can "learn by doing" as the receiver is built. The manual even provides information on resistor and capacitor color codes, soldering techniques, use of tools, etc. If you have ever had the urge to build your own radio receiver, the outstanding features of this popular Heathkit deserve your attention.

CABINET: Proxylon impregnated fabric covered plywood cabinet available for the BR-2 receiver as shown. Complete with aluminum panel, reinforced speaker grill, and protective rubber feet. Shipping weight 5 lbs., part No. 91-9A.....\$4.95*



HEATHKIT CRYSTAL RECEIVER KIT

The crystal radio of Dad's day is back again, but with big improvements! The Model CR-1 employs a sealed germanium diode, eliminating the critical "cat's whisker" adjustment. It is housed in a compact plastic box, and features two Hi-Q tank circuits, employing ferrite core coils and variable air tuning capacitors. The CR-1 covers the standard broadcast band from 540 kc to 1600 kc, and no external power is required for operation. Could prove valuable for emergency signal reception. This easy-to-build kit is a real "learn by doing" experience for the beginner, and makes an interesting project for all ages.

MODEL CR-1

\$8⁷⁵

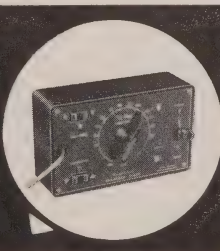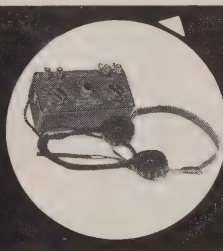INCLUDING NEW
EXCISE TAX*
Shpg. Wt. 3 Lbs.



HEATHKIT ENLARGER TIMER KIT

The Model ET-1 is an easy-to-build device for use by amateur or professional photographers in controlling the timing cycle of an enlarger. It covers the range of 0 to 1 minute with a continuously variable, clearly calibrated scale. The timing period is pre-set, and the timing cycle is initiated by depressing the spring-return switch to the "print" position. Front panel provision is made for plugging in the enlarger and a safelight. The safelight is automatically turned "on" when the enlarger is "off". Handles up to 350 watts. The timing cycle is controlled electronically for maximum accuracy and reliability. Very simple to build in only one evening, even by a beginner.

MODEL ET-1

\$11⁵⁰

Shpg. Wt. 3 Lbs.

COMPREHENSIVE INSTRUCTIONS . . .


The step-by-step assembly instructions provided with each Heathkit are the finest available anywhere. Each manual begins at the beginning, and assumes no previous training or experience on the part of the kit builder. This means that our kits can be built successfully by anyone who can follow instructions. As a matter of fact, new manuals are tested by having the kit built by someone in our office who has had no previous experience in electronics. This is your guarantee of complete and thorough instruction material.

HEATHKIT HIGH FIDELITY

Preamplifier Kit

- * 5 switch-selected inputs, each with its own level control.
- * Equalization for LP, RIAA, AES, and Early 78's.
- * Separate bass and treble tone controls, and special hum control.
- * Clean, modern lines and satin-gold enamel finish.

Literally thousands of these preamplifiers are in use today, because the kit meets or exceeds specifications for the most rigorous high-fidelity applications, and will do justice to the finest available program sources. Provides a total of 5 inputs, each with individual level controls (three high-level and two low-level). Frequency response is within 1 DB from 25 CPS to 30,000 CPS, or within 1½ DB from 15 CPS to 35,000 CPS. Hum and noise are extremely low, with special balance control for absolute minimum hum level. Tone control provides 18 DB boost and 12 DB cut at 50 CPS, and 15 DB boost and 20 DB cut at 15,000 CPS. Cabinet measures only 12-9/16" W. x 3¾" H. x 4⅞" D, and it is finished in beautiful satin-gold enamel. 4-position turnover and 4 position roll-off controls provide "LP," "RIAA," "AES," and "early 78" equalization, and 8, 12, 16, and 1 flat position for roll-off. Derives operating power from the main amplifier, requiring only 6.3 VAC at 1 ampere and 300 VDC at 10 MA. Easy to construct from step-by-step instructions and pictorial diagrams provided.

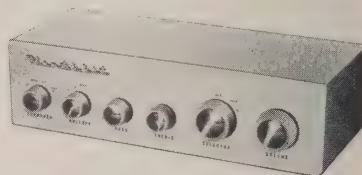

MODEL
WA-P2

(With Cabinet)
Shpg. Wt. 7 Lbs.

\$21.75 INCLUDING NEW
EXCISE TAX*


HEATHKIT HIGH FIDELITY FM TUNER KIT

- * Illuminated slide-rule dial covers 88 to 108 MC.
- * Modern circuit emphasizes sensitivity and stability.
- * Housed in attractive satin-gold cabinet to match WA-P2 and BC-1.

This amazing new FM tuner can provide you with real high-fidelity performance at an unbelievably low price level. Covering 88 to 108 MC, the modern circuit features a stabilized, temperature-compensated, oscillator, A.G.C., broadbanded

IF circuits, and better than 10 UV sensitivity for 20 DB of quieting. A high gain, cascaded, RF amplifier is used ahead of the mixer to increase overall gain and reduce oscillator leakage. It employs a ratio detector for high efficiency without sacrifice in high-fidelity performance. IF and ratio transformers are pre-aligned, as is the front end tuning unit. This means the kit can be constructed by a beginner, without elaborate test and alignment equipment. The FM-3A is designed to match the WA-P2 preamplifier and the BC-1 AM tuner. An illuminated slide-rule dial is employed for frequency indication. Step-by-step instructions and large pictorial diagrams assure success.

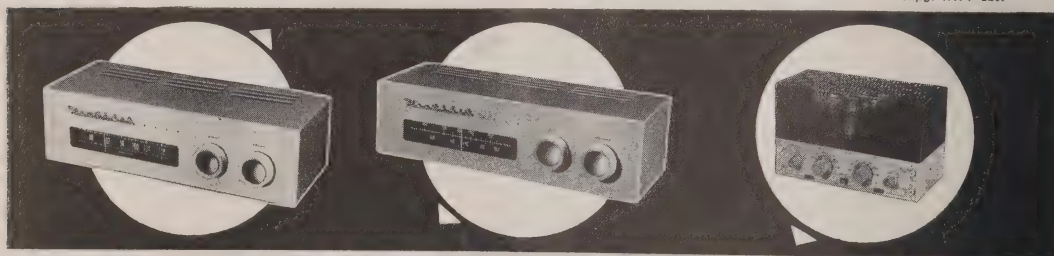MODEL FM-3A
\$26.95*
INCLUDING NEW
EXCISE TAX*
(With Cabinet)
Shpg. Wt. 7 Lbs.



HEATHKIT BROADBAND AM TUNER KIT

This AM tuner has been designed especially for high-fidelity applications. It incorporates a low-distortion detector, a broadband IF, and other features essential to usefulness in high-fidelity. Special voltage-doubler detector employs crystal diodes for low distortion. Sensitivity and selectivity are excellent. Audio response is ± 1 DB from 20 CPS to 2 kc, with 5 DB of pre-emphasis at 10 kc to compensate for station roll-off. Covers the standard broadcast band from 550 to 1600 kc. Incorporates a 10 kc whistle-filter and provides a 6 DB signal-to-noise ratio at 2.5 UV. RF and IF coils are pre-aligned, and power supply is built-in. Incorporates AVC, two outputs, and two antenna inputs.

MODEL BC-1
\$26.95
INCLUDING NEW
EXCISE TAX*
(With Cabinet)
Shpg. Wt. 8 Lbs.

HEATHKIT ELECTRONIC CROSS-OVER KIT

This unusual device functions to separate low frequencies and high frequencies so that they may be fed to separate amplifiers and to separate speakers. This eliminates the need for conventional cross-over circuits, since the Model XO-1 does the complete job electronically. Cross-over frequencies of 100, 200, 400, 700, 1,200, 2,000 and 35,000 CPS are selectable with front panel controls on the XO-1, and a separate level control is provided for each channel. Minimizes intermodulation distortion problems. Handles unlimited power, since frequency division is accomplished ahead of the power stage. Attenuation is 12 DB per octave, with sharp "knee" at cut-off frequency.

MODEL XO-1
\$18.95
Shpg. Wt. 6 Lbs.

HEATHKIT ADVANCED-DESIGN



MODEL W-5M
Shpg. Wt. 31 Lbs.
Express Only

\$59⁷⁵

MODEL W-5+

Consists of Model W-5M plus Model WA-P2 pre-amplifier.

Shpg. Wt. 38 Lbs.
Express only.....**\$81.50***

* Full 25 watt output with KT-66 output tubes.

* All connectors brought out to front chassis apron.

* Protective cover over all above-chassis components.

HEATHKIT DUAL-CHASSIS—WILLIAMSON TYPE HIGH FIDELITY AMPLIFIER KIT

This 20-watt high-fidelity amplifier employs the famous Acrosound Model TO-300 "ultra-linear" output transformer and uses 5881 output tubes. The power supply is built on a separate chassis, and the two chassis are inter-connected with a power cable. This provides additional flexibility in mounting. Frequency response is ± 1 DB from 6 CPS to 150 kc at 1 watt. Harmonic distortion is only 1% at 21 watts, and IM distortion is only 1.3% at 20 watts. (60 and 3,000 CPS). Output impedance is 4, 8, or 16 ohms. Hum and noise are 88 DB below 20 watts. A very popular high-fidelity unit employing top-quality components throughout.

MODEL W-3M: Shpg. Wt. 29 Lbs. Express only.....**\$49.75**

MODEL W-3: Consists of Model W-3M plus Model WA-P2 pre-amplifier. Shpg. Wt. 37 Lbs. Express only.....**\$71.50***

HEATHKIT 7-WATT AMPLIFIER KIT

This amplifier is more limited in power than other Heathkit models, but it still qualifies as a high-fidelity unit, and its performance definitely exceeds that of many so-called "high-fidelity" phonograph amplifiers. Using a tapped-screen output transformer of new design, the Model A-7D provides a frequency response of $\pm 1\frac{1}{2}$ DB from 20 to 20,000 CPS. Total distortion is held to a surprisingly low level. Output stage is push pull, and separate bass and treble tone controls are provided. Shpg. Wt. 10 Lbs.



MODEL A-7E: Similar to the A-7D, except that a 12SL7 tube has been added for pre-amplification. Two inputs, RIAA compensation, and extra gain.

MODEL A-7D

\$18⁶⁵

INCLUDING NEW EXCISE TAX*

\$20.35*

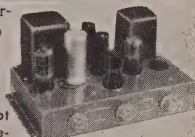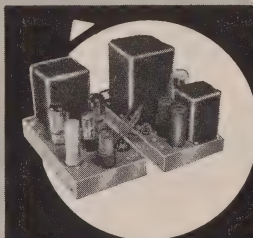

HIGH FIDELITY

Amplifier Kit

This 25 watt unit is our finest high-fidelity amplifier. Using a special design peerless output transformer, and KT-66 output tubes by Genalex, the Model W-5M provides performance characteristics unsurpassed at this price level. Frequency response is ± 1 DB from 5 to 160,000 CPS at 1 watt. Harmonic distortion is less than 1% at 25 watts and IM distortion is less than 1% at 20 watts (60 and 3,000 CPS, 4 to 1). Hum and noise are 99 DB below 25 watts. Damping factor is 40 to 1. Input voltage for 5 watts output is 1 volt. Tubes employed are a pair of 12AU7's, a pair of KT-66's and a 5R4GY rectifier. Measures 13-3/32" W. x 8 1/2" D. x 8 1/4" H. Output impedance is 4, 8, or 16 ohms. Featured, also, is the "tweeter saver" which suppresses high frequency oscillation, and a new type balancing circuit requiring only a voltmeter for indication. This balance is easier to adjust, and results in a closer "dynamic" balance between output tubes. The Model W-5M provides improved phase shift characteristics, reduced IM and harmonic distortion, and improved frequency response. Conservatively rated high-quality components are used throughout to insure years of trouble-free operation. No technical background or training is required for assembly. Step-by-step instructions are provided for every stage of construction, and large pictorial diagrams illustrate exactly where each wire and component is to be placed. An amplifier for music lovers who can appreciate subtle differences in performance. Just ask the audiophile who owns one!

HEATHKIT SINGLE CHASSIS—WILLIAMSON TYPE HIGH FIDELITY AMPLIFIER KIT

The 20-watt Model W-4AM Williamson type amplifier is a tremendous high-fidelity bargain. Combining the power supply and main amplifier on one chassis, and using a special-design output transformer by Chicago Standard brings you savings without a sacrifice in quality. Employing 5881 output tubes, the frequency response of the W-4AM is ± 1 DB from 10 CPS to 100 kc at 1 watt. Harmonic distortion is only 2.7% at this same level. Output impedance is 4, 8, or 16 ohms. Hum and noise are 95 DB below 20 watts.

MODEL W-4AM: Shpg. Wt. 28 Lbs. Express only.....**\$39.75**

MODEL W-4A: Consists of Model W-4AM plus Model WA-P2 pre-amplifier. Shpg. Wt. 35 Lbs. Express only.....**\$61.50***

HEATHKIT 20-WATT HIGH FIDELITY AMPLIFIER KIT

This high-fidelity amplifier features full 20-watt output using push pull 6L6 tubes. Built-in preamplifier provides 4 separate inputs, selected by a panel-mounted switch. It has separate bass and treble tone controls, each offering 15 DB boost and cut. Output transformer is tapped at 4, 8, 16, and 500 ohms. Designed primarily for home installations, but also used extensively for public address applications. True high-fidelity performance with frequency response of ± 1 DB from 20 CPS to 20,000 CPS. Total harmonic distortion only 1% (at 3 DB below rated output).

MODEL A-9B
\$35⁵⁰

Shpg. Wt. 23 Lbs.

HEATH COMPANY

A Subsidiary of Daystrom, Inc.

BENTON HARBOR 20, MICH.




All prices marked with a ‡ include a 10% federal excise tax that now applies to receivers, tuners and some amplifiers, even though they may be in kit form. Since the tax is in effect as of July 5, 1956, we have no choice but to reflect it in our kit prices. This note is just to let you know we are not increasing our prices on some kits, but merely including this new tax in them.

Thank you,
HEATH COMPANY

HEATHKIT HIGH FIDELITY

Range Extending SPEAKER SYSTEM KIT

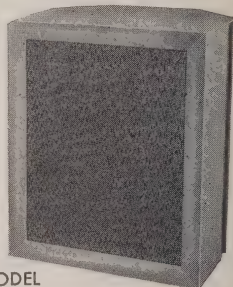- * High quality speakers of special design — 15" woofer and compression-type super-tweeter.
- * Easy-to-assemble cabinet of furniture-grade plywood.
- * Attractively styled to fit into any living room. Matches Model SS-1.




MODEL
SS-1B

\$99⁹⁵

Shpg. Wt. 80 Lbs.

This range extending unit is designed especially for use with the Model SS-1 speaker system. It consists of a 15" woofer, providing output between 35 and 600 CPS, and a compression-type super-tweeter that provides output between 4,000 and 16,000 CPS. Cross-over frequencies are 600, 1,600, and 4,000 CPS. The SS-1 provides the mid-range, and the SS-1B extends the coverage at both ends of the spectrum. Together, the two speaker systems provide output from 35 to 16,000 CPS within ± 5 DB. This easy-to-assemble speaker enclosure kit is made of top-quality furniture-grade plywood. All parts are pre-cut and pre-drilled, ready for assembly and the finish of your choice. Complete step-by-step instructions are provided for quick assembly by one not necessarily experienced in woodworking. Coils and capacitors for proper cross-over network are included, as is a balance control for super-tweeter output level. The SS-1 and SS-1B can provide you with unbelievably rich audio reproduction, and yet these units are priced reasonably. The SS-1B measures 29" H. x 23" W. x 17½" D. The speakers are both special-design Jensens, and the power rating is 35 watts. Impedance is 16 ohms.

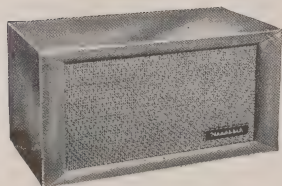HEATHKIT HIGH FIDELITY SPEAKER SYSTEM KIT



MODEL
SS-1

\$39⁹⁵

Shpg. Wt. 30 Lbs.

- * Special design ducted-port, bass-reflex enclosure.
- * Two separate speakers for high and low frequencies.
- * Kit includes all parts and complete instructions for assembly.

This speaker system is a fine reproducer in its own right, covering 50 to 12,000 CPS within ± 5 DB. However, the story does not end there. Should you desire to expand the system later, the SS-1 is designed to work with the SS-1B range extending unit — providing additional frequency coverage at both ends of the spectrum. It can fulfill your present needs, and still provide for the future. The SS-1 uses two Jensen speakers; an 8" midrange-woofer, and a compression-type tweeter. Cross-over frequency is 1,600 CPS, and the system is rated at 25 watts. Nominal impedance is 16 ohms. The cabinet is a ducted-port bass-reflex type. Attractively styled, the Model SS-1 features a broad "picture-frame" molding that will blend with any room decorating scheme. Pre-cut and pre-drilled wood parts are of furniture grade plywood. The kit is easy-to-build, and all component parts are included, along with complete step-by-step instructions for assembly. Can be built in just one evening, and will provide you with many years of listening enjoyment thereafter.

HEATH COMPANY

A Subsidiary of Daystrom, Inc. BENTON HARBOR 20, MICH.

ORDER BLANK

NOTE: All prices subject to change without notice.

Enclosed find () check () money order for
Please ship C.O.D. () postage enclosed for _____ pounds.

On Express orders do not include transportation charges — they will be collected by the express agency at time of delivery.

ON PARCEL POST ORDERS include postage for weight shown. ORDERS FROM CANADA and APO's must include full remittance.

Name _____

Address _____

City & Zone _____ State _____

(PLEASE PRINT)

SHIP VIA

- ☐ Parcel Post
- ☐ Express
- ☐ Freight
- ☐ Best Way

QUANTITY	ITEM	MODEL NO.	PRICE

BUILD THIS...

UNIVERSAL EXPERIMENTAL CHASSIS

By KURT FREUND

The breadboard brought up to date, featuring slide-in panels

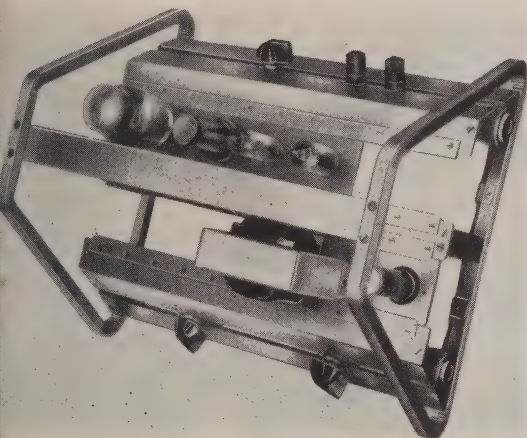


Fig. 1, above—Top view of the universal chassis—some components are mounted.

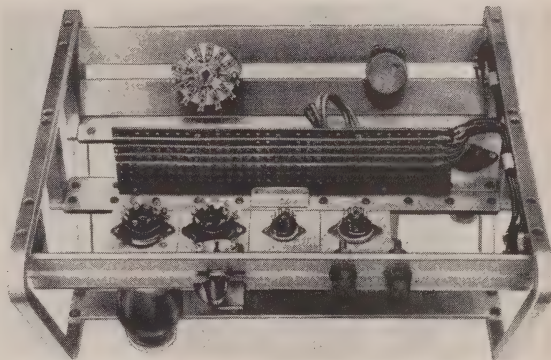


Fig. 2, right—Underside view shows some components and the power-line distribution.

AN important problem in constructing electronic equipment is to provide a suitable mounting base. This is especially true for experimental work where the number of components and their final arrangements can seldom be accurately predicted. Breadboards, although versatile, are unsuitable for present-day components. Despite frequent improvements they still introduce constructional complexities. In the universal experimental chassis described here, the advantages of earlier breadboards are retained while several other innovations are introduced for assembling temporary and semipermanent circuitry.

Basically, the new chassis (Figs. 1, 2) consists of two spring-loaded gaps into which can be inserted a number of square mounting panels. The end frames have been especially designed to permit tilting the chassis to either side at a convenient working angle. They also serve as carrying handles. Ample clearance from the bench surface protects mounted components. The square slide-in panels, which serve as mounts for tube sockets and other components, can be inserted in any one of four rotational positions for best base-pin arrangement. If necessary, rectangular panels could be used for larger parts.

For easier construction, individual

panels can be made to carry complete subassemblies by using socket turrets or by directly suspending components from the tube sockets. Such units can be inserted in their required sequence. When modification or dismantling is required later, they can be removed from the chassis simply by disconnecting the power supply and coupling leads. A small gap between adjacent plates will allow feeding through leads to grid caps. Controls, rotary switches and terminals can be mounted on the sides of the chassis and, like the slide-in panels, placed anywhere along its entire length.

The chassis was designed to be used with external power sources. Power is distributed by bus bars along the center. Each side has its own system separately terminated at one end, permitting construction of two independent circuits. For larger circuits requiring the use of both sides the distribution systems can be strapped and supplied through either of the terminating receptacles.

Construction

Consideration has been given to the availability of materials. The design and construction have been simplified to use only standard semihard aluminum stock and most of the material is used as purchased. There is a minimum of machine work. In fact, the complete chassis can be constructed without the

aid of power tools if it is necessary.

The parts and their dimensions are illustrated in Fig. 3. A number of identically dimensioned parts can be clamped together and faced simultaneously. The end brackets are cut from a $\frac{3}{8}$ -inch square bar. The slots (milled or cut by hacksaw) provide an easy method of making certain that the material bends at the required place with a minimum of bulging. The chassis cross rails are cut from a $1 \times \frac{1}{2}$ -inch bar and require only facing. Strips of flexible aluminum are used for the springs. Other materials such as tempered brass or phosphor bronze are equally suitable. All six pieces forming the end supports are cut from one 8-inch length of $1\frac{1}{2} \times \frac{3}{8}$ -inch bar.

The triangular supports A can be obtained by two diagonal cuts and the rectangular supports B by a cut along the center of a $2\frac{1}{2}$ -inch portion of the same material. Holes for the power-supply receptacles can be bored in two of the triangular pieces. The square slide-in plates are cut from a $1\frac{1}{4} \times \frac{1}{2}$ -inch strip and should be kept to fairly close tolerances to prevent binding when inserting them into the chassis. Examples of slide-in plates are shown in Figs. 3, 4. However, these can be made to suit individual requirements. The bus bars are lengths of 16-gauge tinned copper wire. A punched plastic card

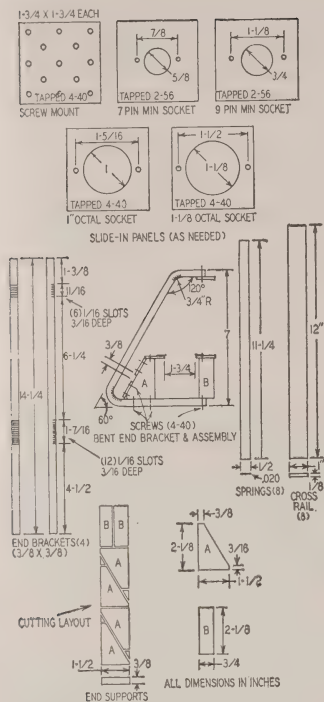


Fig. 3—Diagram shows the parts forming the chassis, and suggested dimensions.

(Alden 650 ATMS-D) forms the mounting base for four rows of conductors on each side. The conductors are insulated from each other and each side is separately terminated in a suitable receptacle. The card may be obtained from Alden Products, Brockton, Mass.

In general, all parts, except the springs, are fastened together by flat-headed 4-40 machine screws. Tapped holes, receiving the screws to a depth of at least $\frac{1}{4}$ inch, are used throughout. The springs can be either riveted or bolted by 2-56 screws. Bolting has the advantage of easier replacement of springs in case of damage.

While constructing a number of these chassis, some difficulty was sometimes encountered in aligning separately drilled holes. To avert this, the following practical, even if somewhat unconventional, method was devised:

Components which are to be bolted together are clamped in their required positions on a piece of angle iron or a mounting fixture, as shown in Figs. 5, 6. Tapping holes are then drilled through both parts. Inserting scrap pieces of $\frac{3}{8}$ -inch material as spacers results in uniform gaps in the chassis sides; slide-in panels may be used in gaps of the chassis top.

Assembly procedure

1. Mount springs to both faces of the cross rails forming the chassis top. Let

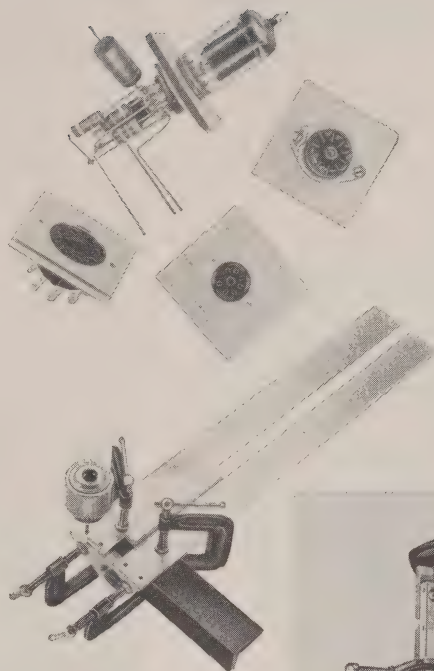


Fig. 5—Method of clamping parts to a portion of angle iron for drilling. A scrap piece of $\frac{3}{8}$ -inch material is shown being used as a spacer.

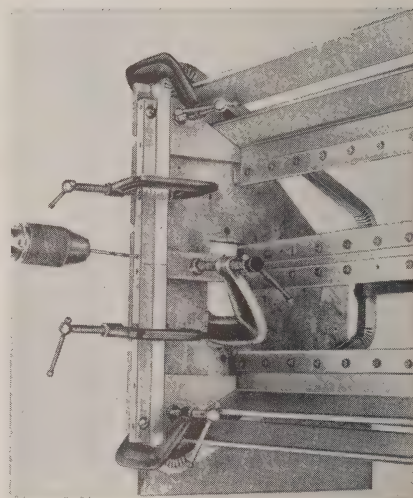


Fig. 6—Assembly of end frame and cross rails. A slide-in plate may be inserted in each gap, serving as a spacer.

Fig. 7—Modification of center rail permits unlocking either gap.

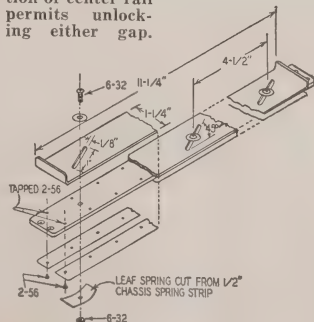


Fig. 8—A meter holder attachment.

RADIO

them protrude $\frac{3}{8}$ inch beyond each edge. The springs should extend to within $\frac{3}{8}$ inch of each end. On the center rail, mount springs to both edges.

2. Attach end supports to their corresponding cross rails, clamping and drilling at both ends as indicated in Fig. 5.

3. Mount chassis on the end brackets, inserting slide-in panels as spacers (Fig. 6).

4. Using the center portion of mounting fixture, attach cross rail to top of end brackets.

5. To complete the chassis, bolt the punched-card assembly to the center cross rail and solder connections to the terminating receptacle.

Modifications and accessories

So far, the construction has been kept to simple cutting and drilling. Where more extensive shop facilities are available the versatility of the chassis can be greatly increased. A disadvantage of the above construction is that centrally located plates cannot be removed without disturbing adjacent ones. This can be overcome by replacing the top springs of the center rail with a solid strip which can be moved sideways so that either chassis gap can be freed. This modification is shown in Fig. 7. A piece of 1/16 inch thick hard aluminum, 12 x 1 1/4 inches, replaces the top springs. Three angular slots are filed in this strip which is held against the center rail by spring-loaded screws. When the strip is in its central position, both chassis gaps are locked. Pushing or pulling one end tab moves the strip aside, opening either gap and permitting removal or insertion of any of the desired plates.

Meters are best mounted directly on the chassis. A suitable attachment which will accommodate up to a 3 1/2-inch meter is shown in Fig. 8 and affords full protection from all sides. It consists of two A type supports mounted on a slide-in plate. An 1/8-inch clearance is cut into the support. Two spring strips (1/2-inch chassis spring) and a spiral spring or strong elastic band hold the meter securely.

Materials for experimental chassis

4—end brackets, 4 feet 9 inches of $\frac{3}{8}$ x $\frac{1}{2}$ -inch bar; 8—cross rails, 8 feet of 1 x $\frac{1}{2}$ -inch bar; 8—springs, 7 feet 6 inches of $\frac{1}{2}$ x .02-inch strip; 4—end supports A, 2—end supports B, 8 inches of $\frac{1}{2}$ x $\frac{3}{8}$ -inch bar; slide-in panels, 1 1/4 x 1/8-inch bar.

Experience has indicated that the structure is sturdy and the all-metal construction has provided adequate shielding up to reasonably high frequencies. The chassis described is both practical and versatile and is proving to be an indispensable unit for the experimenter in the laboratory, lecture room and ham shack.

I wish to express my thanks to Drs. C. C. Lucas and W. G. B. Casselman of the Banting and Best Department of Medical Research, University of Toronto, for their helpful suggestions in preparing this paper.

END

NEW SAMS BOOKS



"SERVICING AND CALIBRATING TEST EQUIPMENT"

by Milton S. Kiver

This book shows you how to keep your test instruments in reliable working order. Tells you how to determine proper operation, how to avoid erroneous indications. Explains typical calibration procedures; gives method for performance record-keeping. Covers most frequently used equipment. Chapters: Pitfalls to Avoid When Using Test Equipment; Simple Ways to Check Instrument Accuracy; Keeping Instrument Operational Records; Preventative Maintenance Measures; How to Service Your Test Equipment. 145 pages; 5 1/2 x 8 1/2"; illustrated. Order today, postpaid only... **\$2.75**



"TV SERVICING GUIDE"

by Leslie D. Deane
and Calvin C. Young, Jr.

This new book shows how to apply proper trouble-shooting procedures based on analysis of symptoms. Most trouble symptoms are illustrated by picture-tube screen photos, and possible causes for each symptom are given. Chapters cover: General trouble-shooting and isolating procedures; troubles in every section of the TV receiver circuit. Each chapter shows how to locate and eliminate trouble in the section covered. 132 pages, 8 1/2 x 11"; illustrated. Order today, postpaid only... **\$2.00**

SAMS BOOKS keep you ahead in ELECTRONICS

USE HANDY ORDER FORM BELOW

Sams books cover every phase of Electronics for the service technician, engineer, student or experimenter. Listed below are a few of the many valuable Sams books available at electronic parts distributors and leading book stores.

USE THIS ORDER FORM

☐ SERVICING & CALIBRATING TEST EQUIPMENT... **\$2.75**

☐ **Color TV Training Manual.** Prepares the Technician for Color TV service work. Covers principles of the Color TV system; Color receiver circuits; installation and servicing sets. Includes color blocks outlining the use of color test equipment. 260 pages; 8 1/2 x 11"; 300 illustrations. **\$6.95**

☐ **TV Test Instruments.** Revised and enlarged to include latest data on instruments used in Color TV servicing. Tells clearly how to operate each type of test instrument used in TV service work. 180 pages; 8 1/2 x 11"; illustrated. **\$3.50**

☐ **Key Checkpoints in TV Receivers.** Prepared by the Howard W. Sams engineering staff. Provides many applications for general TV service work, including time-saving information on how to make quick tests at key points to determine where trouble lies, and how to check overall performance of the receiver after repair, to insure against callbacks. 182 pages; 5 1/2 x 8 1/2"; illustrated. **\$2.00**

☐ **Analyzing and Tracing TV Circuits.** Presents a new approach to TV servicing. 168 pages, 8 1/2 x 11". **\$3.00**

☐ **Photofact Television Course.** Gives a clear complete understanding of TV principles, operation, practice. Used by thousands of students. 208 pages, 8 1/2 x 11". **\$3.00**

☐ **Radio Receiver Servicing.** Covers the basic receiver types—gives time-saving hints for solving basic troubles, such as dead set, weak set, noisy set, etc. 192 pages; 5 1/2 x 8 1/2". **\$2.50**

☐ **Technical Dictionary.** Over 4,000 definitions of radio, television, electronic, electrical and radar terms. Includes valuable charts, graphs, diagrams and symbols. Flexible binding for "on-the-job" use. 160 pages; 5 1/2 x 8 1/2". **\$2.00**

☐ TV SERVICING GUIDE..... **\$2.00**

☐ **Tape Recorders—How They Work.** Explains recording theory, tape characteristics, motorboard mechanisms, drive motors, amplifiers, magnetic heads, volume indicators, equalization circuits—covers everything you want to know about recorders. 176 pages; 5 1/2 x 8 1/2". **\$2.75**

☐ **Servicing AGC Systems.** Describes the operation and circuit variations of the various types of AGC systems and explains the servicing techniques that can be applied. Illustrated by actual case histories and photographs of symptoms. 132 pages; 5 1/2 x 8 1/2"; illustrated. **\$1.75**

☐ **Transistors—Their Application in Television-Radio-Electronics.** The first practical, complete book on transistors; explains circuitry, installation, testing techniques, theory and servicing. 100 pages; 5 1/2 x 8 1/2" illustrated. **\$1.50**

☐ **So You Want to Be a Ham.** Tells you what you need to know about getting your license and acquiring equipment. Covers such subjects as: Conquering the Code; Getting Your Ticket; Going on the Air; Electronics as a Career; etc. 196 pages; 5 1/2 x 8 1/2"; illustrated. **\$2.50**

☐ **Servicing TV Sweep Systems.** Describes the operation, circuit function and circuit variations of vertical and horizontal sweep systems common to most TV receivers. Tells how to analyze circuits; trouble-shoots for you. 212 pages; 5 1/2 x 8 1/2"; illustrated. **\$2.75**

There is an authoritative Sams book on virtually any Electronic subject in which you're interested. Check below for FREE Book List describing all Sams books.

☐ Send Book List



Look for
SAMS BOOKS
on the
"Book Tree"
at your Parts
Distributor

HOWARD W. SAMS & CO., INC.

Order from your Parts Jobber today, or mail to Howard W. Sams & Co., Inc., Dept. 2-J6, 2201 East 46th St., Indianapolis 5, Indiana.

Send books checked above. My (check) (money order) for \$..... is enclosed.

Name.....

Address.....

City..... Zone..... State.....

(outside U.S.A. priced slightly higher)

10 TIPS

servicing

for transistor radios

*Once upon a time I had
a good transistor that went bad.*

*Just a little carelessness
Gave me one transistor less.*

By STAN SCHENKERMANN

THE radio-TV service technician must again cope with the advance of technology! Transistor radios are coming into his shop in increasing numbers. No doubt he will rise above this challenge with his usual proficiency.

But servicing transistor radios requires some modification of the techniques used for tube radios. To aid technicians entering this new field, the following 10 hints will serve as a guide:

1. Whether a tube or transistor set, A superhet is a superhet.

The block diagram of a transistor radio is the same as for a conventional tube receiver. Fig. 1 shows the schematic of a transistor radio put out by Raytheon. Fig. 2 is a block diagram of the set. Note that it is almost the same as for conventional tube jobs.

2. In checking transistors you should Replace with ones known to be good.

Substitution is the only reliable check. A transistor may seem good on

a transistor checker and still cause poor operation.

3. Your substitute should be the kind That in the radio you find.

Transistors by different manufacturers may be similar, but they are probably not similar enough, at present, for direct interchange.

4. A rose is a rose by any name, But tubes and transistors are not the same.

Even with the power switch off, the impedances of the transistor are not infinite as are the tube's. Always remove all transistors when making ohmmeter measurements. If the transistors are in, the ohmmeter current may damage them. Of course, you will

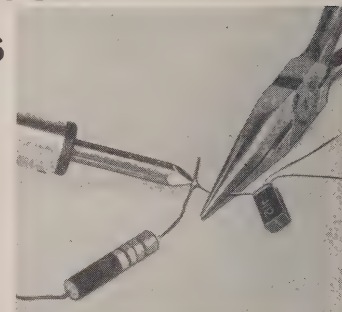


Fig. 3—Using pliers as a heat sink.

also obtain incorrect readings.

5. Transistors with heat cannot co-exist Protect them from it or they won't transist!

Transistors are very temperature-sensitive and can be permanently damaged by the heat from a soldering iron. Use a pencil type iron of not more than

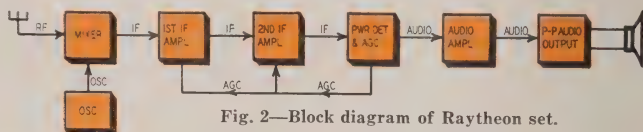


Fig. 2—Block diagram of Raytheon set.

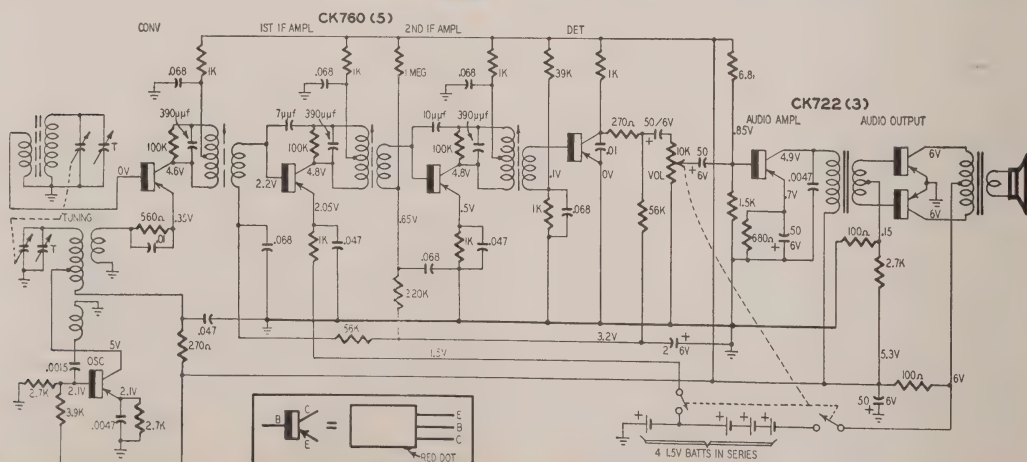


Fig. 1—Schematic diagram of the Raytheon chassis 8RT1 transistorized portable radio—unit uses eight transistors.

Courtesy Raytheon Mfg. Co.

RADIO

35-40 watts and small-diameter multiple-core 60/40 solder. Remove the transistor when soldering at or near its socket, or use a pair of long-nose pliers as a heat sink. This is done by grasping the transistor electrode to which you are soldering, with the pliers between the soldering point and the transistor body. (See Fig. 3.)

6. Many transistors have laid down and died

Simply because of wrong bias applied.

Be sure that transistors are inserted in their sockets so that the proper polarity bias is applied. There are a

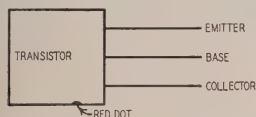


Fig. 4—Identifying transistor leads using a red dot near the collector.

number of schemes are used to specify which electrodes are the emitter, base and collector. Fig. 4 shows one method where a red dot is placed near the collector. Fig. 5 shows a pin-spacing method.

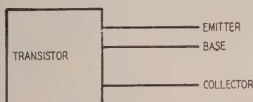


Fig. 5—The pin-spacing method of identifying transistor electrodes.

7. With a new transistor you may find That the whole set must be realigned.

This is due to the nonuniform transistors produced at the present stage of the art. Even rearranging the original order of the transistors may throw the set out of alignment.

8. When aligning you should know Enough to keep your signal low.

Transistors, because they work at such low levels, can be easily overloaded by what may be a small signal for a tube. Furthermore, the entire alignment procedure should be repeated two or three times for best results. The input and output circuits of the transistor are not isolated from each other, as they are in tube sets. Tuning one transistor stage affects the tuning of the others and repetition is the only way of insuring perfect alignment.

9. Transient currents shouldn't be passed

Through transistors you want to last.

Have the power switch off when removing or installing batteries or transistors. That way you will never subject the transistors to those damaging transients.


10. To your customers suggest

That mercury oxide cells are best.

Replacement batteries of the mercury oxide type will give about five times the playing life of conventional flashlight batteries. Although initial cost is higher, the long-term cost per playing hour is much less. **END**

Sarkes Tarzian

"Time Proved" HIGH DENSITY Rectifiers

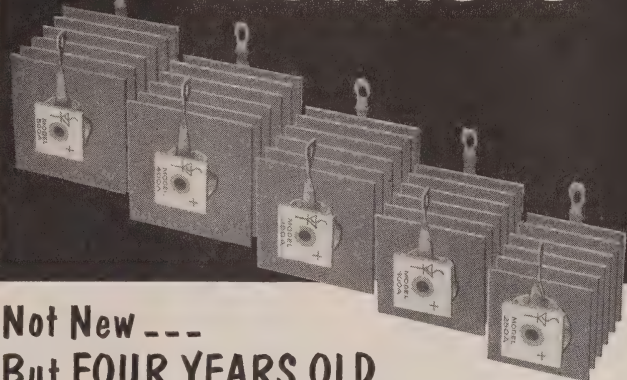

Not New --- But FOUR YEARS OLD

Better for you and better for your customers because hundreds of thousands have been field tested and proven during the past four years. Don't be fooled by offers of extremely small plate sizes and narrow spacings. We have found during four years of laboratory and field testing that there is a practical minimum cell size and spacing that are needed for maximum performance and minimum service call backs.

The Tarzian High Density Rectifiers are Time Proved—don't be fooled by unrealistic ratings and sizes.

SPECIFICATIONS

Model No.	Max. A.C. Input Volts	Max. D.C. Load Current	Plate Size	Overall Length	Replaces Model
250A	130	250	1.25" sq.	1 7/8"	200-250
300A	130	300	1.4 " sq.	1 7/8"	300
350A	130	350	1.6 " sq.	2 5/32"	350
400AD	130	400	1.8 " sq.	1 1/4"	400
500AD	130	500	1.8 " sq.	1 5/16"	500

All Sarkes Tarzian Replacement Rectifiers are truly universal and will plug-in on original set replacements on Motorola, Westinghouse, Arvin and Sylvania sets.

Send for your copy of the latest Replacement Guide. Address Dept. R-3

Sarkes Tarzian, Inc., Rectifier Division
415 N. COLLEGE AVENUE, BLOOMINGTON, INDIANA

In Canada: 700 Weston Rd., Toronto 9, Tel. Murray 7535 • Export: Ad Auriema, Inc., New York City


Superior's New Model 770-A

The **FIRST**

Pocket-Sized

VOLT-OHM MILLIAMMETER

USING THE NEW "FULL-VIEW" METER

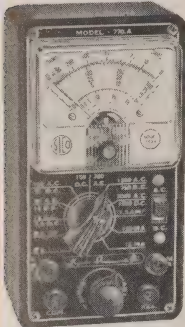

Specifications

6 A.C. VOLTAGE RANGES: 0-15/30/150/300/1500/3000 Volts. 6 D.C. VOLTAGE RANGES: 0-7.5/15/75/150/750/1500 Volts. 2 RESISTANCE RANGES: 0-10,000 Ohms, 0-1 Megohm. 3 D.C. CURRENT RANGES: 0-15/150 Ma., 0-1.5 Amps. 3 DECIBEL RANGES: -6 db to +18 db, +14 db to +38 db, +34 db to +58 db.

The Model 770-A comes complete with self-contained batteries, test leads and all operating instructions.

71% MORE SCALE AREA!


Yes, although our new FULL-VIEW D'Arsonval type meter occupies exactly the same space used by the older standard 2 1/2" Meters, it provides 71% more scale area. As a result, all calibrations are printed in large easy-to-read type and for the first time it is now possible to obtain measurements instead of approximations on a popular priced pocket-sized V.O.M.

- Compact — measures 3 1/2" x 5 7/8" x 2 1/4".
 - Uses "Full View" 2% accurate, 850 Microampere D'Arsonval type meter.
 - Housed in round-cornered, molded case.
 - Beautiful black etched panel.
- Depressed letters filled with permanent white, insures long-life even with constant use.

\$15⁸⁵
NET

Superior's New Model 670-A

SUPER-METER

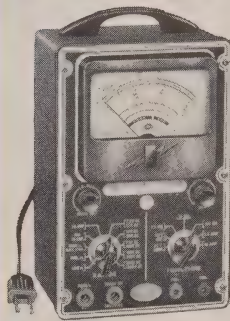

A COMBINATION VOLT-OHM MILLIAMMETER PLUS CAPACITY REACTANCE INDUCTANCE AND DECIBEL MEASUREMENTS.

D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Volts. A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts. OUTPUT VOLTS: 0 to 15/30/150/300/

1,500/3,000 V. D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes. RESISTANCE: 0 to 1,000/100,000 Ohms 0 to 10 Megohms. CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd. (Good-Bad Scale for checking quality of electrolytic condensers). REACTANCE: 50 to 2,500 Ohms, 2,500 Ohms to 2.5 Megohms. INDUCTANCE: .15 to 7 Henries 7 to 7,000 Henries. DECIBELS: -6 to +18, +14 to +38, +34 to +58.


ADDED FEATURE:

Built-in ISOLATION TRANSFORMER reduces possibility of burning out meter through misuse.

The Model 670-A comes housed in a rugged crackle-finished steel cabinet complete with test leads and operating instructions.

\$28⁴⁰
NET

Superior's New Model TV-60

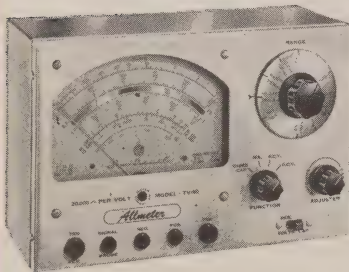

FEATURES

- ✓ A sensitive, accurate Volt-Ohm-Milliammeter with giant meter and mirrored scale.
- ✓ An accurate direct-reading Capacity meter.
- ✓ A Kilovoltmeter.
- ✓ An R.F. Signal Tracer.
- ✓ An Audio Signal Tracer.
- ✓ Giant recessed 6 1/2 inch 40 Microampere meter with mirrored scale assures accuracy and easy-reading. All calibrations are printed in large easy-to-read type. Fractional divisions are easily read with the aid of the mirrored scale.

20,000 OHMS PER VOLT

A L M E T E R

Includes services never before provided by an instrument of this type.

- ✓ The line cord, used only when making Capacity measurements, need be plugged in only when using that service. It is out of the way, stored in its pliofilm compartment at all other times.
- ✓ A built-in Isolation Transformer automatically isolates the Model TV-60 from the power line when the capacity service is in use.
- ✓ Selected, 1% zero temperature coefficient metallized resistors are used as multipliers assuring unchanging accurate readings on all ranges.
- ✓ Use of the latest type of printed circuit guarantees maintenance of top quality standard in the production runs of this precise instrument.
- ✓ A new Improved type of high-voltage probe is used for the measurement of high voltages up to 30,000 Volts. This service will be required when servicing color TV receivers.
- ✓ Simply plug-in the R.F. probe and convert the Model TV-60 into an efficient R.F. SIGNAL TRACER permitting the measurement of stage-gain and cause of trouble in the R.F. and I.F. circuits of A.M., F.M., and TV receivers.
- ✓ Plug in the Audio probe and convert the Model TV-60 into an efficient AUDIO SIGNAL TRACER. Measure the signal levels and comparative efficiency of hearing-aids, public-address systems, the amplifier sections of Radio & TV receivers, etc.

Read and compare features and specifications below!

SPECIFICATIONS

- 8 D.C. VOLTAGE RANGES: (At a sensitivity of 20,000 Ohms per Volt) 0 to 15/75/150/300/750/1500/7500/30,000 Volts.
- 7 A.C. VOLTAGE RANGES: (At a sensitivity of 5,000 Ohms per Volt) 0 to 15/75/150/300/750/1500/7500 Volts.
- 3 RESISTANCE RANGES: 0 to 2,000/200,000 Ohms, 0-20 Megohms.
- 2 CAPACITY RANGES: .00025 Mfd. to 30 Mfd.
- 5 D.C. CURRENT RANGES: ± 0-75 Microamperes, 0 to 7.5/75/750 Milliampers, 0 to 15 Amperes.
- 3 DECIBEL RANGES: -6 db to +18 db, +14 db to +38 db, +34 db to +58 db.
- R. F. SIGNAL TRACER SERVICE:
Enables following the R.F. signal from the antenna to speaker of any radio or TV receiver and using that signal as a basis of measurement to first isolate the faulty stage and finally the component or circuit condition causing the trouble.
- AUDIO SIGNAL TRACER SERVICE:
Functions in the same manner as the R.F. Signal Tracing service specified above except that it is used for the location of cause of trouble in all audio and amplifier systems.

Model TV-60 comes complete with book of instructions; pair of standard test leads; high-voltage probe; detachable line cord; R.F. Signal Tracer Probe and Audio Signal Tracer Probe. Pliofilm bag for all above accessories is also included. Price complete. Nothing else to buy. Only


\$52⁵⁰
NET

SHIPPED ON APPROVAL
NO MONEY WITH ORDER — NO C. O. D.

Try for 10 days before you buy! If completely satisfied, send down payment after trial and pay balance at indicated monthly rate — **NO INTEREST OR**

FINANCE CHARGES ADDED. If not completely satisfied, return to us, no explanation necessary. (See approval form for complete details.)

**Superior's New
Model TC-55**

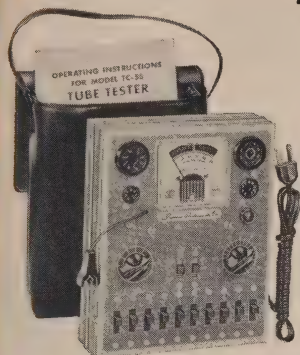

TUBE TESTER

FOR

The Experimenter or Part-time Serviceman, who has delayed purchasing a higher priced Tube Tester. The busy TV Service Organization, which needs extra Tube Testers for its field men.

Speedy, yet efficient operation is accomplished by:

1. Simplification of all switching and controls.
2. Elimination of old style sockets used for testing obsolete tubes (26, 27, 57, 59, etc.) and providing sockets and circuits for efficiently testing the new Noval and Sub-Minar types.

You can't insert a tube in wrong socket

It is impossible to insert the tube in the wrong socket when using the new Model TC-55. Separate sockets are used, one for each type of tube base. If the tube fits in the socket it can be tested.

"Free-point" element switching system

The Model TC-55 incorporates a newly designed element selector switch system which reduces the possibility of obsolescence to an absolute minimum. Any pin may be used as a filament pin and the voltage applied between that pin and any other pin, or even the "top-cap".

Checks for shorts and leakages between all elements

The Model TC-55 provides a super sensitive method of

checking for shorts and leakages up to 5 Megohms between any and all of the terminals. Continuity between various sections is individually indicated. This is important, especially in the case of an element terminating at more than one pin. In such cases the element or internal connection often completes a circuit.

Elemental switches are numbered in strict accordance with R.M.A. specification.

One of the most important improvements, we believe, is the fact that the 4 position fast-action snap switches are all numbered in exact accordance with the standard R.M.A. numbering system. Thus, if the element terminating in pin No. 7 of a tube is under test, button No. 7 is used for that test.

The Model TC-55 comes complete with operating instructions and charts. Housed in rugged steel cabinet. Use it on the bench — use it for field calls. A streamlined carrying case, included at no extra charge, accommodates the tester and book of instructions.

**\$26⁹⁵
NET**

**Superior's New
Model TV-11**



TUBE TESTER

SPECIFICATIONS:

- ★ Tests all tubes including 4, 5, 6, 7, Octal, Lock-in, Peanut, Bantam, Hearing Aid, Thyratron Miniatures, Sub-miniatures, Novals, Sub-minars, Proximity fuse types, etc.
- ★ Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TV-11 as any of the pins may be placed in the neutral position when necessary.
- ★ The Model TV-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible

to damage a tube by inserting it in the wrong socket.

- ★ Free-moving built-in roll chart provides complete data for all tubes.
- ★ Newly designed Line Voltage Control compensates for variation of any Line Voltage between 105 Volts and 130 Volts.
- ★ **NOISE TEST:** Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

The model TV-11 operates on 105-130 Volt 60 Cycles A.C. Comes housed in a beautiful hand-rubbed oak cabinet complete with portable cover

EXTRA SERVICE — can be used as a denser Leakage

Checker. A relaxation

type oscillator incorporated in this model will detect leakages even when the frequency is one per minute.

**\$47⁵⁰
NET**

**Superior's New
Model TV-12**



TRANS-CONDUCTANCE TUBE TESTER

TESTING TUBES

- ★ Employs improved TRANS-CONDUCTANCE circuit. An in-phase signal is impressed on the input section of a tube and the resultant plate current change is measured. This provides the most suitable method of simulating the manner in which tubes actually operate in Radio & TV receivers, amplifiers and other circuits. Amplification factor, plate resistance and cathode emission are all correlated in one meter reading.

- ★ **NEW LINE VOLTAGE ADJUSTING SYSTEM.** A tapped transformer makes it possible to compensate for line voltage variations to a tolerance of better than 2%.

- ★ **SAFETY BUTTON** — protects both the tube under test and the instrument meter against damage due to overload or other form of improper switching.

- ★ **NEWLY DESIGNED FIVE POSITION LEVER SWITCH ASSEMBLY.** Permits application of separate voltages as required for both plate and grid of tube under test, resulting in improved Trans-Conductance circuit.

TESTING TRANSISTORS

A transistor can be safely and adequately tested only under dynamic conditions. The Model TV-12 will test all transistors in that approved manner, and quality is read directly on a special "transistor only" meter scale.

The Model TV-12 will accommodate all transistors including NPN's, PNP's, Photo and Tetrodes, whether made of Germanium or Silicon, either point contact or junction contact types.

Model TV-12 housed in handsome rugged portable cabinet sells for only

**\$72⁵⁰
NET**

ALSO TESTS TRANSISTORS!

**SHIPPED ON APPROVAL
NO MONEY WITH ORDER — NO C.O.D.**

Try for 10 days before you buy! If completely satisfied, send down payment after trial and pay balance at indicated monthly rate — **NO INTEREST OR**

FINANCE CHARGES ADDED. If not completely satisfied, return to us, no explanation necessary. (See approval form for complete details.)

About Testing Picture-Tubes . . .

Of course you can buy an "adapter" which theoretically will convert your standard Tube Tester into a picture-tube tester. Sounds fine - but - it simply doesn't work out that way!

We do not make nor do we recommend use of C.R.T. adapters because a Cathode Ray Tube is a very complex device. and to properly test it, you need an instrument designed exclusively to test C. R. Tubes and nothing else. As compared to a make-shift adapter, which sells for

Superior's New Model TV-40



PICTURE TUBE TESTER

A complete picture tube tester for little more than the price of a "make-shift" adapter!!

The Model TV-40 is absolutely complete! Self-contained, including built-in power supply, it efficiently tests picture tubes in the only practical way to a separate instrument which is designed exclusively to test the ever increasing number of

EASY TO USE:

Simply insert line cord into any 110 volt A.C. outlet, then attach tester socket to tube base (on trap need not be on tube). Throw switch up for quality test... read direct on Good-Bad scale. Throw switch down for all leakage tests.

Tests all magnetically deflected tubes... in the set... out of the set... in the carton!!


SPECIFICATIONS:

- Tests all magnetically deflected picture tubes from 7 inch to 30 inch types.
- Tests for quality by the well established emission method. All readings on "Good-Bad" scale.
- Tests for inter-element shorts and leakages up to 5 megohms.
- Test for open elements.

Model TV-40 C.R.T. Tube Tester comes absolutely complete—nothing else to buy. Housed in round cornered, molded bakelite case. Only

\$15⁸⁵
NET

Superior's New Model TV-50

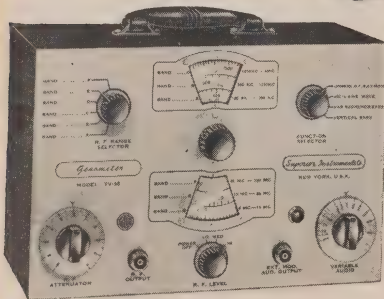

GENOMETER

A versatile all-inclusive GENERATOR which provides ALL the outputs for servicing:

A.M. Radio • F.M. Radio • Amplifiers • Black and White TV • Color TV

7 Signal Generators in One!

- ✓ R.F. Signal Generator for A.M.
- ✓ R.F. Signal Generator for F.M.
- ✓ Audio Frequency Generator
- ✓ Bar Generator
- ✓ Cross Hatch Generator
- ✓ Color Dot Pattern Generator
- ✓ Marker Generator

R. F. SIGNAL GENERATOR: The Model TV-50 Genometer provides complete coverage for A.M. and F.M. alignment. Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.

VARIABLE AUDIO FREQUENCY GENERATOR: In addition to a fixed 400 cycle sine-wave audio, the Model TV-50 Genometer provides a variable 300 cycle to 20,000 cycle peaked wave audio signal.

BAR GENERATOR: The Model TV-50 projects an actual Bar Pattern on any TV Receiver Screen. Pattern will consist of 4 to 16 horizontal bars or 7 to 20 vertical bars.

CROSS HATCH GENERATOR: The Model TV-50 Genometer will project a cross-hatch pattern on any TV picture tube. The pattern will consist of non-shifting horizontal and vertical lines interlaced to provide a stable cross-hatch effect.

DOT PATTERN GENERATOR (FOR COLOR TV): Although you will be able to use most of your regular standard equipment for servicing Color TV, the one addition which is a "must" is a Dot Pattern Generator. The Dot Pattern projected on any color TV Receiver tube by the Model TV-50 will enable you to adjust for proper color convergence.

MARKER GENERATOR: The Model TV-50 includes all the most frequently needed marker points. The following markers are provided: 189 Kc., 202.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc. (3579 Kc. is the color burst frequency.)

THE MODEL TV-50 comes absolutely complete with shielded leads and operating instructions.

Only

\$47⁵⁰
NET

SHIPPED ON APPROVAL
NO MONEY WITH ORDER — NO C. O. D.

Try for 10 days before you buy! If completely satisfied, send down payment after trial and pay balance at indicated monthly rate — NO INTEREST OR

FINANCE CHARGES ADDED. If not completely satisfied, return to us, no explanation necessary. (See approval form for complete details.)

Superior's New Model TV-80

5" OSCILLOSCOPE



The Model TV-80 is a *practical* Radio & TV Oscilloscope. It does not include those requirements which are provided in Scopes intended primarily for laboratory and research work. It does include all the services required for Radio TV Servicing.

When you read the specifications which follow, you will find not a single Radio & TV service requirement has been omitted. Yet, by eliminating "laboratory" features rarely if ever needed by the average Radio-TV Serviceman, SUPERIOR is able to offer a comparatively low-priced scope which provides maximum usage.

SPECIFICATIONS

- ✓ Push-pull vertical and horizontal amplifiers.
- ✓ Cathode follower vertical input circuit.
- ✓ High vertical amplifier sensitivity. .02 volts (20 MV.) per inch.
- ✓ Vertical frequency response flat within 2 db from 20 cycles to 500 Kc.
- ✓ Vertical square wave response from 20 cycles to 50 Kc.
- ✓ High horizontal amplifier sensitivity. .05 volts (50 MV.) per inch.
- ✓ Horizontal frequency response flat within 3 db from 20 cycles to 200 Kc.
- ✓ Wide range horizontal phasing control.

- ✓ Internal linear sweep from 10 CPS to 30 Kc.
- ✓ Positive and negative sweep synchronization.
- ✓ Direct reading peak to peak voltage calibrator.
- ✓ Built-in 60 cycle sine wave sweep phasing control.
- ✓ External beam modulation connections.
- ✓ Direct deflection plate connections easily accessible.
- ✓ Non-glare removable calibrated graph screen.

Model TV-80 comes housed in rugged steel cabinet. Complete with book of instructions.....only

\$127⁵⁰
NET

READ THIS!!

READ THIS!!

READ THIS!!

You don't pay for the Tester you select until AFTER you have examined it in the privacy of your home! All models

SHIPPED ON APPROVAL NO MONEY WITH ORDER — NO C.O.D.

Yes, when you send in the coupon (below) you are merely giving us permission to submit the item(s) you select for your approval. If, after trying it you decide to keep it, then and only then do you send us the down payment and pay the balance at the monthly indicated

rate with not one penny added for interest or finance charges! If not completely satisfied (we can't please everyone) you simply return the unit to us; no explanation necessary.

MOSS ELECTRONIC DISTRIBUTING CO., INC.
Dept. D-273, 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked. I agree to pay down payment within 10 days and to pay the monthly balance as shown. It is understood there will be no finance or interest charges added. It is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and payable.

Name.....

Address.....

City.....Zone.....State.....

☐ Model 670-A... Total Price \$28.40
\$7.40 within 10 days. Balance \$3.50
monthly for 6 months.

☐ Model TV-11... Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00
monthly for 6 months.

☐ Model TV-40... Total Price \$15.85
\$3.85 within 10 days. Balance \$4.00
monthly for 3 months.

☐ Model TV-50... Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00
monthly for 6 months.

☐ Model TC-55... Total Price \$26.95
\$6.95 within 10 days. Balance \$5.00
monthly for 4 months.

☐ Model TV-12... Total Price \$72.50
\$22.50 within 10 days. Balance \$10.00
monthly for 5 months.

☐ Model 770-A... Total Price \$15.85
\$3.85 within 10 days. Balance \$4.00
monthly for 3 months.

☐ Model TV-60... Total Price \$52.50
\$12.50 within 10 days. Balance \$8.00
monthly for 5 months.

☐ Model TV-80—Total Price \$127.50
\$27.50 within 10 days. Balance \$20
monthly for 5 months.

All Prices net, F.O.B., N.Y.C.



PROGRESS MAKES WASTE

It takes courage to discard plans and models . . . especially when they involved time and effort. Yet, we at University, do just that!

In our almost fanatic dedication to achieving perfection, we carry the development of new products to the highest degree possible. In this exacting process, things which do not meet our rigid requirements find their way into the waste basket. Actually *this* kind of waste makes *real* progress.

Too often items are rushed onto the market before they are ready. We introduce products only when they've conformed to traditionally high University standards (customers have always found them worth waiting for).

This philosophy of business has made us countless friends who look to *University* for the latest developments in loudspeakers. Today—University is the leading specialized speaker manufacturer. There are more satisfied users of University speakers than of all other speakers combined. *The University label on a speaker guarantees trouble-free operation and performance that conforms to specs.*

That's why University "sells on sound." Our engineering department will gladly consult with you on any technical requirement.

UNIVERSITY LOUDSPEAKERS, Inc., 80 So. Kensico Ave., White Plains, N. Y.

LISTEN

University sounds better



RADIO SYMMETRICAL VOLTAGE DOUBLER

Analyzing current flow in popular type power supply

By GEORGE P. PEARCE

JUST why is it possible to connect a couple of rectifiers and a couple of capacitors in an alternating current circuit and finish up with over twice the voltage, and direct current at that?

Suppose we have an electronic check valve that will permit current to flow in only one direction and a couple of capacitors. Let us mark the electronic check valve V, the capacitors C1 and C2 and then wire the assembly as shown in Fig. 1. V is connected as a switch between terminals L and P and set so current (electrons) can flow only from


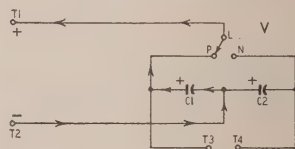


Fig. 1—Diagram shows current flow during first half of input cycle.

P to L. Apply 100 volts (peak) a.c. across terminals T1 and T2. Current will flow as shown, and C1 will charge to 100 volts positive with respect to T2. T3 will also be 100 volts positive since it is connected to the positive side of the capacitor C1.

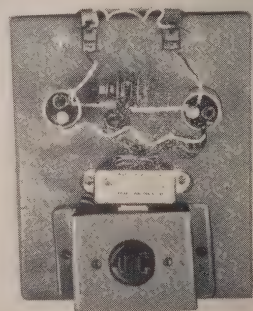After the input voltage passes the 100-volt peak and starts to decrease,



Experimental voltage divider.

RADIO

the capacitor will be prevented from discharging backward because V will not permit current to flow in the reverse direction. Thus, when the line voltage has fallen to zero, there will still be 100 volts across C1.

Suppose that when the voltage reaches zero we instantaneously change the direction of flow through check-valve V, connect from N to L and open-circuit L to P. The line voltage passes zero (current flows in the opposite direction) and continues to fall until it reaches a negative value of 100. This will make the voltage on C2 rise to 100 volts negative with respect to T2. And since T4 is directly connected to this capacitor, the terminal will also be 100 volts negative (Fig. 2). Thus the po-

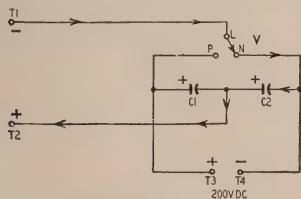


Fig. 2—Direction of current flow during second half of input cycle.

tential drop between terminals T3 and T4 will be from 100 volts positive to 100 negative (with respect to our reference point T2) a 200-volt difference. The line voltage T1 and T2 is 100 volts ac; the voltage between T3 and T4 is 200 dc.

A rectifier such as a selenium type is the same to an electric current as a check valve is to the flow of water. So if we install two rectifiers, each the reverse of the other, we shall then have an arrangement that will accomplish electrically the equivalent switching arrangement as indicated in Figs. 1 and 2. And if the ac line is connected to terminals T1 and T2, C1 and C2 will be continually recharged 60 times per second—on 60-cycle power. If a load is connected between T3 and T4 to permit a current to flow which is in reasonable proportion to the storage capacity of


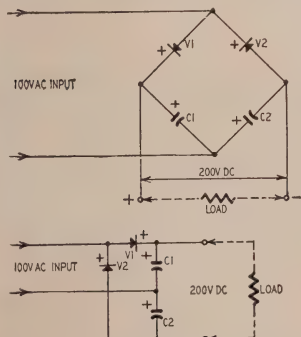


Fig. 3—Above is the symmetrical voltage doubler in the theoretical bridge form; below in the more familiar practical schematic style.

SHOW ANY PICTURE or PATTERN


at any time—ON ANY TV SET

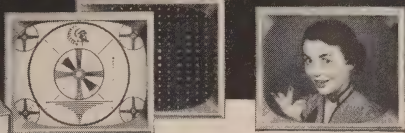

- For Servicing Black & White and Color TV
- For Merchandising and Advertising Promotions
- For Paging, Educational and Industrial Use

New
MODEL 1000

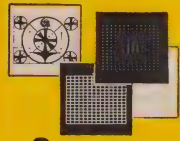B&K DYNA-SCAN PICTURE AND PATTERN VIDEO-GENERATOR



3 SLIDE
TRANSPARENCIES
ARE SUPPLIED

1. Indian Head Pattern
 2. White Dot Pattern
 3. White Line Crosshatch
- Plus One Clear Acetate

These are broadcast quality and assure high-definition TV images. You can also transmit slides of any subject you wish.



MODEL 950

See Your Distributor or Send For Bulletin 1000-E

B & K MANUFACTURING CO.

3726 N. Southport Ave. • Chicago 13, Illinois

Makers of DYNA-QUIK, CRT, CALIBRATOR and DYNA-SCAN



Simplify and speed servicing with this unique, new, COMPLETE FLYING SPOT SCANNER. Produces composite video and sync signal that operates any standard VHF black and white or color TV receiver. Easily reproduces standard Indian Head test pattern or any other pattern—in home, shop or store—for proper TV set alignment; enables you to make all color TV static and dynamic convergence adjustments with stable White Dot and White Line patterns. Can be used with one or more standard TV receivers or fed into master antenna system. Reproduces from any film transparency. Transmits messages typed or written on clear acetate. Size: 16½ in. long, 10½ in. high, 9½ in. wide. Net wt. 28 lbs. **\$199⁹⁵** NET

Model 950 Dyna-Scan Pickup and RF Generator Only

Make your own picture and pattern generator. Just connect Model 950 to any properly modified 10-inch TV set which acts as your external flying spot scanner. Size: 3½ in. high, 10½ in. wide, 5 in. deep. Complete with 3 slide transparencies and 1 clear acetate. Net wt. 5 lbs. . . . **\$69⁹⁵** NET

COLOR TELEVISION

Home Study For Technicians

Now Available the MOST COMPLETE, COMPREHENSIVE COLOR TV HOME STUDY COURSE illustrated with new BLOCK-A-MATICS

This new seven-lesson HOME STUDY COURSE in COLOR TELEVISION was compiled by Albert C. W. Saunders, internationally noted author-lecturer on Radio and TV Servicing, and is the best course available today. It is just off the press with the latest technical information. Lessons are fully illustrated with simplified diagrams including BLOCK-A-MATICS—The New Look In Schematics. Also Color Illustrations.

COMPLETE COURSE—ONLY \$25

For Particulars Write

Saunders Electronics Correspondence School
Dept. CT 137 Federal Street, Boston 10, MASS.


Complete, All in 1 Tester

HICKOK

VHF
UHF

Black & White or Color TELEVISION SWEEP-MARKER-ALIGNMENT GENERATOR

- ★ For complete television IF and RF alignment
- ★ All-electronic sweep ★ Dual markers

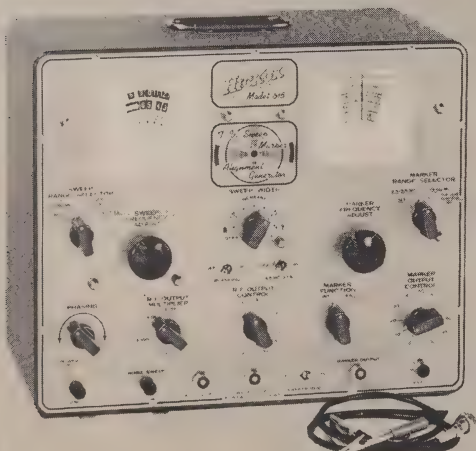

MODEL 615

A complete single-unit sweep and marker generator specifically designed for visual alignment of modern black and white or color TV receivers. Provides strong harmonic output on UHF. Excellent attenuation and sweep linearity. Features all-electronic sweep with no moving parts to become inoperative. Amplitude modulation is less than 0.1 db per megacycle. Strong .25 volt RMS marker. Marker frequency accuracy is at least 0.5% at any setting. Built-in Crystal. Non Parallax knife-edge pointers assure highest reading accuracy.

Ask for a demonstration of the 615 today!

THE HICKOK ELECTRICAL INSTRUMENT CO.
10531 Dupont Avenue • Cleveland 8, Ohio

RADIO

C1 and C2, a voltage will be maintained across the load at approximately twice the line voltage. (The peak ac voltage is equal to the rms voltmeter reading multiplied by the square root of 2 or 1.41.) A typical schematics of this device (both in theoretical form and how it looks in an actual circuit) is shown in Fig. 3.

A handy little voltage doubler is shown in the photo. The transformer voltage output is 6.3 and the dc output of the unit is 13 volts at 50 ma. The capacitors are 100 μ f with a working voltage of 50. END

Thirty-Five Years Ago In Gernsback Publications

HUGO GERNSBACK, Founder

Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some larger libraries still have copies of **ELECTRICAL EXPERIMENTER** on file for interested readers.

In September 1922 *Science and Invention* (formerly *Electrical Experimenter*)

The Slot Machine Radio, by H. Gernsback.

Who Discovered Radio? by A. P. Peck.
Radio Set in Pickle Bottle, by Edgar I. Eisenstadt.

Tikker Reception of C. W.
Chopping Bowl Loud Speaker.

Radio Concerts From a Lamp Socket, by A. P. Peck.

Five Stage Amplifier on 110 Volts A.C.
Radio for the Beginner, No. 7, by Armstrong Perry.

The Simplest Radio Outfit Contest, by Frank Copeman.




"Best TV repair shop in the city! While they are fixing your set, they give you a live replacement to look at!"

TRANSISTOR RADIOS

*Part IV—Some important features
of four popular superhets*

By I. QUEEN

EDITORIAL ASSOCIATE

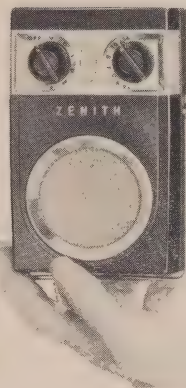

↑
The G-E model 676
transistor radio.

←
Zenith's Royal 500
transistor radio.

EARLY superhet tube receivers used low intermediate frequencies of 175 kc or so. As more broadcast stations went on the air and as they increased their radiated power, a higher if became necessary. Eventually, 455 kc was adopted by most radio manufacturers. The higher if produced less image interference.

The design of a transistor superhet with an if of 455 kc had to await the development of efficient high-frequency transistors and if transformers. Transistor gain falls off with increasing frequency, so only very-high-gain transistors are suitable at high intermediate frequencies. Transistors with a cutoff of at least 2.5 or 3 mc are suitable for use at an if of 455 kc. Among the highest cutoffs now available in junction transistors (RADIO-ELECTRONICS, February, 1956, page 40)

are Raytheon 2N113, 2N114 and G-E 2N137. Having cutoff values of 10, 20 and 10 mc, respectively, any of these will give very high gain at 455 kc.

Modern transistors can provide up to 33 db or more gain in a single stage. A gain of 33 db is equivalent to a power increase of 2,000 times. The specified rf gain of a complete transistor stage usually includes the 3-db loss in a matching transformer.

Raytheon FM-101A (modified)

One of the first superhet receivers designed for 455 kc was Raytheon's FM-101A, a modified version which is shown in Fig. 1. It uses p-n-p transistors operating from a 6-volt battery. Three rf transistors are indicated in the schematic: 2N112, 2N113, 2N114. Gain-wise there is about 1-db difference between them, the higher number

providing the greater gain. The 2N114 has a frequency cutoff of 20 mc!

The receiver has separate transistors for mixer and oscillator functions to provide maximum stability and gain. The variable tuning capacitor has two 355- μ f sections. The large padder (600–1,250 μ f) tunes the oscillator circuit 455 kc higher than the mixer.

Oscillator V1 is stabilized by an emitter resistor and a voltage divider feeding the base. Bias on each element is about 2 volts. Mixer V2 has zero bias since it must rectify as well as amplify. Note the filter network in the oscillator supply lead—this stage must be decoupled and isolated to prevent feedback through the common battery. A fixed 100- μ f capacitor injects the oscillator voltage into the mixer base.

The two if stages (V3, V4) follow circuit principles previously outlined.

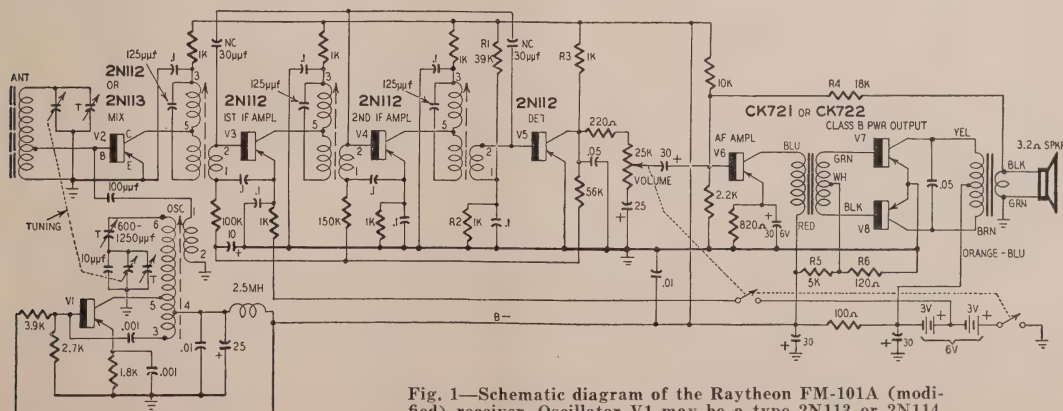


Fig. 1—Schematic diagram of the Raytheon FM-101A (modified) receiver. Oscillator V1 may be a type 2N113 or 2N114.

RADIO

There are decoupling and stabilizing networks in the collector and emitter leads. Neutralizing capacitors NC are 30 μ f.

The if transformers are No. 3015 (made by Automatic Manufacturing Co.), or their equivalent. The primary has 155 turns with a tap at 55 turns. The secondary has 18 turns. The primary is slug-tuned (from the bottom of the transformer) and is shunted by a 125- μ f capacitor. Each transformer is $\frac{3}{4}$ inch high by $\frac{1}{2}$ inch square. There are five terminals, of which only four are wired in circuit.

Detector V5 is biased class B. The biasing resistors are R1 and R2. The voltage across R2 is less than 0.15 volt and only a small bias current can flow through the base. Therefore V5 is near cutoff in the no-signal condition. At this time the collector current is about 0.1 ma and the drop across R3 0.1 volt. When an if signal arrives, collector current increases. On a strong station the drop across R3 may reach 1 volt or more. Therefore a voltmeter across this resistor may be used to measure signal strength and indicate alignment.

The variable dc collector voltage is fed back to both if amplifiers to control their gain. This avc drives the if bases more positive with increasing signal, cutting gain and preventing overload. V3 operates from 3 volts rather than the entire battery. This permits greater control of the stage. The second-stage emitter is self-biased.

Audio stage V6 drives a push-pull class-B output amplifier (V7, V8). These transistors are popular low-output types but, when used in class B, they are capable of 100-mw output. The output stage is held near cutoff by voltage divider R5-R6, so that with no signal very little current flows in the collector circuits.

An af signal drives these transistors into conduction, one at a time. Each transistor can conduct only when its base goes negative, therefore V7 conducts on one half of the cycle and V8 on the other. Both halves are combined to re-create the original signal in the output transformer. The stronger the input signal, the greater the conduction of each transistor. A total of about 27 ma flows at maximum signal. This drops to 1 ma in the absence of a signal. Evidently, we pay only for what we use in a class-B amplifier.

About 1.2 ma is lost in divider R5-R6. This loss cannot be reduced simply by using larger resistors. Relatively large peaks of current may flow in this stage, so low resistance is needed in the input and output circuits. The driver transformer has a secondary resistance less than 50 ohms. This transformer matches 10,000 to 2,000 ohms, base to base. The output transformer has a primary resistance of only 20 ohms. It matches the speaker to 500 ohms, collector to collector. Negative feedback (through R4) is used to reduce distortion.

An interesting feature of this re-

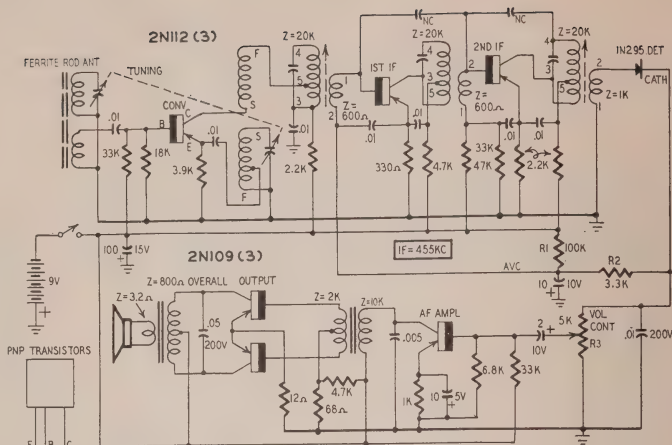


Fig. 2—Schematic diagram of the six-transistor model K-701 DeWald receiver.

ceiver is that it uses components now available to experimenters. All parts are available from mail-order houses or stores specializing in transistors and parts. This circuit is adequately decoupled, filtered and operated well within all ratings. Of course, the home builder cannot make such a circuit as light and compact as the commercially built, printed-circuit receiver with specially manufactured components to fit a small case.

DeWald K-701

This receiver (Fig. 2) uses six transistors of the p-n-p type. It is powered by a 9-volt battery (Eveready 276 or equivalent) which can give about 500 hours of service.

The first transistor oscillates and converts to if. Oscillations are generated by coupling the collector and emitter windings. As in any tickler arrangement, the polarity of each coil is important. In the diagram, s shows the start and f the finish of each winding. To maintain high Q, reduce antenna capacitance and at the same time match the low input impedance, the base is fed from a secondary rather than the antenna coil itself.

The if strip uses the same transistors and neutralizing arrangement shown in the previous receiver. Voltage divider R1-R2-R3 supplies no-signal bias to the first if, and positive bias is supplied by the avc lead. The stronger the signal, the more positive this control voltage and the lower the if gain. Because of the larger voltage supply, it is possible to use larger decoupling resistors here than in the previous circuit.

The secondaries of each of the two if transformers are wound to match 600 ohms, the transistor input. The secondary of the third transformer matches a higher impedance, the crystal diode. This detector supplies positive avc voltage and also feeds the rectified if to the volume control.

The af is fed to a conventional audio

circuit. Each stage is fixed-biased. The push-pull stage is biased to near cutoff by a 70-to-1 ratio voltage divider. Output is about 75 mw maximum.

Fig. 3 shows the parts layout. Set dimensions are $8\frac{1}{2} \times 6\frac{1}{2} \times 2\frac{1}{2}$ inches. This cabinet permits inclusion of a 4-inch speaker, much larger than in tiny pocket sets, and is nonbreakable.

Zenith Royal 500

This receiver uses seven transistors, all n-p-n type. The battery is 6 volts, which may be four penlight (size AA) cells in series. These will supply the set for approximately 50 hours at an operating cost of about 1 cent an hour. If longer life is desired, mercury cells (Zenith Z9) may be substituted. Conelrad frequencies 640 and 1240 kc are

(Continued on page 99)


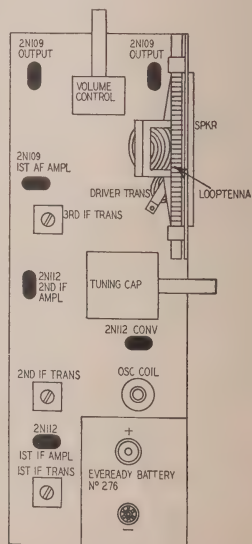


Fig. 3—Parts layout for DeWald K-701.

you get the most for your money in ALLIED'S own **knight-kits**

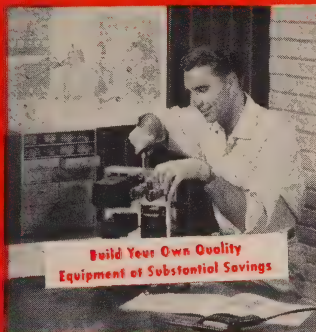THE FINEST ELECTRONIC EQUIPMENT IN MONEY-SAVING KIT FORM



Buy With Confidence From the Pioneers in Electronic Kits


LOWEST COST—our huge buying power means biggest savings for you. You do the easy assembly and your finished instrument is equal in performance and appearance to equipment selling for several times the remarkably low KNIGHT-KIT price.

ADVANCED DESIGN—months of research, development and field-testing go into each KNIGHT-KIT to bring you the latest advances in quality design. And to assure top performance, premium quality parts are supplied in each kit.

EASIEST TO ASSEMBLE—all chassis and panels are punched; all parts are clearly identified—resistors are mounted on cards and values are shown. Instruction manuals are a marvel of clarity, featuring "Step-and-Check" assembly, "King-Size" diagrams and "Spotlight" pictorials. All you need are soldering iron, pliers and screwdriver.

ALLIED stakes its 36-year reputation in the Electronics field on your complete success and fullest satisfaction with KNIGHT-KITS.

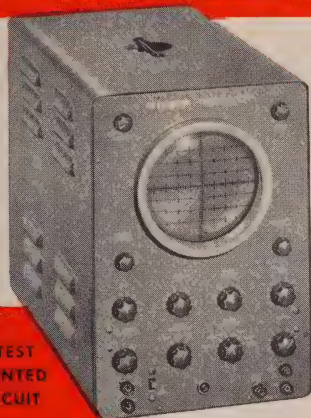TEST EQUIPMENT • HAM GEAR • HOBBYIST KITS • HI-FI KITS



LATEST
PRINTED
CIRCUIT

NEW knight-kit LOW COST GENERAL-PURPOSE 5" OSCILLOSCOPE KIT

Model F-146

\$49⁵⁰

Outstanding value in an all-new, highly versatile 5" oscilloscope kit. Perfect for visual display of all commonly encountered waveforms. Excellent for AM, FM and TV servicing, plus other high-frequency applications. An easy-to-build, easy-to-use, dependable performer that matches or beats commercially wired scopes selling at several times more. Up-to-the-minute kit design features printed circuit, laced wiring harness, and pre-cut wires for quick and easy assembly. Has 4 sweep ranges, 15-150,000 cps. High vertical sensitivity: 25 rms millivolts/inch; input impedance, 3.3 megs and 45 mmf; response down only 3 db at 700 kc. Horizontal sensitivity, 70 rms mv/inch; response down only 3 db at 200 kc; input impedance, 2.2 megs and 30 mmf. Deluxe features include DC positioning controls for fast trace positioning; blanking circuit on all ranges to eliminate retrace lines; graph scope screen and internal, regulated calibrating voltage for highly accurate signal measurements; frequency-compensated vertical attenuator; provision for internal or external, positive or negative synchronization; Phantastron linear sweep generator; high 2nd anode voltage for high-intensity trace. Kit is complete with 5" CRT and all tubes—ready for assembly. Blue steel case with "disappearing" handle. Handsome panel in contrasting gray. Size, 14½ x 9½ x 16" deep. Shpg. wt., 40 lbs.

Model F-146. Complete 5" Oscilloscope Kit. Net only.....**\$49.50**

F-148. RF Demodulator Probe Kit. Net only.....**\$3.45**

F-147. Low-Capacity Probe Kit.....**\$3.45**



Model F-123

\$44⁷⁵

NEW knight-kit TV-FM SWEEP GENERATOR KIT

Guaranteed Linearity • Fool-proof Calibration
Wide-Range Coverage • Electronic Blanking

All-new; precision-designed for lab use, TV and FM servicing, production line testing. Covers 300 kc to 250 mc continuous on 4 bands (all fundamentals). Center frequencies of VHF TV channels appear on scales. Exclusive KNIGHT-KIT sweep circuit assures almost perfect linearity—RF sweep output in excess of 0.15 volts, flat within 1 db, is available on all bands. Sweep width continuously variable, 0-13 mc. Crystal-controlled marker oscillator with dual crystal socket and selector switch. Phase control provides blanking shift, 0 to 180°. Step-type and continuous output controls; separate marker amplitude control. Filter connected to 0-50 mc output jack provides 20 db attenuation of frequencies above 50 mc, to assure pure, fundamental output. 5-volt horizontal sweep voltage (for scope) available from front panel. Professional-looking blue-finish steel case with gray panel. Has "disappearing" handle. 8½ x 12 x 7½". With all parts, tubes, test cable, solder and multi-color pre-cut wire. Less crystal. Shpg. wt., 13½ lbs.

Model F-123. TV-FM Sweep Generator Kit. Net only.....**\$44.75**

P-286. 4.5 mc Crystal (.005%). Net.....**\$4.80**

P-143. 5.0 mc Crystal (.02%). Net.....**\$3.95**

P-145. 10.7 mc Crystal (.02%). Net.....**\$3.95**

EASY PAYMENT TERMS

If your total KNIGHT-KIT order is over \$45, take advantage of our liberal Time Payment Plan—only 10% down. Write for application form.

ALL PRICES NET F.O.B. CHICAGO

order from

ALLIED RADIO


100 N. WESTERN AVE., CHICAGO 80, ILLINOIS

SEE FOLLOWING PAGES

ALLIED'S own knight-kits...better by far

knight-kit 5" ALL-PURPOSE WIDE-BAND OSCILLOSCOPE KIT

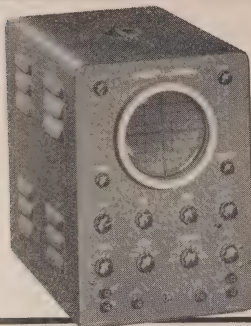2 Printed Circuit Boards • 5 Mc Width for Color TV



Model F-144

\$69⁰⁰

Wide-band, 5" Oscilloscope; equals or betters the performance of commercially-wired 'scopes costing several times the price. Two printed circuit boards and laced wiring harness assure wiring accuracy and reduce assembly time. Ideal for lab use, color TV servicing and high frequency applications. Provides unusually wide sweep range—from 15 to 600,000 cps. Locks in at frequencies as high as 9 mc. Vertical response, 5 cycles to 5 mc. Response, down only 1 db at 3.58 mc color burst frequency; down only 3 db at 5 mc. High vertical sensitivity of 25 mv/inch. Input capacity 20 mmf and 3.5 megs. Outstanding features: cathode-follower vertical and horizontal inputs; 2nd anode provides 1400 volts high-intensity trace; push-pull vertical and horizontal amplifiers; positive and negative locking; faithful square wave response; frequency-compensated attenuator; Z-axis input for intensity modulation; one volt P-P calibrating voltage; astigmatism control; blanking circuit to eliminate retrace lines; DC positioning control. Complete with CRT, all tubes and parts. Handsome, professional, blue-finished steel case with "disappearing" handles. 14½ x 9½ x 16". Shpg. wt., 40 lbs.

Model F-144, Wide-Band 5" Oscilloscope Kit. Net only.....**\$69.00**
F-148, Demodulator Probe. Net...**\$3.45** F-147, Low Capacity Probe, 12 mmf. Net...**\$3.45**

NEW knight-kit VOLTAGE CALIBRATOR KIT




Model F-136 **\$12⁷⁵**

Permits the use of any scope as a precision peak-to-peak AC voltmeter. Provides a true square-wave voltage on scope screen. Range switch and calibrated potentiometer permit selecting any voltage between .01 and 100 volts, in 4 ranges. Fifth position of switch feeds external signal to scope for comparison.

Constant output on line volt. variation from 80-135 v. ±6% on all ranges. Shunt capacitance only 15 mmf. Use any 20,000 ohms/volt VOM or a VTVM for initial calibration. Direct coupling of output provides ground reference for DC scopes. Portable case, 7¼ x 5¼ x 4¼". Ready to build. Shpg. wt., 5 lbs.

Model F-136, Voltage Calibrator Kit. Net...**\$12.75**

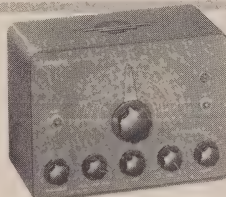knight-kit LOW COST RF SIGNAL GENERATOR KIT




Model F-145 Build this wide-range extremely stable RF signal generator and save two-thirds the cost of a comparable

wired instrument. Ideal for alignment of RF and IF stages in radio and TV sets, and for trouble-

shooting audio equipment. Delivers output on fundamentals from 160 kc all the way out to 110 mc; useful harmonics to 220 mc. Has built-in 400-cycle sine-wave audio oscillator for modulating RF; audio is also available externally. Features high-stability Colpitts circuit with precision-wound coils—no calibration necessary. Has input for external modulator. Maximum audio output, 10 volts. RF output, over 100,000 micro-volts. Step and continuous-type output attenuators. With all parts, tubes, wire and solder. Portable case, 7 x 10 x 5". Shpg. wt., 10 lbs.

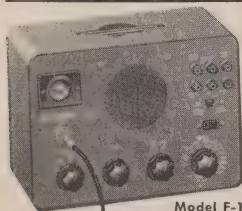Model F-145, RF Signal Generator Kit. Net only.....**\$19.75**



Model F-135


\$26⁵⁰

knight-kit

VISUAL-AURAL SIGNAL TRACER KIT

A remarkable value in an instrument which permits visual and aural signal tracing of RF, IF, video and audio circuits—has highest gain in its price class. Traces the signal from the antenna to the speaker. Reproduces signal at plate or grid connection of any stage. Identifies and isolates "dead" stages. Features: usable gain of 91,000; "magic eye" with calibrated attenuators for signal presence indication and stage-by-stage gain measurements; built-in 4" PM speaker; single probe with plug-in head gives instant choice of RF or audio tracing. Provides noise test; built-in watt meter calibrated from 25 to 1000 watts; provision for external scope or VTVM. Blue-finish steel case. Shpg. wt., 13 lbs.

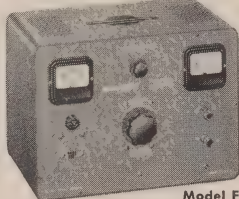Model F-135, Signal Tracer Kit. Net only.....**\$26.50**



Model F-129

\$37⁹⁵


NEW

knight-kit

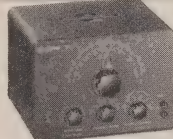6-12 VOLT BATTERY ELIMINATOR KIT

A valuable new unit for servicing auto radios, mobile gear, etc. Delivers continuously variable filtered DC output from 0 to 15 volts. Provides DC output at 0-8 volts or 0-15 volts. Continuous current rating: 12.5 amps at 6 volts, 10 amps at 12 volts. Can also be used as battery charger. Oversize rectifiers and transformer for better regulation and long life. Two meters provide simultaneous current and voltage readings; ranges: 0-15 volts DC; 0-20 amps DC. Doubly protected: fused primary and automatic-reset overload relay for secondary. Heavy-duty binding posts. Blue-finish steel case with "disappearing" handle. With all parts, solder and pre-cut wire. 9 x 12½ x 7¼". Shpg. wt., 20 lbs.

Model F-129, Power Supply Kit. Net only.....**\$37.95**



Model F-137 **\$37⁵⁰**

knight-kit

AUDIO GENERATOR KIT

An ideal audio frequency source for checking audio circuits and speaker response. Covers: 20 cps to 1 mc in 5 ranges. Output voltage: 10 volts into 600 ohms impedance. Offers the flat response of a lab standard—±1 db to 1 meg. Generator imp., 600 ohms. Less than .25% distortion from 100 cps through the audible range; less than .5% when driving 600 ohm load at maximum output. Cont. var. step-attenuated output. 17 lbs.

Model F-137, Audio Generator Kit. Net only.....**\$37.50**

knight-kit RESISTANCE SUBSTITUTION BOX KIT



Model F-139 Simplifies determination of resistor values needed in a circuit. 36 standard and 1 watt resistance values between 15 ohms and 10 megohms with an accuracy of 10%. 18-position switch; also slide switch for multiplying values by 1000. Extra switch wafer serves as tie points, eliminating buss bar. 5 x 3 x 2". Complete with test leads and clips. 2 lbs.

Model F-139, Resis. Sub. Box Kit. Net...**\$5.95**

knight-kit CAPACITANCE SUBSTITUTION BOX KIT




Model F-138 Makes it easy to find capacitor values needed in a circuit. Provides 18 standard capacitor values from .0001 mfd. to .22 mfd., ±20%. Values are 600 volts, except .15 and .22 which are 400 volt. 18-position switch selects all values quickly and easily. In bakelite case, 5 x 3 x 2". Complete with all parts, test leads and clips. 2 lbs.

Model F-138, Cap. Sub. Box Kit. Net...**\$5.95**

QUALITY ELECTRONIC TEST EQUIPMENT IN MONEY-SAVING KIT FORM

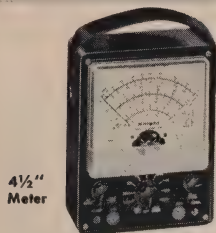...easiest to build...you get more...**YOU SAVE MORE**



4½" Meter

Model F-128 **\$16⁹⁵**

knight-kit

1000 OHMS/VOLT VOM KIT

Exceptional accuracy and versatility at amazing low cost. Ideal for service shop, lab and Amateur use. Uses 4½" meter (400 microamp movement) with separate scales for AC voltage and current, DC voltage and current, decibels and resistance. 38 ranges include: AC, DC and output volts, 0-1-5-10-50-100-500-5000 (1000 ohms/volt sensitivity); Resistance, 0-1000-100,000 ohms and 0-1 meg.; Current, AC or DC, 0-1-10-100 ma and 0-1 amps; Decibels, -20 to +69 in 6 ranges. Uses 1% precision resistors. 3-position function switch and 12-position range switch. Complete kit with bakelite case, (6¼ x 5¼ x 3¼"), battery, pre-cut wire, solder and test leads. Shpg. wt., 2½ lbs.

Model F-128, 1,000 ohms/volt VOM Kit. Net only **\$16.95**




Model F-140 **\$29⁵⁰**

knight-kit

20,000 OHMS/VOLT VOM KIT

Outstanding quality and performance at extremely low cost. Features 32 ranges; full vision 4½" meter; accuracy ±2% of full scale; 50 microampere sensitivity for 20,000 ohms/volt input resistance on DC; front panel "zero adjust" Single switch selects function and range. Range: AC, DC and output volts, 0-2.5, 10-50-250-1000-5000; Resistance, 0-2000-200,000 ohms and 0-20 meg.; DC ma, 0-1-10-100; DC amps, 0-1-10; Decibels, -30 to +63 in 6 ranges. Uses precision 1% multipliers. Moisture-resistant film-type resistors. Complete kit with bakelite case (6¼ x 5¼ x 3¼"), batteries, pre-cut wire, solder and test leads. Shpg. wt., 5 lbs.

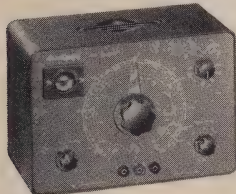Model F-140, 20,000 ohms/volt VOM Kit. Net only **\$29.50**



knight-kit RESISTOR-CAPACITOR TESTER KIT

Model F-124 Measures capacitance and resistance by accurate bridge method; checks for opens and shorts in paper, mica and ceramic capacitors; shows power factor of electrolytics. Large dial shows capacitance and

resistance at a glance; balanced-bridge circuit with "magic eye" null indicator measures power factor from 0-50%. Tests capacitors with rated voltages applied. 5 test voltages: 50, 150, 250, 350, 450. Capacity ranges: 10 mmf to 1000 mfd in 5 ranges. Resistance ranges: 100 to 50,000 ohms and 10,000 ohms to 5 megs. Accuracy, ±10%. Automatic discharge feature prevents after-test shock. Blue-finished steel case, 5 x 3 x 2". With tubes and all parts. Shpg. wt., 8 lbs.

Model F-124, Resistor-Capacitor Tester Kit. Net only **\$19.50**



Model F-149

\$8⁵⁰


NEW knight-kit TRANSISTOR & DIODE CHECKER KIT

Checks leakage-to-gain ratio and noise level of all junction, point contact and barrier transistors. Also checks diodes, forward and reverse current conduction of selenium rectifiers; useful for continuity and short checks. Easy-to-read meter. Features: spring-return leakage gain switch; calibration control; separate sockets for PNP and NPN transistors. Headphones or signal tracer may be used with checker for noise measurements. Case, 5 x 3 x 2". With 22½ volt battery. 2½ lbs.

Model F-149, Transistor Checker Kit. Net **\$8.50**

EASY PAYMENT TERMS: If your total KNIGHT-KIT order is over \$45, take advantage of our liberal Time Payment Plan —only 10% down. Write for application blank.

ALL PRICES NET F.O.B. CHICAGO

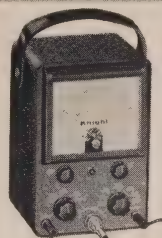

knight-kit VTVM KIT with Printed Circuit Board


Model F-125 An extremely stable, and highly accurate VTVM. Greatly simplified wiring—entire chassis is a printed circuit board. Maximum convenience in arrangement of scales; 3X AC and DC scale design permits utilization of best portion of each scale for most accurate readings.

Also measures peak-to-peak for FM and TV work. Ranges: AC P-P volts, 0-4-14-40-140-400-1400-4000; AC rms volts and DC volts, 0-1-5-15-50-150-500-1500; resistance, 0-1000-10K-100K ohms and 0-1-10-100-1000 megohms; db scale, -10 to +5. AC response, 30 cycles to 3 mc. Low-leakage switches and 1% precision resistors. Balanced-bridge circuit. 4½" meter, 200 microamp movement. Polarity reversing switch. Input res., 11 megs. Shpg. wt., 6 lbs.

Model F-125 Printed Circuit VTVM Kit. Net only **\$24.95**

F-126, Hi-Voltage Probe; extends DC to 50,000 Volts **\$4.75**

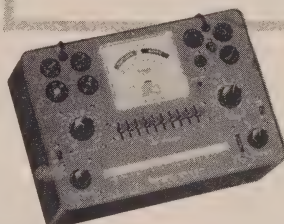F-127, Hi-Frequency Probe; extends AC to 250 mc. **\$3.45**



Model F-143

\$29⁷⁵

knight-kit LOW-COST TUBE TESTER KIT

Offers high accuracy, top versatility and convenience at lowest cost. Tests 4, 5, 6 and 7-pin large, regular and miniature types, octals, localts, 9-pin miniatures and pilot lamps. Features test for new 600 ma series string tubes. Tests for open, short, leakage, heater continuity and quality (by amount of cathode emission). 4½" square meter with clear "GOOD-?-REPLACE" scale. With line-voltage indicator and line-adjust control. Choice of 14 filament voltages from .63 to 117 volts. Blank socket for future type tubes. Universal-type selector switches for any combination of pin connections. Single-unit, 10-lever function switch. Entire switch assembly is installed as a single unit—saves time and greatly simplifies construction. Illuminated roll chart lists over 600 tube types. Shpg. wt., 14 lbs.

Model F-143, Counter Model Tube Tester Kit. Net only **\$29.75**

Model F-142, Portable Model Tube Tester Kit. Net only **\$34.75**

F-141, TV Picture Tube Adapter for above. Net only **\$3.75**



Model F-119

\$12⁵⁰

knight-kit LOW-COST

"IN-CIRCUIT" CAPACITOR CHECKER KIT


Tests capacitors while they are still wired in the circuit! Saves time and bother; an essential instrument for the service technician. Just press a button and the "magic eye" instantly shows opens and shorts (not leakage). Tests opens and shorts on any capacitor of 20 mmf or greater capacity, even if it is in parallel with a resistance as low as 50 ohms. Tests for shorts may be made on any capacitor even when it is shunted by as low as 20 ohms. Blue-finish steel case, 7¼ x 5¼ x 5". With tubes, all parts, wire and solder. Easy to assemble. Shpg. wt., 5 lbs.

Model F-119, Cap. Checker Kit. **\$12.50**

order from **ALLIED RADIO** 100 N. WESTERN AVE., CHICAGO 80, ILL. →

ALLIED'S own MONEY-SAVING knight-kits

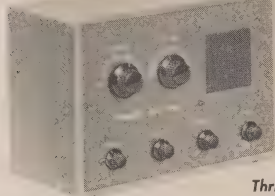FAMOUS knight-kits FOR HOBBYISTS & EXPERIMENTERS... FASCINATING, INSTRUCTIVE...



knight-kit
"SPACE SPANNER"
BAND SWITCHING
RECEIVER KIT

Model S-243 \$15⁹⁵

Thrilling Short Wave and Broadcast

Famous 2-band AC-DC receiver in easy-to-build kit form at a very low price. Pulls in thrilling short-wave (6 to 17 mc) and standard broadcast. It's fun listening to amateur, aircraft, police and marine radio. Features highly sensitive regenerative circuit. Bandswitch selects broadcast or short wave. Has 4" PM speaker and beam-power output tube for plenty of volume; headphone connectors for weak signal listening; slide switch cuts out speaker. Uses 12AT7 regenerative detector and audio amplifier, 50C5 power output, 35W4 rectifier. Six controls: Bandspeed; Main Tuning; Antenna Trimmer; Bandswitch; Regeneration; Audio Gain. Includes tubes and all parts. 7 x 10½ x 6". Shpg. wt. 4½ lbs.

Model S-243. "Space Spanner" Receiver Kit. Net only. . . . \$15.95

S-247. Matching Cabinet for above. 2 lbs. Net. . . . \$2.90




Model S-295 \$14⁷⁵

NEW knight-kit TWO-WAY INTERCOM KIT

New low-cost, easy to build intercom system kit. Ideal for use in home or office. Consists of Master unit and Remote unit, each with press-to-talk switch. Remote unit may be left "open" for answering calls from a distance, for "baby-sitting", etc. Remote may also be connected for "private" operation—cannot be "listened-in" on, but it can be called and can originate calls. Master unit includes high-gain 2-stage amplifier; each unit has 4" PM dynamic speaker. Complete with Antique White cabinets (4¾ x 6½ x 4¾"), all parts, tubes and 50 feet of cable (up to 200 feet of cable can be added). For AC or DC. Shpg. wt., 7 lbs.

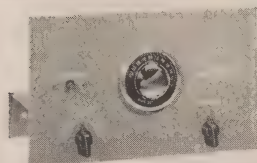Model S-295. Two-Way Intercom Kit. Net only. . . \$14.75



Model S-740 \$11⁷⁵

knight-kit

"OCEAN HOPPER" RECEIVER KIT

Tops for exciting broadcast, long wave and short wave reception. Highly sensitive regenerative-type circuit. Excellent headphone reception; can be used with 3-4 ohm PM speaker on strong broadcast band stations. Supplied with plug-in coil for standard broadcast; covers long wave and popular short wave bands with coils below. Pulls in thrilling foreign broadcasts, police, amateurs and aircraft. Controls: Main Tuning, Bandspeed, Antenna Tuning, Off-On-Regeneration. With all parts and tubes (less extra coils and headset). AC or DC. Shpg. wt., 5 lbs.

Model S-740. "Ocean Hopper" Kit. . . . \$11.75

EXTRA PLUG-IN COILS

S-741. Long Wave, 155-470 kc. Net.79¢

S-742. Short Wave, 1.65-470 kc. Net.79¢

S-743. Short Wave, 2.9-7.3 mc. Net.65¢

S-745. Short Wave, 7-17.5 mc. Net.65¢

S-744. Short Wave, 15.5-35 mc. Net.65¢



Model S-735 \$17²⁵

knight-kit

"RANGER II" SUPERHET RADIO KIT

Thousands have built and enjoyed the "Ranger" Broadcast Band Receiver. Carefully engineered for easy construction and powerful, sensitive performance. Latest Superhet circuit; tunes 540 to 1680 kc; covers entire broadcast band and exciting police calls. Features automatic volume control, built-in preformed loop antenna, ball-bearing tuning condenser. Develops excellent tone quality from Alnico V PM dynamic speaker. Supplied with following tubes: 12SA7GT converter; 12SK7GT IF amp.; 12SQ7GT det.-AVC-audio; 50L6GT audio output; 35Z5GT rect. Complete with handsome brown plastic cabinet (6 x 9 x 5) tubes, speaker, all parts, and instruction manual. AC or DC operation. Shpg. wt., 8 lbs.

Model S-735. "Ranger II" Superhet Radio Kit. Net only. . . . \$17.25



Model S-730 \$19⁹⁵


knight-kit

3-WAY PORTABLE RADIO KIT

A low-cost portable radio covering the full standard broadcast band from 535 kc to 1650 kc. Delivers excellent reception on AC or DC current or from self-contained batteries. Sensitive Superhet circuit features automatic volume control, economical operation. Includes powerful 5" Alnico PM dynamic speaker, efficient ferrite loop-stick antenna. Supplied with following tubes: 1R5 converter; 1U4 IF amplifier; 1U5 detector-AVC-audio; 3V4 audio output. Complete with attractive portable case (7½ x 10 x 5½"), tubes, speaker, all parts and instruction manual. Shpg. wt., 6 lbs.

Model S-730. 3-Way Portable Radio Kit (less batteries). Net. . . \$19.95

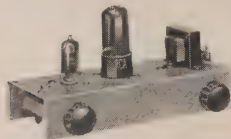J-651. Battery Kit for above. . . . \$2.50



knight-kit LOW COST PHONO AMPLIFIER KIT

Model S-790 \$8⁹⁵

It's easy to build this fine-performing, low-cost compact phono amplifier. Ideal for use in a portable phonograph—simply add any

record player and a 3 to 4-ohm speaker. Amplifier works with crystal or ceramic cartridges. Inverse feedback circuit for rich, clean tone quality. Delivers full 1½-watt output with less than 25 volt input. Includes efficient tone control; has AC outlet, controlled from amplifier switch. Complete with tubes and all parts. Size only 4½ x 7 x 4"—fits into almost any portable phono case. Shpg. wt., 3 lbs.


Model S-790. Phono Amplifier Kit. Net only. . . . \$8.95

FAMOUS knight-kit CRYSTAL SET KIT

Thousands of beginners have started in radio and electronics by building the KNIGHT-KIT crystal set. This feature-packed set delivers loud, clear reception of local broadcast stations. A germanium crystal diode detector assures high sensitivity and simple operation—no crystal adjustment required. "Hi-Q" coil boosts sensitivity. Ball-bearing variable capacitor for easy tuning. With all parts and simple-to-follow instructions. Shpg. wt., 1 lb.

Model S-261. Crystal Set Kit. Net only. . . . \$2.15

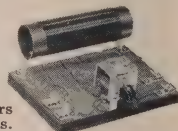S-267. Accessory Kit. 2000-ohm headphones and all parts for outdoor antenna. . . . \$2.95



Buy with confidence from ALLIED — America's Pioneer in Electronic Kits

finest quality electronic equipment in lowest-cost kit form

EASY-TO-BUILD HIGH PERFORMANCE KITS • WIDELY USED BY MANY LEADING TRAINING SCHOOLS




NEW knight-kit ELECTRONIC PHOTOFLASH KIT

Model S-244
\$28.50

New feature-packed photoflash kit—designed for top quality dependability—available at a

money-saving low price. Ideal for black and white or color photography. Xenon-filled reflector-bulb assembly gives over 10,000 flashes at less than 1/4¢ each! 1/700-second flash freezes the fastest action. Has 50 wait-second output. Provides light approximating daylight in spectral quality; permits the use of outdoor-type film indoors. Film guide number for color (ASA10) is 45. Designed for "X" or "O" shutters only. Requires sync cable (available from any photo supply dealer) and either battery or AC supply listed below. Complete outfit with battery weighs only 3 1/2 lbs. Kit includes all parts, carrying case and easy-to-follow instructions. Shpg. wt., 3 lbs.

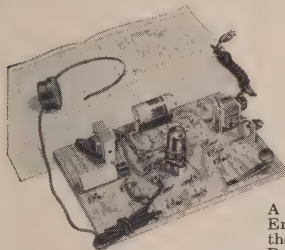Model S-244. Electronic Photoflash Kit. Net.**\$28.50**
S-246. AC Power Supply Kit. Easy to assemble.**\$3.75**
J-626. Battery for above (Burgess U-200)**\$8.47**



FAMOUS knight-kit LAB KITS


6-IN-1 RADIO LAB KIT

Model S-770
\$7.95

Build Any
of 6 Electronic
Projects

A fascinating and instructive kit. Enables you to build any one of the following projects: Standard Broadcast Receiver; Wireless Broadcast Station; Code Practice Oscillator; Code Practice Broadcaster; Signal Tracer; Sine Wave Generator. Perfect for beginners. Once basic wiring is completed, circuits may be changed without soldering. Safe to build and operate; only tools needed are screwdriver, pliers and soldering iron. The ideal kit for students and beginners in electronics. Kit includes mounting board, tube, all parts and easy-to-follow instruction manual. Less headphone (also serves as mike). Shpg. wt., 6 lbs.

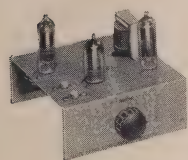Model S-770. "6-in-1" Lab Kit. Net only.**\$7.95**
J-112. Single 1000-ohm headphone for above.**\$1.05**
C-100. Antenna kit for above.**\$1.05**



knight-kit WIRELESS BROADCASTER KIT

Model S-705
\$9.50

This fascinating unit makes it possible to "broadcast" with phonograph or microphone through any standard radio receiver up to 50 feet away—without any connection to the set. May be used with crystal or magnetic cartridge, or with microphone. Broadcasts a clear, full-toned signal. High-gain stage permits using magnetic cartridge without need for external preamp. Complete with all parts, tubes, wire and solder (less microphone). 4 1/2 x 5 x 6". Easy to assemble. Shpg. wt., 3 lbs.



Model S-705. Wireless Broadcaster Kit. Net only.**\$9.50**
S-556. Microphone for above with 5-ft. cable.**\$3.95**

knight-kit PHONO OSCILLATOR KIT

Model S-760
\$5.85

This low-cost phono oscillator may be used with any crystal phonograph for "broadcasting" recorded music through any standard radio receiver up to 50 feet away. Requires no direct connection to radio set. Operates on any frequency between 600 and 800 kc. Has controls for adjustment of modulation level and selection of clear frequency on radio receiver. Uses 50L6GT tube and 35Z5GT rectifier. Complete with all parts, tubes and instructions. 4 3/4 x 4 3/4 x 4 3/4". Shpg. wt., 1 lb.

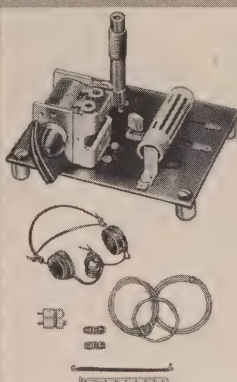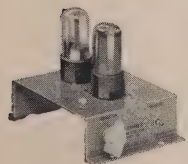Model S-760. Phono Oscillator Kit. Net only.**\$5.85**



knight-kit TRANSISTOR RADIO KIT


Printed Wiring • Works from Penlight Cell

Model S-765
\$4.35

Smooth
Variable Capacitor
Tuning

Experiment with the marvel of transistors! Printed circuit requires no wiring—just assemble with a few solder connections and enjoy excellent reception over the full AM broadcast band. No tubes to burn out—no crystal. Compact—fits in the palm of your hand—operates for months from a single penlight cell. Transistor provides plenty of power for strong headphone reception. Complete with all parts, transistor and penlight cell. Shpg. wt., 8 oz.

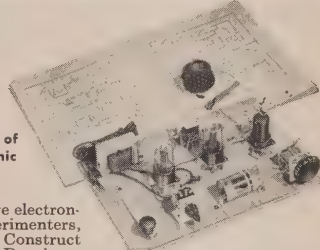Model S-765. Transistor Radio Kit **\$4.35**
S-266. Accessory Kit. 4000-ohm headphones and all parts for outdoor antenna.**\$3.15**



10-IN-1 LAB KIT

Model S-265
\$12.65

Build Any of
10 Electronic
Projects

A wonderfully instructive electronics kit. Ideal for experimenters, beginners—fun to build. Construct a sensitive Broadcast Receiver; Amplifier (for phono or mike); Wireless Phono Oscillator; Home "Broadcast Station"; Code Practice Oscillator; Capacity-Operated Relay, or any one of four other fascinating projects. Low voltages; safe to build and operate. Only tools needed are soldering iron, screwdriver and pliers. Perfect for self-instruction in circuit fundamentals, and packed with practical applications. Kit includes mounting board, tubes, all parts, hardware, microphone, and 12-page builders' manual. Shpg. wt., 10 lbs.

Model S-265. "10-in-1" Lab Kit. Net only.**\$12.65**
J-112. Single 1000-ohm headphone for above.**\$1.05**
C-100. Antenna Kit for above.**\$1.05**



knight-kit CODE PRACTICE OSCILLATOR KIT

Model S-239
\$3.95

Transistor
Circuit—
Powered by
Penlight Cell

An ideal code practice oscillator. Uses transistor circuit. Extremely low current consumption—powered by single penlight battery. Provides crisp, clear tone (400 to 600 cps). Has input jack for earphone; screw-type terminal strip for key. In compact bakelite case (2 3/4 x 3 3/4 x 1 1/2") with anodized aluminum panel. Complete with all parts, transistor, battery and easy-to-follow instructions. Shpg. wt., 1 lb.

Model S-239. Code Practice Kit.**\$3.95**

See Next Page for Amateur Kits

ALL PRICES NET F.O.B. CHICAGO

order from **ALLIED RADIO** 100 N. WESTERN AVE., CHICAGO 80, ILL. →


ALLIED'S own knight-kits give you the most for your money

BUILD YOUR OWN QUALITY HI-FI AMPLIFIER!

knight-kit BASIC 25-WATT LINEAR-DELUXE HI-FI AMPLIFIER KIT


Model S-755
\$44⁵⁰

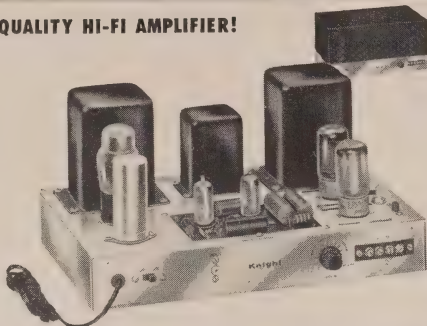Williamson-Type Circuit
Printed Circuit Board
Chrome-Plated Chassis



This super-quality hi-fi basic amplifier is designed to satisfy the most critical listener. Intended for use with tuners incorporating built-in preamp or with separate preamp. Incorporates latest Williamson-type circuit and has potted matched transformers. Delivers maximum output of 45 watts. Frequency response is: ± 0.5 db, 10 cps to 120 kc, measured at 20 watts. Harmonic distortion is only .15% right up to 30 watts. Intermodulation distortion is only .27% at 10 watts and only 4% at 20 watts, using 60 cps and 7 kc, 1:4 ratio. Hum level is -85 db below full rated output. Output impedance, 4, 8, 16 ohms. Input voltage for 25-watt output is 1.8 volts. Uses two 12AU7's, two 5881's, and a 6V4. Etched circuit is utilized in voltage amplifier and phase inverter stages to speed assembly. Has output tube balancing control, variable damping control, and on-off switch. Handsome chrome-plated chassis, 14 x 9 x 2". Overall height, 7". A deluxe true hi-fi amplifier equal in performance to amplifiers selling at over twice the price. Complete with all parts and tubes. Easy to assemble. Shpg. wt., 27 lbs.

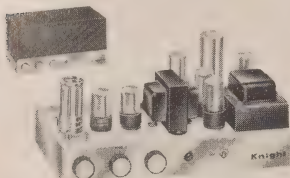
Model S-755, Basic 25 Watt Hi-Fi Amplifier Kit. Net only **\$44.50**
S-759. Metal enclosure for above; black finish. 3 lbs. Net **\$4.25**



knight-kit 10-WATT HI-FI AMPLIFIER KIT

Model S-753 Chrome-Plated Chassis
\$23⁵⁰
Famous for wide response and smooth reproduction at low cost. Only 0.5 volt drives amplifier to full output. Frequency response: ± 1 db, 30-20,000 cps at 10 watts. Harmonic distortion less than 0.5% at 10 watts. Intermod. distortion less than 1.5% at full output. Controls: on-off-volume, bass, treble. Input for crystal phono or tuner. Chromed chassis; punched to accommodate magnetic cartridge preamp. Matches 8 ohm speakers. Shpg. wt., 14 lbs.

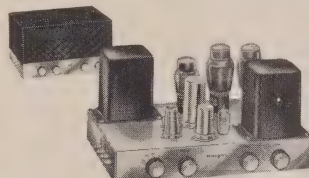Model S-753, Amplifier Kit. Net **\$23.50**
Model S-235, Preamp Kit for above **\$3.10**
S-757, Metal Enclosure. 3 lbs. **\$3.95**



knight-kit 20-WATT HI-FI AMPLIFIER KIT

Model S-750 Chrome-Plated Chassis
\$35⁷⁵
True hi-fi for less! Frequency response, ± 1 db, 20-20,000 cps at 20 watts. Distortion, 1% at 20 watts. Hum and noise level: tuner input, 90 db below 20 watts; phono 72 db below 20 watts. 4 inputs: magnetic phono, microphone, crystal phono or recorder, and tuner. Controls: Bass, Treble, Volume, Selector. With compensation positions for 78 and LP records. Built-in Preamp. Outputs: 4, 8, 16 and 500 ohms. 23 lbs.

Model S-750, 20-Watt Kit. Net **\$35.75**
S-758, Metal Enclosure. 3 lbs. **\$4.15**
S-752, Chrome-plated escutcheon for cabinet installation of amplifier. Net **\$1.40**

LOW-COST TOP QUALITY KITS FOR THE HAM



knight-kit

Model S-255 50-WATT CW TRANSMITTER KIT Built-in Pi-Type Antenna Coupler

\$43⁷⁵

Check the features packed into this new transmitter kit and you'll see why it's one of the greatest Amateur values ever offered. Compact and versatile, it is the perfect low-power rig for the beginning Novice or seasoned veteran. Features: 50 watts input to 807 final; high-efficiency 6AG7 modified-Pierce oscillator takes crystal or VFO without circuit changes; bandswitching coverage of 80, 40, 20, 15, 11-10 meters; pi-section antenna output matches line impedances from 50 to 1200 ohms — permits use with any type of antenna; no separate antenna tuner required. Clean, crisp, cathode keying of oscillator and final. Power take-off plug supplies filament and B-plus voltages for other equipment. Copper-finished chassis and cabinet interior, filtering, shielding, bypassing, and coaxial SO-239 antenna connector provide excellent TVI suppression. Meter reads either plate or grid current of final. Jacks for VFO, crystal and key. Supplied with all parts and tubes. Less crystal and key. $8\frac{1}{2} \times 11\frac{1}{4} \times 8\frac{3}{4}$ ". Shpg. wt., 18 lbs.

Model S-255, 50-Watt Transmitter Kit. Net **\$43.75**



knight-kit SELF-POWERED VFO KIT

Model S-725
\$28⁵⁰

Complete with built-in power supply! Careful design and voltage regulation assure high stability. Excellent oscillator keying characteristics for fast break-in without clicks or chirps. Full TVI suppression. Has plenty of bandspread: separate calibrated scales for 80, 40, 20, 15, 11 and 10 meters; vernier drive mechanism. 2-chassis construction keeps heat from frequency determining circuits. Output cable plugs into crystal socket of transmitter. Output on 80 and 40 meters. With Spot-Off-Transmit switch for "no swish" tuning. Extra switch contacts for operating relays and other equipment. With all parts and tubes. 8 lbs.

Model S-725, Self-Powered VFO Kit. Net. **\$28.50**



NEW knight-kit AMATEUR RF "Z" BRIDGE KIT

Model S-253
\$5⁸⁵

Measures standing wave ratio (SWR) and impedance of antenna systems; also for adjusting antenna networks for optimum results. Any VOM may be used for null indicator. High accuracy with 20,000 ohm/v VOM. Correction factor info supplied for other VOM's. With coax input and output connectors. Meters both input and bridge voltage. Calibrated dial gives direct impedance reading; includes 1% precision resistor for precise calibration adjustment. With all parts and handy plasticized SWR chart. $1\frac{1}{2}$ lbs.

Model S-253, "Z" Bridge Kit. Net only **\$5.85**

ALLIED RADIO

100 N. WESTERN AVE., CHICAGO 80, ILL.

Our
36th year

ALLIED RADIO CORP., Dept. O2-J-6, 100 N. Western Ave., Chicago 80, Ill.

Ship me the following KNIGHT-KITS:

Quantity	Description	Model No.	Price

\$ _____ enclosed. For parcel post include postage (express is shipped collect).

Name _____

Address _____

City _____ Zone _____ State _____

← *order Today*

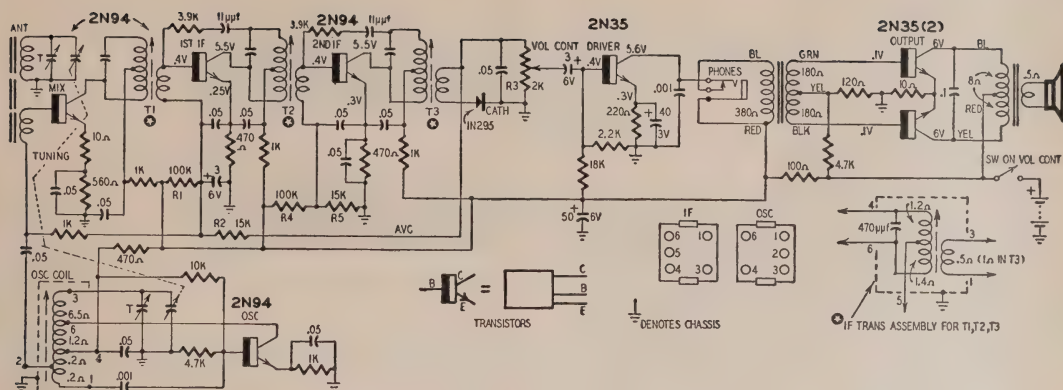


Fig. 4—Zenith model 500 Royal is a seven-transistor superheterodyne.

(Continued from page 92)

plainly marked on the dial. The case has a three-position handle. It can swing up for portable use, slide down to serve as a table support or hug the bottom of the case when placed in a pocket or purse.

Fig. 4 shows the schematic, with voltages indicated on if and af transistor elements. Note that the voltage on each n-p-n type reads higher on the base than on the emitter to permit conduction.

Separate transistors function as mixer and oscillator. The oscillator tuning capacitor is across the upper portion of the coil. Tap 4 (of the coil) is grounded for rf, placing it at emitter potential. Tap 6 connects to the collector. Terminal 1 connects to the base through a capacitor. This arrangement may be recognized as equivalent to a tapped Hartley which oscillates because it feeds base and collector out of phase; the intermediate tap is for the emitter.

The converter and first if are gain-controlled. In the absence of signal, both stages are biased from voltage divider R1-R2-R3 (volume control). On arrival of a signal, *negative* AVC voltage is fed into the base of each stage to reduce gain and prevent overloading. The second if stage is fixed-biased by R4-R5. Both if stages are neutralized, using both resistance and capacitance. Neutralization is between collector and base of the same stage.

A 1N295 diode detects and furnishes AVC (negative) voltage. The audio channel uses three 2N35 high-gain transistors. A jack provides an outlet for an earphone for private listening. There is no need to disconnect the output stage during this time because there is negligible drain by a class-B stage operating at zero signal.

Undistorted power output is 100 mw, with a maximum of 180 mw. The receiver has a sensitivity of 500 microvolts per meter for 50-mw output.

G-E models 675, 676

Both of these sets use five transistors, all of which are p-n-p except the detector. A single transistor operates as an oscillator-mixer. Another is the audio output stage which can deliver up to 40 mw at 10% distortion and an audio peak of 60 mw. The receivers (Fig. 5) are plate-wired.

V1 is the converter transistor. Mixing is done by a series connection of T1 (the antenna loop) and T2 (the oscillator coil). Inductive coupling between the base and collector windings generates the local oscillations. V1 is biased for detection (otherwise it cannot produce the desired if beat). This bias is set by voltage divider R1-R2-R3. A blocking capacitor prevents the coils from shorting R1.

Note the absence of neutralization. To make this possible V2 is operated at less than maximum voltage (13.5

volts) to stabilize it. The emitter is returned to a -4.5-volt tap rather than to ground directly or through a resistor. A nearly equal voltage drop is needed at the base, and this is generated in the larger series resistor R4 and the drop across R5. Some degeneration is introduced by omitting bypass capacitance across the 4.5-volt tap of the battery. In other words, collector current is bypassed to ground through C1. To return to the emitter it must flow *through the battery* to the -4.5-volt tap. There is no bypassing through this portion of the battery.

V3, also unneutralized, receives nearly full voltage since its emitter is directly grounded. In this stage regeneration is lowered by resistor R6 shunting the transformer secondary. R6 is normally 470 ohms. However, if regeneration occurs in spite of it, damping may be increased by using a still lower resistance; it should be as large as possible without producing instability.

V4 is biased for detection by the voltage divider, 47,000 and 220 ohms. High frequencies are bypassed through a .05- μ f capacitor, but audio appears across the volume control. Note the direct coupling to the output stage. While this means less than optimum matching, it is a convenient coupling method, and eliminates power losses in a transformer.

When V4 delivers greater output (as it does when the signal is stronger), a larger *negative* drop appears across the volume control since the detector is p-n-p. Thus V5 (a p-n-p type) is driven to greater conduction so it can handle the greater signal impressed on it.

Tuning and alignment are as specified on the diagram. First, adjust the if transformers, starting with the last and working forward. Couple the signal generator loosely to the high end of the antenna loop. Now the high-frequency end of the broadcast band may be aligned, then the low-frequency end. Repeat the alignment if it proves necessary.

TO BE CONTINUED

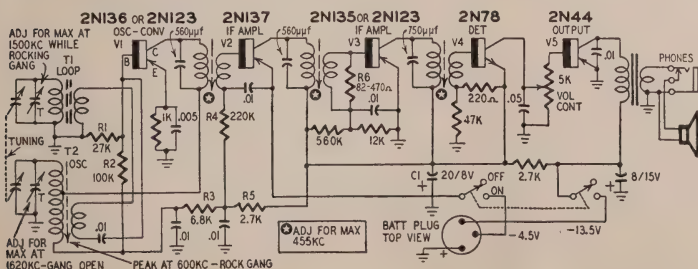


Fig. 5—General Electric models 775 and 676 use five transistors.

Phase-Shift Chart

By H. P. MANLY

Nomogram provides rapid calculation of impedance effects in series circuits

PHASE shift is important in automatic frequency control, synchronized sweep, tone correction, chrominance and color oscillator sections—to mention only a few of its applications in modern electronics. Phase-shift circuits consist of capacitors or inductors or both, and usually resistors, in series or parallel combinations.

The number of degrees by which voltage across a series resistor is shifted with reference to the source voltage varies with the amounts of resistance, capacitance or inductance and operating frequency. Problems are simplified by combining capacitance or inductance, and frequency, in a single term—reactance, at the operating frequency. Knowing ohms of reactance and ohms of resistance we may read phase shifts in degrees for any series circuit on the chart of Fig. 1.

On the chart are sloping lines for phase shifts of 0 to 90° at intervals of 5°. The resistance and reactance scales may be multiplied or divided by any number, but both by the *same* number, to bring them into a range for any resistance and reactance in a problem. Reactance for any capacitance and frequency may be read directly from alignment charts in the December, 1955, issue of RADIO-ELECTRONICS or both capacitive and inductive reactances may be computed from formulas at the end of this article.

Here are the rules:

1. Phase difference between voltage across a resistor and voltage across either a capacitor or inductor in series always is 90°.

2. With only capacitance and resistance in series the resistor voltage *leads*

source voltage, capacitor voltage *lags* source voltage.

3. With only inductance and resistance in series the resistor voltage *lags* and inductor voltage *leads* source voltage.

4. With capacitance, inductance and resistance in series it is necessary to determine the separate capacitive and inductive reactances, then take their difference as the net reactance for use on the chart. Consider the net as capacitive if capacitive reactance is the larger, inductive if inductive reactance is the larger.

To illustrate how phase shift is read assume, as in Fig. 2, 5,000 ohms resistance and 1 μ f capacitance in series, at 60 cycles. Capacitive reactance may be determined from an alignment chart as about 2,600 ohms. Mentally we multiply the resistance and reactance scales of the phase-shift chart by 100, then go to 5,000 ohms along the resistance scale and down to a point opposite 2,600 ohms on the reactance scale.

At the intersection for resistance and reactance we read on the angle lines and their scale that voltage across the resistor leads the source voltage by about 27°. Since the difference between resistor and capacitor voltages always is 90°, the capacitor voltage in this problem must lag the source voltage by 90–27° or 63°.

In Fig. 3 we have a fixed resistor of 1,000 ohms, an adjustable resistor of 10,000 ohms and a capacitor of .033 μ f in series, at 1,000 cycles. What will be the limits of phase shift when adjusting the 10,000-ohm resistor through its range? For an alignment chart we read about 4,800 ohms capacitive reactance for .033 μ f at 1,000 cycles. Spot-

ting the intersections for 1,000 ohms minimum resistance and for 11,000 ohms maximum resistance along the reactance line for 4,800 ohms on the phase-shift chart shows the total shift will be from about 23.5 to 78°.

Voltage phase across a resistor may be shifted with respect to source voltage by a variable capacitor in series with the resistor. In Fig. 4 we assume a 150–650- μ f mica trimmer in series with a 47,000-ohm fixed resistor and a 10-kc source. From the alignment chart for capacitance we read reactance of about 100,000 ohms for 150 μ f at 10 kc, about 25,000 ohms for 650 μ f. On the phase-shift chart we spot intersections for these two reactances along a vertical line for resistance of 47,000 ohms and on this line read the limits of phase shift as 28° for maximum and 65° for minimum capacitance.

In Fig. 5 we have 250 mh inductance and .01 μ f capacitance in series with a 10,000-ohm resistor at 5 kc. This requires determining both kinds of reactance and taking their difference. From an alignment chart we read capacitive reactance as about 3,100 ohms for .01 μ f at 5 kc. Computing the inductive reactance from a formula gives 7,860 ohms for 250 mh at 5 kc. The difference is 4,760 ohms of net reactance, inductive because the inductive reactance is greater than the capacitive reactance.

Spotting the intersection for 10,000 ohms resistance and 4,760 ohms reactance on the phase-shift chart indicates a shift of slightly more than 25°. Voltage across the resistor lags source voltage because the net reactance is inductive.

If there is any confusion as to

The Book that Launched Thousands of Careers is yours FREE in a new edition

TELLS HOW YOU CAN BE SUCCESSFUL IN RADIO-TV-ELECTRONICS

Send for Your Free Copy Today!



Brand New Edition Now Available

Brings you completely up to date—answers important questions on newest career developments in Electronics—including Radar, Guided Missiles, Servomechanisms, Computers, as well as Aeronautical Electronics, Broadcasting (AM, FM, TV), Military, Navy and CAA Electronics, Communications and Electronics Manufacturing.

YOU CAN PLOD ALONG for years, getting paltry increases, enjoying little security, finding your work dull and drab.

Then something happens. Things look up. Your earnings rise.

"Luck," some may say. "Contacts," others may suggest.

But in your heart, you will know the answer: "Training." And it all may have started the moment you sent for a free booklet, "Your Future in the New World of Electronics." This booklet tells you where you stand in Electronics.

Tremendous expansion leaves this gigantic industry pleading for trained men. Top manufacturers sold billions of dollars worth of electronic merchandise in 1955. By 1960, the radio-electronics industry should do no less than 15 billion dollars per year, not counting military orders.

Today, there are over 132,000,000 radios in use. There are 38,000,000 TV sets and 477 TV stations in operation. Color TV is coming into high gear. Countless positions must be filled—in development, research, design, production, testing and inspection, manufacture, broadcasting, telecasting and servicing. To fill these posts, trained men are needed—men who somewhere along the line take time to improve their knowledge, their skills. Men who, today, perhaps, take two minutes to send for a booklet.

"Your Future in the New World of Electronics" shows how CREI Home Study leads the way to greater earnings through the inviting opportunities described above.

However, CREI does not promise you a "snap." With an accredited technical course such as this, you

must *study* to convert your ambition into technical knowledge you can sell in the fabulous Electronics market.

Since 1927, CREI has provided thousands of professional electronics men with technical educations. During World War II CREI trained thousands for the Armed Services. Leading firms choose CREI courses for group training in electronics, among them United Air Lines, Canadian Broadcasting Corp., Trans-Canada Airlines, Douglas Aircraft Co., Glenn L. Martin Co., Columbia Broadcasting System, All-American Cables and Radio, Inc., Gates Radio Co., Canadair Ltd., Federal Electric Corp. and U. S. Information Agency (Voice of America).

CREI courses are prepared by recognized experts, in a practical, easily understood manner. You get the benefit of time-tested study assignments, of personal supervision of a CREI Staff Instructor who *knows* and *teaches* you what industry wants. You learn on your own time, during hours selected by you. This complete training is the reason graduates find CREI diplomas keys-to-success in Radio, TV and Electronics. CREI alumni hold top positions in America's leading firms. CREI's Placement Bureau finds better positions for ad-

vanced students and graduates. Although CREI does not guarantee jobs, requests for personnel far exceed current supply.

Now is the time of decision. Luck will not propel you forward unless it finds you trained. Contacts won't budge you an inch unless you have the skill to back them up. The answer is: Technical Training... and willingness to learn. Together they will bring you increased earnings in this new Age of Electronics. Fill out the postage-free reply card and mail it now. We'll promptly send you your free copy of "Your Future in the New World of Electronics." The rest—your future—is up to you.

MAIL THIS POSTAGE-FREE POSTCARD TODAY

CAPITOL RADIO ENGINEERING INSTITUTE

ECPD Accredited Technical Institute Curricula

Dept. 149-C

3224 16th St., N. W., Washington 10, D. C.

(R. N. Oct., 56)

BA

Please send me your course outline and **FREE** Illustrated Booklet "Your Future in the New World of Electronics"... describing opportunities and CREI home study courses in Practical Electronic Engineering.

CHECK
FIELD OF
GREATEST
INTEREST

- ☐ Practical Radio Electronics Engineering
☐ Broadcast Radio Engineering (AM, FM, TV)
☐ Practical Television Engineering
☐ Practical Aeronautical Electronics Engineering

Name _____ Age _____

Street _____

City _____ Zone _____ State _____

Check: ☐ Home Study ☐ Residence School ☐ Veteran

To help us answer your request intelligently, please give the following information:

EMPLOYED
BY _____

TYPE OF
PRESENT WORK _____

SCHOOL
BACKGROUND _____

ELECTRONICS
EXPERIENCE _____

IN WHAT BRANCH OF ELECTRONICS
ARE YOU MOST INTERESTED?

MAIL THIS
POSTAGE-FREE
POSTCARD TODAY

See Our Ad On The Next Page

CREI prepares you quickly for success in

The future is in your hands!

The signs are plain as to the future of the trained men in the electronics industry. It is a tremendous industry, and—at the *present time* there are more jobs than there are trained men to fill them. But—when there's a choice between a trained and untrained applicant, the trained man will get the job. Your biggest problem is to decide on—and begin the best possible training program.

**CREI Home Study . . .
The Quick Way to Get There.**



Since 1927, CREI has given thousands of ambitious young men the technical knowledge that leads to more money and security. The time-tested CREI procedure can help *you*, too—if you really want to be helped. CREI lessons are prepared by experts in easy-to-understand form. There is a course of instruction geared to the field in which you want to specialize. You study at *your* convenience, at *your* rate of speed. Your CREI instructors guide you carefully through the material, and grade your written work personally (not by machine).

Industry Recognizes CREI Training.

CREI courses are prepared, and taught with an eye to the needs and demands of

industry, so your CREI diploma can open many doors for you. Countless CREI graduates now enjoy important, good-paying positions with America's most important companies. Many famous organizations have arranged CREI group training for their radio-electronics-television personnel. To name a few: All American Cables and Radio, Inc.; Canadian Broadcasting Corporation; Columbia Broadcasting System; Gates Radio Company; Hoffman Radio Corporation; Federal Electric Corporation; Glenn L. Martin Company; Douglas Aircraft Co.; Pan American Airways, Atlantic Division; U.S. Information Agency (Voice of America); Canadair Limited; Trans-Canada Air Lines; United Air Lines. Their choice for training of their own personnel is a good cue for *your* choice of a school.

Benefits Felt Right Away.

Almost immediately you feel the benefits of CREI training. Your employer, when informed of your step toward advancement (only at your request), is certain to take new interest in you and in your future. What you learn in CREI Home Study can start helping you do a better job immediately.

- **RADAR**
- **GUIDED MISSILES**
- **SERVO-MECHANISMS**
- **COMPUTERS**
- **AERONAUTICAL ELECTRONICS**
- **BROADCASTING, AM, FM, TV**
- **MILITARY, NAVY, CAA ELECTRONICS**
- **COMMUNICATIONS**
- **ELECTRONICS MANUFACTURING**

CREI also offers Resident Instruction

at the same high technical level—day or night, in Washington, D. C. New classes start once a month. If this instruction meets your requirements, check the coupon for Residence School catalog.

PAYS FOR ITSELF QUICKLY. Your very first raise could repay your investment in CREI training, and leave you a profit the very first year. Your increases in pay thereafter are all pure profit, and you'll be prepared for many more promotions and pay raises in the future years of your life.



From San Francisco Examiner, April 1, 1956

Industry Calls for CREI Training by Name . . . So Should You!

Here you see an actual help-wanted ad, one of many which specify "CREI or equal" training. This proves that industry approves CREI training, even insists on it!

Send card today for this fact-packed booklet. It's free.



Take 2 minutes to send for this booklet right now. We'll promptly send your copy. The rest—your future—is up to you.

1st Class

Permit No. 288-R

Sec. 34.9 P.L.R.

Washington, D. C.

BUSINESS REPLY CARD

No Postage Stamp Necessary If Mailed in United States

3c Postage Will Be Paid By

CAPITOL RADIO ENGINEERING INSTITUTE

3224 16th Street, N.W.

Washington 10, D. C.

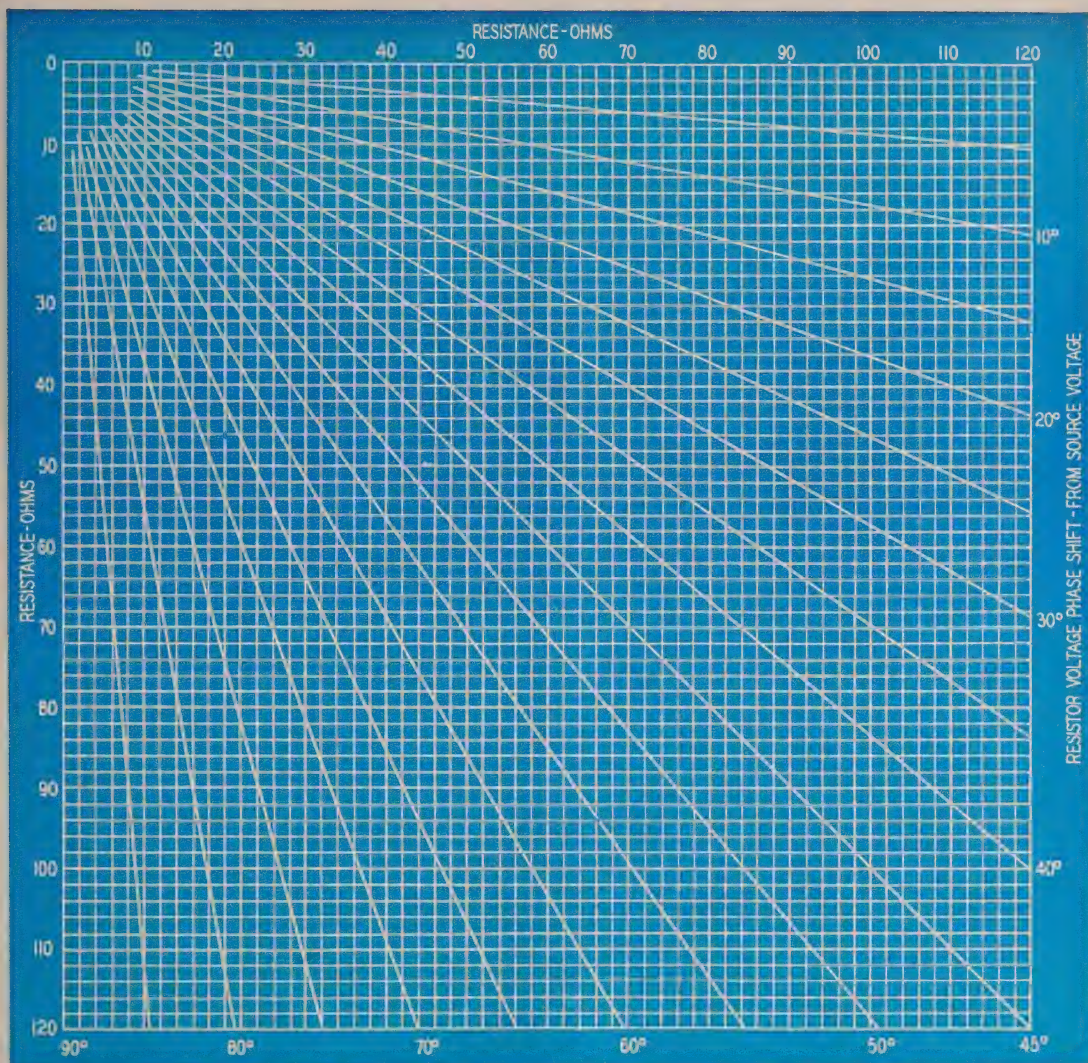


Fig. 1—Phase-shift chart for computing voltage lead or lag in circuits containing resistance, inductance and capacitance.

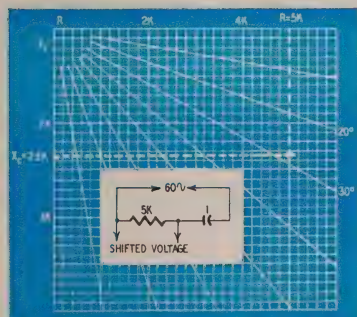


Fig. 2, above—A simple R-C series circuit.

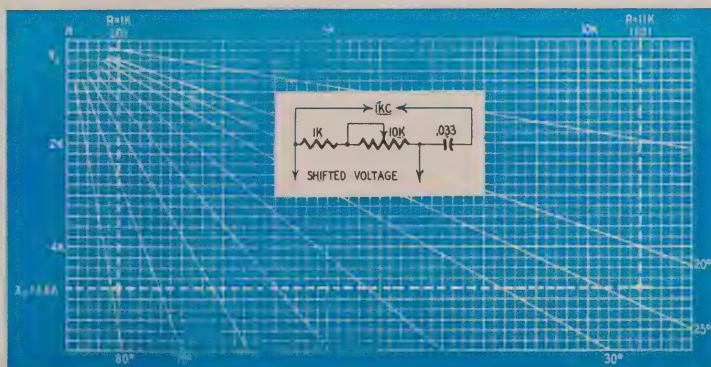


Fig. 3, right—R-C circuit with potentiometer.

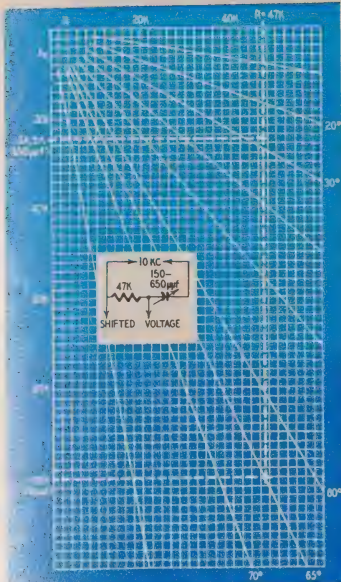


Fig. 4—Resistor and variable capacitor.

whether one voltage leads or lags some other voltage, look at it this way. The resistance line across the top of the phase-shift chart represents voltage across the resistor. The reactance line down the left-hand side represents voltage across a capacitor or inductor. Any diagonal line drawn from zero to an intersection represents source voltage.

As in Fig. 6, all these lines are to be considered as rotating together counterclockwise around the zero point as a center, but without changing their relative positions. If, during this rotation, some voltage line would arrive at any given point around the circle before another voltage line, the first voltage is leading the second—it gets there first. Of course, the second voltage is lagging the first one—it gets there later.

Color problems

The phase-shift chart may be used for solving problems in chrominance and color oscillator sections of color TV receivers. Chrominance signals, their components and phase relations often are shown as in Fig. 7, where are marked the values for two problems to be solved with the phase-shift chart.

The first problem (Fig. 8) is to put together two color-difference signals and find the resultant chrominance signal. The color-difference signals consist of 51.5 voltage units of $-(R-Y)$ and 28.5 voltage units of $-(B-Y)$. Since color-difference signals are in quadrature (separated by 90°) we may place them on our phase-shift chart as shown. The resultant is a line drawn from zero to the intersection. This line lags the $-(R-Y)$ voltage by about

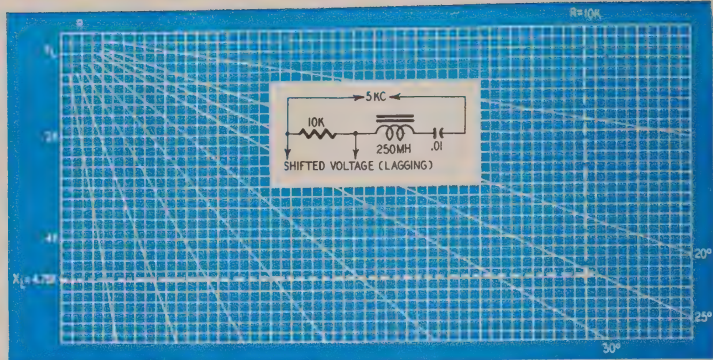


Fig. 5—Graph of circuit containing inductance, capacitance and resistance.

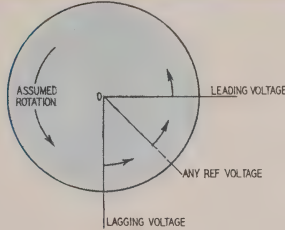


Fig. 6—Relationship of ac voltages.

29° and, of course, leads the $-(B-Y)$ signal voltage by the difference between 90° and 29°, 61°. On a color-phase chart such as that of Fig. 6 we would identify this resultant as a chrominance signal for green.

Reversing the procedure, we may commence with a chrominance signal voltage for some known color and determine the color-difference signals from which it is formed. Fig. 9 represents an orange chrominance signal of 60 voltage units strength lagging the $-(B-Y)$ signal or reference phase by 50°. On the phase-shift chart we spot a point which is 60 units distant from zero and on the 50° radial line. Following upward from this point we come to 38 units on the $-(B-Y)$ axis, and following to the left we come to 46 units on the $R-Y$ axis. Thus we learn that the orange chrominance signal is the resultant of 38 units of $-(B-Y)$ voltage combined with 46 units of $R-Y$ voltage.

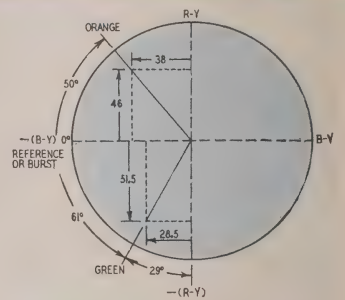


Fig. 7—Color TV phase relationships.

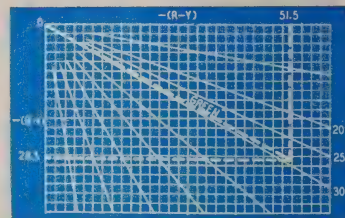


Fig. 8—Finding resultant color signal.

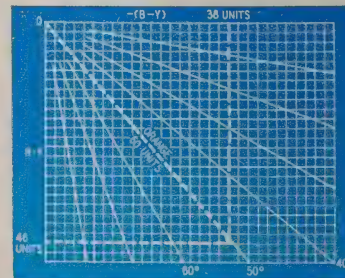


Fig. 9—Finding components of signal.

Reactance Formulas

Capacitive reactance, ohms

$$X_c = \frac{160,000}{\text{cycles} \times \mu f}$$

$$X_c = \frac{160}{\text{kc} \times \mu f}$$

$$X_c = \frac{160,000,000}{\text{kc} \times \mu \mu f}$$

$$X_c = \frac{0.160}{\text{mc} \times \mu f}$$

$$X_c = \frac{160,000}{\text{mc} \times \mu \mu f}$$

Inductive reactance, ohms

$$X_L = \text{cycles} \times h \times 6.28$$

$$X_L = \text{cycles} \times mh \times .00628$$

$$X_L = \text{kc} \times mh \times 6.28$$

$$X_L = \text{kc} \times \mu h \times .00628$$

$$X_L = \text{mc} \times \mu h \times 6.28$$

END



Pyramid Division / New York



HE PROVED IT FOR HIMSELF!

The new Pyramid Imp is smaller, yet better than any other molded paper tubular capacitor; Operates at full rating of 100°C (212°F—boiling point); Exceeds moisture resistance requirements of U. S. Government specifications MIL-C-91A; Copperweld leads are securely imbedded to withstand 4 360° bends without breaking.

These features, plus an almost indestructible thermo-setting plastic encasement make Pyramid Imps your best molded paper tubular capacitor.

For full information on Pyramid capacitors and rectifiers, see your local distributor or write to




DISTRIBUTOR DIVISION

PYRAMID ELECTRIC COMPANY

1445 Hudson Blvd., North Bergen, N. J.

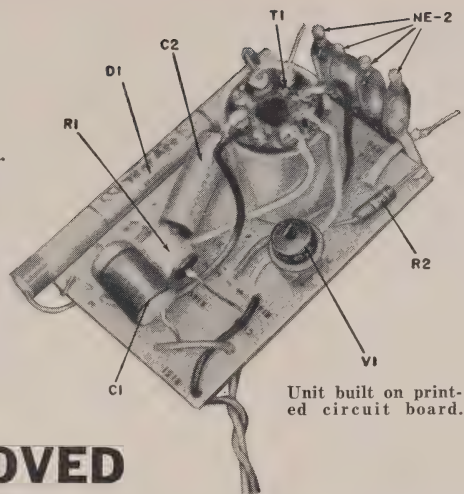*Transistor-oscillator
type unit
is smaller and
more efficient*



Unit built on printed circuit board.

IMPROVED SUPPLY POWERS G-M COUNTER

By THOMAS G. KNIGHT

HERE is an improved version of the power supply used in the Transistor-Operated Geiger Counter (RADIO-ELECTRONICS, April, 1956).

Improvements include much smaller physical size, increased power efficiency and replacement of the vacuum-tube diode by a selenium rectifier. An off-the-shelf transformer eliminates hand winding required in the original. The present low cost of transistors makes construction of this power package even more attractive than when the original model was devised.

Fig. 1 is a schematic of the unit. A tapped primary winding on the high-voltage stepup transformer is used instead of a separate feedback winding. The transformer is a UTC Ouncer type O-2 (line to grid) with only half of the primary used. Oscillation is guaranteed with the connections shown, there being no ambiguity as to the polarity of feedback pulses. If the primary terminals are not connected as shown, the unit will not oscillate and the transistor may be damaged. If the secondary output connections are changed from those shown, capacitive loading of the output voltage (by the internal-winding capacitance of the transformer) will lower the voltage.

The selenium-rectifier polarity must also be correct to rectify the highest-amplitude pulses. The selenium rectifier (type S3Y30PL) is manufactured by and available from the Union Switch & Signal Co., Swissvale, Pa., at a cost

of \$1.05. It is a very small ($\frac{1}{4}$ -inch diameter) high-efficiency type. Extremely high back (inverse) resistance and good forward conductance result in very efficient operation.

Four NE-2 neon bulbs in series with a 4.7-megohm resistor make up the voltage regulator; filtering is handled by a .01- μ f capacitor.

Any high-voltage half-wave rectifier, including vacuum diodes or selenium rectifiers, will work with the improved high-voltage power supply, provided the peak inverse voltage rating is high enough (at least 1,000). If selenium rectifiers are used, their reverse current must be very low, about 1 microampere or less, for the power supply to deliver peak voltage. This requires a good-quality selenium stack of at least 30 cells in series. Of course, vacuum diodes such as the Victoreen 5799 or Sylvania 5785 may also be used with practically zero reverse current. However, the necessity for heating the filament is a real disadvantage. Cold-cathode gas diodes such as the 5517 or CK1013 are not recommended due to a 100-volt drop across the diode which lowers the available useful voltage output of the power supply.

High-voltage low-current selenium rectifiers are the best choice due to their small size, efficient operation and long life. I have found that selenium stacks of 30 (or more) 26-volt cells and 2.5-ma current rating are best. More than 30 cells in series reduces the reverse current and raises the useful output volt-

age. However, a penalty is paid in longer length and higher cost.

Conventional 135-volt 50- to 75-ma selenium rectifiers may work but six or more are needed in series (increasing cost) and their distributed capacitance and size are excessive.

The S3Y30PL symbol represents a $\frac{1}{4}$ -inch-diameter Bakelite tube 1 $\frac{11}{16}$ inches long containing 30 2.5-ma cells in series. An axial wire lead $1\frac{1}{2}$ inches long extends from each end of the tube. This rectifier is rated at 390 volts rms for a capacitor-input filter and has a 1,080 peak inverse voltage rating. It will deliver 2.5 ma of dc. However, in this power supply it is called upon to deliver only 3 or 4 microamperes.

Primary power may be drawn from any 6-volt source. Current drain at 6 volts input is under 2 ma. At this rate 4 penlight cells (size AA) will operate the unit continuously for well over 200 hours. For normal field use, as in a Geiger counter, say for 6 hours of operation per day 5 days a week, these same 4 cells should provide over 10 weeks of operation. And batteries can be replaced for only a few pennies! Mercury batteries or larger dry cells will provide even longer operation. This power unit is constructed on a printed-circuit card.

The transistor-oscillator type power source has many advantages over conventional types such as 300-volt dry batteries (too expensive) and vibrators (too inefficient besides generating radio-

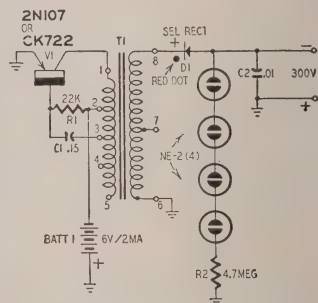


Fig. 1—The high-voltage power supply.

frequency interference). In fact, I have this power pack with a Geiger tube built into a portable radio-Geiger counter combination. Both functions may be performed at the same time, the output of the Geiger tube being fed into the antenna of the portable receiver (Fig. 2)! This feature may also be used with a car radio (any radio in fact), thus permitting testing of rock samples for radioactivity.

After the unit is wired up, correct operation will be indicated by a steady or flashing glow of the neon bulbs a few seconds after power is applied.

Power output, though minute, is sufficient to operate from one to a dozen or more 1B86 counter tubes in parallel.

The case of the transformer may be grounded if necessary. However, it is

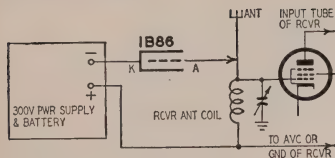


Fig. 2—Setup for feeding signals from geiger tube to receiver antenna circuit.

best left floating with respect to ground to minimize capacitance to ground.

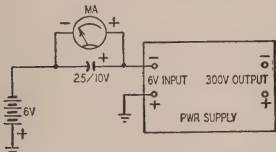


Fig. 3—Measuring the current gain.

The only problem that may confront the constructor is the choice of R1 and C1 in the oscillator circuit. The values shown should operate in most cases. Slight variations in transformer characteristics may make it necessary to use other values. If the output is too low at 6 volts, 2-ma input, increase or decrease the value of C1.

Incidentally, when inserting a meter in the battery leads to measure current drain, it is necessary to bypass the meter with a 25- μ f (or larger) electrolytic capacitor to neutralize the meter inductance (Fig. 3). If the input current is not between 1½ and 2 ma, increase R1 if current is low and decrease it when current is high. Where necessary choose values of C1 and R1 so that with 2-ma battery input current, the neon bulbs emit a steady light or fast flashing rate (approximately 10 or more flashes per second).

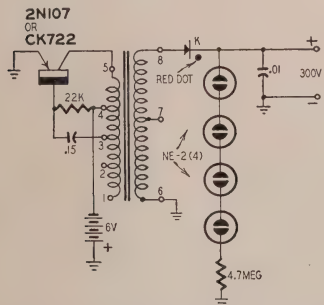


Fig. 4—A positive-voltage supply.

Parts for power supply

R1—22,000 ohms, ½ watt (see text); R2—4.7 meg-ohms, ½ watt; C1—0.15 μ f (see text); C2—0.1 μ f, 600 volts; V1—2N107 or CK722 transistor; BATT 1—4 penlight cells or equivalent; T1—UTC O-2 oncuer; D1—selenium rectifier (see text); 4 NE-2 neon lamps; I sheet of Bakelite or insulating board.

This particular circuit generates the high voltage with the positive side grounded. To furnish a negative high-voltage ground it is necessary to connect the transistor, rectifier and transformer as in Fig. 4.

END

TECHNICIANS: ARE YOU NOW QUALIFIED FOR ENGINEERING WORK?

THEN HERE IS YOUR OPPORTUNITY FOR
AN ENGINEERING ASSIGNMENT WITH
THE RCA SERVICE COMPANY!

... And you'll be eligible for educational benefits through RCA's liberal Tuition Refund Plan, a real boost toward that actual engineering education you're interested in! Many other company-paid benefits, of course. Excellent starting salaries • pleasant suburban locations • relocation expenses paid.

Which of these engineering fields do you prefer?

- Missile Electronics
- Navigational Aids Planning & Design
- Naval Electronic Systems Installations Planning
- Specifications Engineering Writing

ARRANGE FOR CONFIDENTIAL INTERVIEW WITH
REPRESENTATIVES OF RCA ENGINEERING MANAGEMENT
AT A LOCATION CONVENIENT TO YOU

Please send complete resume to:

Mr. John R. Weld
Employment Manager, Dept. Y-8J
Radio Corporation of America
Camden 2, New Jersey




RCA SERVICE CO., INC.


PHOTOELECTRIC LIGHT COMPUTER

By JOHN R. SATTER

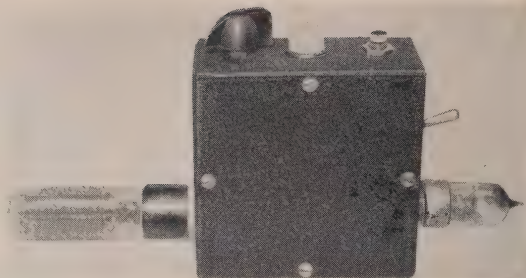*Handy device
for photographic
darkroom use*



The complete photoelectric unit.

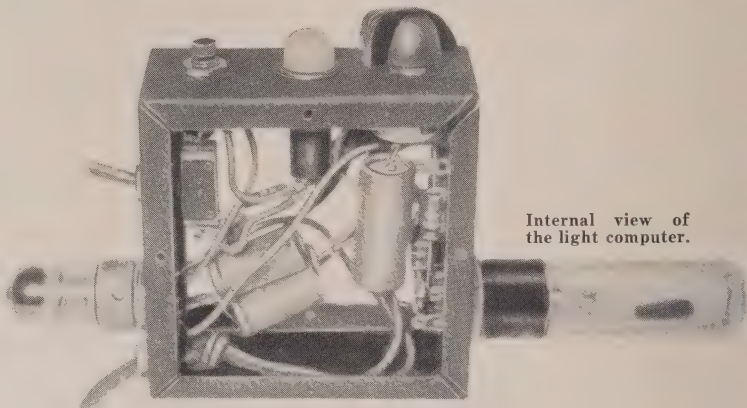

Internal view of the light computer.

THE most time-consuming part of darkroom work is making test strips to find the proper exposure time for each negative. With this computer, test strips are banished forever from your darkroom. It will, at the flick of a finger, let you determine exactly how much light is striking your enlarging easel, regardless of negative density or the size of the enlargement.

By using a high-gain vacuum tube this instrument is much more sensitive than light meters available for general use. And, since no expensive microammeter is necessary, the cost of parts is limited to approximately \$10—less if the constructor has an electronic junkbox available. Eyestrain is at a minimum since the indicator is an illuminated bulb rather than a meter, most difficult to read by the light in a darkroom during enlarging operations.

To keep the weight of the computer to a minimum, no filament transformer is used. Instead, a 3- μ f paper capacitor is the filament dropping reactor. Consuming no power in itself, there is no heat generated as with a resistor, and power consumption of the instrument is limited to approximately 2 watts. Layout of parts and the method of wiring is not critical.

Operation and application


When the pushbutton switch is depressed, plate voltage is applied to V1-a, causing plate current to flow. The magnitude of the plate current depends upon the bias, set by the

potentiometer in the cathode circuit. If the potentiometer is set so that the neon bulb across the plate load resistor is just extinguished in total darkness, the unit will be most sensitive. The phototube conducts more current as the light falling on its cathode becomes brighter, thereby reducing the bias and allowing more plate current to flow in V1-a. More current flow produces a larger voltage drop across the plate load resistor. This continues until the voltage drop is great enough to fire the neon lamp.

To calibrate, make an enlargement at some convenient exposure time in the usual way. Then, with the phototube placed on the easel under the darkest portion of the projected negative image, adjust the potentiometer so that the neon bulb is just extinguished. Thereafter it is necessary only to place the phototube over the darkest portion of any projected image and close the enlarging lens diaphragm until the neon bulb is just extinguished. With the same predetermined exposure, all the brightest portions of the positive prints will have the same tone.

The light computer may also be used to judge the contrast of paper required for a given negative by noting the difference between positions of the bias adjustment for the lightest and darkest portions of a projected negative image. The greater the bias difference needed to extinguish the lamp, the greater is the contrast of the negative and the softer the paper contrast required.

Exposure time may also be indicated

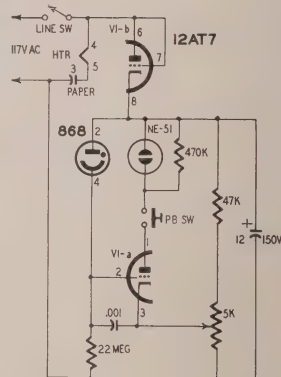

Schematic of the light computer.

Parts for light computer

1—47,000, 1—470,000 ohms, 1—22 megohms, 1/2 watt, resistors; 1—5,000-ohm potentiometer, 2 watts; 1—.001, 1—3 μ f, paper capacitors; 1—12- μ f 150-volt electrolytic capacitor; 1—12AT7 and socket; 1—868 phototube and socket; 1—NE-51 and socket; 1—spst pushbutton switch; 1—spst switch; 1—metal box, approximately 4 x 4 x 2 inches; 1—line cord; 1—knob.

using the same principles set forth above.

The pushbutton switch should never be operated with normal room lights on; doing so will overload the neon bulb. The darkroom light should also be shaded from the enlarging easel or erroneous readings may result. After an evening of use this instrument will become an indispensable part of your darkroom equipment.

END

Technicians' News

GUILD PLANS EXHIBIT

A brochure issued by the Radio & Television Guild of Long Island (N. Y.) indicates that plans for the Long Island Electronics Fair have reached the concrete stage. Exhibitors are offered an unobstructed space of 90 x 130 feet in a building which forms part of the State University of New York at Farmingdale. Fifty-one booths are planned for the hall, and an antenna system covering all local TV channels is being set up for exhibitors as well as a closed-circuit system which will carry color signals during exhibit hours. Plans for technical lectures and other activities are being made but had not been published at the time of writing.

TV SERVICING ENDED

A new circular slide-rule type of device (see photo below) makes the set owner his own troubleshooter, according to a New Jersey company selling the device. Prepared for the man who found the fix-it-yourself books popular a few years ago too difficult, it has a number of pictures showing screen defects. These are distributed around a revolving outer dial, and it is necessary only to turn the picture with the fault to the index point to establish the tubes at fault and the adjustments to be made. To aid in adjustments, the rear of a "typical" chassis is shown so Mr. Set Owner will know where to reach for his width control and where

for the centering or focus. There is even a drawing to drive home the point that miniature tube pins should go in the corresponding socket holes when replacing tubes.

The owner then "removes the tubes, has them tested and replaces them and his set is working like new again."

100 FIRMS SUPPORT CODE

A nine-point code to govern TV service companies' advertising tactics has been subscribed to by more than 100 firms in the Memphis, Tenn., area, according to George V. Morse, Jr., manager of the Memphis Better Business Bureau.

Firms are pledged, among other things to: make no extremely low-price quotations on service calls, make no discount offers for a first service call, to issue no coupons entitling the holder to special service discounts, to avoid underselling or underpricing claims and to make no statements disparaging to competitors.

Some 300 complaints and inquiries on TV service have been received by the Memphis BBB during the first five months of this year, Mr. Morse said. Most of the complaints were based on the cut-price call, which economical set-owners found extremely expensive in the long run.

Mr. Morse stated radio and TV were in seventh place among the categories most active from the standpoint of the BBB.



COMPLETE TRAINING FOR BETTER RADIO-TV SERVICE JOBS



Let these two great new Ghirardi training books teach you to handle all types of AM, FM and TV service jobs by approved professional methods—and watch your efficiency and earnings soar!

Completely modern, profusely illustrated and written so you can easily understand every word, these books pave the way to fast, accurate service on any type of home radio-TV-electronic equipment ever made. Each book is brand new. Each contains the latest data on the latest methods and equipment—NOT a rehash of old, out-of-date material. Each is co-authored by A. A. Ghirardi whose famous RADIO PHYSICS COURSE and MODERN RADIO SERVICE were, for 20 years, more widely used for military, school and home study training than any other books of their type!

THE NEW Ghirardi

RADIO-TV SERVICE LIBRARY

Almost 1500 pages and over 800 clear illustrations show step-by-step how to handle every phase of modern troubleshooting and servicing.

1—Radio and Television Receiver TROUBLESHOOTING & REPAIR

A complete guide to profitable professional methods. For the novice, it is a comprehensive training course. For the experienced serviceman, it is a quick way to "brush up" on specific jobs, to develop improved techniques or to find fast answers to puzzling service problems. Includes invaluable "step-by-step" service charts. \$20 pages, 417 illus., price \$6.75 separately.

2—Radio and Television Receiver CIRCUITRY AND OPERATION

This 689-page volume is the ideal guide for servicemen who realize it pays to know what really makes modern radio-TV receivers "tick" and why. Gives a complete understanding of basic circuits and circuit variations: how to recognize them at a glance; how to eliminate guesswork and useless testing in servicing them. 417 illus. Price separately \$6.50.

New low price... You Save \$1.25!

If broken into lesson form and sent to you as a "course," you'd regard these two great books as a bargain at \$50 or more! Together, they form a complete modern servicing library to help you work faster, more efficiently and more profitably.

Under this offer you buy them both for only \$12.00. You save \$1.25 on the price of the two books—and have the privilege of paying in easy installments while you use them.

10-DAY FREE TRIAL

Dept. RE-96, RINEHART & CO., Inc.
232 Madison Ave., New York 16, N.Y.

Send books below for 10-day FREE EXAMINATION. In 10 days, I will either remit price, (plus postage) or return books postpaid and owe you nothing.

☐ Radio & TV Receiver TROUBLESHOOTING & REPAIR (Price \$6.75 separately)

☐ Radio & TV Receiver CIRCUITRY & OPERATION (Price \$6.50 separately)

☐ Check here for MONEY-SAVING COMBINATION OFFER... Save \$1.25. Send both of above big books at special rate of only \$12.00 for the two. (Regular price \$13.25... you save \$1.25.) Payable at rate of \$3 (plus postage) after 10 days if you decide to keep books and \$3 a month for 3 months until \$12 has been paid.

Name

Address

City, Zone, State

Outside U.S.A.—\$7.25 for TROUBLESHOOTING & REPAIR; \$7.00 for CIRCUITRY & OPERATION; \$13.00 for both books. Cash with order, but money refunded if you return books in 10 days.

NEW

PHAOSTRON PROBE-LITE

ILLUMINATED TEST PROBE
SELF-CONTAINED
SEE WHAT YOU ARE TESTING!

\$250
LIST

It is just like having an extra hand. Simply insert the probe from your tester into the jack of the Probe-lite and the Probe-lite becomes alive to instantly give you a brilliant, pre-focus spotlight on the area that you are testing plus a long, extra slender, probe tip for making electrical contact in difficult places which previously were inaccessible. It could pay for itself the first time you use it.

GET A FREE PROBE-LITE

If you are the fortunate owner of a Phaostron "555" or "555A" VOM, we will send you a Probe-lite free. Mail us the warranty page you will find in your instruction manual. We will send you a new Probe-lite and return your warranty. Be sure you include your correct name and address.

This offer is good until October 1, 1956.



PHAOSTRON

PHAOSTRON INSTRUMENT & ELECTRONIC CO., 151 Pasadena Avenue, South Pasadena, Calif.

TECHNICIANS' NEWS

(Continued)

NATESA CONVENES SEPT. 14

The annual convention of the National Alliance of Television & Electronic Service Associations will be held at the Sheraton Hotel, Chicago, Sept. 14-16. It will undoubtedly be the largest NATESA has held and the business to come before the delegates will include some of the most important the organization has ever handled.

A full program of lectures and demonstrations—so timed as to be compatible with the business meetings—will cover both the technical and business problems of the service operator. Entertainment has not been overlooked and an interesting time is promised to all.

NEW MID-STATES GROUP

Technicians from High Point, Greensboro and Winston-Salem, N. C., met June 14 to lay the groundwork for an association of TV-radio service shops in the central part of the state. The group will be known temporarily as the Tri-City Technicians' Association. Officers elected for a three-month period are Jim Hornaday, High Point, president; Van Sickles, Winston-Salem, vice president; Joe Woods, Greensboro, secretary; C. B. Steele, Greensboro, treasurer. It is hoped that the group may serve as the basis for a state-wide organization, and to that end all full-time shops in the area—not merely the three cities—have been invited to join and a monthly schedule of meetings has been set up. All interested are asked to communicate with Joe Woods, 1708 Spring Garden St., Greensboro, N. C.

12% OF SERVICE IN N. Y.

Preliminary reports of the census of business conducted by the U. S. Bureau of the Census, indicate that as of 1954, 12% of the nation's radio and TV repair shop income was being earned in New York. Illinois received 9.1%, California 9%, Pennsylvania 6.7% and Ohio 6%. Unfortunately the report did not give any data later than 1954.

The report brought out the further interesting fact that the income of radio and TV shops increased more than 200% between 1948 and 1954, the 1948 receipts being \$100 million and the 1954 income \$313 million.

DETROIT APPOINTS BOARD

The committee to enforce Detroit's new TV servicing ordinance has been appointed by the Mayor. It consists of Alexander Weiss, G and G Radio and Television; Ralph Carew, University Radio; Lawrence Howard, Radio Electronic Television Schools; Patrick Brennan, Independent Television Repairmen's Association; Edgar Love, chief engineer WWJ-TV; Edwin C. Denstaedt, director of communications for the Detroit police department, and Heilborn B. Love, chief of the bureau of electrical inspection of the city's department of buildings and safety engineering.

END

COLOR'CEPTOR

Designed for Perfect Color
Reception on all 12 VHF channels

Sensationally New!

New **WINEGARD**

Engineering Development

Increases Antenna Sensitivity **47%** . . .

Doubles Front-to-Back Ratios!

If awards were given for antenna performance, the new WINEGARD COLOR'CEPTOR would win them all! That's right! In side-by-side field tests, competing with other types of antennas in all parts of the United States, the amazing COLOR'CEPTOR outperformed all others tested. These tests included sensitivity (where the COLOR'CEPTOR averaged 47% more gain on the high band and 30% more gain on the low band**) . . . picture quality (both color and black-and-white on all 12 VHF channels) . . . ability to reject co-channel interference . . . consistency of reception in fringe areas under changing atmospheric conditions . . . and horizontal directivity (the ability to reject multipath signal reflection and ghosts).

These tests were conducted by fifty independent servicemen selected at random throughout the country, whose final decisions were in no way influenced by the Winegard Company. However, Winegard did furnish non-reactive 300 ohm line pads, into which test lines were terminated to insure accurate gain test results.

Besides being an outstanding antenna electrically, the new COLOR'CEPTOR is unmatched in quality of materials and workmanship. It comes in a beautiful gold anodized finish at no extra cost.

WINEGARD **COLOR'CEPTOR** Gives You
Clear--HIGH DEFINITION Pictures in

COLOR

BLACK & WHITE



**Model CL-4X with Power-Pack (see reverse side)

NATIONALLY



ADVERTISED

WINEGARD

3000 Scotten Blvd.

BURLINGTON, IOWA

COMPANY

(see details on reverse side)



**MODEL
CL-4X
List Price
\$44.90**



**MODEL
CL-4
List Price
\$29.95**

Here are the **FACTS!**

FIRST high gain all-VHF channel antenna expressly designed for Color TV!

FIRST with POWER-PACK. Gives exceptional signal boost on all 12 VHF channels!

FIRST all-channel 18-element yagi. Extra elements that give extra performance!


FIRST gold anodized aluminum antenna at no extra cost! (salt-spray tested for corrosion resistance)

FIRST dual-spaced Electro-Lens* director system (ask for Bulletin CL-1000 on engineering specifications)

*Patent No. U. S. 2700105
and Canada No. 511984
Other Patents Pending

"Power Pack" gives Big Power Boost to COLOR'CEPTOR

The exclusive Winegard POWER-PACK converts the regular 11-element model CL-4 COLOR'CEPTOR into an ultra-sensitive super-powerful 18-element all-channel yagi. The Power-Pack consists of three separate parts — the front five-element Electro-Lens director system (shown outlined in red) that gives a tremendous gain boost on both VHF bands . . . plus the two extra reflector elements (shown as the long elements at the right). The two regular reflector elements, in conjunction with the regular reflector, create a flat sound screen that literally blocks off all signals arriving from the rear and, at the same time, increases the gain uniformly across the low band. The final result is a high performance 18-element yagi that sets new standards for the industry!

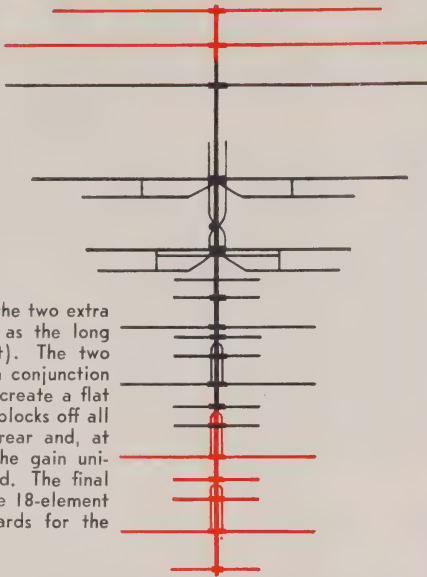

Power-Pack
plugs in easily.


COLOR'CEPTOR CL-4	\$29.95 list
POWER-PACK (PK)	14.95 list
COLOR'CEPTOR with POWER-PACK	
CL-4X	44.90 list
(NOTE: Standard gold anodized finish unless otherwise specified. Available on special order only in green or blue anodized finish or standard aluminum at same prices as above.)	
STACKING BARS (SB-4C)	2.20 list
WEIGHT (Model CL-4) Net	4 lbs. 14 ozs.
Shipping	7 lbs. 8 ozs.
(Model CL-4X) Net	7 lbs. 14 ozs.
Shipping	10 lbs. 8 ozs.
OVERALL DIMENSIONS	
CL-4	WIDTH 110" LENGTH 78"
CL-4X	110" 122½"

Winegard Co.

WHY COLOR'CEPTOR IS FIRST CHOICE FOR COLOR TV RECEPTION

The fact that the antenna you are now using gives satisfactory black-and-white reception is no guarantee that this same antenna will give equally satisfactory performance on all 12 VHF channels in color. Even though you are located in a strong signal area . . . you need the COLOR'CEPTOR for perfect color reception.

The WINEGARD COLOR'CEPTOR is precision engineered and meets all the rigid requirements for perfect color reception, such as flat gain on all 12 VHF channels. In fact, the gain does not vary over ± 1.2 DB on any channel. The Winegard COLOR'CEPTOR also assures 300 ohm impedance match . . . unmatched front-to-back ratios, not on just a few channels, but on all of your stations . . . plus the highest average gain of any all-channel VHF antenna.

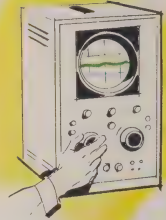

So, if you want the finest color reception possible, use the Winegard COLOR'CEPTOR. If you want crisp, high definition black-and-white pictures, use the COLOR'CEPTOR. If you want an antenna you can install with confidence of tested performance and unequalled results, you want the Winegard COLOR'CEPTOR by all means! No matter how close or how far you are from your TV stations . . . no matter what your reception problems may be . . . the new WINEGARD COLOR'CEPTOR guarantees you the very finest TV pictures possible.

ATTENTION, Service Dealer!

Here's a chance for you to get a gleaming gold super DeLuxe 18-element COLOR'CEPTOR antenna . . . absolutely FREE . . . for your personal use or for set demonstration. See your nearest Winegard jobber, or send coupon for complete details — today!

WINEGARD COMPANY

3000 Scotten Blvd., Burlington, Iowa

Please rush me the following:

- ☐ How to get free COLOR'CEPTOR Antenna
- ☐ Name of nearest distributor
- ☐ Engineering specifications, catalog sheet and other promotional material available to help me sell COLOR'CEPTOR Antennas

FIRM NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

MY NAME _____



WINEGARD



COLOR'CEPTOR

for

PERFECT COLOR RECEPTION

new Devices



HAND-OPERATED NIBBLING TOOL, Model NT-1 cuts any shape of opening in sheet metal without distorting edges. Cuts holes any size or shape over

leverage for easier cutting and one-operation cutting and crimping to prevent cut wire from sliding back through hole of printed-circuit board.—**Utica Drop Forge & Tool Corp.**, Utica 4, N. Y.

POCKET TOOL. Pocket-size wire cutter and stripper. Wire-size adjustment for easy stripping. 5-inch blades. For wire stripping, set adjusting stop to



wire size, close jaws of tool around wire and strip with straight pull. Weighs 2 ounces.—**Jo-EI Co.**, 14209 Leroy Ave., Cleveland, Ohio.

1/2-INCH CAPACITY HAND REAMERS, No. 39. 3/16-inch hole in shank where 3/16-inch screwdriver or pin may be inserted for leverage on extra-

7/16 inch. Cuts in all directions. Capacity: steel, 18 gauge (.046 inch) maximum; aluminum, copper, plastic, etc., 1/16 inch.—**Harrison Radio Corp.**, 225 Greenwich St., New York 7.

PRINTED-CIRCUIT PLIERS, No. 470-5, featuring compound



heavy work. Chrome plating for lasting cutting edge and rust resistance; straight fluted blades. In plastic 1-inch-diameter handle or detached.—**Xcelite Inc.**, Orchard Park, N. Y.

ROOF TOWERS; Model TRT 120, 10-foot triangular roof tower with multiple cross-bracing forming ladder on one side. **Model TRT 60** 5-foot triangular roof tower, cross-braced. **Model TRT 36** 3-foot triangular roof tower, cross-braced. **Model TRT**



30 similar to above, 2 1/2 feet. **Model TRT 6 AG 4** special 7 1/2-foot top section of No. 6G tower with three 2 1/2-foot legs which can be inserted into tower. All towers galvanized, collapsible. Fit roofs with rafters 16 inches on center.—**Rohn Mfg. Co.**, 116 Limestone, Bellevue, Peoria, Ill.

TV ANTENNA, Ground-Master, to eliminate roof-top installations in primary signal areas and to provide performance superior to indoor types. Mounts on ground and resembles trellis. Attractive addition to house when planted with rose or climbing vine. Active elements insu-

lated to minimize effects of moisture. Kit complete with antenna trellis, mounting post, lead-in



and hardware.—**Trio Mfg. Co.**, Griggsville, Ill.

TRIPOD TOWER AND ANTENNA, Minute-Mount, 10-foot factory-assembled noncorrosive aluminum foldout assembly



mast with high-gain antenna. Attached lead-in, 7 insulators, lightning arrester, ground wire and ground rod. Designed for fringe areas.—**Winegard Co.**, Burlington, Iowa.

CONICAL ANTENNA KITS, 16 models ranging from 6 to 10 elements, packaged with such needed accessories as chimney mounts or swivel base, guy wire, standoffs, stacking bars, lead-in, etc. Antennas are all-aluminum, completely preassembled and ready to open like an umbrella.—**Tenna Mfg. Co.**,

Get This Valuable Book

FREE



Yes, you get this big, brand new book, "150 Radio-Television Picture Patterns and Diagrams Explained", absolutely FREE! Just off the press. Gives complete 11 x 22" Schematic Diagrams on leading models Radio and TV Sets. Easy-to-read, large 8 1/2 x 11" pages, with full instructions on how to use the diagrams. A "must" in every repair kit. You get this book as a FREE Gift for asking to see Coyne's new 7-book set, "Applied Practical Radio-Television"!

At Last! Money-Making "Know-How" on Transistors, Color TV and Servicing

Coyne's great 7-volume set gives you all the answers to servicing problems—quickly! For basic "know-how" that's easy to understand you'll find everything you want in Volumes 1 to 5 on over 5000 practical facts and data. Every step from fundamentals to installing, servicing and trouble-shooting all types of radio and TV sets. So up-to-date it covers COLOR TV, UHF and the latest on TRANSISTORS. All this plus Volume 6—NEW Coyne TECHNICAL DICTIONARY with over 4000 definitions of the latest terms, symbols and abbreviations in radio-TV, electronics and electricity.

EXTRA! 900-Page Television Cyclopedic Included And then, for speedy on-the-job use, you get volume 7—the famous Coyne TELEVISION CYCLOPEDIA. It answers today's television problems on servicing, alignment, installation, etc. In easy-to-find ABC order, cross-indexed. Use this 7-volume TV-RADIO LIBRARY FREE for 7 days; get the Servicing Book ABSOLUTELY FREE!


Just For Examining COYNE'S New Set

"Applied Practical Radio-Television"

on 7 DAY FREE TRIAL!

NOW!

7 BIG BOOKS IN ONE GREAT SET!

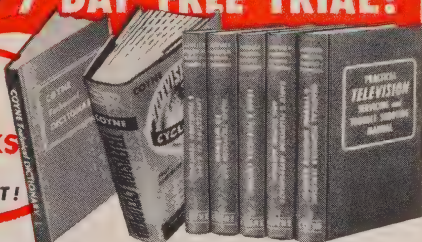

SEND NO MONEY! Just mail coupon for 7-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns & Diagrams. If you keep the set, pay \$2 in 7 days and \$2 per month until \$24.50 plus postage is paid. (Cash price, only \$22.95). Or you can return the library at our expense in 7 days and owe nothing. **YOU BE THE JUDGE.** Either way, the book of TV-Radio Patterns is yours FREE to keep! Offer is limited. Act NOW!

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL, Dept. 95-T1
500 S. Paulina St., Chicago 12, Ill.

YES! Send 7-Volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name.....Age.....

Address.....

City.....Zone.....State.....

Where Employed.....


☐ Check here if you want library sent C.O.D. You pay postman \$22.95 plus C.O.D. postage on delivery. 7-day money-back guarantee.

Educational Book Publishing Division

COYNE


ELECTRICAL SCHOOL

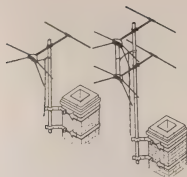500 S. Paulina St., Dept. 95-T1, Chicago 12, Ill.



7580 Garfield Blvd., Cleveland 28, Ohio.

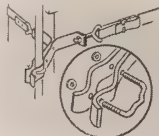ANTENNA MOUNTINGS, Snap-In, with U bolt permit one-hand Spintite fastening of antenna mast. After mast is snapped



into spring-tension mast retainers, insert U bolts and tighten. **South River Metal Products Co., Inc.**, South River, N. J.


PLASTIC TUBULAR CAPACITORS, Gem, for bypass, coupling and buffer applications. Seamless case made of high-grade mineral-filled phenolic material that will not distort, burn or



soften when heated. Rated at 500 volts or higher and impregnated with mineral oil; lower-voltage units, with wax. Leads won't loosen under soldering-

iron heat.—**P. R. Mallory & Co., Inc.**, Indianapolis 6, Ind.

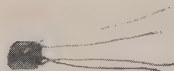TRANSISTOR TRANSFORMERS, flexible coded leads. Open type mountings. Series of five



includes one input, two output and two interstage.—**Merit Coil Products Co., Inc.**, 4427 North Clark St., Chicago, Ill.

SINGLE-UNIT RESISTOR-CAPACITOR Tube-R-Cap, standard size tubular ceramic capacitor incorporating a ceramic-base



resistor in parallel. Length 0.9 inch, diameter 0.28 inch. 470 μ af, 1,500 volts ac; $\frac{1}{2}$ watt. **Centralab Div., Globe-Union Inc.**, 900 E. Keefe Ave., Milwaukee 1, Wis.

ELECTRONIC SWITCHING DEVICE, Neomite relay, for airborne computers and control units. Weighs 1/16 ounce and



measures $\frac{1}{2}$ by $\frac{1}{2}$ inch. Available with 2,000-ohm coil and 1,000-, 500-, 200- and 50-ohm

coils with 100-mw sensitivity.—**Elgin National Watch Co.**, Elgin, Ill.

RADIOHMS $\frac{1}{4}$ -watt miniaturized controls. Completely closed, can be sealed or potted. 28 selections, 20% tolerance, 1,000 ohms to 2.5 megohms. Model JP: plain round shaft, $\frac{1}{8}$ -inch diameter and $\frac{1}{2}$ inch long. Model JL: screwdriver-



slotted shaft.—**Centralab Div., Globe-Union Inc.**, 900 E. Keefe Ave., Milwaukee 1, Wis.

PIC PROBE checks operation of TV receiver—any section of set seen on picture tube. Two coils and network of resistors, capacitors and diodes. Induced into



these windings are horizontal and vertical deflection currents. Integrating circuits form a sawtooth wave from the sweep signal picked up in windings. Sawtooth waves are than fed to horizontal and vertical inputs of oscilloscope, giving a raster. Intensity terminal of the scope is fed with video information from TV set, producing on scope a picture identical to that on TV set screen.—**Radionics Industries**, 3215 W. North Ave., Chicago 47.

ILLUMINATED PROBE, Probe-Lite, combines probe and illumina-



tion source. Tip of cord set inserts in probe jack. Brilliant prefocused light. Long, slender probe tip for difficult areas.—**Phaestron Instrument & Electronic Co.**, 151 Pasadena Ave., So. Pasadena, Calif.

CAPACITOR-RESISTOR ANALYZER, CRA-2, for use in industrial and military electronics, black-and-white and color TV. Leakage current values read directly from meter while rated



operating voltage is applied to capacitor. Accurate insulation-resistance values for many types of capacitors. Power-factor measurements of electrolytics rated as low as 6 volts dc, as high as 600 volts dc. "In circuit" tests for short, open, intermittent high-rf impedance and high power factor.—**Pyramid Electric Co.**, 1445 Hudson Blvd., North Bergen, N. J.

CORNING LOW-POWER RESISTORS

available now through

ERIE
distributors

for Service Replacements

Corning Low-Power Resistors Types LP-4 and LP-5 have been especially designed for radio, TV, and similar applications. They have the highest resistance range of any low-power resistors on the market, and are used by leading manufacturers. They are stable and non-inductive, and impervious to moisture and dirt. Resistance spiralling is automatic and is electronically controlled.

For complete service information and prices . . . see your Erie Distributor.

ERIE
Electronics

ERIE ELECTRONICS DISTRIBUTOR DIVISION

ERIE RESISTOR CORPORATION

Main Office: ERIE, PA.

Factories: ERIE, PA. • LONDON, ENGLAND • TRENTON, ONTARIO



big
reasons
why
QUIETROLE
Reg. U. S. Pat. Off.

is "The Choice of Better Service Dealers Everywhere"

1 MERIT
2 QUALITY
3 RELIABILITY

The original product for quieting noisy controls and switches . . . the universal lubri-cleaner for TV and radio . . .

Say "QUIETROLE" to your distributor . . . be sure you get it.

**NO GUM!
NO GOO!
NO GRIME!**





manufactured by

QUIETROLE
COMPANY INC.
Spartanburg, South Carolina

IN CANADA:



Active Radio & TV Distributors
58 Spadina Ave., Toronto 28, Ont.

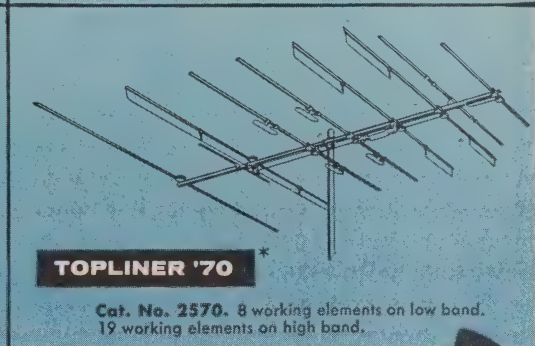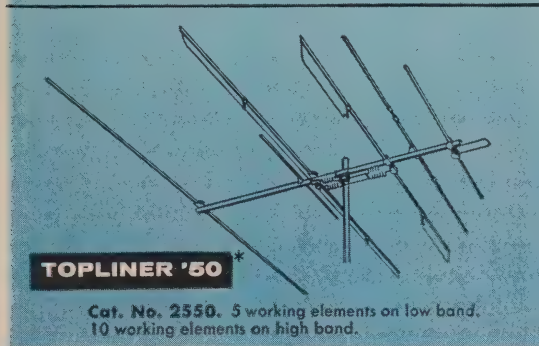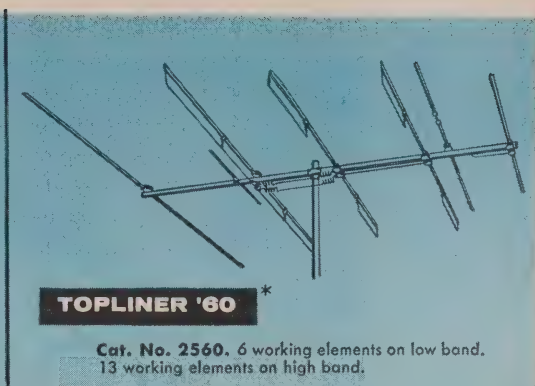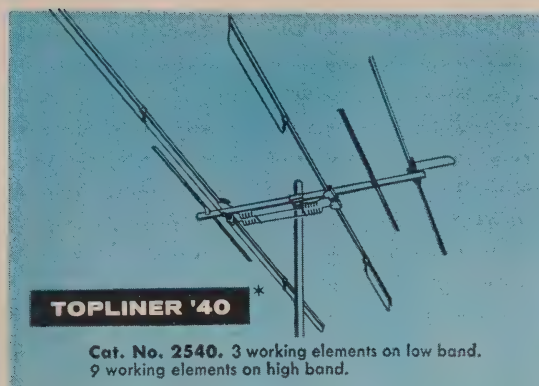Carried by recognized jobbers . . . everywhere!



Topliner Trade-mark antennas **TOP 'EM ALL!**

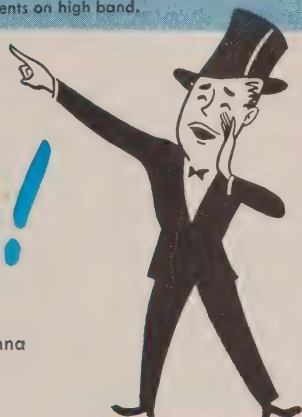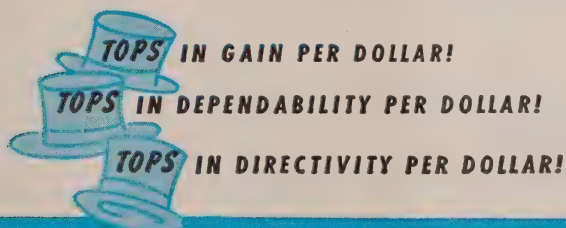Taco again introduces an original antenna design, engineered for results. The Topliner represents better performance than any other antenna now on the market. And, best of all, you get this extra performance at no increase in cost.



RIGHT!

FOR **COLOR**
AND
BLACK & WHITE!

TACO TOP LINE FOR '57

TECHNICAL APPLIANCE CORPORATION, SHERBURNE, N. Y.
 (IN CANADA) Hackbusch Electronics, Ltd., Toronto 4, Ont.

* Pat. Pending

RADIO & ELECTRONICS TRAINING AT HOME

BASIC RADIO

CIRCUITS with NEW Deluxe 1957
PROGRESSIVE RADIO "EDU-KIT"

A Practical Home Radio Course

- * No Knowledge of Radio Necessary
- * No Additional Parts or Tools Needed
- * Excellent Background for TV

FREE SET OF TOOLS, TESTER,
SOLDERING IRON, HIGH FIDELITY,
SIGNAL TRACER, CODE
OSCILLATOR, PRINTED CIRCUIT
SIGNAL INJECTOR

FREE HI-FI, RADIO & TV SERVICING LITERATURE (See Coupon)

WHAT THE "EDU-KIT" OFFERS YOU

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing.

You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service and trouble-shoot radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis.

You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, the Progressive Signal Injector, the Progressive Dynamic Radio & Electronics Tester and the accompanying instruction material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur License. You will build 16 Receiver, Transmitter, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for Television.

Absolutely no previous radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic education in Electronics and Radio, worth many times the complete price of \$19.95. Everything is yours to keep.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want a hobby, a well-paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment.

Here is an excerpt from a letter that we received from Loren DePriest, 1496 4th St., Mansfield, Ohio: "I've spent many pleasant hours in constructing the radios from the schematics in your book, and have received a great deal from them. Being as I am interested in Radio, I consider the money spent for your course as a wise investment. I have learned more from your course by actually doing, than I did from an expensive course."

Many thousands of individuals of all ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you can succeed at a mile.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio.

You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and use of these parts. Then you build a simple radio. With this first set, you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio & Electronics Technician.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 16 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable electrolytic and paper dielectric capacitors, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You will also receive a useful set of tools, a professional electronic soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Oscillator, in addition to F.C.C. type Questions and Answers for the Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book.

FREE EXTRAS

- SET OF TOOLS • RADIO & ELECTRONICS TESTER
- ELECTRIC SOLDERING IRON • TESTER INSTRUCTION
- MANUAL MEMBERSHIP IN RADIO-TV CLUB • CONSULTATION SERVICE • HI-FI GUIDE • QUIZZES • TV BOOK

UNCONDITIONAL MONEY-BACK GUARANTEE

ORDER FROM AD—RECEIVE FREE BONUS RECEIPT KIT WORTH \$5.00

- Send "Edu-Kit" Postpaid, I enclose full payment of \$19.95.
- Send "Edu-Kit" C.O.D. I will pay \$19.95 plus postage.
- Send me FREE Servicing Literature, "Edu-Kit" include FREE valuable Hi-Fi, Radio and TV Servicing Literature. No obligation.

(Outside USA) no COD. "Edu-Kit" for 105-125 V. \$20.95; 120-250V. \$23.45.)

Name _____

Address _____

PROGRESSIVE "EDU-KITS" INC.

497 Union Ave.,
Room 120-C, Brooklyn 11, N.Y.


Only \$19.95

Reg. U.S.
Pat. Off.




NEW DEVICES

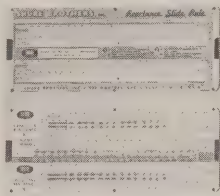REACTANCE SLIDE RULE, for technicians and students. Re-




issue of well known Shure rule for simplifying reactance, resonance and dissipation calculations. Covers frequency range from 5 cycles to 10,000 megacycles.—Shure Brothers Inc., 222 Hartrey Ave., Evanston, Ill.

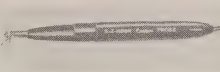TEST PROBE, E-Z Hook Probe simplifies electrical connections. Clamps on to any shape con-




ductor; spring-loaded. Isolation resistor or capacitor may be inserted in probe.—E-Z Hook Test Products, 1536 Woodburn Ave., Covington, Ky.

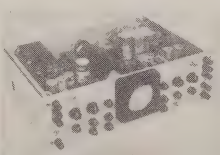INDUSTRIAL OSCILLOSCOPE, low-frequency type. Sensitive to ac and dc. Identical horizontal



and vertical amplifiers for accurate phase-angle measurement, built-in calibration voltage. Can mount in 19-inch relay rack. Response to 500 kc and flat within 3 db from 0-200 kc.—Hycon Mfg. Co., Pasadena, Calif.

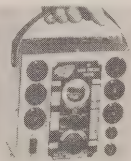
KITESTER, model GCT-5, tests over 125 tube types for control grid emission, grid-cathode



shorts, gas and cathode-heater shorts. 7 wired sockets and 1 spare. Replaceable panel etched with tube lists. Sensitivity: grid emission 0.35 microwatt; grid-cathode leakage 125 megohms; grid-plate or screen 125-250 megohms; cathode-heater leakage 1 megohm; plate or screen to suppressor 0.1 megohm. Can be used as capacitor leakage checker. Dc voltmeter with range to 500 volts.—Seco Mfg. Co., 5015 Penn Ave. S., Minneapolis.

INDUCTION MODULATOR operates on different principle than choppers and other transducers; has no contacts. Coil positioned by dc signal current through it; ac field coils mounted on magnets induce ac voltage in moving coil proportional to position as determined by dc

(Continued)

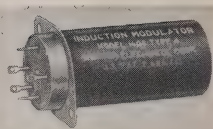

signal. Constant resistance to dc signal input; output waveform sinusoidal. Conversion gain 28 db. Capacitors can be used to make output in quadrature with input.—Weston Electrical Instrument Corp., 614 Frelinghuysen Ave., Newark 5, N. J.

ELECTRONIC CROSSOVER KIT, model XO-1, designed to operate ahead of main power amplifiers. Independent electronic filters, one high pass and one low pass, each with rotary



switch for selecting cutoff frequency. Single input divided into high- and low-frequency portions of spectrum, available at outputs to feed separate amplifiers. No audio power consumed by crossover. Does not affect amplifier damping factor. Each channel has level control. Crossover frequencies 100, 200, 400, 700, 1,200, 2,000 and 3,500 cycles. Attenuation 12 db per octave with sharp knee at cutoff frequency.—Heath Co., Benton Harbor, Mich.

LO-PASS LINE FILTER for use with tape and wire recorders, phonos and playbacks. Eliminates noises picked up through line from motors, ignition, neon, diathermy, lighting and heating



equipment and electrical home appliances. Plugs into ac or dc receptacle; instrument being used plugs into filter. Ground cable attached, its use optional. 3 x 4 inches.—Dynamic Electronics, 73-39 Woodhaven Blvd., Forest Hills, N. Y.

DYNAMIC MICROPHONE, model 124, for broadcast, recording or public address. Instant disconnect feature good for use as



hand microphone. Output —58 db, response 50-13,000 cycles. Three impedances: high, 200 or 50 ohms. 12-foot removable cable, single-conductor shielded on high-impedance models, 2-conductor shielded on low-impedance models. 6 1/2 inches long, 15/16-inch diameter.—Turner Co., Cedar Rapids, Iowa.

High reliability manufacturing of miniaturized paper tubular capacitors -- hermetically sealed in metal cans

To produce subminiature paper capacitors free from any possibility of latent defects, for use in the most critical applications, the Sangamo Electric Company has recently intensified its high reliability program of fabrication and inspection methods.

Incoming materials for these capacitors are rigidly inspected to meet stringent high reliability standards and are stored in areas where temperature, humidity and dust are controlled at all times.

Complete production histories are kept on the basis of small capacitor lots. X-raying of individual units, heat tests, vibration tests, altitude tests, and total destruction tests of a given percentage of all finished units assure components with an extremely low AQL. Testing facilities and resultant performance characteristics are far in excess of military specifications. Specify these high reliability capacitors for your critical applications.

Mail the coupon below for Sangamo's *NEW Engineering Catalog TS-105A*. It contains full information, including an easy-to-follow cross reference showing each variation listed in MIL-C-25 versus the comparable Sangamo unit.



For your design convenience, an exceptionally wide choice of styles — twelve in all — is available with regard to tolerances, circuit assembly, lead styles, mounting brackets, insulating sleeving, and inductive or non-inductive sections.



SC56-7



SEPARATE FACILITIES are maintained for the exclusive processing and manufacture of high reliability capacitors. Only specially trained, highly skilled operators, who wear special clothing to prevent any possible source contamination, work here.



OIL-FILLED CAPACITORS are subjected to vacuum under elevated temperatures, then are individually examined to insure complete hermetic seal.

SANGAMO ELECTRIC COMPANY

Capacitor Division
SPRINGFIELD, ILLINOIS

Please send me your **NEW Engineering Bulletin TS-105A**.

Name


Company

Address

City Zone State

NEW DEVICES

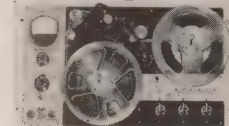HI-FI TAPE RECORDER, SRT-2, for simple plug-in use. Uses transistors and printed circuitry. Nonmicrophonic, hum-free, 30-15,000 cycles. Takes all types of standard magnetic tapes in 5- and 7-inch reels. Installed either vertically or horizontally. Re-



cords and reproduces at 7½ and 3¾ ips. Fast forward-and-rewind speed, 1,200 feet in 45 seconds. Only one mechanical linkage: a cam action which operates pressure roller on capstan. VU meter recording-level indicator, installed in standard 10½-inch mounting rack. Automatic tape lift during fast winding; monitor jack for plug-in earphones. 10½ x 19 x 8½ inches, 35 pounds.—**Radio Corp. of America**, Camden, N. J.

BIAXIAL HI-FI SPEAKER, RCA-501S1, combines 12-inch low-frequency woofer, 3-inch hi-fi tweeter and crossover network. Handles 12 watts continuously with uniform response 40-18,000 cycles. 8-ohm aluminum voice coil and 14.5-ounce Alnico V magnet. Tweeter unit mounted off-axis for smooth acoustical crossover. — **RCA Tube Div.**, Harrison, N. J.

EXPLOSION-PROOF SPEAKERS for hazardous service.

Type HLE-1-30 (see photo) for paging and talk back; HLE-1-42 for maximum sound coverage. Built-in line-matching trans-



formers available.—**Atlas Sound Corp.**, 1451 39 St., Brooklyn 18, N. Y.


ANTISTATIC MAGNETIC CARTRIDGE, B&O A+ Special, single stylus (diamond, sapphire), for professional arms with ½-inch center-spaced mounting holes or standoffs. **B&O 350 A+ Special**, 350-ohms,



30-μv output at 4.4 cm/sec for use with high-level magnetic input professional amplifiers; **B&O 72 A+ Special**, 72-ohms; 15-μv output at 4.4 cm/sec for use with amplifiers having only low-level magnetic input.—**Fenton Co.**, 15 Moore St., New York 4, N. Y.


PHONO CARTRIDGES, Climatic series, weatherproofed. **Model 120ts** high output, high compliance, wide-range turnover containing separate removable, 1- and 3-mil synthetic sapphire needles. **Model 310T**, 3 volts output, compliance of 0.7, frequency response 50-12,000

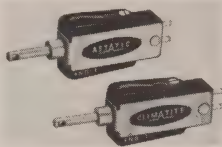cycles. Turnover contains separate 1- and 3-mil synthetic sapphire-tipped needles. **Model 312T**, 0.8 volt output, high com-



pliance of 2, frequency response 30-15,000 cycles. Turnover contains separate 1- and 3-mil synthetic sapphire-tipped needles. **Model 414-1** for 45-rpm changers. Same as **model 310T**, only 1-mil sapphire-tipped needle.—**Astatic Corp.**, Conneaut, Ohio.

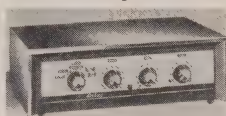AMPLIFIER - PREAMPLIFIER KIT, model FL-10. Tape output unaffected by loudness and tone controls. Williamson type amplifier and built-in preamp. Ultra-linear output circuit uses 2 6V6-GT's. Power output 12 watts at




1% IM; peak power 19 watts; output impedances 4, 8 and 16 ohms; response ±1 db 10-40,000 cycles, ±½ db 40-15,000 cycles below 10 watts. Hum: minimum volume 80 db below 10 watts, aux and tuner —65 db below 10

All specifications given on these pages are from manufacturers' data.


watts, phono hum —55 db below 10 watts. Tone controls ±16 db at 50 and 10,000 cycles. Input levels: aux 0.3 volt, phono 6 mv. Record equalization—LP, RIAA and Eur. 12½ x 4 x 3½ inches.—**Radio Kits Inc.**, 120 Cedar St., New York, N. Y.

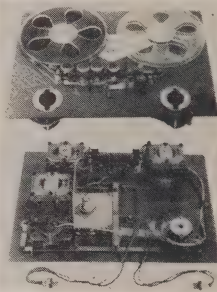HI-FI 3-SPEED DECK Fenton Brenell MARK IV for stereo record playback. Incorporates many improvements over former **Mark II** deck. **Model Bren IV**; upper-track monaural heads (1 R/P and 1 erase), 4 pressure pads and mounting



holes for two additional heads. **Model Bren IV/B**: 4 staggered stereo heads (one pair each upper and lower tracks), 3 motors—capstan, feed and take-up, instantaneous mechanical braking, 3¼- and 7½- or 7½- and 15-ips operation.—**Fenton Co.**, 15 Moore St., New York, N. Y. END

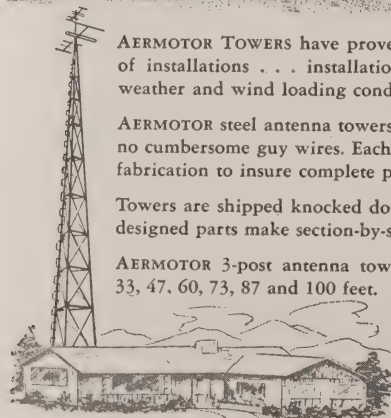When signal conditions demand a **TOWER...** choose one built by **AERMOTOR**



AERMOTOR TOWERS have proven their excellence in thousands of installations . . . installations exposed to the most severe weather and wind loading conditions.

AERMOTOR steel antenna towers are self supporting . . . require no cumbersome guy wires. Each part is heavily galvanized after fabrication to insure complete protection from exposure.

Towers are shipped knocked down in convenient bundles; well designed parts make section-by-section assembly easy.

AERMOTOR 3-post antenna towers are available in heights of 33, 47, 60, 73, 87 and 100 feet.

WRITE FOR ADDITIONAL INFORMATION ABOUT THE AERMOTOR TOWERS AND A DEALER FRANCHISE IN YOUR TERRITORY.

SINCE 1888, MANUFACTURERS OF QUALITY BUILT TOWERS

• **AERMOTOR COMPANY** •

2500 W. ROOSEVELT RD.—CHICAGO 8, ILLINOIS U.S.A. DEPT. 12 U 9


HOUSE CURRENT Anywhere

Now, while fishing, camping, business trips, anywhere you drive, you can enjoy many of the conveniences usually available only at home, shop, or office:



- Electric Shavers
- Car Polishers
- Radios—Lights
- Phonographs
- Dictation Machines
- Tape Recorders
- Hand Vacuum Cleaners
- Small Do-It-Yourself Tools
- Heating Pads

"101" USES

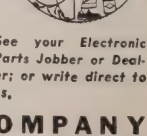

See your Electronic Parts Jobber or Dealer; or write direct to us,

Trav-Electric CONVERTERS

No installations. Just plug into cigar lighter. That is all. Priced as low as \$11.95.



TERADO COMPANY
1057 Raymond Ave. St. Paul 14, Minn.

RADIO-ELECTRONICS

**Systems
Career: a**
**laboratory
for
learning**



*... an exciting and rewarding
career awaits the E.E. or Physics
graduate who joins this highly
respected Engineering team.*

As a Field Engineer at Hughes, through training and assignment you will become familiar with the entire systems involved, including the most advanced electronic computers. With this knowledge you will be ideally situated to broaden your experience and learning for future application in either the military or commercial field.

The national respect which Hughes commands in the field of advanced electronics is in no small part due to the technical support provided by the Field Engineers. Other contributors to the suc-

cess of the Field Service and Support Division are the Technical Manuals Engineer, Training School Engineers, Technical Liaison Engineers, and Field Modification Engineers.

This Hughes activity is a highly trained organization of expert engineers, giving support to the armed services and airframe manufacturers using the company's equipment. Locations are in Southern California, continental U.S., overseas. We invite you to join this team. For further information write us at the address below.

HUGHES

**Some extra advantages for
Field Engineers include:**

Training at full salary for 3 months before assignment.

Generous moving and travel allowance between present location and Southern California (Culver City).

Additional compensation plus complete travel and moving on assignments away from Culver City.

Ideal living conditions in the unsurpassed climate of Southern California.

Reimbursement for after-hours courses at UCLA, USC, or other local universities.

Employee group and health insurance paid by company, retirement plan, sick leave, and paid vacations.

Scientific Staff Relations
RESEARCH AND DEVELOPMENT LABORATORIES
HUGHES AIRCRAFT COMPANY
Culver City, California

Radio-TV
servicemen
prefer

QUAM

Adjust-a-Cone

SPEAKERS

Because they know from actual field experience that Quam speakers give longer, trouble-free operation.

*Brand Name Surveys; Survey of brand preferences of electronic replacement components, April 1956, reported Quam Speakers preferred by almost twice as many servicemen as the next most popular brand.

Quam Speakers have been built under the same management for over 30 years.

**QUAM-NICHOLS
COMPANY**

234 East Marquette Road
Chicago 37, Illinois

*QUAM, the quality line,
for all your speaker needs*


For Your Protection

RADIO-ELECTRONICS is continually alert to maintain a high level of integrity in our advertising columns. In the case of tube advertising—which has suffered special abuses—we insist that all advertisers must warrant that their tubes are:

New and unused
Not mechanical or electrical rejects
Not washed or rebranded
(See page 57 of the January, 1956, issue)

We investigate carefully when we have grounds to suspect that any advertiser is not living strictly up to these rules.

new
Records

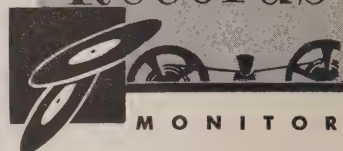

Note: Records below are 12-inch LP and play back with RIAA curve unless otherwise indicated.

BRUCH: *Violin Concerto No. 2*
WIENIAWSKI: *Violin Concerto No. 2*
Heifetz with RCA Victor Symphony
conducted by Izler Solomon
RCA Victor LM-1931

No record library could be complete without a Heifetz recording and this one provides an excellent sample of his violin mastery. The Bruch No. 2 is less familiar than his No. 1 and not as melodic. The second and third movements of the Wieniawski, however, will be familiar to all who love the fiddle for they are often performed individually as encores or concert selections. The Heifetz fiddle is warm and has a beautiful tone but the recording is possibly not as clean as Capitol's Milstein records and with some wide-range cartridges it may be advisable to roll off above 10 kc. The definition is very good and the detail of the music and instrumentation is clear and sharp. Beside the excellent fiddle in the Wieniawski there is a nice middle bass throughout, good plucked bass in portions and fine big brass choirs.

BRAHMS: *Hungarian Dances*
(Complete)
Vienna State Opera Orchestra
conducted by Mario Rossi
Vanguard VRS-473

If I were limited to four or five test and demonstration records, this would certainly be one. I know of no record which presents a greater variety of test and demonstration material or a more spectacular sound. It has a real gypsy brightness, an exemplary acoustic liveness, superb definition, lovely high highs, a good bass, a very great variety of instrumentation and orchestration, big attacks and sharp stops, and some of the sprightliest music ever written. The first band on each side is particularly spectacular but each of the some 20 dances has its own worth-while qualities as music, sound or test material. I cannot recommend this too highly and can practically guarantee that the rest of the family will like it as well as you do.

JANACEK: *Sinfonietta*
Taras Bulba
Jascha Horenstein conducting Pro
Musica Symphony of Vienna
Vox PL-9710

The best test record I have received for some time, this is not especially useful for routine demonstration or showoff but it will do a fine job of testing the real mettle of the finest hi-fi equipment. *Taras Bulba's* programmatic music expressing three deaths is very violent in spots, with a great deal of complex and subtle instrumentation in the peaks which are unusually clean except in the final band. The system which can reproduce the music with all the detail should be good enough for anybody.

The elaborately orchestrated *Sinfonietta* also presents a severe test of definition. Aside from this there is a notably fine low bass; in portions the organ pedal underlies the tympani and basses for some especially gratifying low lows. The tympani are excellent, especially in the third movement. The strings are very loud and pickups which reproduce their high end without roughening the tone can safely be presumed to be both good and in good condition. There are some good highlights in spots as well. In short, there is a little of everything and a lot of it

New RCA WR-46A Video Dot/Crosshatch Generator.

Produces stable, sharp patterns at high-level video output for convergence adjustments.

Saves installation time; enables more precise convergence adjustments.



Magnified view shows sharply defined Dot pattern produced by WR-46A on typical picture tube.

PRICE...
\$179.50*

- high-level video output permits direct connection to grid or cathode circuits of color picture tubes—eliminates pattern distortion which may be caused when generator signals are fed through rf, if, or vt channels—results in clean, extremely sharp pattern display
- permits simultaneous display of pattern with broadcast picture in background to assure that convergence adjustments are made at correct horizontal and vertical scanning rates
- switch-selection of four types of patterns is provided: "V" bars for vertical dynamic tilt and amplitude convergence adjustments; "H" bars for horizontal dynamic phase and amplitude convergence; Crosshatch for simultaneous check of "V" and "H" convergence adjustments; Dots for center-screen static-convergence adjustments and for "touching up" dynamic convergence
- has Brightness Equalizer Control for "V" and "H" elements in crosshatch pattern
- vertical sync is frequency-divided from horizontal sync, resulting in interlaced scanning and exceptional freedom from "jitter", "crawl", and "sync-hunting"
- light weight • portable.

Simplify, Speed-up Color TV Servicing!

RCA WR-61B Color-Bar Generator.


Provides crystal-controlled signal source for trouble-shooting, and adjusting color-phasing and matrixing circuits.

WR-61B simplifies the usually complex measurement of the relative gains of the 3 chrominance channels (R-Y, B-Y, G-Y). With the WR-61B the relative gains of these channels can be measured at the output of each demodulator stage. This simplified method of measuring gain is possible because the subcarrier output of the generator is constant for all color-phase angles. Curve A shows WR-61B output as it would appear on a scope. Curve B shows the output signal of one of the demodulators.

Outstanding features of WR-61B: generates signals for producing 10 different color-bars simultaneously—including bars corresponding to R-Y, B-Y, G-Y, I, and Q, signals

- excellent signal source for localizing trouble ahead of or following the 2nd detector
- accepted as a standard for checking accuracy of color-phasing in many TV stations and network operations
- light weight • portable.

*User price (optional)

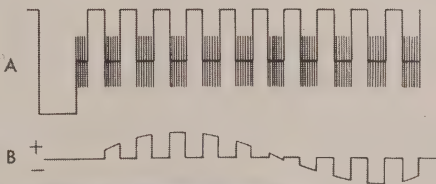

PRICE...
\$247.50*

RCA TEST INSTRUMENTS ARE AVAILABLE THROUGH YOUR RCA DISTRIBUTOR.



TEST EQUIPMENT

RADIO CORPORATION OF AMERICA, HARRISON, N. J.



...another
MALLORY
service-engineered
product

*right every
time in less
time...with*

MALLORY Midgetrols®

Control replacements are faster
... and every job is sure to satisfy
... when you use Mallory
Midgetrols.

Line switches are a cinch to
attach; no need to take the
control apart.

Custom-fitted shafts take only
seconds; just cut to length and
insert the kind of tip your job
needs.

Long, quiet life assures customer
satisfaction...ends costly
call-backs.

Get Midgetrols from your
Mallory distributor, in resis-
tance values and tapers to fit
all popular TV and radio
circuits.

P. R. MALLORY & CO. Inc.
MALLORY

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

- Capacitors
- Vibrators
- Resistors
- Power Supplies
- Controls
- Switches
- Rectifiers
- Filters
- Mercury Batteries

NEW RECORDS

(Continued)

demanding enough to winnow the superb systems from the merely adequate. The music is interesting and grows with repeated playing. Congratulations to Vox for a good job of recording a difficult subject.

GRIEG: *Peer Gynt Suites 1 and 2* IPPOLITOFF-IVANOFF:

Caucasian Sketches

Felix Slatkin conducting

Hollywood Bowl Orchestra

Capitol P-8329

If you have one of the few superlative speaker systems capable of doing drums real justice, this recording is for you. The two sides have as interesting a variety of tone, size and damping of drums as I know of, and in *Arabian Dance* of the *Peer Gynt* they are recorded practically life-sized. But this could well be also one of the most popular of all demonstration records on any system, even the moderate ones. The music is popular, played with spirit and with a bright bandshell liveness. Ranging all the way from soothing mood music to spectacular fortissimos, it has a little of just about everything including some very nicely damped plucked basses. There are plenty of high highs to go with the big drums and the middle highs are very sweet. *Arabian Dance*, *Anitra's Dance* and *Procession of the Sardar* are fine demonstration pieces, and the first of these is, in my opinion, absolutely top-drawer.

SMETANA: "From My Life" Quartet GLAZUNOV: *Five Novelettes*

Hollywood String Quartet

Capitol P-8331

Chamber music not only provides a good change of pace for the listener but also sounds much more natural in most living rooms than a full orchestra. This is an exceptional offering of unusual string quartet music. *Five Novelettes* particularly is very different, delightful music which manages within the limited means of the four instruments to get an amazing variety of tonal color. But the Smetana quartet, too, is novel within its more conventional framework. The recording is excellent and the sound has a notable presence.

BARTOK: *Concerto for Orchestra* Reiner conducting Chicago Symphony RCA Victor 1M-1934

Though modern in date (1943) this will not offend the ear of classicists. Nor will it offend the hi-fi ear. It is one of RCA Victor's best recordings. Very little spectacular material here, it is fairly typical of the opulent yet well-balanced sound currently most popular with recording engineers. There is an excellent and pretty heavy bass, good drums, very nice traps and some brassy brass in spots. As good a way to start learning to like Bartok as any I know of.

SURINACH: *Hollywood Carnival* GLANVILLE-HICKS: *Sinfonia Pacifica* *Three Gymnopedies* Surinach conducting MGM Chamber Orchestra

MCM E-3336

What the hi-fi world has needed for some time is a percussion record with some amusing music to sting the drums, etc., on. Carlos Surinach has filled this order in the *Hollywood Carnival* which offers some highly satirical impressions of the movies. Three separate percussion sections present no fewer than 18 percussion instruments in superlative renditions of their gamuts. They are contrasted with the typically sharp brassy familiar from previous works of this composer, and a string background. The record is rather dead acoustically but this produces in the normal living room a very fine illusion of closeup presence and realism—something not always achieved.

For dessert, as it were, Peggy Glanville-Hicks provides some additional percussive material in the *Sinfonia Pacifica*. Section, or movement, three has some especially fine drums in a jazzy impression of Hindustani music. The *Gymnopedies* are a mood-music change of pace.

A Hi-Fi Frolic with Strauss
Paulik conducting Vienna State
Opera Orchestra

Vanguard VRS-476

Another superb presentation of the music of the several Strausses in the authentic Viennese style, with superb recording quality and very hi-fi throughout but without any exaggeration of tonal balance. That great big drum is here very dull and highly damped, just barely audible but gratifyingly so on systems which reproduce it at all. There are fine kettle drums, fine double basses, lovely high highs and all sorts of percussive rattlers, janglers, etc., including the water whistle.

There are innumerable sharp attacks and stops to test stability and hangover characteristics. The definition is superb. The music, with the *Blue Danube* thrown in for lagniappe, should delight just about everybody. All you need to enjoy the illusion of being right in the Brahmsaal in Vienna, besides a first-class hi-fi system is a big stein of beer.

WEBER: Oberon, Der Freischuetz,
Euryanthe

SCHUBERT: Rosamonde

MEDELSSOHN: Fingal's Cave, Ruy
Blas

Perlea conducting Bamberg
Symphony

Vox PL-9590

Six favorite overtures played with characteristic bravura and well recorded with a nice auditorium aliveness, sharp strings, good basses and drums and an overall big sound which should provide a good test for stability when played loudly and will show off good systems nicely at any levels.

FRESCOBALDI: Toccata in G Minor
12 Partitas on Aria Ruggeria
Capriccio on Battle Air known as
Frescobalda

SCARLATTI: Six Sonatas

Sylvia Marlowe, Harpsichord

Capitol P-8336

BACH: 15 Two-Part Inventions

Concerto in D Minor

Wanda Landowska, Harpsichord
(plus orchestra)

RCA Victor IM-1974

Master and pupil, and the Capitol recording does far better for the pupil. In fact, Marlowe's disc is one of the best harpsichord recordings, most faithful to tone. The contrast between damped and undamped strings is especially well indicated; the variety of harpsichord stops is greater, the tone is more resonant and sharper and better defined to my ear. But the *15 Two Part Inventions* in the Landowska disc present more of the "accompanying" transients. The concerto was recorded in 1938 and presents a rather pathetic contrast. I know of no better example showing the progress made in 20 years. The distortion is almost unendurable on a fine system (though I don't remember that it bothered me at all on the original shellacs) and the harpsichord is a mere shadow of its real self. I recommend the Marlowe for those who want harpsichord music for pleasure both in music and tone; the other for collectors and merely for demonstrating progress and showing what distortion sounds like.

MOZART: Musical Joke (K522)
Divertimento No. 11 (K251)

Reiner conducting Members of NBC
Symphony

RCA Victor IM-1952

Another offering for the Mozart birthday celebration and this one presenting two lesser known works. *Musical Joke* is amusing and has some divertingly different effects. The *Divertimento* is soothing. The sound is excellent. END

Name and address of any manufacturer of records mentioned in this column may be obtained by writing Records, RADIO-ELECTRONICS, 154 West 14th St., New York 11, N.Y.

... another
MALLORY
 service-engineered
 product

Etched Cathode

prevents
 "middle age hum"
 in capacitors



Do your capacitors have etched cathodes? If not, chances are they are developing "middle age hum"—may cost you some dissatisfied customers.

All Mallory FP's, and all popular Mallory metal and cardboard tubular electrolytics, have etched cathodes—at no extra cost to you. Ask your Mallory distributor why this is important... or write directly to us.

P. R. MALLORY & CO. Inc.
MALLORY

- Capacitors
- Vibrators
- Resistors
- Power Supplies
- Controls
- Switches
- Rectifiers
- Filters
- Mercury Batteries

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

Always

Specify Stancor

the most complete line in the industry

When you need a flyback or any other transformer for TV, radio or any electronic application


JUST RELEASED... 11 NEW EXACT REPLACEMENT FLYBACKS FOR ZENITH - G.E. - ARVIN



A-8266



A-8275, 6, 7

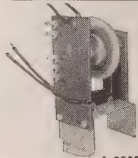

A-8282

Stancor Part No.	Replaces Part No.
A-8266	G. E. RTO-161
A-8273	Zenith S-19408
	Zenith S-20099
A-8274	Zenith S-21317
A-8275	Zenith S-22130
A-8276	Zenith S-22154

Stancor Part No.	Replaces Part No.
A-8277	Zenith S-21219
A-8278	Arvin E-40117
A-8279	Arvin E-41024
A-8280	Arvin E-42721
A-8281	Arvin E-24681
A-8282	Arvin E-41852



FREE: The latest up-to-date Stancor TV Transformer Replacement Guide and Catalog—from your distributor or write us for your copy.

CHICAGO STANDARD TRANSFORMER CORPORATION

3503 ADDISON ST. • CHICAGO 18, ILL.

Export Sales: Roburn Agencies, Inc., 431 Greenwich St., New York 13, N. Y.

TAPE RECORDERS

Tapes—Accessories
Nationally Advertised Brands
UNUSUAL VALUES
Send for Free Catalog
DRESSNER
69-02 RE: 174 St.
Flushing 65, N. Y.

MERITAPE
Low Cost, High
Quality Records
ing Tape—in
boxes or cans.

NEW & BETTER TEST CONNECTOR



Ask your jobber for the new E-Z-HOOK Test Probe. Patented hook design . . . stays on . . . easier to use . . . safer. Ideal for scope and meters. Built-in Terminal Board . . . saves time—money . . . easy to build own detector and special test assemblies. The most for \$1.39! E-Z HOOK TEST PRODUCTS, 1534 Woodburn, Covington, Kentucky.

ENGINEERING B. S. DEGREE IN 27 MONTHS

Prepare for unlimited opportunities of the Electronic Age! Earn your B.S. degree in 27 months at Indiana Technical College. Intensive, specialized course. Comprehensive training in math and electrical engineering, advanced radio theory and design, television, electronics. Modern laboratories. Low rate. Also B.S. DEGREE IN 27 MONTHS in Aeronautical, Chemical, Civil, Electrical and Mechanical Engineering. G.I. approved. Enter September, December, March, June. Earn part of your expenses in Fort Wayne while studying. Write for catalog.

INDIANA TECHNICAL COLLEGE
1796 E. Washington Blvd., Fort Wayne 2, Ind.

Please send me free information on B.S. ENGINEERING DEGREE IN 27 MONTHS as checked.
☐ Electronics ☐ Chemical ☐ Aeronautical
☐ Civil ☐ Mechanical ☐ Electrical

Name _____

Address _____

new

Tubes Transistors



New releases this month run the gamut from improved image orthicons to silicon diodes. Transistor-wise, this month's feature is a unit capable of delivering 3 amperes.

Image orthicons

The 5820, for black-and-white, and the 6474, for three-tube color cameras, are improved image-orthicon television camera tubes produced by RCA. A Micro-Mesh screen, a 750-mesh unit, replaces the 500-mesh screen heretofore standard in both tube types.

The mesh of 750 lines per inch eliminates all traces of moiré patterns and is "more than adequate" for the present 525-line TV system. So fine is the grid forming the mesh that the minute openings represent more than 60% of total screen area.

Power transistors

The H5, H6 and H7 have been announced by Minneapolis-Honeywell Regulator Co. These germanium p-n-p alloyed junction power transistors (see photo) are hermetically sealed and designed for operation on 28-volt systems where they can deliver 3 amp-



eres. They are capable of dissipating 10 watts at a case temperature of 158° F. Maximum emitter current is 3.5 amperes rms; maximum base current 500 ma rms. Maximum power conductance ratings are: H5, 35 mhos; H6, 71 mhos; H7, 141 mhos. Average cut-off frequencies are: H5, 12.5 kc; H6, 10 kc; H7, 8.5 kc.

Silicon rectifiers

The 1N537 and 1N538 silicon rectifiers have been announced by G-E. Occupying a total volume of only .03 cubic inch and weighing .07 ounce, the diodes come with pigtail leads. Both are hermetically sealed.

The silicon rectifiers are rated at a maximum dc output current of 250 ma at 150°C. They may be designed into circuits for outputs of up to 750 ma where lower temperature conditions prevail. Maximum leakage current over their entire ambient operating temperature range of -65°C to 150°C is 0.5 ma.

High current loads can be carried

NEW TUBES AND TRANSISTORS (Continued)

without the use of any heat sink. Thus, the new units are suitable for computer power supplies and for guided missiles, blocking, magnetic amplifiers, other low-leakage applications and a wide variety of high-temperature electronic equipment power supplies.



The 1N537 is rated at a maximum peak inverse voltage of 100; the 1N538 at 200. Maximum surge current for both is 10 amperes. Full-cycle average forward voltage drop is a maximum of 1/2 volt for both.

6CD6-GA

The 6CD6-GA, a high-perveance beam power tube of the glass-octal type for use as a horizontal-deflection amplifier tube in TV receivers, has been announced by RCA. It is smaller and more compact than the 6CD6-G, but features a modified mount design to maintain the same high perveance and to permit operation at higher ratings.


The 6CD6-GA has a maximum peak positive-pulse plate voltage rating of 7,000 and a maximum plate dissipation of 20 watts. These ratings in addition to low mu-factor, high plate-current rating at low plate voltage and a high operating ratio of plate current to grid-2 current enable a 6CD6-GA, in suitable circuits, to deflect fully picture tubes having a deflection angle of 90°.

Like the 6CD6-G, its structure provides for cool operation of both grids 1 and 2 to minimize grid emission and also for maximum distribution of heat to prevent plate hot spots.

The 6CD6-GA is unilaterally interchangeable with the 6CD6-G. Its heater requirements are 2.5 amperes at 6.3 volts.

2N170

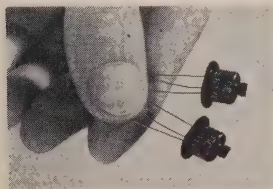A new high-frequency n-p-n transistor for radio hobbyists, the 2N170, was announced by G-E. Its introduction marks the first time the price of a high-frequency transistor has reached the level of equivalent electron tubes. It is being sold at "considerably less than \$2."



In a typical common-emitter circuit the 2N170 has a power gain of 22 db



ACTUAL SIZE

PRECISION 110

'THIN-LINE' POCKET-SIZE Model
20,000 ohms-per-volt V.O.M.

Model 110:
Complete with vinyl case, ohmmeter batteries, heavy-duty banana-plug test leads and manual. Dimensions 1 1/4" x 3 1/2" x 5 3/8". Shipping weight 3 lbs. Net Price \$32.50

— Also Available —
Model 100: Similar to Model 110 above, except 1000 ohms per volt AC and DC. Net Price \$26.95

- Full-Range Instrument Performance
small-sized instrument convenience
- Fits Your Pocket... Fits Your Tube-Caddy...
the ideal extra V.O.M. for field and service
- Extra-High Sensitivity
20,000 ohms per volt DC... 5000 ohms per volt AC
- Extra-Low... Extra-High Voltage Ranges
1.5 volts full-scale extra-low AC and DC
3000 volts full-scale extra-high AC and DC
- Extra-Wide Resistance Ranges
self-contained up to 20 megohms
- Complete Current Ranges Up to 600 ma
- Complete Decibel Ranges from -20 to +70 db
- 3 1/2" Full-View Meter... Long, Easy-Reading Scales



PACE
THE METER OF PRECISION

Available at leading electronic parts distributors.

PRECISION Apparatus Company, Inc.
70-31 84th Street, Glendale 27, L. I., N. Y.


Export: 458 Broadway, New York 13, N.Y., U.S.A. • Cables: MORHANEX
Canada: Atlas Radio Corp. Ltd. • 50 Wingold Ave., Toronto 10, Ontario

SERVICE DEALERS! You Can't Afford to Miss This!

PLUS profits on every service call



MODEL 200:
Completely
New,
Automatic.
100-300
Watt Loads.

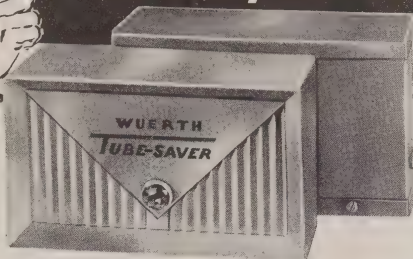

MODEL 100A:
Adjustable
Time Relay.
150-400
Watt Loads.
U.S. Pat.
2,756,382



WUERTH TUBE-SAVER

Triples Life of all Tubes TV HI-FI

- Triples Tube Life verified by independent tests
- Keeps Screen Bright
- Keeps Picture Stable
- Hi-sound Fidelity
- Used by Armed Forces
- Virtually Eliminates Burned-out Tubes

This amazing new invention lengthens tube life and brings new Plus Profits. Every service call you make means a sure sale. Builds store traffic, makes friends. Saves tubes from "starting shock" by Thermal Cushion Action. Arrests untimely breakdowns of expensive tubes and vital components. Saves picture tubes.

35 MILLION TV, HI-FI SET OWNERS

New Automatic Model 200 is entirely self-adjusting. Red Jewel Pilot light shows precise timing of "Thermal Cushion Action." Equally good for old or new sets. Simply plug it in. Pays for itself in saving of tubes. Every set owner a ready buyer with 35 million set owners waiting to be sold. Get in the profit parade of this newest, most wanted television accessory. Ask your wholesaler, or write us.

\$9.95 LIST
BOTH MODELS



SERVICE DEALERS & JOBBERS: Write us today for full details of our SPECIAL INTRODUCTORY OFFER that spells new Plus Profits for you.

Copyright 1955

WUERTH TUBE-SAVER CORPORATION

9125 LIVERNOIS AVENUE, DETROIT 4, MICH.

The important OCTOBER issue of RADIO-ELECTRONICS on sale SEPT. 25. Reserve your copy now!

EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 2 to 40 WPM. Always ready—no QRM.

ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.



INSTRUCTOGRAPH COMPANY

4701 Sheridan Rd., Dept. RC, Chicago 40, ILL.

MUST MOVE OUR WAREHOUSE

Set Builders — Experimenters

GIANT SURPRISE KIT \$4.95

25-30 lbs. of brand new RADIO PARTS . . . no junk . . . Transformers, Filter and Bypass Condensers, Resistors, Wirewound, Carbon, Volume Controls, Sockets, Wire, Variables, Chassis and Gang Switches. Parts that every Service Man, Experimenter or Ham needs. Express or Freight Shipments Only. No C.O.D.

NEWARK SURPLUS MATERIALS CO.

324 PLANE ST., Newark, N. J.

NEW TUBES

(Continued)

at 455 kc, making it useful in if circuits. Alpha, or maximum frequency cutoff with useable gain, is 4 mc. Maximum ratings are: collector to base voltage (emitter open), 6; collector current, 20 ma; emitter current, —20 ma; collector dissipation (25°C), 25 mw.

6903

A head-on type of multiplier phototube, the 6903 is intended for detecting and measuring ultra-violet radiation and for other applications involving low-level radiation sources.

The 6903 is constructed with a fused-silica faceplate which transmits radiant energy in the ultra-violet region down to and below 2,000 angstroms. At 2,000 angstroms, the spectral sensitivity is more than 50% of the maximum response. The spectral response covers from about 2,000 to 6,500 angstroms, maximum at approximately 4,400 angstroms.


Other design features include a semi-transparent cathode having a minimum diameter of 1½ inches; 10 electrostatically focused multiplying (dynode) stages; a focusing electrode with external connection; the capability of multiplying feeble photoelectric current produced at the cathode by a median value of 400,000 times.

5725

A "premium" sharp-cutoff pentode of the 7-pin miniature type, the 5725 is intended particularly for use in gated amplifier circuits, delay circuits, gain-controlled amplifiers and mixer circuits. Constructed to give dependable performance under conditions of shock and vibration, this tube, which is similar to the 6AS6, is especially suited for use in critical industrial applications and in mobile and aircraft equipment.


The 5725, announced by RCA, includes separate base-pin terminals for grids 1 and 3. Each of these grids has a sharp-cutoff characteristic and can be used independently as a control electrode.

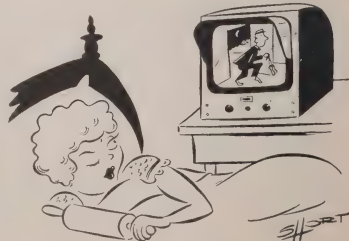Featured in the design of the 5725 is a compact structure in which special attention has been given to features which improve its strength for both shock and vibration, and a pure tungsten heater having high mechanical strength to give long life under conditions requiring frequent "on-off" switching. END



Please print the circuit of a simple transformerless type audio amplifier for use with a high-output crystal pickup.—N. J. S., Blowing Rock, N. C.

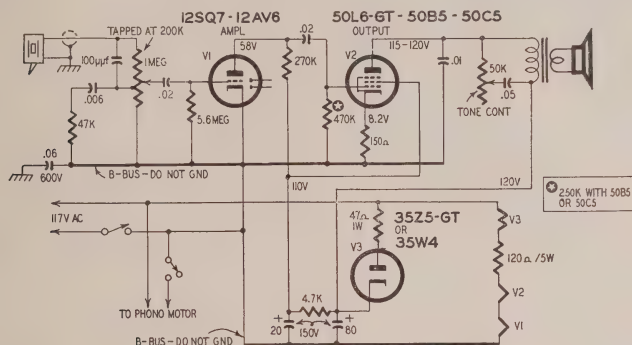Use caution when constructing this and other transformerless apparatus and take care to minimize shock hazards by completely enclosing the ampli-




Here is the circuit of a simple amplifier that will deliver a maximum output of approximately 1.5 watts. You can use any of the tubes listed in any combination.

fier in a nonmetallic cabinet with any protruding mounting screws and bolts insulated or countersunk. Use a plastic tone arm and spring type slip-on knobs on the controls.

I have an ac-dc radio-phonograph to which I'd like to add inverse feedback and a tone control. What general rules that I can follow in making the

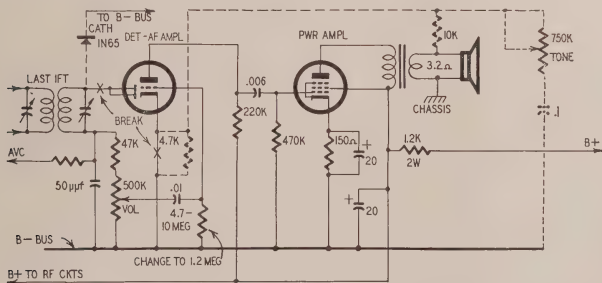a 6SQ7, 12AT6 or similar type and the power amplifier is a 50C5, 50L6-GT or equivalent. Inverse feedback and tone control circuits are shown in dashed



modification?—H. O. M., Greensboro,
N. C.


The diagram shows a typical audio circuit as used in an ac-dc type radio or phono amplifier. The input stage is

lines. The feedback network is designed as described in "Improving Your TV Audio" in the January, 1956, issue. The tone control is between feedback loop and ground.

Several TV boosters, phono pre-amplifiers, control units and similar devices have a built-in switch or relay that turns them on when the audio

amplifier, TV set or other equipment is turned on. Please explain how these units work and tell me where I can obtain one.—L. A. W., Florence, S. C.

at your Jobber . . .

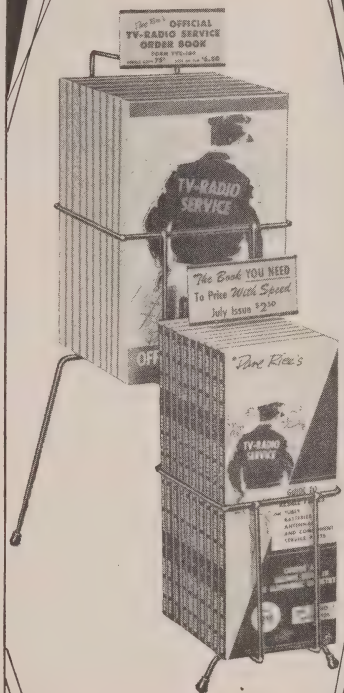

*In this rack you will find
The Biggest Service Help
The Largest Value
In These Perfect Partners*


Dave Rice's Official Pricing Digest—a quick check for over 60,000 prices—revised 4 times every year. Pocket sized.

and

Dave Rice's Official TV-Radio Service Order Book which provides separate listings for picture tubes, receiving tubes, parts and components, serial numbers, labor and state and local taxes. 5½x8½—50 sets of triplicate orders—carbons bound in.

ELECTRONIC PUBLISHING CO. INC.
180 North Wacker Drive Chicago 6, Illinois

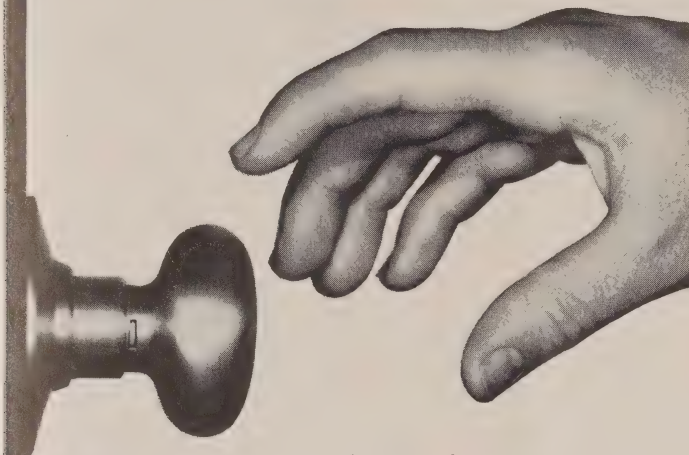How to open the door to a whole new world of opportunity



The doors of IBM open into the newest, fastest-growing, perhaps the one "unlimited" field in electronics: digital computer development, design, manufacture and installation and maintenance in the field. Furthermore, IBM is an acknowledged leader and pioneer in this field, where the opportunity to advance is always open.

Greater responsibilities await the ambitious man at IBM. Advancement is based solely on individual performance. Capability, talent and creative ideas are soon rewarded.

Excellent salaries prevail—and extensive training, liberal benefits, good working conditions, superb facilities.

Stability is assured by a 42-year record of solid growth through diversified service to all industry.

Field Engineers. You will be responsible for the performance, evaluation, reliability testing, and maintenance of the world's largest computer for Project Sage—the electronic "nerve center" of America's continental air defense warning system.

Immediate assignments in the East Coast and Midwest areas.

Liberal expense allowance

Open the door for *your* opportunity now by writing, giving details of education . . . and experience, to: Nelson O. Heyer, IBM, Room 3109, Military Products Division, Kingston, New York.

Customer Engineers: opportunities are also available, locally, for technicians to service IBM machines, after training with pay. Contact your nearest IBM office.

DATA PROCESSING
ELECTRIC TYPEWRITERS
TIME EQUIPMENT
MILITARY PRODUCTS


IBM
®

INTERNATIONAL
BUSINESS MACHINES
CORPORATION

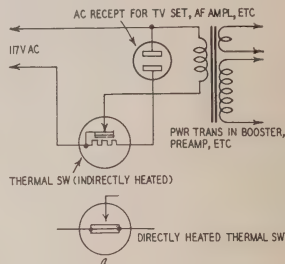QUESTION BOX

(Continued)

Thermal switches or relays have a bimetallic strip that bends and closes a contact when heated. In some units the bimetal strip is heated directly by current flow through it. Others have an auxiliary heater that carries the current drawn by the main equipment.



In the average unit the contacts are rated at around 0.5 amp at 115 volts and the load drawn by the main equipment (amplifier, TV set and the like) ranges from 0.1 to 3 amps. The diagram shows the circuit connections, using an indirectly heated unit. The diagram of a directly heated unit is shown at *a*. The switch may be a Blonder-Tongue TR-3 or equivalent.

VOLTMETER QUERY


I'm having trouble with the transistorized voltmeter described in the December, 1954, issue. I used high-grade parts throughout. The calibration is good up to about half-scale on all ranges. The top half of each range is very crowded. For example, on the 50-volt range 25 volts input will deflect the meter to 0.5 ma (mid-scale) but 50 volts deflects the needle only up to 0.55 ma. The other ranges exhibit the same trouble. I tried replacing the CK722 and even substituted a CK722 for the CK721 without improving the performance. What causes this trouble and how can I eliminate it?—L. W. G., New Kensington, Pa.

Mr. Turner reports that this trouble is caused by excessive static collector current (I_{co}) in the first transistor. This drives the second transistor to saturation and crowds the readings above mid-scale. This can be cured by selecting a transistor with low I_{co} . Ordinarily these transistors have such low static collector current that this trouble does not occur. Apparently you had the misfortune of purchasing two units with unsatisfactory characteristics for this application. **END**

CORRECTION

Mr. Cerveny states that there is a transposition of text material on page 35 in his article "Color Demodulator Alignment" in the July issue.

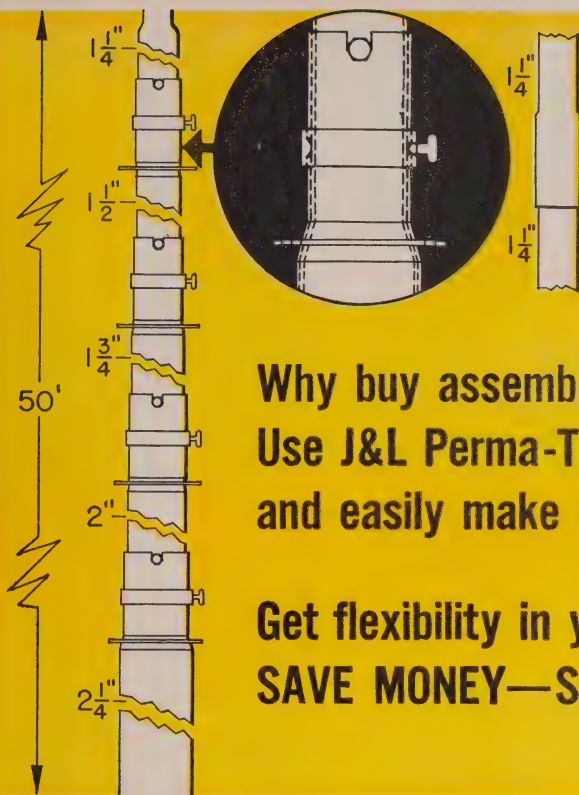The text beginning with the sentence starting on line 11 of the third column and continuing through the 24th line should be inserted between lines 58 and 59 of the second column.



Same 1 1/4-inch piece of Perma-Tube can be used for telescoping masts or with another 1 1/4-inch piece to make smaller 2-piece masts.

Why buy assembled telescoping masts?
Use J&L Perma-Tube in 10-foot lengths
and easily make your own

Get flexibility in your stock
SAVE MONEY—SAVE SPACE

Only J&L Perma-Tube offers:

- Joint design which provides instant field assembly.
- Machine-fitted joints that insure close tolerance for high strength and rigidity.
- Guy wire ring position that eliminates all binding and guy wire interference.

Buy only a carton each of five different sizes of Perma-Tube (1 1/4 to 2 1/4-inch) and make any telescoping TV mast up to 50 feet in height. Hardware—cotter keys or bolts, clamps and guy rings—may also be secured from your distributor.

You can now “tailor-make” your own TV masts up to 50 feet high by using standard 10-foot lengths of 16-gage Perma-Tube—and save money. Five diameters are available in easily-handled cartons from your local distributor. Largest base section OD is 2 1/4 inches and each telescoping section is 1/4-inch smaller, the smallest section having an OD of 1 1/4 inches.

Corrosion-resistant Perma-Tube is treated with Vinsynite—then coated both inside and outside with a metallic vinyl resin base. It's made of a special, high-strength, J&L steel tubing. A 10-foot section of 1 1/4 inch diameter by 16 gage is capable of supporting a weight at its center point of 200 pounds with a minimum of deflection and permanent set.

J&L Perma-Tube — best for strength and rust protection

Jones & Laughlin
 STEEL CORPORATION • PITTSBURGH



NEW!

flexlife

PLASTIC INSULATION

makes
ALL
COLUMBIA
Microphone
Cable

more
flexible
more
durable



Our NEW Flexlife Plastic Insulation now used in our microphone cables and test lead wire provides flexibility as good as rubber with much neater appearance and far greater life.

Send for your samples today! no cost or obligation.

Available from leading distributors

Columbia
WIRE & SUPPLY CO.

2850 Irving Park Road
Chicago 18, Illinois

Technotes




PHILCO 48-1000

An extremely dark picture accompanied by unstable sync was found to be due to a leaky capacitor connected between the triode and diode plates of the age amplifier tube. This capacitor leaks and disturbs normal age action. It places a positive voltage on the age bus which is then fed to the grids of the rf and if tubes. Replace the capacitor with a .01- μ f 600-volt molded type.
—J. E. Ryan

MAGNAVOX CHASSIS CT 358

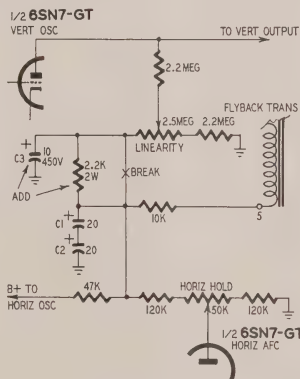A pronounced hook appeared in the top 20 lines or so of the picture. The cause was pulses from the vertical oscillator feeding back into the horizontal circuits despite electrolytics C1 and C2. The pulses upset the horizontal oscillator directly and, via the horizontal afc, indirectly. This caused the hook at the top of the picture.



The remedy consists of adding a decoupling filter in the feed to the vertical linearity control. This line is the B-plus supply to the vertical oscillator, the source of the offending pulses. Break circuit as shown, insert a 2,200-ohm 2-watt resistor and the bypass capacitor C3, a 10- μ f 450-volt electrolytic.—E. A. Chang


HORIZONTAL JITTER

Shaking of bushes in a strong side wind is a good description of the jitter displayed intermittently on a Sparton model 22312. After several false starts, the age line was grounded by a jumper. The trouble did not recur after hours of monitoring. Further checking disclosed that a 2- μ f, 50-volt, positive-ground capacitor hooked on the age line to filter the spurts of age voltage

SPECIFY NORELCO

**F.R.S.*

for Top Performance
speaker replacements

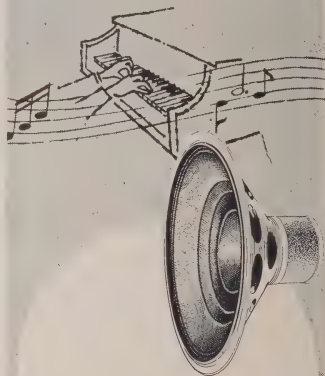

Based on economy alone, any one of the Norelco FRS twin-cone speakers is your best choice.

Aside from price, these speakers have been designed and manufactured by audio craftsmen—to produce unexcelled sound qualities. In a single FRS speaker, sound is reproduced so perfectly that listeners have difficulty in distinguishing recorded performance from those which are live.

FRS Twin Cones are both operated by the same magnet and voice coil. The smaller cone radiates frequencies above 10,000 c/s and diffuses lower frequencies. Frequencies below 10,000 c/s are generated by the larger cone while reflecting frequencies above this frequency.

Price from \$59.98 to \$6.75 in all standard impedances and sizes from 12 inches to 5 inches.



ADD TO... and improve any sound system with **Norelco®**
*FULL RESONANCE SPEAKERS



Send to Dept. D-9 today for more details.


North American Philips Co., Inc.
100 East 42nd Street
New York 17, N. Y.

RADIO-ELECTRONICS

delivered by the age keyer had an intermittent loss of capacitance. Disconnecting this capacitor, with the set performing normally, produced the jitter. The unfiltered pulses resulted in a spurious modulation of the horizontal sync by the spurts on the age line feeding through the if.—A. Philip Monroe

G-E MODEL 21T7

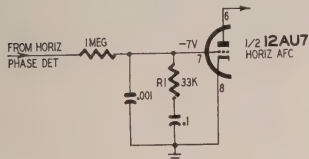A jagged effect on circles, like the teeth on a cog wheel, was the complaint of the owner of this set. The effect was more pronounced than simple interlace trouble resulting in the pairing of lines with somewhat similar distortion of circles.



Resistance checks localized the trouble to R1, 33,000 ohms, which had increased in value to about 150,000 ohms. This resistor (see diagram) is part of the grid filter network of the 12AU7 horizontal reactance tube. Replacing the resistor eliminated the cogwheels in the picture.—Alfred Roberts

FAINT PIX ON WARMUP

On an RCA KCS77 chassis the picture would come on very faint when the set was turned on. After about 10 minutes the picture would suddenly blossom to full strength. I checked the picture and horizontal output tubes. All were normal, except that one of the 6BQ6's had a loose plate cap. I put the output tubes back and, when the picture came on weak, I pressed down on the loose plate cap. This caused the picture to jump to full strength. I dented the

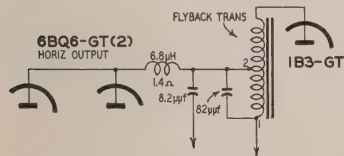


plate cap for better contact with the plate wire and resoldered this joint.

The trouble was that only one of the horizontal output tubes (see diagram) was functioning and the loss of high voltage produced a dim picture. As the heat from the tube with the bad cap expanded the plate wire, after about 10 minutes it contacted the cap, restoring normal operation.—A. R. Clawson

PURE OIL 518 RADIO

In case of birdies due to if oscillations, decouple the B-plus feed to the screen grid of the 12SA7 converter by inserting a 2,200-ohm 1-watt resistor between the screen grid and the electrolytic capacitor. In place of the pres-

THE Senco Line is "Mighty Fine"

Each Senco item is designed with the serviceman in mind. Created by highly qualified design and service engineers to **SAVE COSTLY SERVICE** time, Senco products **HAVE RAPIDLY GROWN** in acceptance—Now are leaders in low cost test instruments and accessories. Attractive packaging, informative literature and unsurpassed quality, truly guarantee a "line that is mighty fine."



Model FC4-66

Dealer Net

With Leads \$2.95

SENCO FILAMENT CHECKER

Quickly finds any open filament. Especially handy for servicing series filament TV sets and radios; only checker that checks all octals, localts, 7 and 9 pin minatures automatically. Also continuity and voltage tester.


Without Leads \$2.75

NEW SENCO TRANSISTOR CHECKER

Now wanted and needed by every serviceman, approved by leading mfrs. Provides these 4 important checks on all transistors: Open—short—current gain—leakages.

Checks forward to backward resistance of all diodes.

Dealer Net \$15.95

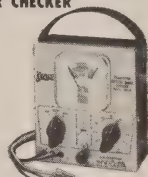

Model TDC22



UP-DOWN VOLTAGE BOOSTER


Model LB2

A practical line voltage regulator—half the price of others. Increases power line voltage ten volts, decreases it ten volts, or restores it to normal with the flick of a switch, rated up to 300 watts. Handles all black and white TV sets. Dealer Net \$5.97

Model LB2N

Same as Model LB2, but with neon lamp. Glows @ 126V indicating high line voltage.

Dealer Net \$7.17

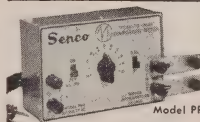

Model PP2

PEAK TO PEAK COMPARISON METER

A completely assembled Peak to Peak Meter at half the price of a kit. A must when servicing AGC, Sync Separators, Etc. Dealer Net \$8.75



Model LC-2

TUBE AND CAPACITOR LEAKAGE CHECKER

A highly accurate tester for detecting leakage between tube elements. "Two Testers In One" A reliable instrument for indicating capacitor leakage with 50 volts applied. Quickly indicates * Grid to cathode leakage * Grid emission * Heater to cathode leakage * Gassy tubes Checks 70 Critical Tube Types Complete with Leads and Wired \$24.95 Kit form \$19.95 Leatherette Carrying Case \$2.00


ALIGN-O-PAK BIAS SUPPLY for TV ALIGNMENT and AGC TROUBLE-SHOOTING



Model BE3

NOW—Provides any DC voltage from 0 to 18 volts DC positive or negative. Completely isolated power supply with less than 1/10 of 1% ripple.

Dealer Net \$7.85

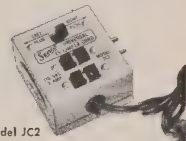

Model JC2

UNIVERSAL TV JUMPER CORD

Jumps power from TV back to chassis. No more plugging into wall sockets—moving of furniture—winding and unwinding cords. It's universal—fits any set. NO SHOCK HAZARD.

Dealer Net \$1.95

All products carry standard 90 day warranty. Available at leading distributors everywhere. Manufactured by **SENCO SERVICE INSTRUMENTS CO.** 171 Official Road • Addison, Ill.

Attention . . .

Service Technicians' Associations

Club Members
Student Groups

Special subscription rates to RADIO-ELECTRONICS are available to associations, clubs, schools, employe groups, etc. For information write—

G. Aliquo
RADIO-ELECTRONICS

154 West 14 St., New York 11, N.Y.

Up-to-the-minute!



This brand new edition of **MANDL'S TELEVISION SERVICING** gives you the most detailed trouble-shooting procedures and servicing techniques for every TV flaw.

MANDL'S TELEVISION SERVICING Rev. Ed.

By **MATTHEW MANDL** \$6.50

Every feature that made this book invaluable to thousands of technicians and servicemen has been retained. In fact, each subject has been re-examined in the light of recent developments and brought completely up-to-date.

EASY TO LEARN

Simple, clear explanations of the fundamentals of monochrome and color TV. Complete servicing instructions for UHF and VHF.

- Plus:**
- Cascade tuners, automatically focused tubes and other devices.
 - The latest types of tuners and circuits (including theory and servicing of printed circuits).
 - Transistor theory and servicing principles.

You'll learn the time-saving methods used by the experts without unnecessary theory or involved mathematics.

COMPLETE EDUCATION IN SERVICING

The Master Index to Common Television Troubles—which has been expanded to include many new references—lists the various trouble symptoms with the possible causes for each and the page on which full servicing instructions are given.

Every step is fully illustrated with large, clearly marked schematics, and other helpful illustrations.

Become An Expert In...

CLOSED - CIRCUIT AND INDUSTRIAL TELEVISION

By **EDWARD M. NOLL** \$4.95

This one book could guarantee your future! It gives you, in clear non-mathematical terms, both the theory and practical techniques needed to handle closed-circuit transmission systems, scanning processes, picture signals, sync and deflection generators, cameras, and video amplifier systems.

THE ONLY BOOK IN ITS FIELD

This specially designed, paper-bound volume is packed with technical know-how, industrial applications, and hundreds of photographs and drawings.

2 one-way tickets to the best jobs in TV

Study one or both FREE for 10 days without obligation

CLIP AND MAIL TODAY

The Macmillan Company, Dept. RE-2
60 Fifth Ave., New York 11, N. Y.

Please send me:

- ☐ **MANDL'S TELEVISION SERVICING \$6.50**
☐ **CLOSED-CIRCUIT AND INDUSTRIAL TELEVISION \$4.95**

I will either remit the full price or return the book(s) in 10 days. (Save: Send check or money order now and we pay delivery charge.)

Name
Address
City Zone State


TECHNOTES

(Continued)

ent .01- μ f bypass capacitor from the screen grid to chassis, insert a 0.1- μ f capacitor.—E. A. Chung

MILKING A PIX TUBE

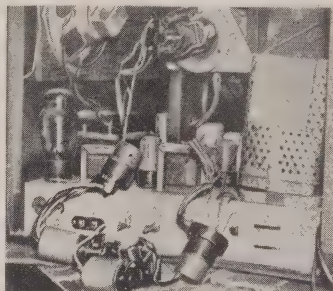
Like the farmer who tries to milk the last drop from his cow, this set owner (see photo) used not one brightener or rejuvenator but four! Despite this array of voltage boosters, the picture-



tube heater did not fail. I'm surprised he didn't try to buy rejuvenators for the rest of the tubes!—*Alfred Roberts*


DU MONT RA-340/341 342/343

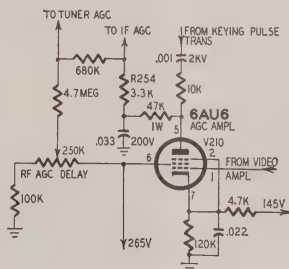To prevent horizontal line displacement due to erratic firing of the horizontal oscillator when no station is being received or when the fine tuning



We are closing out the balance of the KITS that we still have in stock at the new low price as shown in the bargain column at right. **\$94.99** for only

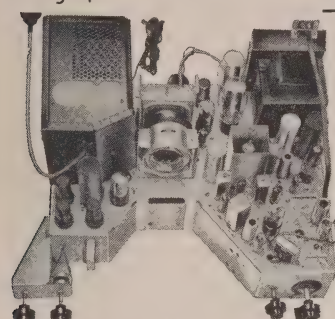We are closing out the balance of the KITS that we still have in stock at the new low price as shown in the bargain column at right. **\$94.99** for only



\$94.99

Build your own

#630

Super Deluxe TV CHASSIS

With a

#630 SUPER DELUXE 31-TUBE TV KIT
OPERATES 16" TO 21" PICTURE TUBES • Engineered in strict adherence to the genuine RCA #630 plus added features • FULL 4MC. BANDWIDTH • CATHODE RAY TUBE • FULL 100% CONVERSION • NON-FLICKER • POWER TRANSFORMER • KEYS • AGC • 12" SPEAKER • CONDENSERS AND RESISTORS at rated capacities and tolerances. You receive a COMPLETE SET OF PARTS and TUBES, everything needed is included (less wire & CRT). All I.F. Coils and Transformers are factory pre-aligned and tuned. You will enjoy building it with a LIFE-SIZE easy to follow step-by-step INSTRUCTIONS* included with each kit. **NOTHING BETTER AT ANY PRICE!**
 Special for this sale.....only **\$94.99**


CUSTOM-BUILT CABINETS FROM FACTORY TO YOU

3 LEADING 1956 STYLES

in Mahogany or walnut (blond 10% extra) • Ready drilled for use • 630 TV chassis and cut out for only 16 1/2" • 20" • 24" picture tube at no extras in price • Also supplied with undrilled knob panel for any other TV set • **EVERYTHING NECESSARY** for an easy perfect chassis and CRT assembly is included • Each cabinet is delivered complete as pictured with mask, safety glass, mounting brackets, backboard, back-up hardware and assembling instructions • **FACTORY** in an air conditioned carton from **FACTORY TO YOU**

GEM \$35.91

WESTCHESTER

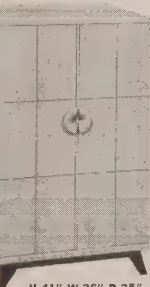

• 674

H-25" W-26" D-22"

—CBS, DUMONT OR THOMAS PICTURE TUBES

BRAND NEW in Factory Sealed Cartons — With a Full Year Guarantee
THESE SPECIAL PRICES ARE FOR THIS SALE ONLY

17"	# 17BP4A	\$21.66	21"	# 21EP4B	\$29.21	24"	90° # 24CP4A	\$44.89	27"	90° # 27EP4A	\$69.31
				Aluminum			Aluminum			Aluminum	

21" TV CONVERSION KIT

Convert any Size, any Make TV RECEIVER to operate the 21" or any 70° Picture Tube. COMPLETE SET OF ESSENTIAL PARTS includes matched set of Todd 70° COSINE DEFLECTION YOKE and TODD HV FLYBACK TRANSFORMER, FOCALIZER, 20KV FILTER, DRIVE TRIMMER, LINEARITY COIL, CONDENSERS, RESISTORS.

List Price **\$22.50**

Special for this Sale..... **\$12.95**
Incl. CONVERSION MANUAL Step-by-Step Instructions

27" TV CONVERSION KIT

Convert any Size, any Make TV RECEIVER to operate the 27" or any 90° Picture Tube. **COMPLETE SET OF ESSENTIAL PARTS** includes matched set of Todd 90° COSINE DEFLECTION YOKE and TODD 18KV FLYBACK TRANSFORMER, 30KV FILTER, 6AX4 TUBE, YOKE BRACKETS, WIDTH CONTROL CONDENSERS, RESISTORS.

List Price \$20.75

Special for this Sale.....
Incl. CONVERSION MANUAL Step-by-Step Instructions,
illustrations for mounting TV Sets flush with wall ex-
tending into garage, closet or wall recess included.



H-39" W-25" D-23"

#630^{SUPER}_{DE LUXE} TV CHASSIS

LICENSED UNDER RCA PATENTS
COMPLETE READY TO PLUG IN AND PLAY
TOP BRAND (\$200 value) for 21", 24"
or 27" Picture Tube

Special for this Sale only

\$160.20

\$169.20
(less CRT)

Catalog on request

STANDARD CASCODE TUNER


For better all around performance
Complete with tubes and Brooks CASCODE
MANUAL with step-by-step instructions and
all extra parts needed. **\$15.97**

- PULSE KEYED AGC KIT

Finest, most accurate and the easiest Kit to install in any make TV RECEIVER including the No. 630 Improves performance and insures a steady picture.

COMPLETE SET OF PARTS \$2.95
Including 6AU6 tube & Instructions

UNIVERSAL Picture Tube MOUNTING BRACKETS

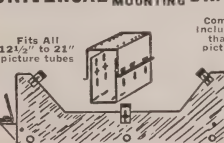

\$4.97

BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N.Y.

TELEPHONE
Portland 7-2359

RADIO-ELECTRONIC CIRCUITS (Continued)

making a call. Plug the master station's line cord into the adapter and run three leads from the doorbell circuit to the adapter as shown in the diagram.

When the bell rings, the transformer voltage energizes the coil of RY1 through the normally closed contacts A and C. The relay operates, opening contacts A and C and locks in through contacts B and C and the normally closed contacts of thermostatic time-delay relay RY2. Contacts A, B and C are adjusted for a make-before-break arrangement (C contacts B before breaking with A) to prevent chattering and insure proper operation. Energizing the relay also closes contacts D and E to apply power to the intercom through the receptacle. (The intercom's line switch must be on at all times when using the adapter.)

RY2 is an Amperite type 115C120 whose contacts open 120 seconds after voltage is applied to its heater. It opens the circuit and turns off the intercom after 2 minutes—a desirable feature, especially when no one is at home. The spst switch is thrown to ON when the conversation exceeds 2 minutes and is thrown to OFF when it ends.

RY1 is a Guardian series 200 or equivalent type with dpdt contacts and an ac coil to match in the voltage supplied by the bell transformer.

In systems with more than one remote, each additional remote turns on the master with a normally open push-button switch connected across terminals 2 and 4 on the adapter's terminal strip.

SCOPE TESTS FLYBACKS

Meter type flyback testers are almost nonexistent here in England. British TV technicians use a scope to check flyback transformers for shorted turns. The method used could hardly be simpler. All you need is access to the scope's sawtooth sweep voltage! If it is not available at the front panel, you can install an output jack.

Turn the set off and apply the sawtooth voltage to the transformer primary through a .001- μ f capacitor and connect the scope's vertical input leads across the primary as in Fig. 1. In many cases it will be most convenient to attach the leads to the horizontal output plate and the damper cathode. The grounded vertical input lead may also be connected to points 1, 2 or 3 with equally good but slightly different results. On some sets this connection can be made to the chassis.

Briefly here's how it works: The flyback from the scope sets the transformer ringing just as a normal flyback in the set would. Without the damper to stop them the oscillations continue for perhaps 10 to 15 cycles or more, gradually dying away. Being triggered by the scope's sweep signal they are automatically synchronized and a steady trace as in Fig. 2-a will appear on the scope. This is the normal pattern for a good transformer. Any shorted turns in the transformer will damp these

ARKAY Kits . . . lead the field



introducing ARKAY Model FL-30 Hi-Fi Amp & Pre-Amp

new!
new!

SPECIFICATIONS:
Power Output—30 watts @ 1% 1M
Peak Power—45 watts
Output Impedance—4, 8, 16 ohms
Frequency Response— ± 1 db 10-40,000 cps below 28 watts
 $\pm \frac{1}{2}$ db 20-20,000 cps
Hum—Minimum volume—120 db below rated output
Controls—(6) Function selector, loudness, bass, treble, level set, 5 position level compensation control
Tone controls— ± 16 db @ 50 and 10,000 cps

\$49.95

Featuring a transistorized Front End with a reluctance pick-up, this engineering masterpiece assures the finest in high fidelity reproduction. Record equalization for more than 30 labels (LP, RIAA and Eur.) Complete with rose gold panel and black cabinet.



ARKAY Model HFT-7 Hi-Fi AM-FM Tuner

Extremely low noise characteristic. Automatic frequency control with provisions for AFC erase. Allows pinpoint, high selectivity tuning. Foster Seeley discriminator, high efficiency AM loop stick antenna and temperature compensated oscillator circuit.

less cover **\$29.95**



ARKAY Model 14T21 new! TV KIT

Very latest design used in sync. circuits results in excellent stability with extremely low noise characteristics. A. G. C. circuit results in maximum sync. hold characteristics. The only vertical chassis construction, series-string-heater type tubes, vertical retrace blanking circuits, and many more features.

\$79.50



ARKAY Model B-8 Hi-Fi Speaker System

Arky Kit Model B-8 is a new hi-fi speaker system in kit form. Measures 12 x 12 x 24 . . . Is a base reflex, ducted-port and is equipped with a frequency woofer and high frequency exponential speaker together with a variable balance control for adjustment of tweeter.

\$35.95



ARKAY RADIOS

Arky manufactures a complete line of radios unmatched in the industry in quality and performance. They include: transistor portables, table models, multi-band receivers, portables, and many other models. There is certain to be one to fit your requirements.

\$23.95



ARKAY Model FM-6 FM Receiver Kit

Extremely sensitive and stable . . . grounded grid front-end; Foster-Seeley Discriminator. Temperature compensated oscillator circuit. 3 double tuned IF stages, limiter and discriminator give top selectivity and sensitivity.

\$23.95



ARKAY Model PR-3 Personal Portable

For the person who wishes a personal radio that will fit into his pocket comfortably. Uses 3 miniature tubes and makes a handsome gift in a plastic cabinet of modern design. Two earphones can be connected at the same time. Size: 3" x 5" x 1 3/4".

\$12.95

Write today for full details on the remarkable units in the ARKAY line. You will receive our catalogue ABSOLUTELY FREE along with the name of your nearest dealer. Write today to Dept. RE-9.

ARKAY KITS, inc. • 120 Cedar Street • N. Y., N. Y.

LÔÖK . . . what RADIO-ELECTRONICS has in store for you in the months ahead . . .

- **UNDERGROUND ANTENNA**
By Harry J. Miller
- **THE NEW MOTION-PICTURE SOUND**
By Aaron Nadell
- **AUDIO TRANSFORMERS**
By Norman H. Crowhurst
- **A SELF-CALIBRATING MARKER GENERATOR**
By Richard Graham
- **SIMPLE TRANSISTOR SHORTWAVE RECEIVER**
By Joseph Braunbeck
- **IMPROVING SOUND IN AM RADIOS**
By Albert Stratmoen
- **A HOME INTERCOM SYSTEM**
By John F. Millar
- **SELLING EXTRA TELEVISION SERVICE**
By Matthew Mandl

The OCTOBER issue of RADIO-ELECTRONICS goes on sale Sept. 25th at better parts distributors and newsstands

One year \$3.50

SUBSCRIPTION RATES

Two years \$6.00


Three years \$8.00

RADIO-ELECTRONICS

154 West 14th St., New York 11, N.Y.

HI-FI Fen-tone IMPORTS

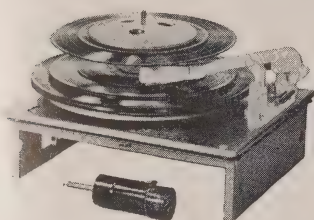
**MANY SURPRISES
HIGHEST FI
LOWEST PRICES**



Fen-tone REX AA

Selected by all Hi-Fi authorities as the most perfect intermix record changer ever built. Americanized version of world-famous Rex A changer. Patented intermix—plays 10 in any size between 6" and 12" without pre-setting. RUMBLE WOW and FLUTTER are practically non-existent. Short spindle supplied for use as Hi-Fi record player. Plug-in shells for all make cartridges. Truly the greatest Hi-Fi value ever!

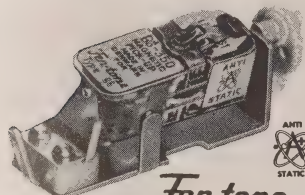Audiophile Net\$59.50
(45 rpm spindle — Net \$3.50 add'l.)



Fen-tone

Scientists have brought you new magic — the B&O A+ professional anti-static cartridges for ABSOLUTE FIDELITY. (Pat. Pending).

Now you can enjoy static-free, dust-free, noise-free reproduction, longer lasting records and prolonged stylus life with a brilliance never before dreamed of!

Audiophile Net:

Dual Sapphire\$ 9.78
Single Sapphire\$ 9.30
Single Diamond\$21.30
Micro Diamond St. Sapphire.....\$21.78



FREE! 1956 *Fen-tone* Catalog. The above are only samples of the many terrific values in the new 1956 *Fen-Tone* Hi-Fi catalog including mikes, tape decks, cartridges, record changers, silent listening devices, etc.


FENTON COMPANY
15 Moore Street, New York 4, N. Y.

Sold through better
Audio Distributors.
See yours today!

West of Rockies,
prices slightly higher.




RADIO-ELECTRONIC CIRCUITS (Continued)

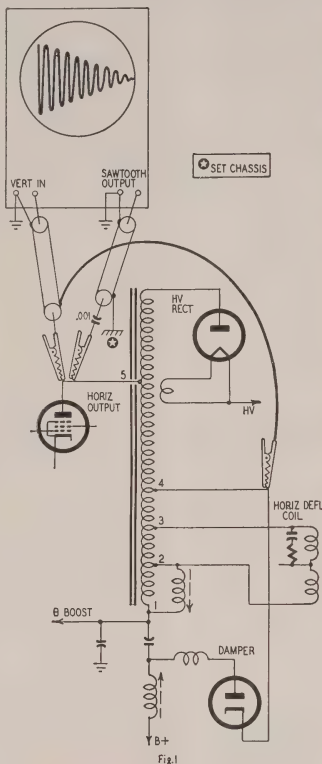

oscillations heavily and the trace will appear as Fig. 2-b.

The choice of sweep frequency is not at all critical. On one make of scope I found 1,500 cycles best, while another gave good results on 3 kc.

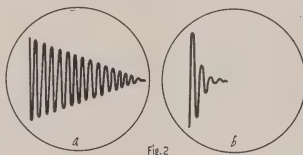Remember that this is a comparative test. The best way is to find which speed most suits your instrument and stick to that. In my case I set the fine frequency control to maximum and



chose position 2 on the coarse frequency control. The same applies to the vertical gain; choose the setting which gives optimum results and always return to that same setting.

When a faulty trace is obtained, first disconnect the deflection coils. If the trace still indicates a short circuit, disconnect the remaining leads from the transformer one by one. If the trace suddenly goes normal, check for a short in the width control, yoke or other component just removed.

Experiment with various types of horizontal output transformers to learn the specific characteristics of each.—*Peter E. Clement, Essex, England* END

don't just say capacitors

Ask For Sprague By Catalog Number

Know what you're getting . . .
get exactly what you want.
Don't be vague . . . insist on
Sprague. Use complete
radio-TV service catalog
C-610. Write Sprague Products
Company, 81 Marshall Street,
North Adams, Mass.

SPRAGUE

WORLD'S LARGEST
CAPACITOR MANUFACTURER

Cartoons

RADIO-ELECTRONICS pays \$3.00 for
good cartoon ideas and \$15 and
up for finished work.

RADIO-ELECTRONICS
154 W. 14 St. New York 11, N. Y.

ask the
"Man-on-the-Roof"
why he prefers

South River

**COMBINATION PEAK
& FLAT ROOF MOUNT**

MODEL PFM-30
(Fits Masts
up to 1 1/2")

MODEL PFM-30 LM
(Fits Masts
up to 2")

Features the patented South River
"Walk-Up" — "Drop-Lock" mast
socket for easy installation on either
Peak, Flat or Pitched roofs. Heavy
gauge pipe mast socket has two
heavy duty screws and locknuts
to secure mast. Factory assembled
and supplied in a heavily plated rust
resistant finish. U.S. PAT. #2734708

WRITE FOR NEW 1956 CATALOG

SOUTH RIVER
MFTAL PRODUCTS CO., INC.
South River, New Jersey

pioneer &
outstanding
producer of
finest line
of antenna
mounts

UNDERCOVER STORY PROVES JERROLD SUPERIORITY

...MODEL 2300 RF AMPLIFIER FOR MASTER TV ANTENNA SYSTEMS

The new Jerrold Model 2300 is a high gain (38 db minimum), high output (.3 volt/channel) broad band amplifier specifically designed for use in large TV master antenna systems. It insures easy, low-cost installation and requires minimum maintenance. But the real reason for better performance and longer life is the undercover story.

SPECIFICATIONS:

FREQUENCY RESPONSE: ± 1 db—Channels 2 thru 6 and 7 thru 13

GAIN: 38 db min.

GAIN CONTROLS: Hi and Lo, 16 db range


TILT CONTROLS: Separate Hi and Lo

RATED OUTPUT (MAX.): .3v/channel for 9 channel operation

TUBE COMPLEMENT: 4-6BQ7A, 2-12BY7A, 1-6CB6

POWER REQUIREMENTS: 117 volts AC 63 watts


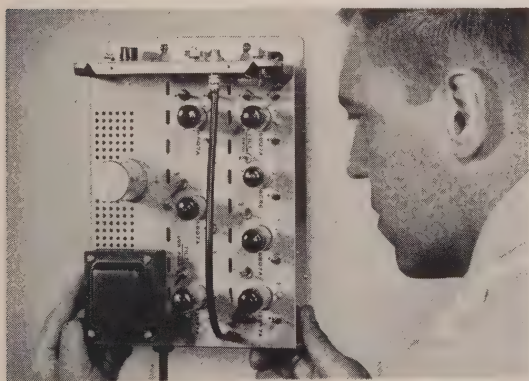
LIST PRICE for MODEL 2300—\$164.00
slightly higher west of the Rockies




Model 2300 may be shelf or wall mounted. It may be used singly or in cascade. It has wide application for TV master system use in motels, apartment houses, hotels, schools and for line extenders in community antenna systems.

Jerrold never compromises with quality—that's why Jerrold equipment always means a more consistent and better picture on the TV screen. Yet Jerrold equipment actually costs less to install, is easier to maintain and lasts longer.

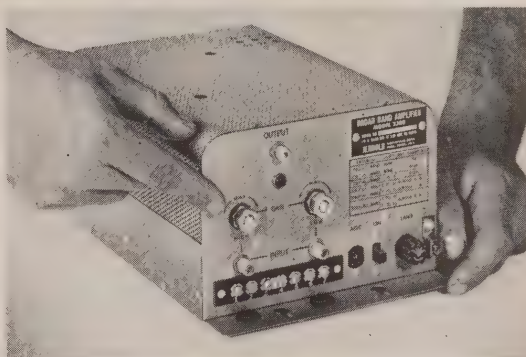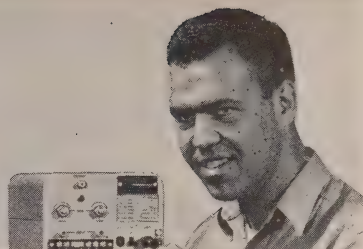For complete information on the Model 2300 broad band amplifier write today for Jerrold Technical Bulletin #544 or see your nearest Jerrold Distributor.



Universal input circuit permits use of a variety of 72 ohm or 300 ohm antennas—broad band or separate hi-lo arrays. An alignment tilt control (reached through hole in cover) can be adjusted so that the Jerrold Model 2300 will work with various lengths of coax cable without need for external line equalizers. Unit is housed in handsome silver-gray metal housing with perforated cover for ample ventilation.

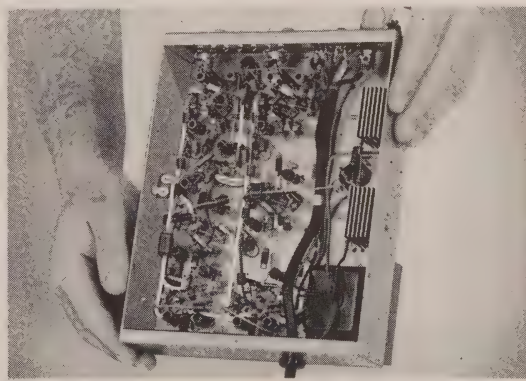


Positive Match input and output circuits provide extremely low VSWR over the entire VHF Band resulting in clear, no-smear pictures on all channels. Slug-tuned coils mean easy alignment... no tweezers or coil dope needed. Overrated components in all circuits insure longer trouble-free life.

JERROLD


ELECTRONICS CORPORATION

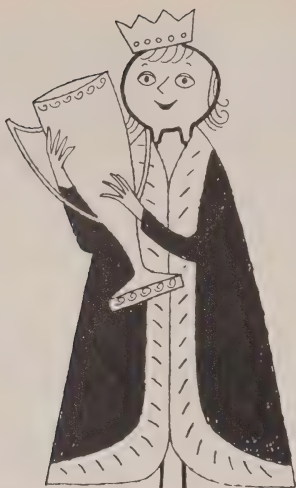23RD AND CHESTNUT STREETS
PHILADELPHIA 3, PENNA.



The Ceramic Capacitor with the "Million Dollar" Body

Over a million dollars was spent to make C-D the only plant in the world in which a ceramic capacitor is completely made from raw powder to finished unit. Scrupulous supervision and control of quality is paramount in the production of a C-D Ceramic. "Quality"—had top priority. The "Million Dollar Body" is proof of the rugged stability, the consistent uniformity and dependable long life of C-D Ceramics. Ask your nearby C-D Distributor for a catalog or write direct to Cornell-Dubilier Electric Corporation, South Plainfield, N. J.

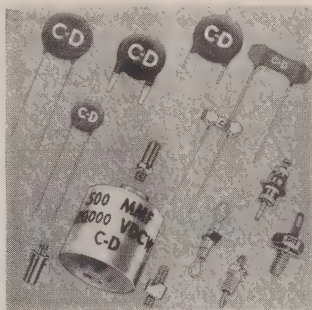

Cornell-Dubilier capacitors

South Plainfield, N. J.; New Bedford, Worcester & Cambridge, Mass.; Providence & Hope Valley, R. I.; Indianapolis, Ind.; Sanford, Fuquay Springs & Varina, N. C.; Venice, Calif., & subsidiary, The Radiart Corporation, Cleveland, Ohio.

Si vous lisez le français technique, vous devez lire

ELECTRONIQUE INDUSTRIELLE

la grande revue française de technique moderne
Specimen gratuit sur demande

EDITIONS RADIO

9, rue Jacob — Paris 6^e — France

What ARTICLES would you like to see published in RADIO-ELECTRONICS?

Maybe YOU are the man to write them!

Ask for an Author's Guide

RADIO-ELECTRONICS

154 W. 14 St.

New York 11, N.Y.

Patents





CONTROL DEVICE

Patent No. 2,717,356

James H. Foster, Erie, Pa. (Assigned to Erie Resistor Corp.)

This control device consists of a capacitor whose capacitance varies with applied voltage. It is basically a dielectric body made of barium and strontium titanate. This mixture has a dielectric constant that varies considerably with applied potential. One side of the dielectric body has three metallic electrodes, A, B and C. A resistive coating connects B and C. A and B are terminals of a capacitor, B and C are resistor terminals.

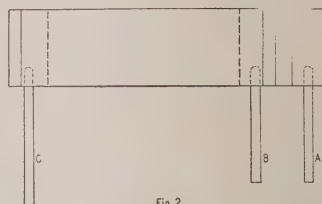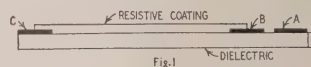

Capacitance between A and B varies with the voltage between them. When current flows between B and C there is heating of the titanate and further increase in dielectric constant. For maximum effect, A and C are strapped together as a single terminal and B is used as the second terminal. An applied voltage now produces a greater change in capacitance than is possible when the resistor or capacitor is used alone.


The effect of the polarizing voltage is almost instantaneous. The heating effect requires about 20 seconds for full stabilization.

AND-OR NETWORK

Patent No. 2,729,753

Raymond W. Ketchledge, Whippany, N. J. (Assigned to Bell Telephone Labs, Inc.)

Relay and switching networks often require *and* or *or* circuits. In the *and* type each of several inputs must be energized before an output is obtained; in the *or* type any of several inputs will produce output. The diagram shows a combination *and-or* network. It contains several stages of spark gaps which may be fired in turn. When any spark gap breaks down, its spark initiates a shock wave which carries ions. This

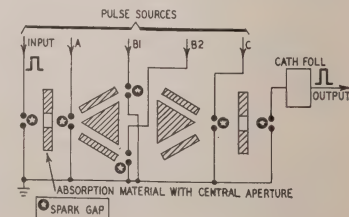

RCA'S MISSILE TEST PROJECT



**is attracting Creative Engineers
and Scientists who are bound
toward success**

*Specific fields
include:*

**TELEMETRY
RADAR
TIMING
COMMUNICATIONS
DATA PROCESSING
OPTICS**

Request Your Interview NOW...

*RCA Engineering management
will arrange an interview at the
time and place you find most
convenient. Please send complete
resume of education and
experience to:*

**Mr. H. N. Ashby, Technical Employment
Missile Test Project, Dept. N-15J
RCA Service Company, Inc., P.O. Box 1226
Melbourne, Florida**

MTP... the Missile Test Project of the RCA Service Company, Inc. . . . at the Air Force Long Range Missile Test Center . . . is the largest missile-testing range and laboratory in the world! The responsibility for providing precision instrumentation for advanced stage missiles with a vast range of performance characteristics means new engineering and planning organizations and—real opportunity for rapid individual growth.

Here you will encounter instrumentation problems that challenge the state of the art and stimulate your creative ability in Aero, Ballistic and Space techniques.

Your rewards will include all the fascination, excitement and satisfaction of achievement in new frontiers of scientific knowledge . . . plus top salary.

What's more, you'll enjoy the pleasant climate and ideal living on Florida's central east coast, where Patrick Air Force Base, site of the MTP, is located.

RCA offers many additional advantages: Complete facilities . . . Planned advancement program . . . Professional recognition . . . Liberal program of company-paid benefits . . . Relocation assistance. You should have a Bachelor's or advanced degree in EE, ME, Physics or Mathematics and two or more years' experience.



Tmks. ®

RADIO CORPORATION of AMERICA

AMPHENOL

TWIN LEAD HANKS

Now... 25 FOOT HANKS



in addition to 50, 75, 100 ft. put-ups



make your
Selling job
EASIER!

At your request AMPHENOL now provides new 25 foot hanks in two popular types of Twin Lead. Add these to your AMPHENOL Twin Lead Display Board—and watch your sales and profits increase while your selling job gets easier! Your growing Twin Lead market includes: those who buy a second set (black & white or color) or replace worn-out lead-in or need extra lengths for moving sets.

Don't wait for your customers to ask—stock and display AMPHENOL Hanks in all the popular sizes listed below.

Part No.	Description	Available in Hanks of			
		25 ft.	50 ft.	75 ft.	100 ft.
214-318	Indoor*—60 mil, 7/28 pure copper cond.	✓	✓	✓	✓
214-056	Standard—60 mil, 7/28 pure copper cond.	✓	✓	✓	✓
214-559	Steelcore—72 mil, 7/28 copperweld cond.		✓	✓	✓
214-298	Rotator—4 conductor—7/28 pure copper cond.		✓	✓	✓
214-100	Century—100 mil, 7/28 pure copper cond.		✓	✓	✓
Now Available in Coils					
214-271	Air-Core**—U.S. Pat. 2543696 7/28 pure copper cond.		✓	✓	✓

*Indoor is the newest AMPHENOL Twin Lead. It's made of pure virgin natural polyethylene to harmonize with any interior.

**Now famous AMPHENOL Air-Core is available in pre-cut coils.

Remember: for finest quality, virgin polyethylene is used in all AMPHENOL Twin Leads.

AMPHENOL ELECTRONICS CORPORATION

chicago 50, illinois

AMPHENOL

PATENTS

(Continued)

wave is transmitted to the next gap in line. The wave alone is not sufficient to fire a gap, but if the latter is pulsed at the same instant, breakdown will occur. Absorption material (shaded sections) is placed between the gaps to guide the shock wave from one gap to the next.


When the initial gap is fired by a signal pulse, the shock wave travels down to the next gap. This one will also fire if pulse A occurs at the same instant. The next stage is an *or* stage which may be fired by either pulse B1 or B2. All stages in the series constitute an *and* network because each stage must be excited by a pulse before output can occur. The last gap is coupled through a cathode follower.

The gaps may be spaced by 0.1 inch and the electrodes in any gap may be .05 inch apart. Breakdown voltage is about 5 kv.

ELECTROLUMINESCENT LAMP

Patent No. 2,728,870

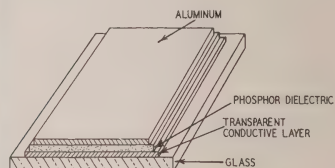Warren Calvin Gungler, Peabody, and Robert Emmett Cleary, Danvers, Mass. (Assigned to Sylvania Electric Products, Inc.)



Electroluminescence is the term applied to light generated when a phosphor is excited by an electric field. As shown in the diagram, the lamp may consist of a phosphor dielectric between two conductive layers. The phosphor is embedded in a plastic material and may contain zinc sulphide with small amounts of lead, copper and chlorine. When 600 volts ac is applied between conductors, the phosphor gives off light that is visible through the glass plate.

This inventor finds that efficiency is greatly increased if the phosphor dielectric is heated while voltage is applied, permitting the phosphor particles to align themselves in the direction of the electric field. After cooling, the particles retain their positions and can emit more light for a given power.

RADIATION DETECTOR

Patent No. 2,728,862


Pierre L. de Bourgknecht, Boston, Mass. (Assigned to Tracerlab, Inc., Boston)

Radiation detectors are most useful when they can measure over a very wide range, perhaps from a million to one. This can be done by this measuring circuit that functions logarithmically.

The diagram shows in ionization chamber under the influence of a radiation source. The current through the chamber and the diode is a linear function of the radiation count. As the count increases, a greater voltage appears across the diode. This is amplified and indicated on the meter. The amplifier output heats the diode filament. Thus more intense radiation increases diode emission and lowers its internal resistance.

The lower resistance reduces the voltage across

RADIO ACTIVE SOURCE

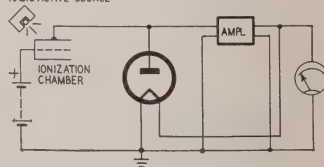

it and almost (but not quite) offsets the initial voltage rise. As a result even a considerable increase in radiation shows only a slight rise in the meter deflection.

RADIO-ELECTRONICS

END-OF-RECORD DETECTOR

Patent No. 2,739,238

John E. Bartelt, Poughkeepsie, N. Y. (Assigned to IBM, New York, N. Y.)

Data for computers are fed in as pulses recorded on magnetic tape. It is important to determine when the end of a recording has been reached, so the computer can go to the next step without delay. In this circuit designed for that purpose, V1 (Fig. 1) is one triode of a 12AV7; V2-V3 are triodes of a second 12AV7. The diodes are 1N54's or equivalent.

Inverter V1 receives the pulses from the tape and feeds them to V2-V3, a one-shot multivibrator. Normally, V2 is blocked and V3 conducts since the latter has the smaller plate resistor load. R1 and C1 control the timing of the

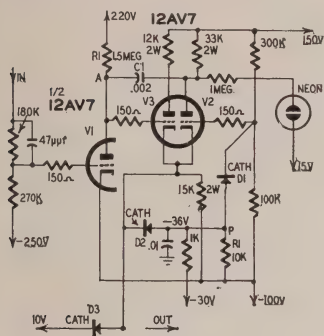


Fig. 1

multivibrator. With the constants shown in the diagram, the multivibrator remains "flipped" for about 400 μ sec, after which it returns to its normal condition. Flipping occurs when a positive pulse is received at the in terminal.

The cathodes of V2-V3 are normally very positive because heavy current flows into V3. The positive cathodes block D2 while D3 conducts. The output terminal is 10 volts positive. At this time the plate of V2 (which is blocked) is at 150 volts, and there is sufficient potential difference to ignite the neon lamp which therefore indicates that no signal is being received.

Upon receiving pulses (through V1) the multivibrator flips. V2 now conducts and V3 is blocked. V2 has a larger plate resistor so less current flows through it than did through V3. The multivibrator's cathodes are less positive than previously and D2 now conducts while D3 is blocked. The output from this circuit is -36 volts.

The grid of V2 returns to a voltage divider which maintains it at -38 volts. Thus D1 is blocked. During conduction this grid may pass considerable current. This flows through D1, so the voltage-divider action is not disrupted. When V2 conducts, its plate voltage drops, whereupon the neon lamp is extinguished.

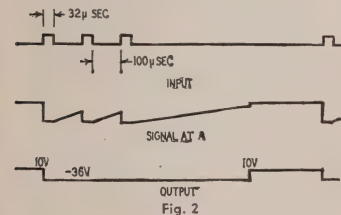



Fig. 2

Fig. 2 shows the operation of this circuit. It assumes tape pulses that are 32 μ sec wide and spaced 100 μ sec apart. Since the period of the multivibrator is 400 μ sec, the spacing between pulses is too short to permit it to flop back to normal. This can occur only 400 μ sec after the last pulse arrives.

The end of a recording is indicated when the output voltage rises from -36 to 10 and when the neon lamp lights. END

THE RADIAL SLOT RADIATOR

BY FRAZIER-MAY

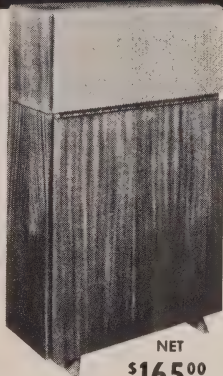

NET
\$165.00
COMPLETE

Write for free literature
on our complete line.

... the **NEWEST** principle
in loud speaker design ...

PRESENTING—

THE **SYMPHONY**

(for corner placement)

As described by Monitor in July Issue, **RADIO ELECTRONICS**

• The Frazier-May Symphony is truly the greatest value on the American Market for the discerning listener who requires the ultimate in frequency range, dynamic response and cleanliness of reproduction in a compact size and at a low price.

• The added performance of the two slot radiators, both fed by individual units on correctly designed loading plugs, provides a smooth, even, acoustical crossover without the inherent reflections from conventional electrical type networks. The frequency response of the Symphony is uniform from 32 cycles to 12,000 cycles and with the use of specially designed components, each built to work in conjunction with the other; the low initial movable mass; eliminates intermodulation distortion; overshoot of woofer drivers and the ability to handle steep wave fronts of percussive instruments without hangover.

• This is truly a great loudspeaker which must be heard to be believed. Impedance is 8 ohms. Dimensions: 39" high x 22 1/2" wide x 17" front to back. Total shipping weight (in two sections) 97 lbs.

• In all finishes: Dark Mahogany, Honey Brown Mahogany, Silver Fox, and Blond Korina. It will perform like a Cadillac and sell for the price of the Model T. We welcome direct comparison of our new Symphony model with any other speaker — you name the make and price!

THE FRAZIER-MAY SPEAKERS

ARE MANUFACTURED EXCLUSIVELY BY


International Electronics Corporation
2649 BRENNER DR. DALLAS 20, TEXAS

Always mention you saw it in
RADIO-ELECTRONICS
When answering ads

SAVE 1/2 — PAY PART-BY-PART — HAVE FUN

Assembling the Schober

ELECTRONIC ORGAN in KIT form

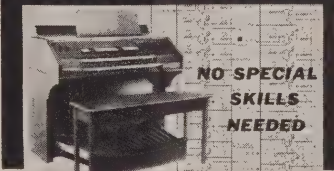

NO SPECIAL
SKILLS
NEEDED

Now you can afford a real, full concert organ, just like those made by the foremost organ manufacturers. Because over 1/2 the cost is saved when you assemble it yourself. And it's REALLY EASY: only 24 separate units, all with printed circuits, and detailed-to-the-smallest-step instructions. In addition, you purchase each of the 24 kits when you are ready for it — and can afford it.

You'll get a real kick out of putting the *Schober Electronic Organ together — and then sitting down and pulling out the stops for Strings, Trumpets, Clarinets, Diapasons, Flutes, etc.

Compact CONSOLE

One of the many exclusive features of this exceptional offer is the handsome console, made by hand in Old World Craftsman manner. It is equally at home in a traditional or modern setting, and takes little more space than a spinet piano.

Free Literature

Complete descriptive booklet and price list are available on request. And, if you wish to hear the glorious pipe organ tone of the Schober Electronic Organ, a 10" long playing recording by Dr. C. A. J. Parmentier, renowned organist, is available for \$2. This is refundable when you order. Write today and see what a fine instrument you can get at such a great saving.

The **SCHOBEL ORGAN CORPORATION**

2248-B Broadway, New York 24, N.Y.

On Display Rm. 518 N. Y. Audio Show

*Designed by Richard H. Dorf

LEARN
HOW

YOUR TV SET REPAIRS
BAD PICTURE TUBES
Tubes Fixed in Seconds

Your TV Set is all you need to make OLD TUBES like NEW. Learn this easy, tried and tested method.

ORDER NOW! Complete instructions \$1.00

TELEPARTS CO.

172 Narragansett St. Edgewood 5, R. I.



"By golly, it is an emergency
call . . . they're out of
JENSEN NEEDLES."



FIELD TECHNICIANS

*Broaden the scope
of your career with Bendix Radio!*

Get
these BIG
ADVANTAGES!

- Professional status
- The prestige of representing the leader in its field.
- Top salaries
- Liberal field allowances


If you have 5 or more years of electronics experience, you benefit many ways as a Bendix Radio Field Engineer.

You will receive full pay while you go to our company-sponsored school in Baltimore. Then, you will be given a key assignment in the United States or overseas with responsibility of maintaining search and surveillance radar equipment made by Bendix Radio.

Write,
call or wire
EMPLOYMENT
SUPERVISOR Dept. V

Bendix Radio

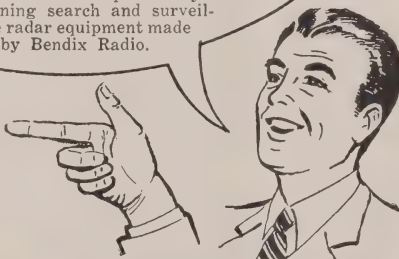DIVISION OF BENDIX AVIATION CORP.
Towson 4, Maryland
(Phone Valley 3-2200)



GET INTO ONE OF THESE TOP OPPORTUNITY FIELDS

ELECTRICITY

— Electronics & TELEVISION —
— Radio-Color TV

TRAIN IN THE GREAT SHOPS OF

Coyne

OLDEST, BEST EQUIPPED
SCHOOL OF ITS KIND IN U.S.

Veterans and Non-Veterans—Prepare for a better job NOW that offers a real future, too! Get practical training in TELEVISION—RADIO—ELECTRICITY—ELECTRONICS—(Refrigeration & Electric Appliance Repair can be included). Learn on real equipment—no advanced education or previous experience needed. Lifetime employment service to graduates.

Finance Plan—enroll now, pay most of tuition later. Part time employment help to students.

FREE BOOK Clip coupon for Big Free Illustrated Book. No salesman will call. Act NOW.

B. W. COOKE President FOUNDED 1899

ELECTRICAL SCHOOL
A TECHNICAL TRADE INSTITUTE OPERATED
NOT FOR PROFIT
500 S. PAULINA ST., CHICAGO, DEPT. 66-81H
ELECTRICITY • TELEVISION • RADIO • REFRIGERATION • ELECTRONICS

B. W. COOKE, Pres., COYNE ELECTRICAL SCHOOL
500 S. Paulina St., Chicago 12, Ill., Dept. 66-81H

Send FREE BOOK and details on:

- ☐ TELEVISION-RADIO
☐ ELECTRICITY-ELECTRONICS

NAME.....

ADDRESS.....

CITY.....STATE.....

the ultimate goal
of the
critical listener

★ marantz

Audio Console
preamplifier, complete \$168*

Power Amplifier
\$198*

*slightly higher
west of
the Mississippi

write for literature

marantz company

44-15 Vernon Blvd., Long Island City 1, N. Y.

try
This
one



KNIGHT MULTIMETER KITS


Some of the Knight 83F140 20,000-ohms-per-volt multimeter kits are supplied with the small penlight cells without paper jackets—just the bare zinc cans. If these cells are installed in the battery holder in this condition, adjacent cans will touch each other as well as the battery retaining strap, and three of the four cells will be shorted out. The instructions do not mention this. The remedy is to wrap each cell with a band of adhesive tape around its middle. This keeps them separated from each other and from the retaining strap and prevents shorts.—John Sareda

(Knight Electronics Corp. reports that some of the flashlight cells supplied with these kits did not have insulated paper jackets and will short when not insulated as mentioned above. The remainder of these cells have been removed from stock and replaced with insulated types. They will be happy to replace the uninsulated ones with insulated types upon receipt of a letter from the customer.—Editor)

DUPLEX SIGNAL TUNING

Duplex signal positioning is an attractive feature, easily installed on most communication receivers, that enables the ham or SWL to switch from one side of the phone QSO to the other and eliminates tuning back and forth across the dial.

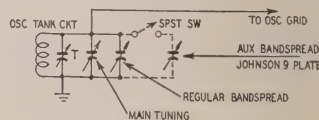The procedure to follow is this: Install at some convenient spot on the receiver front panel an E. F. Johnson or similar 1.8-8.7-μuf miniature variable capacitor with dial plate and knob.



Near by on the panel install a toggle, lever or slide-type spst switch. Wire the switch in series with the grid side of this midget variable as shown. The stator plates go to ground or B minus. In most sets the midget capacitor is wired directly across the bandspread and main tuning capacitors.

With the duplex signal positioning switch open, tune in a QSO. Only phone bands below 50 mc are recommended. Get station A and then wait until the conversation is turned over to station B. When station B takes over, flip the duplex positioning switch closed and

this is



...the new remote control TV tuner by **ALLIANCE**

Selects channels,
Precision tuning is **SUPERIOR**
for each channel!



Retail
Price

\$19⁹⁵

**A New, Fast-Selling Package
Item that All TV Viewers Want!**



3 minute installation by customer

Every viewer a prospect.

A natural companion to the Alliance Tenna-Rotor . . . at a price that's right!

**Performs a double service—switches stations and precision
tunes each channel!**

Needs no tools or wire—safe!—no need to touch back of TV set. Fits nearly
all popular makes. Comes with 90-day guarantee.

Backed by the same kind of potent TV advertising and
intensive merchandising which made Alliance Tenna-Rotor
the No. 1 TV accessory.



Handsome, compact
display carton shows "IT"
in non-breakable black plastic
with gold trim.

Write the Factory


THE ALLIANCE MANUFACTURING CO., INC.
ALLIANCE, OHIO



SPACE

MAN...

with a
Brief Case

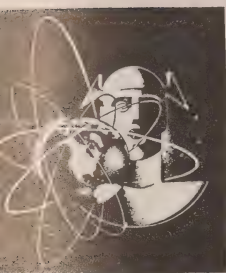

Science has a new kind of space man these days. He carries a brief case.

His mission is as new, as exciting and as challenging as a trip to the moon. In many cases you'll find him on the team at Remington Rand Univac®, one of the engineers or technicians who have given UNIVAC the title,

"First in Electronic Computing Systems"

Futures at UNIVAC are as unlimited as the space above. In fact, new facilities and fresh working conditions are being born each day at Remington Rand Univac which means that new members are needed for the Univac team. This is your chance to establish the career every man wants. Write today.

IMMEDIATE OPENINGS FOR:

At South Norwalk we have immediate openings for Mechanical and Electro-Mechanical Engineers with a bachelor's degree in *Engineering*. Extensive mechanical design background may substitute for some college. Men selected will do basic preliminary design and layout of small mechanisms. Work will require the development of original ideas and the ability to apply logical analysis to design problems.

Send Complete Resume to —

Remington Rand Univac

DIVISION OF SPERRY RAND CORPORATION

Attention Mr. A. L. Crable

Wilson Avenue • South Norwalk, Connecticut





MARTIN CLIFFORD—Engineer, teacher, and editor of the Gernsback Library Books

As a former service technician, I know how much practical knowledge and theory you have to absorb to get ahead. As a teacher, I know too how that knowledge can best be acquired. That's why I sincerely believe that there is no better or more economical way to keep up with modern servicing, new circuits, and TV theory

SERVICE TECHNICIANS—
*This library plan can help
you boost your income
50% or more!*


WHAT THE GERNSBACK TECHNICIANS' LIBRARY PLAN IS ALL ABOUT!

We formed the Library Plan solely for the purpose of providing you with a complete, accurate, up-to-the-minute source of information on TV-radio-hi fi servicing problems of today—and tomorrow **AT THE LOWEST COST POSSIBLE!** We bring out new books by top writers in the field at regular intervals of about three months and we are including books on every phase of the subject—test instruments, record changers, color circuits, tube troubles, hints on rapid repair, plus many, many other important subjects.

HOW TO ENROLL

To join—simply fill in the coupon below. **SEND NO MONEY NOW.** When a new book comes off the press—we will send you a copy for a **FREE 10 DAY** examination in your own home! If you like it, keep it and we will bill you later. If you don't want the book, simply return it and we will send you the next book as soon as it is printed.

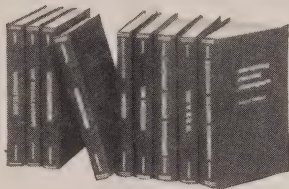than by enrolling in the new low-cost Gernsback Service Technicians' Library. You will get complete, accurate, and up-to-the-minute books on every phase of servicing at a **DISCOUNT OF 27%!** If you read, and apply the information in these books you can increase your income by 50% or more!



Each book is handsomely bound in a durable hard cloth cover.

SPECIAL MEMBERS' DISCOUNT

These big, handsomely bound books are nationally advertised at \$4.60—but by mass production and distribution, we are able to pass them along to members for only \$3.35 each—and we pay the postage. You agree to take a minimum of four books during the whole period of your membership—you may cancel any time after that. Take advantage of this offer and enroll today.

THESE BOOKS ALREADY OFF THE PRESS

These books have already been published. Begin your membership with any one of them or wait for the next book published. Remember—you pay no money now and you may

- **THE OSCILLOSCOPE**—By George Zwick.
An authoritative, easy-to-read guide on how to get more out of your 'scope.
- **PROBES**—By Bruno Zucconi and Martin Clifford.
A valuable book on a too-often neglected subject. Contains construction details as well as theory and operation.

examine any one of these books **FREE** in your own home. Simply indicate your preference in the coupon below.

- **SWEEP AND MARKER GENERATORS FOR TELEVISION AND RADIO**—By Robert G. Middleton.
For faster and more efficient servicing.
- **THE V.T.V.M.**—By Rhys Samuel.
A vacuum-tube voltmeter manual.
- **SERVICING RECORD CHANGERS**—By Harry Mileaf.
A brand-new book. Opens a new source of income to the technician.

THESE BOOKS TO BE PUBLISHED SOON

These books are scheduled for future publication one-at-a-time at three month intervals.

- **RAPID TV REPAIR**—By G. Warren Heath
- **HOW TO SERVICE COLOR TV RECEIVERS**—By Robert G. Middleton

- As a member, you will receive a copy of each book as soon as it is published.
- **TV AND RADIO TUBE TROUBLES**—By Sol Heller
- **TV—IT'S A CINCH**—By E. Aisberg

MAIL THIS MONEY-SAVING COUPON TODAY

GERNSBACK LIBRARY, INC.
154 West 14th St., New York, N.Y.

☐ Start my enrollment with the book checked below. Send me the book postpaid for a **FREE 10-day trial**. Bill me later for the book I keep.

- | | |
|---|---|
| <input type="checkbox"/> THE OSCILLOSCOPE | <input type="checkbox"/> THE V.T.V.M. |
| <input type="checkbox"/> PROBES | <input type="checkbox"/> SERVICING RECORD CHANGERS |
| <input type="checkbox"/> SWEEP AND MARKER GENERATORS | |

☐ Begin my enrollment with the next book published.
☐ **SEND me more information on the GERNSBACK TECHNICIANS' LIBRARY.**


Name Please Print

City

State

New! **POCKET SIZE**
Rejuva-Check
TESTS • REPAIRS
REJUVENATES
ALL PICTURE TUBES
right on the job!

only
\$7.95

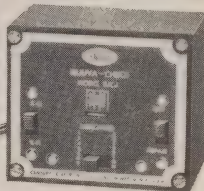

REJUVA-CHECK does everything the big instruments do and then some!
TESTS cathode emission. Indicates leakage between elements. Estimates remaining useful life of CRT.
REPAIRS by removing cathode surface contamination. Clears inter-element shorts and leakage.
REJUVENATES and gives new life to weak, dim tubes by restoring emission.
Simple and easy-to-use!

SEND NO MONEY
FREE 10-DAY SERVICE TEST
TRY BEFORE YOU BUY

Mail Coupon Now! No Obligation!

CENTURY ELECTRONICS CO., Inc.
111 Roosevelt Ave., Dept. RE-9,
Mineola, N. Y.

OK, rush **REJUVA-CHECK** for **FREE 10 day** use on my toughest service calls. After 10 days, I will send \$7.95 plus postal charges or return it without obligation.

Name

Address

City State

☐ **SAVE POSTAL CHARGES!** Enclose \$7.95 with coupon and we pay all postal charges. Same **NO-RISK** refund privilege.

The important **OCTOBER** issue of
RADIO-ELECTRONICS

on sale Sept. 25

Reserve your copy now!

BOX CHASSIS
LMB OFFERS FREE
inside LMB boxes

10 tested kit diagram projects for the builder. Each one of these kit diagrams built by a recognized expert. Kit projects are complete in every detail. Circuit diagram, photo of project both front and rear photo. Rear photo shows wiring and parts. Detailed instructions for building, complete parts list and approximate cost. Complete to build except parts and your distributor can supply the parts. Ask your distributor for the list of LMB kit Diagram Projects. If he does not have them, write to

LMB 1011 Venice Blvd.
Los Angeles 15, Calif.

ATLAS SOUND CORP.

1443 — 39 St., Brooklyn 18, N. Y.

Send **FREE** Buyer's Guide to save me money on public address Loudspeakers, Microphone Stands and accessories.

Name _____ Title _____


Firm _____

Type of Business _____

Address _____

City _____ Zone _____ State _____

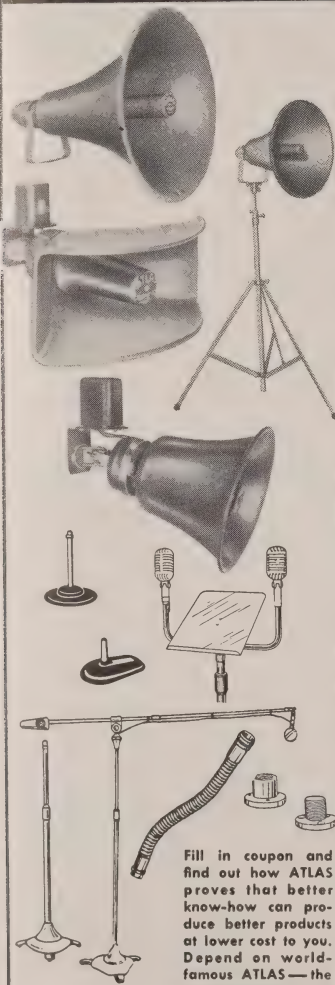HOW to SAVE MONEY on LOUDSPEAKERS and MIKE STANDS



Fill in coupon and find out how ATLAS proves that better know-how can produce better products at lower cost to you. Depend on world-famous ATLAS—the complete quality line with specialist know-how since 1930.



ATLAS SOUND CORP.

1443-39th Street, Brooklyn 18, New York
In Canada: Atlas Radio Corp., Ltd., Toronto, Ont.

TRY THIS ONE

(Continued)

tune in station B. Now the bandspread capacitor is handling station A. And your miniature variable with duplex switch closed will take care of station B. Actually, this same switching can be done with relays operated by the carriers. When station A cuts its carrier, station B is automatically switched over.


Remember that frequency lowers as capacitors mesh. Therefore it is advisable when spotting your stations on the dial to allow sufficient down-frequency coverage so that the complete spectrum of the phone band being used may be covered on the miniature. It sometimes takes practice to become accustomed to this new method of lining up your stations. But soon you will be more than satisfied with the ease with which you will be able to switch quickly from one side of the QSO to the other.

As might be expected, additional wire and other capacitances effect a slight change in the receiver oscillator settings. This may be amply compensated for by readjusting the receiver oscillator trimmer.

So long as the part of the band to be covered when using duplex positioning is below 50 mc, there is only slight rf loss in the receiver when, for instance, station B is a bit down the band from station A. Phone bands are comparatively narrow and the rf circuits are fairly broad so tracking and sensitivity will not suffer too much. This method of tuning works best when both stations are S7 or better.—George D. Philpott

TRANSISTOR SHIPPING TUBE MAKES A HANDY INSULATOR

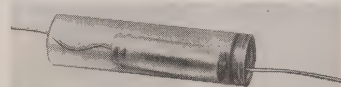
If the negative terminal of an electrolytic capacitor—its outer case—is connected to the chassis, there is no problem of insulation except for the positive lead. However, in many applications the positive terminal is grounded, leaving the capacitor case "hot." This occurs frequently in transistorized portables.



The photograph shows a use for the plastic case in which many transistors are shipped. Punch a hole in its bottom for the pigtail lead and put the capacitor in it. If your transistors have different type cases or subminiature capacitors are employed, a plastic pill tube may be obtained from the drugstore.

If the shipping tube does not hold the capacitor snugly, a piece of tape or cardboard will do the trick. The cardboard from a match cover can be used to wedge it tightly.—Lawrence Shaw

TRIAD SUB-MINIATURE AUDIO TRANSFORMERS

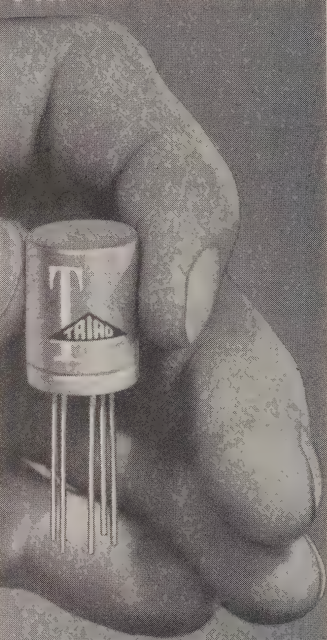

TRIAD's versatile series of sub-miniature hermetically sealed audio transformers are specially designed for audio use, transistor applications and printed circuits. Featuring extremely small size, they incorporate all the construction features that have made TRIAD the symbol of quality in transformers.

Type No.	List Price	Impedance — Ohms	
		Primary	Secondary
JZ-1	\$19.65	600/250/50	60000
JZ-5	20.20	30/12/4	50000
JZ-7	19.65	30/12/4	1000
JZ-13	19.65	15000 (1 Ma.)	135000 C. T.
JZ-15	19.65	20000 (.5 Ma.)	1200/600/100
JZ-25	19.10	10000 (1 Ma.)	200
JZ-26	19.10	1000 (5 Ma.)	50

Write for Catalog TR-56F, listing TRIAD's complete line of quality Transformers.



4055 REDWOOD AVE., VENICE, CALIF.



Business




Merchandising and Promotion

Perma Power Co., Chicago, Ill., de-



signed a new three-dimensional display, shown in the photo above, for its garage-door opener.

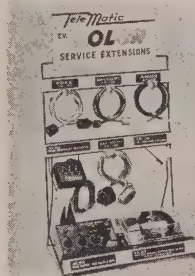Telematic Industries, Brooklyn, N. Y., is promoting its new line of TV



color extensions and service aids through the use of a new counter display.

Rek-O-Kut Co., Long Island City, N. Y., has prepared a recording time table for standard and microgroove

disks. It is available from Rek-O-Kut for 25c.

Futuramic Co., Chicago, has prepared a series of lab lessons for TV trade schools. The lessons show photographically how to use voltmeter probes for troubleshooting by means of signal-tracing techniques.

ORRadio Industries, Opelika, Ala., designed a new self-service package dis-



play for its three most popular Irish brand recording tapes.


Sylvania Electric Products, New York, will sponsor a TV film adventure series, "The Buccaneers" this fall, according to an announcement by Terry P. Cunningham, director of advertising and sales promotion. Sylvania has relinquished its sponsorship of "Beat The Clock" after 5½ years.

Production and Sales

RETMA reported production of 2,862,177 TV sets and 5,585,390 radios for the first 5 months of 1956 compared to 3,238,820 TV sets and 5,853,954 radios for the 1955 period. It also announced retail sale of 2,428,888 TV sets and 2,551,272 radios, exclusive of automobile sets, for the 1956 period. This compares with 2,722,648 TV sets and 2,-

		Recording Time Table									
		STANDARD					MICRO-GROOVE				
		15"	12"	10"	8"	6"	15"	12"	10"	8"	6"
RECORDING SPEED	INCHES	15"	12"	10"	8"	6"	15"	12"	10"	8"	6"
33 1/3 RPM	15"	1:45	1:30	1:15	1:00	0:45	1:45	1:30	1:15	1:00	0:45
	12"	1:30	1:15	1:00	0:45	0:30	1:30	1:15	1:00	0:45	0:30
	10"	1:15	1:00	0:45	0:30	0:15	1:15	1:00	0:45	0:30	0:15
	8"	1:00	0:45	0:30	0:15	0:05	1:00	0:45	0:30	0:15	0:05
	6"	0:45	0:30	0:15	0:05	0:02	0:45	0:30	0:15	0:05	0:02
45 RPM	15"	1:15	1:00	0:45	0:30	0:15	1:15	1:00	0:45	0:30	0:15
	12"	1:00	0:45	0:30	0:15	0:05	1:00	0:45	0:30	0:15	0:05
	10"	0:45	0:30	0:15	0:05	0:02	0:45	0:30	0:15	0:05	0:02
	8"	0:30	0:15	0:05	0:02	0:01	0:30	0:15	0:05	0:02	0:01
	6"	0:15	0:05	0:02	0:01	0:00	0:15	0:05	0:02	0:01	0:00
78 RPM	15"	0:45	0:30	0:15	0:05	0:02	0:45	0:30	0:15	0:05	0:02
	12"	0:30	0:15	0:05	0:02	0:01	0:30	0:15	0:05	0:02	0:01
	10"	0:15	0:05	0:02	0:01	0:00	0:15	0:05	0:02	0:01	0:00
	8"	0:05	0:02	0:01	0:00	0:00	0:05	0:02	0:01	0:00	0:00
	6"	0:02	0:01	0:00	0:00	0:00	0:02	0:01	0:00	0:00	0:00

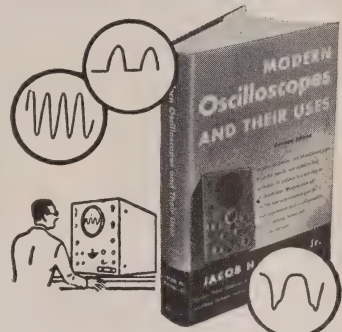HERE'S EVERYTHING YOU NEED TO KNOW ABOUT OSCILLOSCOPES!



Service any Radio-TV ever built EASIER - BETTER - FASTER

Oscilloscopes are gold mines for servicemen who learn to use them fast and accurately—and here, in a completely revised 2nd edition, is THE book that really shows you how.

In plain, easily understood language, MODERN OSCILLOSCOPES AND THEIR USES teaches you just when, where and exactly how to use your oscilloscope. You learn how to handle tough jobs easier and faster than you may have dreamed. Every detail is clearly explained—from making connections to adjusting circuit components and setting oscilloscope controls.

Equally important, you learn to analyze patterns accurately in far less time. Almost 400 illustrations including dozens of pattern photos make things doubly clear.

'SCOPES ARE "GOLD MINES"

when you learn to use them fully!

This big book is more widely used than any other of its type—because it gets right down to "brass tacks." No involved mathematics. No complicated discussions. You learn exactly what the oscilloscope is and exactly how to use it on all types of AM, FM and television service (including color)—from locating troubles in a jiffy to handling tough realignment jobs.

Send coupon for 10-day free trial.

PRACTICE 10 DAYS FREE!


Dept. RE-96, RINEHART & CO., Inc.,
232 Madison Ave., New York 16, N. Y.

Send new 2nd edition of 370-page MODERN OSCILLOSCOPES AND THEIR USES for 10-day FREE EXAMINATION. If book is what I want, I will then send you \$6.50 promptly in full payment. If not, I will return book postpaid in good condition and owe you nothing.

Name.....

Address.....

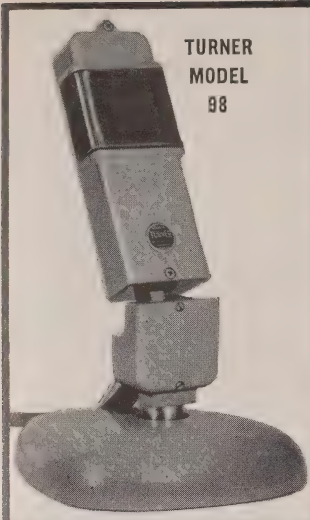City, Zone, State.....
OUTSIDE U.S.A.—Price \$7.00, cash only.
Money back if you return book in 10 days.



**TURNER
MODEL
98**

**A
Quality
Cardioid**
at a low price

The Turner model 98 is a directional microphone ideal for use in broadcasting, recording and public address applications. Directional characteristics make it "live" to sounds in front, "dead" to sounds from the rear. Reduces unwanted audience, mechanical equipment, and background noises. Eliminates acoustical feedback in public address work. Check the specifications, compare the prices. You'll see for yourself why the Turner Model 98 is such an outstanding value in cardioid microphones.

SPECIFICATIONS:

Frequency response—65 to 11,000 c.p.s.; Output level—-52 db; Impedance—Specify 50, 200 ohm or high; Dimensions—6¼ x 1½ x 1; Cable—Detachable 20 ft. single conductor (high impedance) or two conductor (50, 200 ohm) shielded.

LIST PRICES:

Model 98\$59.50
Model 5-98 (with on-off slide switch) 63.50
Matching G-7 Shockmount stand 8.00
Models 98 or 5-98 with chrome finish add \$10.00 to list prices and specify "chrome finish".
Matching C-7 chrome Shockmount stand \$9.50.

THE TURNER COMPANY
909 17th St., N. E.,
Cedar Rapids, Iowa

IN CANADA:
Canadian Marconi Co.,
Toronto, Ontario and Branches

EXPORT:
Ad Auriema, Inc.,
89 Broad St., New York 4, N. Y.

BUSINESS

(Continued)

007,631 radios sold in the first 5 months of 1955.

New Plants and Expansions

Sylvania Electric Products completed a 50,000-square-foot addition to its picture-tube plant in Fullerton, Calif.

P. R. Mallory & Co. moved its New York district sales office to Teaneck, N. J.

Hickock Electrical Instrument Co. opened a new San Francisco branch in Berkeley, Calif. George Ksander, Hickok sales engineer, was named West Coast manager. Bert Clintsman, manager of the new office, and Bill Cotie, manager of the Los Angeles branch, will work with him.

Raytheon Manufacturing Co. purchased a 15-acre site in Goleta, Calif., where it will erect a new engineering laboratory for airborne electronics and infra-red equipment.

Alliance Manufacturing Co., Alliance, Ohio, leased an additional building which will provide 80,000 square feet of floor space for expanded production facilities.

Hycron Electronics Inc., Pasadena, Calif., has realigned its organization to provide for an increase in production and sales. Its engineering facilities will be increased by drawing skilled personnel from the parent company, Hycron Manufacturing Co. Hycron Electronics will also market many products developed by other divisions. Hycron Eastern Inc., Cambridge, Mass., also a subsidiary of Hycron Manufacturing Co., acquired an additional 7,000 square feet.

Olympic Radio & Television, Long Island City, N. Y., purchased Presto Recording Corp., Paramus, N. J. George J. Saliba, president of Presto, will continue to direct operations as vice president and general manager. David Bogen Co., New York City, another Olympic subsidiary, will transfer part of its manufacturing activities to a plant adjoining the Presto factory. **END**


CORRECTIONS

Mr. Queen points out that the ferrite-rd antenna used in his shirt-pocket radio (July) is a type MS-264 rather than the MS-166 specified in the article and that the now-available MS-272 ferrite loop provides better tracking and is highly recommended. Do not remove turns from this unit. Just cut enough off the ends of the form so it fits snugly in the case like the original unit. He also advises that the type MS-126 if transformer has been discontinued and replaced by the MS-268. Headphones should have an impedance of 3,000 ohms or higher.

There are two errors in the signal-tracer diagram on page 81 of the June issue. The switch connected to the second 6BA6's grid is part of the band-switch and should be ganged to the other three sections. The top lead of the secondary of the output 550-1650-kc transformer goes directly to the band-switch fixed contact and should not be connected to tuning capacitor and diode plates.

Another **Futuramic** First!

Our first, "first"

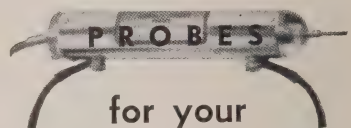

for your
Volt-Ohmmeter
NOW

WHAT

The **Futuramic**
SCROBE

You will wonder
how you got along
without it

WHEN

Ask your distributor

WHO

Futuramic
of course!

2500 W. 23rd St.

Chicago 8, Ill.

Cliffside 4-7345

RADIO-ELECTRONICS

Exclusive at **TERMINAL**... UNHEARD OF SAVINGS!

ALL BRAND NEW FACTORY SEALED



SYLVANIA TEST EQUIPMENT

LIMITED QUANTITIES! ACT NOW!

Radio-TV Service Men — Industry — Laboratories
This is your once-in-a-lifetime opportunity to acquire the world's finest test equipment at a fraction of its original cost.

GUARANTEED Brand new in original Sylvania factory sealed cartons, complete with detailed instruction sheets. Look at the amazing savings!

Never Before! Never Again! Such SENSATIONAL LOW PRICES!


**Type 620 SYLVANIA
TUBE TESTER**



New, portable tube tester tests all common receiving tubes, transmitting and industrial tubes, regardless of basing — also "600 ma" series string television tubes. In-line controls speed efficiency. Reads shorts and leakage directly in ohms — easy-to-read roll chart — gas test — easy switching for all tube bases. Best dollar buy. **Regular Price: \$149.50.**

NOW ONLY \$89⁵⁰


**Type 303 SYLVANIA
POLYMER**

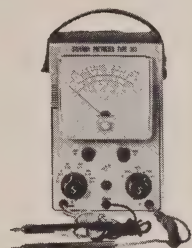

The ultimate in its price range — multi-purpose meter combining high accuracy with functional, smart styling to give "quick readings" under all conditions of ambient lighting. Measures AC and DC volts, and ohms over 6 ranges. **Regular Price: \$54.50.**

NOW ONLY \$34⁵⁰

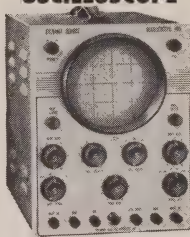**Type 405 SYLVANIA
5" SERVICE
OSCILLOSCOPE**



The smallest 5" 'scope on the market... and the biggest value. Identical horizontal and vertical amplifiers with frequency response within 3 db from 2-700KC, 300 Millivolt sensitivity and 2.2 meg. input impedance. Linear sweeps from 16 to 50 KC. Extremely stable sync. **Regular Price: \$129.50.**

NOW ONLY \$82⁵⁰

**Type 506 SYLVANIA
COLOR-TV DOT GENERATOR**

Extreme sync stability, useful for linearity adjustments, positive gating circuit, wide range of dot spacing, practical dot size. Hard tube sync circuit and special Sylvania output adapter. Extremely compact unit. **Regular Price: \$129.50. NOW ONLY \$69.50**

Type 501 SYLVANIA MARKER GENERATOR
Provides 2 separate signals for marking an oscilloscope trace of response curves. Accurate trap adjustment, freq. spotting, band width measurement and adjustment of popular 4.5 mc. intercarrier sound circuits. VFO covers 15 to 240 mc. range. **Regular Price: \$129.50. NOW ONLY \$69.50**

**Type 600 SYLVANIA
LABORATORY TUBE TESTER**

Mutual conductance and emission test. Conversion transconductance test. Leakage test directly in megohms, gas test, and voltage regulator-thyratron tube test. Factory correlated readings, illuminated meter, roller chart. **Regular Price: \$469.50. NOW ONLY \$369.50**

Model 402 SYLVANIA SYNCHROSCOPE

Continuously variable sweep speed 0.2 us/in. to 800 us/in. Internal trigger generator with rep. rate of 500, 1000, 2000, 4000 p.p.s. Positive pulse trigger output rising to 200 volts peak in 0.3 u sec. at amplitude of 100 volts for 3 u sec. Adjustable output trigger delay from 75 before to 25 u sec. after sweep start. Fixed sweep trigger delay at 90 u sec. **Regular Price: \$708.75. NOW ONLY \$490.00**

Model 402A SYLVANIA SYNCHROSCOPE

Identical with model 402 but with an r-f detector and video-hand amplifier. **Regular Price: \$783.74. NOW ONLY \$540.00**

Model 402B **Regular price \$896.25. NOW ONLY \$602.00**

**Type 228
SYLVANIA C.R.T.
TESTING ADAPTER**




Use with any Sylvania tube tester to check 85% of picture tube troubles without removing tube. Checks electromagnetically deflected types for emission, shorts, leakage, and open filaments. **Regular Price: \$7.60. NOW ONLY \$5.95**

**Type 225 SYLVANIA
TV HIGH-VOLTAGE PROBE**

In conjunction with Sylvania types 301 and 302 polymeters this probe permits measurement of DC voltages up to 30 KV. **Regular Price: \$12.50. NOW ONLY \$6.95**

**Type 301 SYLVANIA
POLYMER**

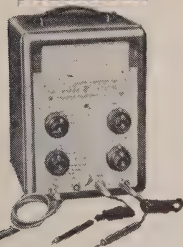

Features an inherently stable circuit from use of 2 Type 7N7 tubes in Sylvania-patented circuit. 1 Ma. meter movement. 6 AC and DC ranges read up to 10,000 volts and up to 30,000 volts DC with Sylvania Type 225 Voltage Multiplier Probe. Resistance measurements to 10,000 meg. True peak-to-peak readings up to 2,800 volts, 17 meg. input impedance. Illuminated meter and screw-on connectors. Shielded AC lead provides AC measurements from 20 cps. to 20,000 cps. with 2.7 meg. impedance. Measures DC current up to 10 amps. **Regular Price: \$109.50.**

NOW ONLY \$69⁵⁰


**Type 302 SYLVANIA
DeLUXE POLYMER**



6 AC and DC volt ranges 0-3, 10, 30, 100, 300, 1000. 6 peak-to-peak volt ranges. 5 RF volt ranges from 0 to 300. Ma in 6 ranges from 0 to 1000. 0-10 amp. DC. Ohms in 6 ranges to 1000 meg and db measurements in 6 ranges from -20 db to +61.4 db. Features new 7" Sylvania meter movement, patented linearity circuit, rf probe, high input impedance, shielded leads. **Regular Price: \$129.50.**

NOW ONLY \$82⁵⁰

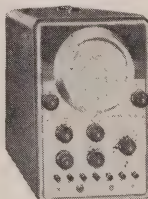**Type 403 SYLVANIA
TV SERVICE
OSCILLOSCOPE**



High quality 7" instrument with identical high-gain dc. amplifiers on horizontal and vertical axes, plus advanced features of higher priced models of special value for TV service. Type 403 permits dc signal level measurements and phase relationship study. 2 preset TV sweeps. Vertical sensitivity 10 millivolts per inch rms. Freq. response flat to 500 kc within 2 db. **Regular Price: \$249.50.**

NOW ONLY \$159⁵⁰

All Items Subject to Prior Sale...FIRST COME...FIRST SERVED! ORDER TODAY!



Terminal Radio CORP.

85 CORTLANDT STREET, NEW YORK 7, N.Y. • Worth 4-3311

MAIL ORDERS FILLED

All Prices F.O.B. New York City.
Please send full remittance or 25% deposit, balance C.O.D.

HUGE EXPANSION SALE!
UNTIL SEPT. 30TH ONLY!
ANY ITEM IN THIS AD FOR

ONE DOLLAR!

MANY NEW ITEMS, KITS, LARGER QUANTITIES!

FREE!
 ANY ITEM IN THIS AD
 FREE with \$10.00 Order!

FREE!
 NEW MAIL FLYER
 Unmatched Bargains!

EARN FREE KITS IN OUR CREDIT BONUS PLAN
 Any order enrolls you. Write for complete information.



WORLD FAMOUS KIT KING DOLLARBUYS!

- 40 MINIATURE RESISTORS. Subminiature, 1/4, 1/2 & 3/4 W. Transistor types, under 20 values: ohms to 4.7. **\$1**
- 2-TUBE AMPLIFIER KIT. Exc. tank & w. 25A tubes. Wt. 2. **\$1**
- 3-PC. NUTDRIVER KIT. Plastic handle, 3/16, 1/4, 5/16, 3/8, 1/2, 5/8, 3/4, 1, 1 1/2, 2, 3, 4, 6, 8, 10, 12, 14, 16, 18, 20, 22, 24, 26, 28, 30, 32, 34, 36, 38, 40, 42, 44, 46, 48, 50, 52, 54, 56, 58, 60, 62, 64, 66, 68, 70, 72, 74, 76, 78, 80, 82, 84, 86, 88, 90, 92, 94, 96, 98, 100. **\$1**
- 20 HI-QUALITY KNOBS. Hi-Fi, recorder, instrument types. Knurled, assorted. Brass insert screws. Wt. 1. **\$1**
- 10 LBS. HARDWARE. 2,000 pcs. screws, washers, nuts, brackets, etc. **\$1**
- 100 PREAMP KIT. For magnetic cartridges. Complete w/ chassis & parts. **\$1**
- 30 TUBE SOCKETS. 4, 6, 7, 8, 9, 10, 12, 14, 16, 18, 20, 22, 24, 26, 28, 30, 32, 34, 36, 38, 40, 42, 44, 46, 48, 50, 52, 54, 56, 58, 60, 62, 64, 66, 68, 70, 72, 74, 76, 78, 80, 82, 84, 86, 88, 90, 92, 94, 96, 98, 100. **\$1**
- 20 STANDARD KNOBS. Radio, TV, appliance types. Assorted colors. **\$1**
- 30 PRECISION RESISTORS. 1/4, 1/2, 3/4, 1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 12, 14, 16, 18, 20, 22, 24, 26, 28, 30, 32, 34, 36, 38, 40, 42, 44, 46, 48, 50, 52, 54, 56, 58, 60, 62, 64, 66, 68, 70, 72, 74, 76, 78, 80, 82, 84, 86, 88, 90, 92, 94, 96, 98, 100. **\$1**
- 20 AC DC LINE CORDS. 10 ft. 1/2, 1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 12, 14, 16, 18, 20, 22, 24, 26, 28, 30, 32, 34, 36, 38, 40, 42, 44, 46, 48, 50, 52, 54, 56, 58, 60, 62, 64, 66, 68, 70, 72, 74, 76, 78, 80, 82, 84, 86, 88, 90, 92, 94, 96, 98, 100. **\$1**
- 20 MICRA CONDENSERS. Famous "Mikes". 30 values: 100 pF to 100 mF. **\$1**
- 100 COIL FORMS. Assorted. **\$1**
- 175-ft. HOOKUP WIRE. 18, 20, 22, 24, 26, 28, 30, 32, 34, 36, 38, 40, 42, 44, 46, 48, 50, 52, 54, 56, 58, 60, 62, 64, 66, 68, 70, 72, 74, 76, 78, 80, 82, 84, 86, 88, 90, 92, 94, 96, 98, 100. **\$1**
- 20 CERAMIC CONDENSERS. 30 values: 100 pF to 100 mF. **\$1**
- 20 POPPER BULBS. 1/4, 1/2, 3/4, 1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 12, 14, 16, 18, 20, 22, 24, 26, 28, 30, 32, 34, 36, 38, 40, 42, 44, 46, 48, 50, 52, 54, 56, 58, 60, 62, 64, 66, 68, 70, 72, 74, 76, 78, 80, 82, 84, 86, 88, 90, 92, 94, 96, 98, 100. **\$1**
- 25 VARIABLES. Air mix and ceramic cases. 30 values: 100 pF to 100 mF. **\$1**
- 10 ELECTROLYTICS. 10, 20, 30, 40, 50, 60, 70, 80, 90, 100, 150, 200, 300, 400, 500, 600, 700, 800, 900, 1000, 1500, 2000, 3000, 4000, 5000, 6000, 7000, 8000, 9000, 10000, 15000, 20000, 30000, 40000, 50000, 60000, 70000, 80000, 90000, 100000. **\$1**
- 4 SILICON DIODES. 1N22, 1N23, 1N105, 1N106, 1N107, 1N199, 1N200. **\$1**
- 12 SWITCHES. Micro switch, AC, mobile, etc. **\$1**
- 30 POWER RESISTORS. Wirewound, 5 to 50 W. **\$1**
- 70 TUBULAR CONDENSERS. Popular type. 30 values: 100 pF to 100 mF. **\$1**
- 40 OL CONDENSERS. Popular type. 30 values: 100 pF to 100 mF. **\$1**
- GERMANIUM DIODES. 1N22, 1N23, 1N105, 1N106, 1N107, 1N199, 1N200. **\$1**

Check items wanted. Return entire ad with check or MO. Include sufficient funds for return postage. C.O.D. orders, 25% down. Rated, net 30 days. Print name, address and amount money enclosed in margin.

HOW TO ORDER

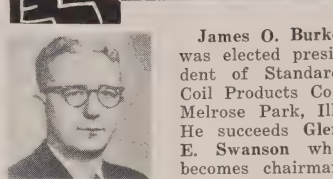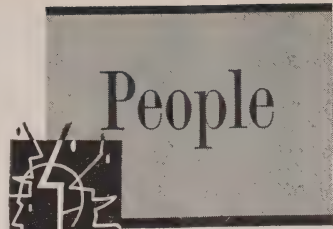Lektron Specialties
 28 GARDEN ST. CHELSEA 50, MASS.
 Visit our salesroom at 131 Everett Ave., Chelsea



James O. Burke was elected president of Standard Coil Products Co., Melrose Park, Ill. He succeeds Glen E. Swanson who becomes chairman of the board of directors. Burke, who had been executive vice president, assumed the responsibilities of president early this spring when Swanson was granted a leave of absence for reasons of health.

William C. McFadden, named executive vice president of Hycon Manufacturing Co., Pasadena, Calif., had previously been vice president and general manager of the Camera and Instruments Division.



DeRo TV AIDS PROFITS

MORE FOR YOUR MONEY

Personna-Tone EXTENSION SPEAKER
 High-quality sound for chair-side TV listening. 4x6 speaker. Selector switch and volume controls for TV set. Personna-Tone or both speakers. Wood veneer cabinet. Complete with cable... **\$9.95**

Dual-Tone VOLUME CONTROL
 For auto radio sound extension. Two volume controls — one for each speaker. Volume of either speaker adjusts to any level independently. Ample cable for... **\$3.95**

All Purpose DeRo-JUVENATOR
 One rejuvenator replaces all! Model RU-5—universal 6-wire for use on all series or parallel filament TV sets, both electronic and electromechanic. Restores brilliance and contrast to... **\$3.95**

Look for This!
Dynamic COUNTER DISPLAY
 DeRo quality parts are packaged for easy identification. Look for the DeRo trademark on all television accessories.

Where Quality Counts—Buy DeRo!


AT ALL LEADING DISTRIBUTORS!

DeRo ELECTRONICS

134 NASSAU ROAD
 ROOSEVELT • LONG ISLAND • N. Y.



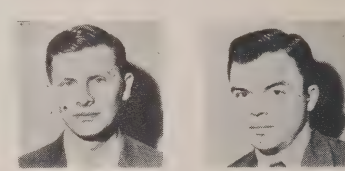George C. Isham (left), new general merchandising manager of Sylvania Electronic Products Sales Dept., New York, was formerly Eastern regional manager of distributor sales for electronic products. Donald J. Hughes (right), advertising and sales promotion supervisor for electronic products, was promoted to advertising manager of electronic products sales.



William H. Dean (left), joined G-C Electronics Manufacturing Co., Rockford, Ill., as sales manager. He had been with a leading parts distributor and Bendix Home Products. Robert C. Kocmoud (right) was promoted to sales promotion manager of the parent company, General Cement Manufacturing Co., and its sales divisions. He has been in its Advertising Dept. a number of years.

WANT BACK ISSUES?

Back numbers of most issues of RADIO-ELECTRONICS are available upon request

This year's issues 35c
 Last year's issues 40c
 Previous year 45c, etc.
 All January TV issues 50c

RADIO-ELECTRONICS
 154 West 14 St. New York 11, N. Y.

Don't just say CAPACITORS

Ask For Sprague By Catalog Number

Know what you're getting... get exactly what you want. Don't be vague... insist on Sprague. Use complete radio-TV service catalog C-610. Write Sprague Products Company, 81 Marshall Street, North Adams, Massachusetts.

SPRAGUE

WORLD'S LARGEST CAPACITOR MANUFACTURER

RADIO-ELECTRONICS

OPPORTUNITY ADLETS

Rates—45¢ per word (including name, address and initials) Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 consecutive issues. Misleading or objectionable ads not accepted. Copy for Nov. issue must reach us before Sept. 15, 1956.

RADIO-ELECTRONICS,
154 West 14 St., New York 11, N. Y.

HIGH-FIDELITY SPEAKERS REPAIRED. Amprite Speaker Service, 70 Vesey St., New York 7, N. Y. RA 7-2580.

"ASIA TRADE INQUIRIES", listing manufacturers, exporters, importers Japan, Hong Kong, Ceylon, Malaya, India, and Philippines. Just \$1 today. ASIA TRADE INQUIRIES, 920-3rd Ave., Box 739, Seattle 4, Wash.

100 Mail order plans—\$2 **BERNZOTT**, 299 East 162 St., N.Y.C.

PROFESSIONAL RECORDING SERVICE: Tapes made, copied, masters cut, processed, pressings made—short runs our specialty—all Ampex 300's, Telefunken & Altec. Hydroflood Lath nonconduction presses. **COMPOENTS CORP.**, 106 Main St., Denville, N.J. Phone: Rockaway 9-0290.

WANTED: Electronics men to qualify for Engineering Degrees by comprehensive examination. No courses. Excellent employment opportunities waiting. **CRAMWELL INSTITUTE**, RE-7, Adams, Mass.

TELEVISION Tuner Repairs. **DAN'S TELEVISION LABORATORY**, 606 Sunrise Highway, Babylon, N. Y.

RULE OTHERS WITH THOUGHTS. Incredible power. (Details—10c). **DELMAR WISDOM**, 846-858 Sunnyside Ave., Chicago 40, Ill.

DIAGRAMS FOR REPAIRING RADIOS \$1.00. Television \$2.00. Give Make, Model. **Diagram Service**, Box 672-RE, Hartford 1, Conn.

PRE-recorded Tapes, low price recording tape, accessories, Catalogue. **EPSCO**, 270 R Concord Ave., West Hempstead, N.Y.

TUBES—T.V. RADIO, TRANSMITTING, AND SPECIAL PURPOSE TYPES BOUGHT, SOLD AND EXCHANGED. Send details to R. E. Gensler W2LN1, 512 Broadway, N.Y. 12, N.Y.

ROAD-MAP to success in mail order business. Get mail order wise Free details. **HARRIGAN**, 24 E. Langhorne Ave., Havertown, Pa.

ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING equipment repaired. **Hazleton Instrument Co.**, 128 Liberty Street, New York, N.Y.

REPAIR orders printed. Tags, statements, letterheads, envelopes. Samples, prices Free. **HOWPRINT**, 723-R Eunice, Webster Groves, Mo.

COMPLETE Television Sets \$11.95. **JONES TV**, 1115 Rambler, Pottstown, Pa.

DIAL-A-MATIC adding machine. Adds (up to 99,999). Subtracts! \$2 Postpaid. **M-LEES**, Box 6792 (R), San Antonio, Texas.

WANTED: AN/APR 4, other, "APR", "TS", "IE", "ARC-1, ARC-3, ART-13, BC-348, etc. Microwave Equipment. Everything Surplus. Special tubes. Test Manuals. High Quality Equipment. **Metco Fast Action, Fair Treatment.** Top Dollar! Little, Fairhills Box 26, Dayton 9, Ohio.

RADIOS Custom for 1952 through 1956 Fords \$38.90. Free literature. **NORDIC RADIO**, Box 552, Evanston, Ill.

PROFESSIONAL Electronic Projects—Organs, Timers, Intermix, Moisturizers, Counters, etc. \$1 each. List Free. **PARKS**, 101 S.E. 57th, Portland 15, Oregon.

TRANSISTOR Radio Kit—complete, powerful—\$7.95. **PARK MAGNETS**, Highland Park, Ill.

FREE Crystal Set literature. Write **POTENTIAL RADIO**, 446 Crown St., Brooklyn, N.Y.

WANT A VERY LOW RESONANCE SPEAKER? Ask your dealer to demonstrate the **RACON "hi-compliance"**, floating cone, foam-suspension loudspeaker or write for literature and prices to **RACON ELECTRIC CO.**, 1261 Broadway, New York 1, N. Y.

FOREIGN jobs list. Technicians needed. **A. RATHE**, Box 26131, Los Angeles 26, California.

ANY GEAR TO SELL? REX PAYS LIKE WANTED—Surplus Military and Commercial Aircraft Electronics: BC-788 . . . 1-152 . . . ARN-7 . . . ARC-1 . . . ARC-3 . . . transmitters . . . receivers . . . test equipment . . . etc. | WANTED—Electronic Tubes: Broadcast . . . transmitting . . . receiving . . . Magnetrons . . . Klystrons . . . miniature . . . sub-miniature . . . ruggedized . . . | TOP Prices Paid! For Fattest Checks—Sell to Rex! Write or phone description for immediate action. R. L. SANETT, W6REX, 1524 S. Eddis Drive, Los Angeles 35, Calif. Phones: REpublic 1-5215 . . . CRestview 1-3856.

MONEY made servicing television sets using special Build-It-Yourself Trouble Shooting Tester from old TV sets. \$2 **STERLING**, 129 West Long Ave., New Castle, Pa.

TRANSISTOR Kits. Free information. **TRANSIT ELECTRONICS**, Box 15-E2, Alden Manor, Elmont, N.Y.

DIAGRAMS! Repair Information! Radios—Amplifiers—recorders \$1. Televisions \$1.50. Give make, model, chassis—Norelco-Phillips & Ampex tubes in stock! **TV MITEE**, Box 101EA, Hicksville, N.Y.

COPYRIGHTED Instructions and diagram for building Antenna Towers. **JOHN R. WARE**, Route 3, Box 408, Kings Mountain, North Carolina.

Here's Why...You Should Buy ... at WRL

... the NEW hallicrafters



SX-101: Look at These Feature Points!

Only \$21⁵³

PER MO.
Just 10% Down
Cash Price: \$395.00

We Carry the Full Line of Hallicrafters Equipment. Send for Complete Info

Today!

JUST OFF THE PRESS • NEW FREE 1957 CATALOG
Over 15,000 Bargains for the Amateur, experimenter, etc.
Ask About WRL's new Globe King 500B, Globe Champ, Globe Chief

RE-9

WRL

WORLD'S MOST PERSONALIZED ELECTRONIC SUPPLY HOUSE

World Radio

LABORATORIES

PH. 2-0277

3415 W. BROADWAY COUNCIL BLUFFS, IOWA

Please Rush Me:

☐ Free Catalog, and info on items checked below:

☐ SX-101 ☐ Other Hallicrafters Models ☐ WRL's Xmtr. Series

Name: _____

Address: _____

City & State: _____

E-Z WAY TOWERS

Looking for a tower that is easy to erect yet strong enough to withstand severe winds? This is it! E-Z Way Towers will stand a wind load of 40-60 lbs. per sq. ft. And with the new E-Z Way portable pin pole it's easy to erect a 120 ft. tower in one piece without leaving the ground. Unbelievable, isn't it? But E-Z Way Towers have been tested and proven. Thousands of E-Z Way Towers are giving outstanding service in all parts of the country and abroad. That's why E-Z Way is the Industry's New Leader. Find out about E-Z Way now!

SEND TODAY FOR FREE CATALOG

Dept. CE, E-Z Way Towers
P. O. Box 5491, Tampa, Florida

Send me your FREE catalogue on the following towers:

☐ AM Radio ☐ Television
☐ Ham Radio ☐ Two-Way Communication

I am interested in a tower _____ ft. high.
I will use a _____ (State type and model) antenna.

Type of Rotor: _____

Name: _____

Address: _____

City: _____ State: _____

E-Z WAY TOWERS Inc.
P. O. Box 5491 • Tampa, Fla.

Telephone 4-2171

★ 20 YEARS
of Serving Hams the World Over

- ✓ Only 10% Down—trade-ins accepted—1-2 Terms—10 Day Trial
- ✓ A WRL Xmtr. for every ham budget
- ✓ Over 800 recommended electronic items with 90 day, new equipment guarantee
- ✓ Highest trade-ins matched or beat
- ✓ Prompt, personalized service! Satisfaction or money back!
- ✓ Full year guarantee on all WRL-manufactured equipment

The World's Largest Distribution of Amateur Radio Equipment

AUDEL'S TV TELLS HOW TO ANSWER RADIO T.V. QUESTIONS SERVICE LIBRARY

HERE IS LATE INFORMATION IN A HANDY FORM FOR TELEVISION AND RADIO REPAIRMEN, SERVICEMEN AND STUDENTS

AUDEL'S T.V. RADIO SERVICE LIBRARY—Highly Endorsed—Over 1500 Pages—1048 Illustrations & Diagrams. 1001 Important Facts & Figures on Modern Television, Radio, Electronic Devices at your finger ends.

INCLUDES TRANSISTORS & Transistor Circuits, Record Changers, Rectifiers, P.A. Systems, Tape Recorders, Phonograph Pick-ups, F.M., Auto Radio; Radio Compass, Short Wave, Radar, etc.

ASK TO SEE IT!
IT WILL PAY TO KNOW!
The Basic Principles—Construction—Installation—Operation—Repairs—Troubleshooting. Shows How to get Sharp, Clear T.V. Pictures. Install Aerials—How to Test. Explains Color Systems. Methods of Conversion, Terms, etc. Includes Ultra High Frequency—Valuable for Quick Ready Reference and Home Study.

\$6 COMPLETE 2 VOLUMES Get This Information for Yourself.
7 DAY TEST—PAY ONLY \$1 A Month
MAIL ORDER

AUDEL Publishers, 49 W. 23 St., N.Y. 10, N.Y.
Mail AUDEL'S T.V. RADIO SERVICE LIBRARY (2 Volumes) \$6 on 7 days free trial. If O.K., I will remit \$1 in 7 days and \$1 monthly until \$6 is paid. Otherwise I will return them.

Name _____
Address _____
Occupation _____
Employed by _____

STAN-BURN

CATHODE RAY TUBE SPECIALS

ONE YEAR GUARANTEE

G.E. Type	STAN-BURN	G.E. Type	STAN-BURN
\$13.25 10BP4	\$10.20	\$31.25 17CP4	\$20.75
10FP4	14.00	3228 18AP4	22.50
16.25 12LP4	13.95	27.40 20AP4	18.95
12QP4	10.50	33.00 21AP4	22.25
12UP4	15.00	27.40 21EP4	20.15
28.95 12UP4	14.50	33.25 21MP4	23.50
18.15 14CP4	13.40	90.75 24AP4	49.00
13DP4	14.50	15.00 25MP4	18.50
31.25 16AP4	15.75	120P4	\$23.75
26.25 16KP4	18.50	15DP4	26.55
31.25 16PP4	18.50	16DP4	26.00
29.00 16LP4	15.25	16BP4	26.00
49.00 18WP4	15.75	17KP4	25.00
22.50 17BP4	19.50	19AP4/B	33.25
28.15 17CP4		21KP4	38.50

STAN-BURN CRT TUBES RCA LICENSED-MFD BY LINCOLN

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

\$20 WORTH OF ELECTRONIC PARTS IN GRAB-BAG QUALITY off. Resistor sockets, coils, speaker, transmitters, resistors, condensers, etc.

ONLY \$1.98 (plus 50c postage)

TAPE RECORDERS—Famous Brand

PC \$249.95 SPECIAL List Pr. \$329.95 SPECIAL

WFO \$109.95 129.00 List Pr. 70.95 59.95

*Write for full illustration details.

ANTENNA ACCESSORIES

*500 JFD DOUBLE "V" ant. box of 10...ea. \$1.39

*500 DOUBLE "V" 15' mounting arrest...ea. 2.09

*100 300 OHM WIRE—1000 Feet...ea. 2.09

*50 MIL 300 OHM WIRE—1000 Feet...ea. 12.49

*100 MIL 300 OHM WIRE—1000 Feet...ea. 13.99

KITS: We stock the following manufacturers

complete line of kits—see reference pages.

EICO—see pages 31, 32 ARKAY—see page 135

QUALITY—see page 133 PRECISE—see page 160

All domestic orders will be shipped prepaid for a

limited time. Send us your list. Order by Manufacturer

and Model Number of item.

TRANS-ATOMIC Transistor Radio—KIT \$6.95; WIRED \$7.95

SENSIPHONE CARPHONES Single \$1.50; Double \$2.50

GERMANIUM DIODE Loopstick Radio Kit \$3.25

AM-FM-SW AUTO RADIO

LeMans Free FM—127.5 MHz. For SIGNAL SEEKER—

1239.95 Includes 14" SPEAKER with GRILLE and

AUTOMATIC ELECTRIC ANTENNA. Simple installation

for all cars. Specify 6 or 12 Volt system.

VW 4 SPEED HI-FI CHANGER—Model 1210 with

Ronette, Sonotone or Astatic flip-over cartridge \$23.95

RC456 4-speed Collaro, Brand-new, Special...\$29.95

45-RPM SPINDLE...\$2.98

WEBSTER Model 140—3-SPEED Automatic with

Ronette, Sonotone or Astatic flip-over car-

tridge...\$22.49

MONARCH 3 SPEED AUTO, INTERMIX

CHANGER with crystal cartridge...\$21.95

Same with British variable reluctance...24.95

15 RPM SPINDLE...1.88

TURBO MONARCH 3 speed MOTOR &

TURNTABLE UNIT (less arm)...\$ 4.95

3 SPEED PORTABLE RECORD PLAYER with MONARCH

CHANGER—Ronette cartridge—Portable Two Tone Car-

tridge Case...\$22.95

PEERLESS PORTABLE BATTERY OPERATED RADIO—

Colors—Green, White, Red or Blue—5 TUBE

IMPORT...\$14.95 less batteries

BATTERY KIT for above...\$ 2.00

JEWEL—Model 5200—5 TUBE

AC DC RADIO...\$12.50

RECORDING TAPE—Top quality 1200 Feet Famous

and BOKED—1 to 3—\$1.69 ea. 6 to 11 \$1.59 ea.

12 or more \$1.49 ea.

HALLICRAFTERS TV

Model 17T3700M—Table Model—Dealers net...\$103.95

Model 215460M—Table Model—Dealers net...\$129.46

SETCHELL-CARLSON 17" PORTABLE TV...\$119.95

HI-FI PACKAGE DEAL

includes: JENSEN K210 SPEAKER, MONARCH AUTO-

MATIC CHANGER with GE BX-100 12" SPEAKER

ENCLOSURE in BLD or MAHOAGANY WOOD (Specify

color) MATCHING BASE FOR CHANG-

ER, 10 WATT HF 10 BUGH AMPLI-

fier. Complete, ready to play. A \$99.50 net

\$113.00 Value for only

or your choice of similar units at relative package

price. Write for prices.

DEALERS: Write for low cost prices and catalogs on

58 models—HALLICRAFTERS, SUPERIOR, NA-

TIONAL, PRECISION, HICKOK, TECHMASTER

G.E., WESTINGHOUSE, TUNG-SOL, MAJESTIC,

FUNDIG, ARKAY KITS, DELCO, GEN, MOTORS.

Address all inquiries to Dept. RE-9.

COMPLETE HIGH FIDELITY DEPARTMENT. SEND US

YOUR LIST FOR LOWEST QUOTATIONS ON ANY ITEM

We invite export inquiries and offers. Our export de-

partment will give special attention to expediting

foreign orders at minimum commissions. We are

authorized distributors for United Motors, all Delco

and Gen. Motors Auto Radio parts in stock.

We also carry a complete line of popular makes of

Radio Tubes at 50/10 discount. Also many other

special purpose and transmitting types, and all elec-

tronic parts and equipment at lowest prices. Send us

a list of your requirements for prompt quotations.

Terms: 20% with order. Balance C.O.D. All prices

F.O.B. NEW YORK Warehouse. Minimum order \$5.00.

Write for our latest price list and Hi-Fi Catalog RE-9.

STAN-BURN RADIO and

ELECTRONICS CO.

55B CONEY ISLAND AVE. • B'KLYN 18, N. Y.

PEOPLE

John R. Ward, appointed controller of Pyramid Electric Co., North Bergen, N. J., comes to the company from CBS-Columbia, where he held a similar position.



Obituaries

Frank A. Poor, founder and vice chairman of Sylvania Electric Products, at Huggins Hospital, Wolfsboro, N. H., after a brief illness, at the age of 76.

Cecil C. Agate, director of advertising for Sonotone Corp., at his home in Orange, N. J., at the age of 68.

Brig. Gen. Stephen H. Sherrill, at Walter Reed Hospital, Washington, D. C., following a heart attack. Awarded the Legion of Merit for supervising the training of 64,000 radar specialists during World War II, he was later commandant of the Eastern Signal School Training Center, Fort Monmouth, N. J.

Col. George P. Dixon, USA (Ret.), at Georgetown University Hospital, Washington, D. C., at the age of 67, executive vice president of the Armed Forces Communications & Electronics Assoc. and former director of communications for the Army Air Forces in Europe. A vice president of IT&T before joining the Armed Forces Com-


munications & Electronics Assoc., he was editor of the association's journal, *Signal*.

Personnel Notes

... Dr. W. R. G. Baker, General Electric vice president, was elected president of RETMA succeeding H. Leslie Hoffman, president of Hoffman Electronics. Other officers include: James D. Seerest, executive vice president and secretary, and Leslie F. Muter, Muter Co., treasurer and chairman of the Finance Committee. Glen McDaniel, New York attorney will continue to act as the general counsel for the association. ... Paul V. Galvin, president of Motorola, was awarded the 1956 Medal of Honor by RETMA at its annual convention in June.

... Mal Parks, Jr., who recently joined Howard W. Sams & Co., Indianapolis, was named general manager of the Magazine Division and *PF Reporter*. Joe Morin, sales manager of *PF Reporter*, takes over additional duties as circulation manager, and Glen Slutz, technical editor, advances to editor.

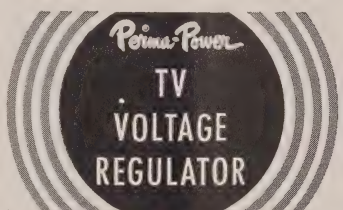... Aldon M. Asherman, according to an announcement by Terry P. Cunningham, Sylvania director of advertising and sales promotion, was appointed advertising manager for four product divisions of Sylvania Electric Products Inc.—Parts, Tungsten and Chemical, Atomic Energy and Electronic Systems. He comes to Sylvania from American Cyanamid. END



10 Volt Line Adjuster...



At All Distributors

manufactured by

Perma-Power COMPANY

4727 N. Damen Ave., Chicago 25, Ill.

manufacturers of electronic equipment since 1928

Exports: SCHEEL INT., Chicago

Almo ... OFFERS

THE WORLD'S MOST RELIABLE TROUBLE SHOOTERS FOR...

- ✓ ENGINEERS
- ✓ SERVICEMEN
- ✓ AMATEURS
- ✓ STUDENTS

World Famous 'Tui' POCKET CIRCUIT TESTER MODEL LP-6

A handy pocket size Circuit Tester with a rotary control switch. Excellent product with measuring device of 1200V, Current, Voltage and Capacity of Condenser, Fine Black Bakelite cabinet.

Response: 140A
AC, DC Volt: 6v 12v 60v 300v 1200v
(300A v/2000V)
DC Current: 300A 3mA 300mA
Resistance: 0~1MΩ 0~10KΩ
Decibels: -20db ~ +17db
Capacity: 0.01μF ~ 250PF

To measure Capacity of Condenser, use OUT (-) and (+) sockets and connect the Condenser with exact AC 100v in series, keeping Center switch at AC 60v Range.


NOW ONLY \$8.95

Almo RADIO CO.

New Location 509 ARCH ST. Downtown Phila., Pa.

Camden, N. J. • Atlantic City, N. J. • Trenton, N. J. • Harrisburg, Pa. • Wilmington, Del. • Salisbury, Md.

BE QUALITY WISE... BUY QUAL-KITS!

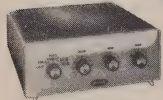

HI-FI AMP. KIT
Complete 6 tube-10 watt amplifier. Push-pull beam power output, built-in pre-amp. 5 position selector switch, 3 position record equalization, LP, RIAA, Eur. Response $\frac{1}{2}$ db. 20-20,000 cps. Output 10 watts at less than 2% IM. Low noise level and harmonic distortion. **\$28.50**

Every kit complete with 28 page fully illustrated instruction and assembly manual. Cover and legs optional.



HI-FI AM-FM TUNER KIT
Advanced 7 tube circuit plus Rectifier for full sensitivity and selectivity. Distortion less than 1%. Sensitivity is 5 uv for 30 db quieting on FM, 25 uv AM. Armstrong FM circuit with limiter, Foster-Seeley Discriminator. 20-20,000 cps response. Full AFC control — no drift. Easy assembly. **\$28.95**

Write for FREE catalog and name of nearest dealer carrying these remarkable units.

QUALITY-ELECTRONICS
319 Church St. Dept. E9 New York 13, N. Y.

DON'T JUST SAY CAPACITORS • DON'T JUST SAY CAPACITORS

Ask For Sprague By Catalog Number

Know what you're getting... get exactly what you want. Don't be vague... insist on Sprague. Use complete radio-TV service catalog C-610. Write Sprague Products Company, 81 Marshall Street, North Adams, Mass.

SPRAGUE®

WORLD'S LARGEST
CAPACITOR MANUFACTURER

DON'T JUST SAY CAPACITORS • DON'T JUST SAY CAPACITORS

SERVICEMEN WHO PUT PRIDE IN THEIR WORK "ALWAYS SPECIFY STANCOR"

CHICAGO STANDARD TRANSFORMER CORPORATION

3509 Addison Street • Chicago 18, Illinois

technical Literature



SERVICE DATA INDEX

1956 Index to Most-Often-Needed Television and Radio Servicing Information lists every radio and TV set in Supreme Publications' 27 volumes of diagrams and servicing information. All sets are listed alphabetically by manufacturer and numerically by model number.

Supreme Publications, 1760 Balsam Rd., Highland Park, Ill., 25c

DRAFTING

Standard and Simplified Drafting Practices (56 pages) devotes 20 pages to standard drafting-room practice. The final 24-page section on simplified drafting starts out with 11 rules as covered in detail by Mr. Bergen in his booklet *Simplified Drafting* and then goes into the specifics of simplified practice. Available to interested parties on company letterhead from Public Relations Dept., American Machine & Foundry Co., 261 Madison Ave., New York 16, N. Y.

SCHOOL BROCHURE

Capitol Radio Engineering Institute has put out a new edition of the brochure *Your Future in the World of Electronics*. It includes a 9-page detailed, factual report on opportunities in the radio electronic industry for technically educated men, by E. H. Rietzke, founder and president of CREI.

The 44-page brochure then discusses the importance of advanced technical training and goes on to describe CREI home study.

Registrar, Capitol Radio Engineering Institute, 3224 16th St. N. W., Washington 10, D. C.

HI-FI TUBES

Tubes that combine the advanced design of Philips of the Netherlands and Amperex engineering research are described in a new brochure.


Amperex Electronic Corp., 230 Duffy Ave., Hicksville, Long Island, N. Y.

AUTO AERIALS

An 8-page catalog describes auto aerials with specifications for front, rear and side mounts and lists accessories. One section illustrates up-to-date dealer displays.

Ward Products Corp., Div. of Gabriel Co., Dept. 56, 1148 Euclid Ave., Cleveland 15, Ohio **END**


Now! WRIST RADIO

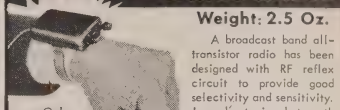

Weight: 2.5 Oz.
A broadcast band all-transistor radio has been designed with RF reflex circuit to provide good selectivity and sensitivity. In moderate signal strength areas, no antenna is required up to a distance of 25 miles from a broadcast station of average power. Good consistent reception can be obtained over 35 miles with the use of a wire from 6 inches to 3 feet. The use of transistors makes it a rugged device not subjected to tube breakage. Rugged high quality components are used throughout. Normally the transistor will not have to be replaced for the life of the instrument. Extreme economy of operation is obtained through the use of special circuitry requiring very low current, thus prolonging the life of the mercury cells. The small size makes it the ideal radio. It can be worn on the wrist where it easily fits under the sleeve of a jacket or worn in a shirt pocket.

FEATURES	SPECIFICATIONS
Two stage transformer coupled amplifier	Band coverage - 550-1600 kc
No whistle regenerative circuit	Sensitivity - 200 microvolts to meter
Light weight - 2.5 ounces total	Output - 2 - 2.5 milliwatts
Battery life - 100 hours	Current drain - 4.5 milliamperes
Stainless steel expansion wrist band	Battery voltage - 2.3 ounces, including batteries
High quality hearing aid receiver	Weight - 2 1/2" long x 1 1/4" wide x 1/2" thick
Printed circuitry throughout	Color - Silver
Rugged plastic case	1 RF Amplifier and detector transistor
No tube replacement or servicing	Audio amplifier transistors
Long life transistors	5 Mercury cells (General Dry Battery, Type 625 or Eveready Type 625) available at your radio supply house or hearing aid dealer
Extreme economy of operation	

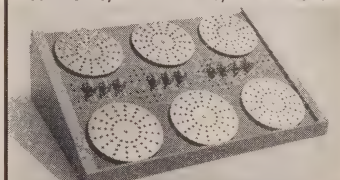GENIAC ELECTRIC BRAIN COMPUTES, PLAYS GAMES, "REASONS"!



BUILD IT YOURSELF in a few hours!

Here's a wonderful kit that gives you a fascinating introduction to the logic machines of our modern age! The devices you can build test intelligence, code and decode, count, play Tic-tac-toe, solve problems! Converts from binary to decimal—reasons in syllogisms—computes!

APPLICATIONS OF GENIAC
SIMPLE COMPUTER CIRCUITS for binary, decimal adding, subtracting, dividing, multiplying machines.
PROBLEMS in symbolic logic, reasoning, comparing.
PSYCHOLOGICAL TESTING and EXPERIMENT.
GAME PLAYING CIRCUITS for tic-tac-toe and nim.
ACTUARIAL ANALYSIS.

WHO ARE OUR CUSTOMERS?
International Business Machines • Westinghouse Electric
Remington-Rand • Barnard College • Manual Missionary College • Southwest Missouri State College • Albert Einstein Medical College • Naval Research Laboratories Board of Education, Tecumseh, Nebraska • Marshfield Public Schools • Los Angeles Public Schools • Kansas State University • Duke University • Coral Gables Senior High School • Bell Telephone Laboratories • and thousands of other satisfied customers.

WHAT COMES WITH THE KIT?
1—SIMPLE ELECTRIC BRAINS, AND HOW TO MAKE THEM...64 page experiment manual. 2—MINDS AND MACHINES...200 page text on computers, automation and cybernetics. 3—WIRING DIAGRAMS for basic GENIAC circuits. 4—BEGINNERS MANUAL 5—GENIAC study guide...the equivalent of a full course in computer fundamentals, lists additional readings. **Only \$19.95**
6—Over 400 parts and components with plastic "PARTS TRAY".

DEALER INQUIRIES INVITED
Oliver Garfield Co., Dept. RE-96
126 Lexington Avenue, New York 16, New York
Please send me:
1 WRIST RADIO
☐ \$29.95 Postpaid
1 GENIAC Electric Brain Construction Kit and Manuals.
☐ \$19.95 (East of Mississippi)
☐ \$20.95 (Elsewhere in the United States)
☐ \$21.95 (Outside the United States)
Returnable in seven days with full refund if not satisfied.
My name and address are attached.

To help you MOVE AHEAD in INDUSTRIAL ELECTRONICS

This Library makes plain methods used
by today's electronics engineers

HERE'S a Library to help you prepare for a top job
in the booming industrial-electronics field... help
save time and work in your present job. Experts
give you basic theory, practices, and methods. They ex-
plain electronic circuits and devices, vacuum tubes, the
analysis and use of electron-tube circuits, and provide a
great amount of other data on electronic equipment!

INDUSTRIAL ELECTRONICS ENGINEERING LIBRARY

4 volumes, 1998 pages, 1637
diagrams, and illustra-
tions

\$24.95—payable on
EASY TERMS

This Library are the sort of prac-
tices that can help you step
front of the "average" elec-
trician—they give the kind of
that could very well mean a
winning job in electronics work.
This practical data on vacu-
um instrumentation, a
great facts on vacuum
tube circuits, and the
analysis of electronic mo-
tion—basic knowledge here
applied in radar, tele-
vision, pulse communication,
wide variety of general
electronic control. Use coupon
for free trial—no obli-



4 Big Volumes

Cage's THEORY AND AP-
PLICATION OF INDUS-
TRIAL ELECTRONICS
Herman's FUNDAMENTALS
OF ELECTRONIC
MOTION
Spangenberg's VACUUM
TUBES
Seely's ELECTRON-TUBE
CIRCUITS

EASY
TERMS • 10-DAY
FREE TRIAL

McGraw-Hill Book Co. Dept. RE-9
327 W. 41st St., New York 36, N. Y.

Send the *Industrial Electronics Engineering*
Library for 10 days' examination on approval.
If 10 days, I will send \$4.95; then \$4.00 monthly
until low price of \$24.95 is paid. If not wanted, I
will return books postpaid.

Name

Address

City Zone State

Employed by

For price and terms outside U. S.,
write McGraw-Hill Int'l., N. Y. C.

RE-9

NEW RECORDING DRIVE




Now, for the first time a
bistressis - synchronous di-
rect drive, giving you ALL
4 smooth positive standard
speeds, plus double-speed
dubbing, plus special
speeds. Recommended for
all direct-drive disc record-
ers and players using as-
sociated wide-range equip-
ment. 30 to 60 day delivery.
\$850 FOB. Write for particu-
lars.

DAMON RECORDING STUDIOS INC.
117 W. 14 St., Kansas City (5), Mo.

NEW! For the First Time!

TEST CONDENSERS IN THE SET!

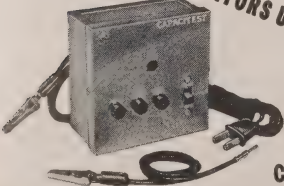

SATISFACTION
GUARANTEED
OR RETURN WITHIN
TEN DAYS FOR REFUND

CAPACITEST, the result
of months
in develop-

ment is a new, compact checker that does a giant job to save you time and money. It will check condensers at 150 Volts, which is approximately the working voltage of a radio or TV set. Others will not give this type of check since the applied voltage is 20 Volts or less. Avoid call-backs by using CAPACITEST. Accurately, quickly, it shows open, shorted, or intermittent capacitors and leaky electrolytics. Compact: 4"x4"x2"—lightweight, for bench or tool kit.

CAPACITEST

Quickly, Accurately checks:

- PAPER, MICA, CERAMIC CAPACITORS
- ELECTROLYTICS
- CONTINUITY
- AC/DC VOLTAGES
- FLASHBULBS

\$10⁹⁵

postpaid
Dlr. Net
complete,
ready for
operation

NOT A KIT

FREE

Special Introductory
Offer for limited time
only: Set of test leads
—include \$3 deposit with
C.O.D.'s. Save PP & COD fees.
Send \$10.95 & we'll pay postage.

BAR JAY The Barjay Co. 145 West 40 Street New York 18, N.Y.

Interference on TV-FM with mosley 'tunable' Wave Traps

New! High Q series-resonant Wave
Traps for eliminating and reducing
interfering signals on TV and FM.

Easy to install...Simply mount on
set antenna terminal strip and attach
transmission line to solderless screw
connectors on Wave Trap. "Tune out"
undesirable signals from amateur, FM,
taxicab and other transmitters.

Mosley Wave Traps may be used on
any receiver input from 50 to 600 ohms,
balanced or unbalanced. To select proper
Wave Trap, choose type whose
range includes the frequency of inter-
fering signal.

Available in 6 frequencies listed below.



Cat. Nos.

- WT.7...6.8—8.5 mc
- WT.14...13.8—16mc
- WT.21...16—21mc
- WT.41...27—55mc
- WT.78...47—110mc
- WT.165...100—230mc

List Price \$4.57

Mosley Electronics Inc.

8221 ST. CHARLES ROCK ROAD, ST. LOUIS 14, MISSOURI

Books



TECHNICAL MANUAL, Sylvania
Tubes. Sylvania Electric Products Co.,
1740 Broadway, New York 19, N. Y.
5½ x 9½ inches, loose-leaf binding,
pages not numbered. \$2.

Intermediate in price as well as con-
tent between the cheapest tube hand-
books and the elaborate affairs selling
for more than \$10, this manual con-
tains a surprising number of features
found in the more expensive books.
The purchaser obtains for 1 year
supplements to insert in his book, thus
keeping up-to-date with the newer
tubes. (Incidentally, tube tester set-
tings for users with Sylvania tube
testers are included. No doubt these
could be converted to other testers,
solving the problem of new tubes with-
out checking data.)

A tube-data section of abridged infor-
mation on obsolete and discontinued
types as well as on a number of more
popular tubes is very useful. Other
sections cover picture tubes, special
tubes (including crystal diodes but not
transistors), resistance-coupling data
and an appendix of useful information.

Resistance-coupled amplifier data is
given for two sets of input signal values
—representing high and low input
levels, and the percentage of distortion
is given for each.

COLOR TELEVISION STANDARDS,
by Donald G. Fink. McGraw-Hill Book
Co., New York, N. Y. 6 x 9¼ inches,
520 pages. \$8.50.

Compatible color TV has been accom-
plished only through the intensive
efforts of many scientists. In 1950, the
NTSC (National Television System
Committee) was organized by the TV
industry for the purpose of setting up
standards for color. At that time,
several systems were being proposed
and confusion was beginning to mount.
No existing system could provide a
satisfactory and compatible color pic-
ture. The NTSC went to work to deter-
mine the problems and how to solve
them. By the middle of 1953, a final
report was forthcoming, and this forms
the basis of our present-day color sys-
tem. This book covers the activity of
the NTSC, details of the final standard
signals, latest types of color films and
processes and definitions relating to
color TV.

As examples of the contents, one
committee report describes in very
simple language the features of a
compatible color signal. Another panel
was given a questionnaire regarding

the subjective factors of color TV. These questions (and the panel's answers) form a very interesting report on such topics as: depth of field, fidelity, surrounding room brightness and other characteristics of a color picture. Still another group was assigned the task of making field tests of the finally standardized color signal. Their results appear in the book.—*IQ*

TAPE RECORDERS, by Charles G. Westcott. Howard W. Sams & Co., Inc., Indianapolis, Ind. 5½ x 8½ inches, 177 pages. \$2.75.

A tape recorder is mechanical as well as electronic and therefore needs description from both viewpoints. This introductory book makes a good job of it. Prospective buyers will find here which important factors differentiate one recorder from another. Hi-fi fans will be interested in the discussions on wow and flutter and also how noise and hum are reduced. Technicians will note especially the typical schematics and the hints on maintenance and lubrication.

The book begins with a history and brief theory of magnetic recording. The transport mechanism receives considerable attention and there is data on motors. Several exploded views show the insides of a few recorders. As for the electronic end, chapters appear on volume indicators, bias oscillators, equalizers and amplifiers. There is a chapter on tape characteristics and another (very, very brief) on test procedures.

WORLD RADIO HANDBOOK FOR LISTENERS. Edited and published by O. Lund Johansen, Copenhagen, Denmark. Distributed in U. S. by Gilfer Associates, New York. 168 pages. \$2.

The 10th edition of an internationally known listing of broadcast and TV stations of the world. Prepared mainly for the shortwave listener but lists long- and medium-wave stations (151-1875 kc) as well. Shortwave stations are listed by country and by frequency. The listings by country also include mailing addresses, hours of operation, QSL'ing information and a few bars of the stations' identifying musical themes. END



ALL NEW BIGGER THAN EVER!

NEWARK'S
Complete
ELECTRONICS
Catalog No. 65
Here's everything in Industrial
Electronics, High Fidelity,
Radio, TV and Amateur
Equipment

Write
today

NEWARK
ELECTRIC COMPANY

Mail Order Division . . . Dept. RE-9
223 W. Madison St., Chicago 6, Illinois
4736 W. Century Blvd., Inglewood, Calif.

COYNE
TELEVISION
RADIO-COLOR TV

Only from famous COYNE do you get this modern up-to-the minute TV Home Training. Easy to follow instructions—fully illustrated with 2150 photos and diagrams. Not an old Radio Course with Television tacked on. Includes UHF and COLOR TV. Personal guidance by Coyne Staff. *Practical Job Guides* to help you EARN MONEY QUICKLY IN A TV-RADIO SALES AND SERVICE BUSINESS—part time or full time. COSTS MUCH LESS—pay only for training—no costly "put together kits."

SEND COUPON FOR FREE BOOK

SEND COUPON BELOW for Free Book and full details including EASY PAYMENT PLAN. NO COST OR OBLIGATION—NO SALESMAN WILL CALL.

B. W. COYNE, Pres.

COYNE
ELECTRICAL SCHOOL



FOUNDED 1889

ATECHNICAL TRADE INSTITUTE OPERATED NOT FOR PROFIT
500 S. Paulina St. Dept. 66-HTA Chicago 12, Illinois

COYNE ELECTRICAL SCHOOL
Television Home Training Div.
500 S. Paulina St., Chicago 12, Ill., Dept. 66-HTA
Send FREE BOOK and details of your Television Home Training offer.

Name _____
Address _____
City _____ State _____

Gernsback Library books can help you Get ahead in TV, Radio, High Fidelity



Basic Audio Course—Audio fundamentals from theory of sound to advanced techniques. No. 66. 224 pages.
☐ Paper cover \$2.75
☐ Hard cover \$5.00

NEW—Servicing Record Changers—Important steps illustrated with detailed line drawings. No. 59. 224 pages.
☐ Paper cover \$2.90
☐ Hard cover \$4.60

NEW! Maintaining Hi-Fi Equipment—Joseph Marshall explains hi-fi servicing techniques. No. 58. 224 pages.
☐ Paper cover \$2.90
☐ Hard cover \$5.00

The V.T.V.M.—How to use the V.T.V.M. to best advantage. No. 57. 224 pages.
☐ Paper cover \$2.50
☐ Hard cover \$4.60

NEW—High-Fidelity Circuit Design—By Crowhurst and Cooper. Includes Cooper's "Audio Feedback Design" series from RADIO-ELECTRONICS. No. 56. 304 pages.
☐ Hard cover only \$5.95
☐ Sweep and Marker Generators for Television and Radio—No. 55. 224 pages.
☐ Paper cover \$2.50
☐ Hard cover \$4.60

Probes—No. 54. 224 pages.
☐ Paper cover \$2.50
☐ Hard cover \$4.60

Radio-Control Handbook—How to build R/C systems. No. 53. 192 pages.
☐ Paper cover \$2.25
☐ The Oscilloscope—Get more out of your scope. No. 52. 192 pages.
☐ Paper cover \$2.25
☐ Hard cover \$4.60

☐ **Transistors—Theory and Practice**—For the practical man—theory and application in circuits. No. 51. 144 pages. Paper cover \$2.00

☐ **TV Repair Techniques**—Practical hints save you hours of servicing time. No. 50. 128 pages. Paper cover \$1.50

☐ **Radio & TV Test Instruments**—How to build 22 test instruments for modern servicing. No. 49. 128 pages. Paper cover \$1.50

☐ **High-Fidelity—Design, Construction, Measurements**—How to achieve top performance! Amplifier construction details. No. 48. 128 pages. Paper cover \$1.50

OTHER GERNSBACK LIBRARY BOOKS

Paper cover editions

☐ **Radio & TV Hints**—No. 47. 112 pages. \$1.00

☐ **Television Techniques**—No. 46. 128 pages. \$1.50

☐ **Radio Tube Fundamentals**—No. 45. 96 pages. \$1.00

☐ **Basic Radio Course**—No. 44. Hard Cover. 176 pages. \$2.25

☐ **Model Control by Radio**. No. 43. 112 pages. \$1.00

☐ **High-Fidelity Techniques**—No. 42. 112 pages. \$1.00

☐ **Practical Disc Recording**—No. 39. 96 pages. 75c

See your distributor or use this form

GERNSBACK LIBRARY, INC.
154 West 14th St.
New York 11, N.Y.

Enclosed is my remittance of \$..... for which send me postpaid the books checked above.
Prices 10% higher in Canada

Name..... (please print)

Street.....

City..... State.....

SCHOOL DIRECTORY

LEARN TV

Work on late model sets—using modern equipment and service techniques: under qualified technician instructors. Short resident and correspondence courses—no unnecessary math or theory—also UHF and Color TV.

APPROVED FOR VETERANS... day and night classes.
Write for free literature, Dept. 1A for residence—Dept. IAC for correspondence.

V.S.I. TELEVISION SCHOOL

4570 Firestone Blvd.
South Gate, California

GET INTO ELECTRONICS

You can enter this uncrowded, interesting field. Defense expansion, new developments demand trained specialists. Study all phases radio & electronics theory and practice: TV, FM, broadcasting, servicing, aviation, marine, police radio, 18-month course. Graduates in demand by major companies. H.S. or equivalent required. Begin January, March, June, September. Campus life. Write for catalog. VALPARAISO TECHNICAL INSTITUTE
Dept. C Valparaiso, Indiana

ENGINEERING DEGREES

(Under and Postgraduate)

E.E. Major in Electronics,
Earned Through Home Study.

AMERICAN COLLEGE OF ENGINEERING

Residential courses also Available

Box 27724(M), HOLLYWOOD 27, CALIF.

SENDING CODE RECEIVING SPEED

Be a "key" man. Learn how to send and receive messages in code by telegraph and radio. Commercial needs thousands of men for jobs. Good pay, adventure, interesting work. Learn at home quickly through famous Candler System. Qualify for Amateur or Commercial License. Write for FREE BOOK.

CANDLER SYSTEM CO.
Dept. 3-R, Box 525, Denver 1, Colo., U.S.A.



wanted career men

Train for a career instead of a job. Demand for our graduates exceeds supply. Effective placement. Modest costs. Small classes. Well-equipped labs. Beautiful campus. Approved for Vets. Enter Sept., Jan., March, June.

BACH. SCI. DEGREE IN 27 MONTHS

Complete Radio Eng. courses: TV, UHF, FM, Electronics. Also Mech., Civil, Elec., Chem., Aero. Eng. 36-month B.S. in Bus. Adm. (Gen. Bus., Acctg., Motor Transport Mgt.)... capable students faster. Prep courses. Write Jean McCarthy, Director of Admissions, for catalog and "Your Career in Engineering & Commerce."



TRI-STATE COLLEGE

2496 College Avenue, Angola, Indiana

Get Your F.C.C. LICENSE Quickly!

Guaranteed preparation, in a MINIMUM of TIME, for F.C.C. commercial operator examinations. Our highly specialized training is available by correspondence or in resident classes in WASHINGTON, D.C. and HOLLYWOOD, CALIF. Write for our free booklet with complete details.

GRANTHAM School of Electronics

Desk 4-E, 1505 N. Western Ave.
Hollywood 27, Calif.

TELEVISION

PREPARE FOR A GOOD JOB!

BROADCAST ENGINEER
ELECTRONICS
RADIO SERVICING

Television Servicing

(Approved for Veterans)

BUILDING AIRCONDITIONED
SEND FOR FREE LITERATURE

BALTIMORE TECHNICAL INSTITUTE

1425 EUTAW PLACE, BALTIMORE 17, MD.

'At the most practical school in the west'



TV REPAIRMEN EARN TOP MONEY!

IN JUST 12 MONTHS, COMPLETE TV SERVICE TRAINING, INCLUDING COLOR TV. Streamlined course gives you all essentials for a good job as service technician. Graduates in great demand; jobs are plentiful in this growing field. Other electronic courses in radio operation and maintenance. Day or evening classes. Opportunity for employment in local industry. Approved for Korean veterans.

Write for Catalog 111 Today

INDIANAPOLIS ELECTRONIC SCHOOL

312 E. Washington, Indianapolis 14, Indiana



FINISH HIGH SCHOOL AT HOME!

No classes to attend. Easy spare-time training covers big choice of subjects. Friendly instructors; standard texts. Full credit for previous schooling. Diploma awarded. Write now for FREE catalog!

WAYNE SCHOOL Catalog HKE-5
2527 Sheffield Ave., Chicago 14, Illinois

ENGINEERING

Prepare for unlimited opportunities in electronics! B.S. degree in 27 mo. Intensive, specialized courses. Math, electrical engineering, TV, advanced radio theory & design. Modern labs. Low rate. Earn board. Also Aeronautical, Chemical, Civil, Electrical, Mechanical Engineering. G. I. approved. Enter September, December, January, June.



INDIANA TECHNICAL COLLEGE

1596 E. Washington Blvd., Fort Wayne 2, Indiana

RADIO-TV ELECTRONICS



CREI graduates in big demand. ECED- Accredited Technical Institute Curricula. New classes start monthly. Free placement service for grads. Courses: Radio Engineering, Broadcast or TV Engineering; resident studies leading to "Associate in Applied Science" degree. Write for free Residence School catalog. Approved for veterans.

CAPITOL RADIO ENGINEERING INSTITUTE

Dept. RE, 3224 — 16th St., N.W., Washington 10, D.C.

RADAR

Our school is now introducing a correspondence course in Radar, Microwaves, and Loran. Get your FCC endorsement, high paying job in industry as a radar technician. Special introductory offer. Write

PROGRESSIVE ELECTRONICS INSTITUTE

P.O. Box 27764 Los Angeles 27, Calif.



RCA INSTITUTES, INC.

A service of Radio Corporation of America
350 West 4th St., New York 14, N.Y.

OFFERS COURSES IN ALL TECHNICAL PHASES OF RADIO, TELEVISION, ELECTRONICS

Approved for Veterans
Write Dept. RE-56 for Catalog

LEARN TV SERVICING UHF—COLOR—VHF

Master the latest, up-to-the-minute TV and Color TV developments.

You can Earn to \$5,000-\$10,000 a year in TV servicing after a few short months. Education or age is no barrier. Find out how you can EARN WHILE YOU LEARN in our big Shops and Laboratories. You work with the latest equipment. Waste no time with Non-Entails, Math or Design Theory. Complete information in our FREE booklet. Address Dept. E-56, Approved for veterans. Free Placement Service.

WESTERN TELEVISION INSTITUTE

341 W. 18th St. Los Angeles, Calif.

Dept. E-56

Mail me information about training.

Name _____

Address _____

Your choice of school is highly important to your career in



INDUSTRIAL ELECTRONICS



RADIO



TELEVISION

Become an ELECTRICAL ENGINEER or an ENGINEERING TECHNICIAN at

MSOE in Milwaukee

Choose from courses in: ELECTRICAL ENGINEERING Bachelor of Science degree in 36 to 42 months with a major in electronics or electrical power.

ELECTRICAL TECHNOLOGY Engineering Technician certificate in 12 months in electronics, radio, or electrical power.

Associate in Applied Science degree in 18 months in radio and television.

TECHNICAL SERVICE Service certificate in 6 months in electricity; in 12 months in radio and television.

MSOE — located in Milwaukee, one of America's largest industrial centers — is a national leader in electronics instruction — with complete facilities, including the latest laboratory equipment, visual aid theater, amateur radio transmitter — offers 93 subjects in electrical engineering, electronics, radio, television, electrical power, and electricity.

Advisory committee of leading industrialists. Courses approved for veterans. Over 50,000 former students. Excellent placement record.



TERMS OPEN JULY, SEPTEMBER, JANUARY, APRIL

Choose wisely — your future depends on it. Write for more information today!

MILWAUKEE SCHOOL OF ENGINEERING

Dept. RE-956, 1025 N. Milwaukee St.
Milwaukee 1, Wisconsin

Send FREE career booklets on:

☐ Electrical Engineering ☐ Radio-Television

I am interested in _____ (Name of course)

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

If veteran, give discharge date _____

MS-31

LAFAYETTE SENSATIONAL VALUES! IN COMPLETELY WIRED TEST EQUIPMENT at LESS than the PRICE of KITS!

LAFAYETTE SIGNAL GENERATOR

NEVER BEFORE HAS A COMPLETELY WIRED AND TESTED INSTRUMENT OF SUCH ACCURACY AND QUALITY BEEN OFFERED AT SUCH A PRICE!

- FREQUENCY 120 KC TO 260 MC
- 120 KC TO 130 MC ON FUNDAMENTALS
- LABORATORY ACCURACY AND QUALITY

A completely wired and tested instrument not to be confused with units sold in kit form at almost the same price, but with a quality and accuracy of instruments 3 to 4 times its price. Six overlapping ranges generate signals of 120KC - 320KC, 320KC - 1000KC, 1MC - 2MC - 11MC, 11MC - 38MC and 37MC - 130MC all on fundamentals with calibrated harmonics from 120MC to 260MC. Selector switch gives instant choice of ranges. Switch gives choice of internal modulation of 400 CPS or use of any external carrier at other frequencies. For audio testing the 400 cycle signal can be used separately. With 400 CPS output, RF output is in excess of 100,000 volts across 1 megohm. Large clear 5 inch etched dial plate and pointers are protected by transparent plastic bezel. Common AF terminals for EXT-MOD input and INT-AMF for audio tests eliminate need for special AF output connectors. Machine engraved panel lettering. Handsome gray metal case with carrying handle. Measures $6\frac{1}{2}'' \times 10'' \times 4\frac{1}{2}''$. Comes complete with pair of leads. AC line cord and plug. Operates on 105-125V 50-60 cycle AC. Shpg. wt., 8 lbs.

22.50

Outputs are unmodulated RF, modulated RF and 400 CPS output. AF output is in excess of 100,000 volts across 1 megohm. Large clear 5 inch etched dial plate and pointers are protected by transparent plastic bezel. Common AF terminals for EXT-MOD input and INT-AMF for audio tests eliminate need for special AF output connectors. Machine engraved panel lettering. Handsome gray metal case with carrying handle. Measures $6\frac{1}{2}'' \times 10'' \times 4\frac{1}{2}''$. Comes complete with pair of leads. AC line cord and plug. Operates on 105-125V 50-60 cycle AC. Shpg. wt., 8 lbs.

LAFAYETTE LSG-10 SIGNAL GENERATOR

22.50

LAFAYETTE CAPACITANCE-RESISTANCE TESTER WITH "IN-SET QUICK CHECK"

COMPLETELY WIRED AND TESTED

- TWO INSTRUMENTS IN ONE
- CHECKS ELECTROLYTIC, PAPER, MICA AND CERAMIC CONDENSERS
- DIRECT READING CAPACITY SCALES FROM .00001 MFD TO 1000 MFD
- CHECK FOR OPEN SHORTS, LEAKAGE AND INTERMITTENTS
- 2 RESISTANCE RANGES FROM 100 TO 5 MEGOHM

Here is a "must" for servicemen and lab technicians. A completely self-contained AC operated capacitance and resistance bridge, plus a quick check for the set testing. Large 5 direct reading scale has 4 ranges of .00001 to .05 MFD, .001 to .5 MFD and 20-1000 MFD. Resistance ranges are 100-50,000 OHMS and 10,000 to 5 megohm. Quick check feature enables you to check capacitors for shorts, open or intermittent while in circuit—no need to remove them from the set till you're sure they need replacement. Leakage test switch gives you checking leakage under correct potential. Separate power factor control from 0 to 50%. Operation is simple and accurate, using magic-eye tube as the null detector. Attractively finished steel case with etched panel and rounded corners. Measures $14\frac{1}{2}'' \times 8\frac{1}{4}'' \times 5\frac{1}{2}''$. Shpg. wt. 3.9 lbs.

34.50

you choice of 25, 150, 250, 350 or 450 volts power factor control with continuous settings from 0 to 50%. Operation is simple and accurate, using magic-eye tube as the null detector. Attractively finished steel case with etched panel and rounded corners. Measures $14\frac{1}{2}'' \times 8\frac{1}{4}'' \times 5\frac{1}{2}''$. Shpg. wt. 3.9 lbs.

MODEL LC-4

NET 34.50

NEW!

LAFAYETTE CAPACITOR-RESISTANCE TESTER COMPLETELY WIRED AND TESTED

21.50

- CHECKS ALL TYPES OF CONDENSERS FOR CAPACITY, LEAKAGE, OPEN SHORTS OR INTERMITTENT CONDITION
- DIRECT READING SCALES FROM .00001 TO 1000 MFD AND 100 TO 5 MEGOHMS

A stable and accurate bridge type circuit measures capacitance in 4 ranges of .00001-.005 MFD, .001 to .5 MFD, .1 to 50 MFD and 20 to 1000 MFD. Two resistance ranges of 100-50,000 and 10,000 to 5 megohms. Check leakage under actual load with choice of 25, 150, 250, 350 or 450 volts available by selector switch. Power factor control from 0 to 50%. Checks for leakage, open, short, or intermittent operation. All readings taken directly off scales after setting magic eye to maximum. Completely self-contained power supply. Attractively finished steel case with rounded corners and etched panel. Operates from 110V AC. Size $9\frac{1}{2}'' \times 7\frac{1}{4}'' \times 5\frac{1}{4}''$. D. Shpg. wt. 10 lbs.

MODEL LC-15

NET 21.50

FM-AM TUNER KIT

- SIMPLIFIED DETAILED INSTRUCTION MANUAL
- MEETS FCC REQUIREMENTS FOR RADIATION
- GROUNDING GRID TRIODE AMPLIFIER

- ARMSTRONG FM CIRCUIT WITH FOSTER-SEELEY DISCRIMINATOR
- AFC DEFEAT CIRCUIT WITH FRONT PANEL CONTROL

The excellence of its design and the quality of its components combine to provide this compact high-fidelity FM-AM tuner with superb characteristics normally found in units costing several times as much, and with performance unbelievable at this low price. Features Armstrong FM circuit with limiter and Foster-Seeley discriminator. Simplified tuning control. Attractive etched copper-plated and lacquered finish.

FREQUENCY RANGE: FM, 88-108 MC; AM, 530-1650 KC. **ANTENNA INPUT:** FM, 300 ohms; AM, Ferrite loopstick and high impedance external antenna. **CONTROLS:** 2 — a function control for FM, PHONO, TV and a tuning/AFC defeat control. **DISTORTION:** Less than 1% rated output. **FREQUENCY RESPONSE:** FM, ± 5 db 20 to 20,000 cps; AM, ± 5 db 100 to 10,000 cps. **SENSITIVITY:** FM, 5uv for 30 db quieting; AM, Loop sensitivity 80uv/meter. **SELECTIVITY:** FM, 200 KC bandwidth, 6 db down — 375 KC FM discriminator peak to peak separation; AM, 8 KC bandwidth, 6 db down. **IMAGE REJECTION:** 30 db minimum. **HUM LEVEL:** 50 db below 100 mc. **POWER SUPPLY:** 2-12AT7, 1-6BA6, 1-6BE6, 2-6AU6, 1-6AL5 plus 1-6X4 rectifier. **SIZE:** $5\frac{1}{4}'' \times 9\frac{1}{4}'' \times 3\frac{1}{4}''$ wide x $9\frac{1}{4}''$ deep (excluding knobs). **CONSUMPTION:** 30 watts. For 110-120V 60 cycles AC. Less metal case, Shpg. wt., 9 lbs.

KT-100.....Metal cage for above, shpg. wt., 3 lbs.....Net 32.50
ML-100.....Net 5.00

NEW POCKET AC-DC VOM MULTITESTER

2,000 ohm per volt Sensitivity on both DC and AC

160 ua 3" METER
1% PRECISION
RESISTORS
SILVER CONTACT
SELECTOR SWITCH

FULL SCALE RANGES

DC Volts: 0-10; 0-50; 0-500; 0-1000 Volts — AC
Volts: 0-10; 0-50; 0-500; 0-1000 Volts — DC Current:
500 ua and 500 ma
Resistance: 0-10K; 0-1 Meg
— Decibels: —20 to +22;
+20 to 36 db (0 db =
0.775 V) — Capacity: 250
mf to .2 mfd — 005 mfd
to 1 mfd — Output Ranges:
0-10; 0-50; 0-500; 0-1000
volts



7.95

Best Buy in America! A very accurate and sensitive VOM. This Multitester is a complete instrument (not a kit) with high quality and a sensitive 160 microamp meter; 2000 ohm per volt on both AC and DC. Single selector switch, 1% accuracy and ruggedness. In attractive plastic front panel, with metal bottom for ruggedness and shielding. First capacity range requires 50 volt AC source. Second capacity range requires 10 volt AC source. Size $4\frac{1}{4}'' \times 3\frac{1}{2}'' \times 1\frac{1}{4}''$. Complete with test leads and batteries. Shipping weight, 1.5 lbs.


RW-27A

Complete 7.95

HIGH SENSITIVITY 20,000 OHM PER VOLT DC 10,000 OHM PER VOLT AC MULTITESTER

LOOK AT THESE FULL SCALE RANGES!

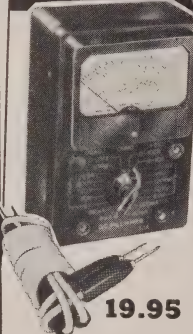D.C. Volts: 0-6; 0-30; 0-120; 0-600; 0-1200; 0-6000 Volts — AC Volts: 0-6; 0-30; 0-120; 0-600; 0-1200 Volts — RESISTANCE: 0-10K; 0-100K; 0-1 Meg; 0-10 Megohms — D.C. CURRENT: 0-60 Microamp; 0-6; 0-60; 0-600 Milliamps — DECIBEL: —20 to +27 db (0 db = 0.774V) — CAPACITY: .0001-.01; .001-.15 mfd — INDUCTANCE: 20-2000 millihenry — OUTPUT RANGES: 0-6; 0-30; 0-120; 0-600; 0-1200 Volts



19.95

The new Lafayette high sensitivity Multitester is a complete instrument (not a kit). In addition to its unusual sensitivity of 20,000 OHMS PER VOLT D.C. AND 10,000 OHMS PER VOLT ON A.C., and the extraordinary number and scope of its ranges, it is packed with features that would make it cost at least twice as much if made in this country. Uses 1% precision resistors, silver contact selector switch, 25 ua 3" meter. Dependable, rugged and accurate. Even the test leads are heavy duty with high voltage insulation. Voltage source required for low capacity range of either high range high capacity and inductance scale is 6V AC. Attractive plastic front and metal bottom. Size $6\frac{1}{4}'' \times 4\frac{1}{4}'' \times 2\frac{1}{4}''$. Complete with batteries and leads. Shipping weight 1.5 lbs.

RW-30A

Singly, Each 19.95

In lots of 3, Each 19.25

SLIM HIGH OUTPUT DYNAMIC MICROPHONE

Reg. Price \$41.50 Net 9.95

A pencil-slim design, high output PA Dynamic Microphone of exceptional quality, at a price that is 1/2 the price of comparable microphones on the market today. Very smooth response, 50-11,000 ohms. Omnidirectional, tiltable head. Switch on side gives range of either high impedance (50,000 ohms) or low impedance (250 ohms). Instantly removable bracket permits use either on stand or as a hand mike. Features exceptional mechanical strength. Cast case with satin chrome finish. $2\frac{1}{2}''$ long; $1\frac{1}{4}''$ barrel diameter. Shipping weight 2 lbs.

PA-29.....In lots of 3, Each 9.25
Singly, Each 9.95

FREE! BUILD YOUR OWN TRANSISTOR RADIOS 32 PAGE CATALOG

100 SIXTH AVE., NEW YORK, N. Y.
BOSTON, MASS., 110 Federal St.
PLAINFIELD, N. J., 139 West 2nd St.
NEWARK, N. J., 24 Central Ave.
BRONX, N. Y., 542 E. Fordham Rd.

DEPT. JI-1

LAFAYETTE
JAMAICA 33; N. Y. 165-08 Liberty Ave. Write for FREE Bargain Packed Catalog!

FREE!

LAFAYETTE CATALOG



ELECTRONIC CATALOG PACKED WITH MONEY SAVERS

Packed with the largest selection of Electronic, Radio and T.V. Parts, and equipment, PA, Hi-Fi systems, tubes, antennas, Transistor Kits, parts and components, Test Equipment, new build your own kits, tools, books, Microscope, drafting equipment, Binoculars, Telescopes, All Radio, TV and Ham supplies — ALL AT GREAT SAVINGS — For the economy minded servicemen, dealer, engineer and technician. **CHUCK FULL OF BUYS! SEND FOR YOUR FREE COPY TO-DAY.**

only **LAFAYETTE** can do it!

OUR DIRECT IMPORTATIONS

YOU SAVE IMPORTERS PROFIT!

SAVE
33 1/3-50%

PROFESSIONAL TRANSCRIPTION TURNTABLE AND VISCOUS-DAMPED TONE ARM

THE FINEST TRANSCRIPTION TURNTABLE AND TONE ARM FOR THE PROFESSIONAL USER AND THE AUDIOPHILE

PK-100A TRANSCRIPTION TURNTABLE



New 3-speed instrument with built-in stroboscope and viewer for exact speed determination, and magnetic brake for instantaneous speed variation. Precision engineered to meet professional standards for wow, rumble and flutter content. Heavy 12" cast aluminum rim-driven turntable. Variable speed control permits adjustment of each speed within $\pm 7\%$ using efficient frictionless magnetic brake. Heavy-duty constant speed 4-pole induction motor freely suspended and isolated by shock-mountings to eliminate vibration transfer. R-C filter network suppresses "pop" in speaker. Truly a delight for the connoisseur. Size: 13 1/2" x 14" and requires 2 3/4" clearance above and 3 3/4" below motorboard. For 110-130V and 60/50 cycle AC. Power consumption 12 watts. Handsome hammertone gray finish. Shpg. wt., 20 lbs. **Net 49.50**

PK-90 VISCOUS-DAMPED TONE ARM


This transcription arm assures dependable and stable operation, utilizing the "floating action" principle of "viscous-damping." The arm is supported at a single point by a pivot and jewel bearing having negligible friction. Damping is accomplished by a silicone fluid occupying the gap between a ball and socket. This damping control permits high compliance and negligible tracking error, and prevents damage to either record or stylus should the tone arm be accidentally dropped. Low frequency resonance, skidding and groove-jumping are likewise minimized. The tone arm accepts all records up to 16" and accommodates virtually all hi-fi cartridges by means of precisely engineered adapters which simplify installation and provide proper stylus pressure.

This tone arm is a quality companion to the PK-100 with matching finish. Shpg. wt., 2 1/2 lbs. **Net 19.50**

NEW! HIGH FREQUENCY TWEETER WITH ACOUSTIC LENS

DIRECT IMPORTATION MAKES THIS PRICE POSSIBLE!

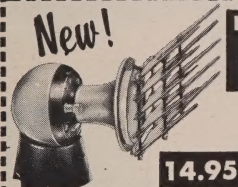- FREQUENCY RESPONSE FROM 2000 CPS TO BEYOND AUDIBILITY
- LOUVERED ACOUSTIC LENS FOR UNIFORM SOUND DISPERSION
- HANDLES 25 WATTS OF POWER
- PRICED EXCEPTIONALLY LOW



14.95

New high frequency tweeter featuring a louvered acoustic lens for uniform sound dispersion and capable of handling up to 25 watts of distortion-free power. The directional tendency of high frequency notes is overcome by the natural wide dispersion angle of the short horn and the acoustic lens which disperses and radiates the high notes smoothly throughout the entire listening area. The lens is detachable for panel mounting, with a separate base for the tweeter furnished for external mounting where desired. Aluminum voice coil has 16 ohms impedance. Size: 4 1/4" long x 3" diameter, lens extends 2 1/2". Requires a crossover network, preferably one with a level control, such as the LN-2. With full instructions. Shpg. wt., 5 lbs. **Net 14.95**

HW-7

METAL-CASED CONE TYPE HI-FI TWEETER

FREQUENCY RESPONSE 2000 -16,000 CPS • HANDLES 20 WATTS OF POWER

Highest quality cone type high frequency tweeter having a range from 2000 to 16,000 cycles. Especially efficient at higher end of audio spectrum where other cone type tweeters tend to lose clarity and volume. Entirely closed in a metal case with a base so that it can stand by itself or be mounted on a flat surface with mounting bracket supplied. Rated to handle 20 watts of power. A crossover network is required: the Lafayette LN-2 is ideal. Voice coil impedance 8-16 ohms. Size: 3 1/8" x 2 1/2" x 3" Diam. Shpg. wt., 3 lbs. **Net 5.95**



HK-3

CROSSOVER NETWORK • CAPACITIVE-INDUCTIVE NETWORK WITH CROSSOVER AT 2000 CPS

The frequencies above 2000 cycles are channeled to the high frequency tweeter by means of the high-Q inductance and capacitance comprising this efficient crossover network. The highs and lows are brought into acoustic balance by means of a continuously variable level-brilliance control. Control has a 2 1/2' ft. long cable for remote mounting. Network matches 8-16 ohm speakers with insertion loss reduced to a minimum. Enclosed in metal case 6" L x 2 1/2" H x 2 3/8" D. With full instructions. Shpg. wt., 8 lbs. **Net 8.75**



8.75

LN-2

NEW!

IMPORTED 12" HI-FI COAX. SPEAKER

- FREQUENCY RANGE 30-15000 CPS
- HANDLES 20 WATTS OF POWER
- COMPLETE WITH LEVEL CONTROL
- POWERFUL TSK-5 MAGNETS
- SPECIAL SHEEPSKIN-EDGED CONE

A Lafayette exclusive import and exceptional value. Consists of a 12" woofer, coaxially mounted 2 1/2" tweeter and a built-in crossover network. The specially processed fibre cone has a sheepskin edge to suppress unwanted nodal vibrations and insure beautiful tone quality. Highly efficient TSK-5 magnets. Level control provides variation to 6 db cut. Maximum input 20 watts. Impedance 8 ohms. Rugged all-metal frame. If made in this country, would cost at least \$49.50. Shpg. wt., 11 lbs. **Net 29.50**


SK-58

Reg. Price

44.50

Net

29.50

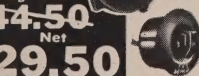

New!

LAFAYETTE Mail Order Center

Lafayette Radio
DEPT JI-2

165-08 Liberty Ave.
JAMAICA 33; N. Y.

SEND
FREE
LAFAYETTE
CATALOG

NAME _____

ADDRESS _____

CITY _____

ZONE _____

STATE _____

CUT OUT
AND MAIL
TODAY!



TEST 5 TUBES in 4 SECONDS EACH...ACCURATELY!

WITH THE NEW ADVANCED ENGINEERED

precise

MODEL 116

Gm. & Em. ULTRAFAST TUBE & TRANSISTOR TESTER



Completely
NEW!

PRECISE MODEL 116K in kit form.....\$69.95
PRECISE MODEL 116W factory wired.....\$119.95
Incl. carrying case and cover

Servicemen know the Precise Model 111 (the winner in an independent survey) easily rates "the finest tube tester in the field" at any price, BUT FOR AN ON THE JOB QUICK-TEST . . . the fastest, most accurate is the PRECISE Model 116. What's more you test tubes the foolproof method inherent in the famous Precise Model 111.

Did you ever wish you could plug in 5 of the same type tubes at once and check each one individually by rotating a switch? YOU CAN WITH THE PRECISE MODEL 116—Plug in 5 IF tubes and let them heat up at once and then check each one separately by rotating the TUBE BANK switch. ACTUALLY CHECK 5 TUBES IN 20 SECONDS, 4 SECONDS PER TUBE.

The Precise Model 111 taught the lesson that IF amplifier tubes (like the 6BC5 or 6AU6) should be tested for Gm (mutual transconductance) while the power amplifiers (like the 6L6) should be tested for Em (emission)—that's ULTRAFAST Model 116 test! It checks each section of each tube separately . . . by rotating the FUNCTION SWITCH . . . each triode of a dual triode is checked individually . . . each diode and the triode of a duo-diode-triode is separately tested and not lumped as in other testers . . . and a pentode is tested as a pentode—not a diode. TRANSISTORS, SHORTS, GAS, LIFE, Em, Gm etcetera can be tested with the PRECISE Model 116.

You can inexpensively extend the Precise Model 116 to test filament current, etc. The Model 116 gives an accurate, ultra-fast (3 basic knobs for testing) check of television tubes!


No Surplus—An etched panel—beautiful Moleskin covered wood carrying case and cover and specially simplified instructions makes the PRECISE MODEL 116 THE FINEST FAST-CHECK TUBE TESTER AND DOLLAR EARNING TRAVELING COMPANION A TV SERVICEMAN EVER HAD.

Not yet at your distributor. Order NOW to insure early delivery.


SEE YOUR LOCAL DISTRIBUTOR FOR PROOF OF WHAT WE OFFER—OR WRITE US FOR DOCUMENTARY RESULTS OF AN INDEPENDENT SCIENTIFIC SURVEY.



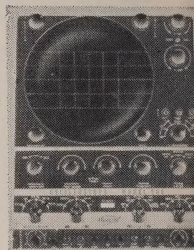
THE FAMOUS MODEL #111
111K \$79.95
111W \$139.95
Incl. Carrying Case & Cover



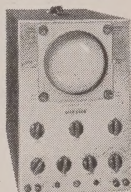THE FIRST LOW PRICED
7" COLOR SCOPE
300K \$99.95
300W \$199.50



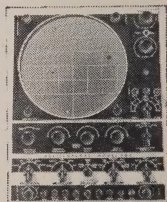LOW PRICED 5" SCOPE
315K \$49.95
315W \$84.95




THE FIRST AND ONLY
8 1/2" COLOR SCOPE
308K \$129.50
308W \$229.50



LOWEST PRICED
WIRED 4 1/2" VTVM
909K \$25.98
909W \$37.50



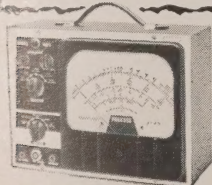
RF-AF-BAR GENERATOR
with pre-assembled* head
630K \$33.95
630KA* \$38.95
630W \$53.95



THE FINEST VOLT, REG,
7" VTVM KIT
9071K \$35.95
9071W \$49.95



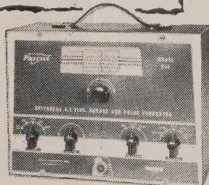LOW PRICED RF SIGNAL GENERATOR
"BEST BUY" IN GEN. FIELD
610K \$23.95
610KA pre-assembled head..... \$28.95
610W \$39.95



UNIV. AF, SINE, SQ, & PULSE GEN.
635K \$33.50
635W \$52.50

Prices slightly higher in the West. Prices and specifications subject to change without notice.

PTAK \$2.25
PTAW \$4.25

SEE THE MANY MORE PRECISE INSTRUMENTS AND PROBES AT YOUR DISTRIBUTOR TODAY

precise DEVELOPMENT CORP. OCEANSIDE, NEW YORK, U.S.A.

WRITE FOR CATALOG RE 9-6

Your next step to


Perfection

IN HIGH FIDELITY



CIRCLOTRON AMPLIFIERS

and
MUSIC CONTROL
CENTERS

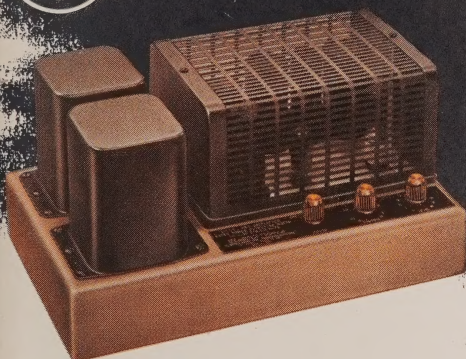

Model A20CL Music Control Center and 20-watt Power Amplifier. Features unique, exclusive "Presence" control. Response 20-20,000 cps. ± 1.0 db at rated 20 watts, 40 watts peak. Controls include Playing Selector, Loudness, Bass, Treble, Volume and Power, Phono-Selector. Power Amplifier utilizes Circotron Circuit and Variable Damping Control. Low-boy style. **Net, \$124.50**

Model A15CL Music Control Center and 15-watt Power Amplifier. Similar to Model A20CL above except Power Output 15 watts rated, 30 watts peak. Controls include Power, Bass, Treble, Volume, Playing Selector and Phono-Selector. **Net, \$99.50**

Model PC1 Music Control Center. Serves as control for line amplifiers. Has self-contained, shielded, low-noise power supply. Features exclusive E-V "Presence" control. Other controls include Playing Selector, Loudness, Bass, Treble, Volume, Power and Phono-Selector. **Net, \$99.50**

Model PC2 Music Control Center. Serves as control for line amplifiers. Controls include Playing Selector, Bass, Treble, Phono-Selector, Volume and Power. Self-contained, shielded, low-noise power supply. **Net, \$67.00**

Model A15 Circotron Amplifier. Power output: 15 watts rated, 30 watts on peak. Response: $\pm .5$ db 20-50,000 cps. **Net, \$69.50**

Model A20 Circotron Amplifier. Power Output: 20 watts rated, 40 watts on peak. Response: $\pm .5$ db 20-60,000 cps. **Net, \$85.00**

Model A30 Circotron Amplifier. Power Output: 30 watts rated, 60 watts on peak. Response: $\pm .5$ db 20-75,000 cps. **Net, \$108.00**

Model A50 Circotron Amplifier. Power Output: 50 watts rated, 100 watts on peak. Response: $\pm .5$ db 20-75,000 cps. **Net, \$169.00**

Model A100 Circotron Amplifier. Power Output: 100 watts rated, 200 watts on peak. Response: $\pm .5$ db 20-50,000 cps. **Net, \$261.00**

Prices slightly higher west of the Rockies.

Featuring the new, vital PRESENCE CONTROL

With the thrilling new PRESENCE CONTROL, you take the leader's baton and conduct the orchestra to suit your own listening pleasure in the ELECTRO-VOICE MUSIC CONTROL CENTER. Balances vocals to orchestra and room acoustics for true high fidelity. Just like the network and recording studios, the PRESENCE CONTROL gives mid-range program equalization never before available in home systems. Low-boy styling is skillfully blended with mocha, satin brown, and brushed brass trim for a beautiful appearance that matches blonde or mahogany cabinets.

With ELECTRO-VOICE CIRCLOTRON AMPLIFIERS, you come closer than ever to perfection in high-fidelity reproduction. The famous Circotron Circuit provides unity coupling between output tubes; eliminates switching transients and removes DC from output transformer. The exclusive Variable Damping Control greatly reduces loudspeaker low-frequency distortion and voice-coil override. Permits matching amplifier, speaker and enclosure to room...for the closest approach to reality of reproduction.

See your E-V High Fidelity Distributor or write for Bulletin 222-W69

Electro-Voice[®]

Producers of famous E-V High-Fidelity Speaker Enclosures and Systems

Export: 13 East 40th Street, New York 16, U. S. A.


Cables: ARLAB

Advanced
engineering
and precision-
manufacture
build

LONG LIFE

into RCA

RECEIVING TUBES

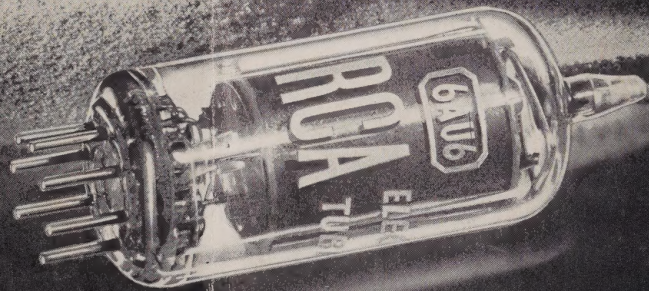

A receiving tube that delivers, and keeps on delivering at maximum performance levels doesn't just happen—it has to be made to happen!

Stringent quality control checks govern each part and each process in the manufacture of all RCA Receiving Tubes. Take the RCA-6AU6, for instance: The control grid is silver-plated to minimize grid emission and to give low contact potential; carefully processed cathode materials minimize leakage and mica support is specially treated to insure low inter-electrode leakage; result—Long Life! To insure noise-free performance—is “receiver-tested.” Avoid costly callbacks—standardize on RCA. Tell your distributor to fill your tube order with RCA Tubes only.



RECEIVING TUBES
RADIO CORPORATION OF AMERICA

